Wireless World

RADIO AND ELECTRONICS

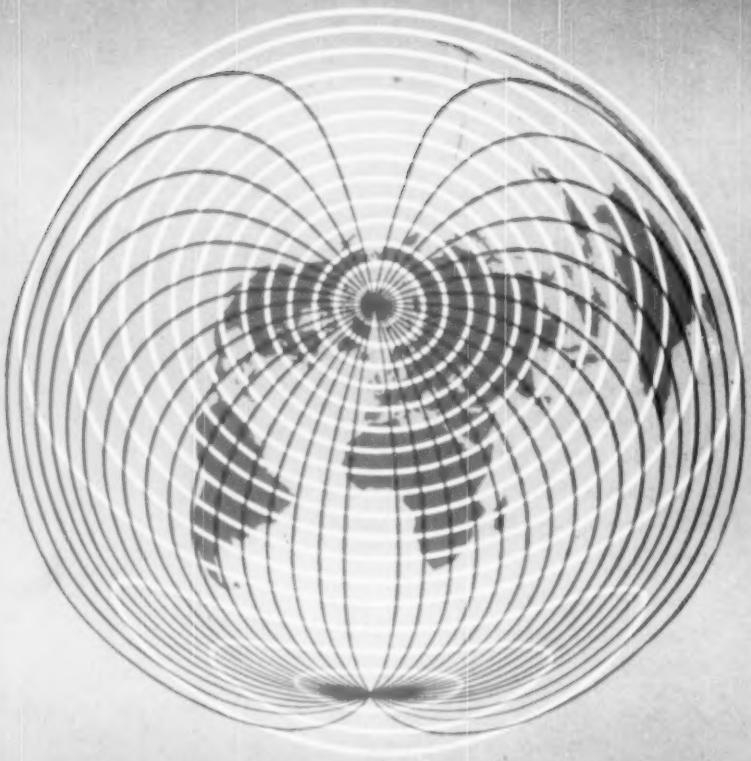

Vol LVI No. 5 Two Shillings May 1950

A GOOD SET DESERVES A BICC T/V DOWNLEAD

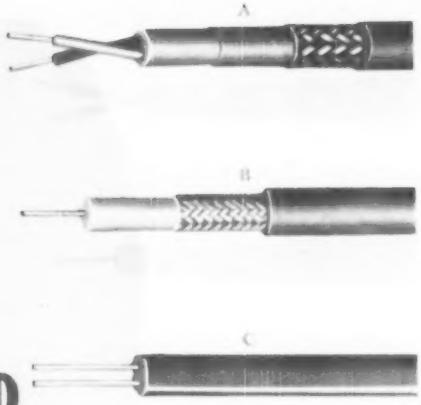

A
80-ohm screened twin cable. T3109

B
71-ohm solid dielectric coaxial cable. T3022

C
80-ohm unscreened twin cable. T3066

Use BICC Downleads for all your T V installations. They're made to close specifications from first grade materials to ensure a long dependable life and precise characteristics. Keep your customers satisfied by giving them the *best possible* results.

Further information on BICC T V Downleads is available in Publication No. 244A T Write to-day for a free copy.

B.I. Callender's **T/V DOWNLEADS**

keep your customers satisfied!

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

AVO

REGD TRADE MARK

Precision
ELECTRICAL TESTING INSTRUMENTS

The "AVO" ELECTRONIC TESTMETER

This instrument, which is an up-to-date example of current instrument practice, has been developed to meet the growing demand for an instrument of laboratory sensitivity built in a robust and portable form, for use in conjunction with electronic and other apparatus where it is imperative that the instrument should present a negligible loading factor upon the circuit under test.

The instrument consists basically of a balanced bridge voltmeter. It incorporates many unique features and a wide set of ranges so that in operation it is as simple to use as a normal multi-range testmeter.

The instrument gives 56 ranges of readings as follows :—

D.C. VOLTS : 2·5mV. to 250V. (Input Resistance 11·0 megohms.)
25mV. to 10,000V. (Input Resistance 110·0 megohms.)

D.C. CURRENT : 0·25μA. to 1 Amp. (250mV. drop on all ranges).

A.C. VOLTS : 0·1V. to 2,500V. R.M.S. up to 2 Mc/s. With diode probe external 0·1V. to 250V. R.M.S. Useful measurements can be made up to 200 Mc/s. the applied voltage being limited to 100V. above 50 Mc/s.

A.C. OUTPUT POWER : 5mW. to 5 watts in 6 different load resistances from 5 to 5,000 ohms.

DECIBELS : —10db. to + 20db.

CAPACITANCE : ·0001μF. to 50μF.

RESISTANCE : 0.2 ohms to 10 megohms.

INSULATION : 0·1 megohm to 1,000 megohms.

The thermionic circuit gives delicate galvanometer sensitivity to a robust moving coil movement, which it is almost impossible to damage by overload. The instrument is quickly set up for any of the various tests to be undertaken, a single range selector switch automatically removing from the circuit any voltages and controls which are not required for the test in question.

Size : 12½in. × 9in. × 5½in.
Weight : 12½lbs.

The instrument operates on A.C. mains, 100 - 130V. and 200 - 250V., 50 - 60 c.s.

PRICE £35

Fully descriptive pamphlet available on application.

Sole Proprietors and Manufacturers

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE · DOUGLAS STREET · LONDON · S.W.1 *Telephone:* VICTORIA 3404/9

E.T.M.3

A

just what we keep on saying—

is drained.—P. G. E.

Women's Voices

ELIZABETH CHRISTINE BROWN suggests that the reception of women's voices is worse than that of men's because they are pitched higher. Surely this is a reflection on the inability of most commercial wire less receivers to reproduce the top frequencies, on which the clarity of voices depends. Given a wireless of adequate performance, I can assure her that women's voices are received as well as men's. It does seem to be the habit of many manufacturers to spend a disproportionately small amount of the cost of a set on the loudspeaker. After all it does make the noise.—R. C. Henderson, Oxford.

Letter to RADIO TIMES *Aug. 12th 1949*

its the

Loudspeaker that **COUNTS!**

REPRODUCERS AND AMPLIFIERS LIMITED
FREDERICK STREET WOLVERHAMPTON ENGLAND
Telephone Wolverhampton 22241 Telegrams "Audio Wolverhampton"

R&A

Where quick Infra-red heating is specified . . .

RADIANT HEATING LTD

CAN HELP YOU A LOT

Radiant Heating Ltd are the makers of gas equipment that is ideally suited to the precision, speed and economy demanded by modern production techniques in the radio, electronic and electrical industries. If you need advice on any problem concerning Heating our Technical Staff will be happy to help you.

Write to:

RADIANT WORKS, 9 BARNSBURY PARK, LONDON, N.1. *Phone: NORth 1677/8*

W.W.1.

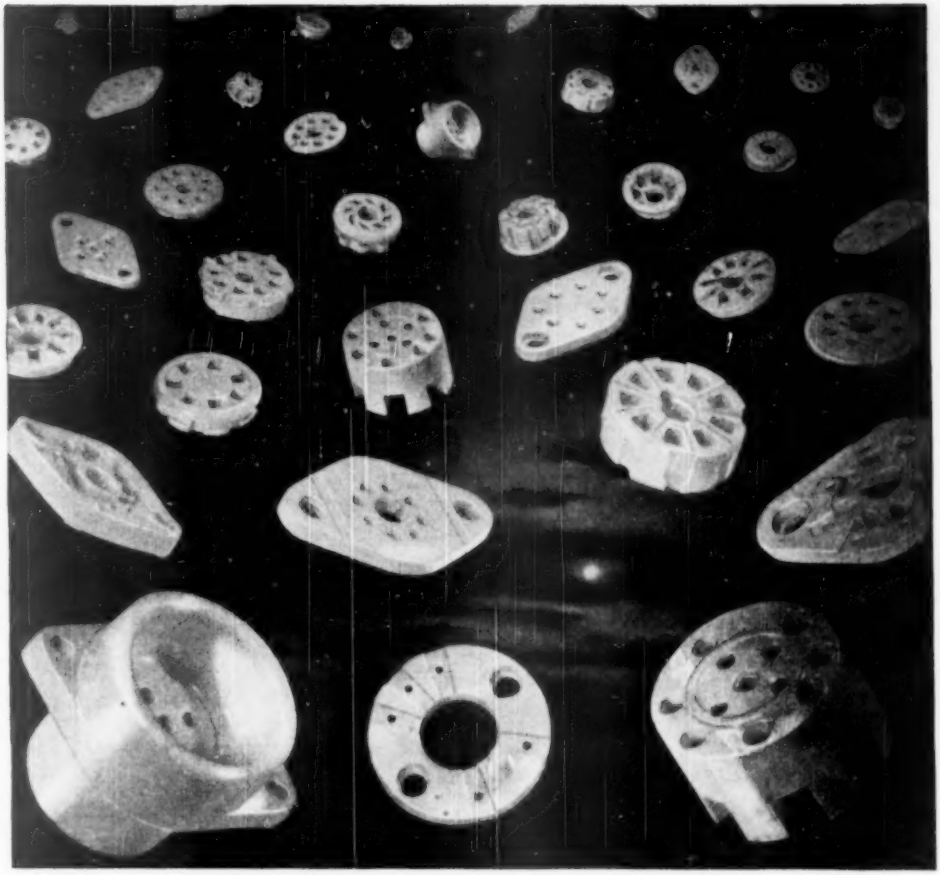

CERAMICS

FOR VALVE HOLDERS

and all radio components

FREQUENTITE – FARADEX – TEMPRADEX

STEATITE & PORCELAIN PRODUCTS LTD.

Stourport on Severn, Worcestershire Telephone: Stourport 111 Telegrams: Steatain, Stourport

R.P.38

ALPHA
BATTERIES

★ *First for quality*
★ *First for performance*
★ *First for reliability*
★ *First for long-life*

Alpha offer a range of batteries for radio and lighting second to none in high quality performance. Remember, too, that amongst the Alpha range of batteries for lighting, is the unique Leak-proof battery which will operate or store in any climate.

ALPHA ACCESSORIES LTD.
SALES OFFICE, GRAMOPHONE BUILDINGS
BLYTH ROAD, HAYES, MIDDLESEX
Telephone: Southall 2468, Ex. 793

SO SMALL–
IT DOES A BIG JOB

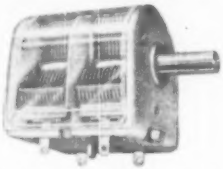

Miniature in Size, but big in performance. *The M.M. 2 Gang Condenser* has frame dimensions of only 1⅛"x1⅛"x1⅛". Complete with dust cover. Cat. No. 4702. PRICE 10/6

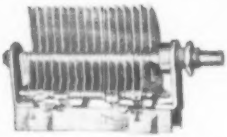

TYPE 604 (illustrated) is a low-loss shortwave condenser suitable for Chassis or one-hole fixing. Brass vanes are soldered to supports and electroplated.

TYPE 603 is a split stator condenser of similar construction.
The S.1 series in both types are particularly suitable for low power transmitters.

PRICES: Type 604 15/3—17/0
Type 603 16/0—17/6

PRECISION COMPONENTS BY

JACKSON
BROS (LONDON) LIMITED
KINGSWAY · WADDON · SURREY
Tel. Croydon 2734-5 Grams. Wireless, Southway, London

An achievement of some magnitude in diminutives

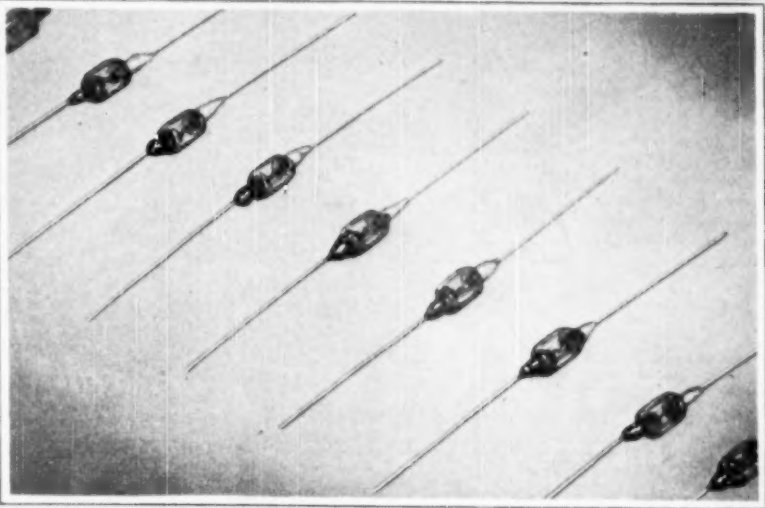

The new G.E.C. Germanium Crystal Rectifiers

Designed for soldering into circuits

1. Provides a high frequency Diode requiring no heating power.
2. Very small in physical size.
3. Of low forward and high reverse impedance.
4. Extremely low shunt capacitance — only 1PF.
5. So constructed as to give a unit of high stability and consistency.
6. Outstanding in its property to resist severe mechanical shock or vibration.
7. Indefinitely long life.

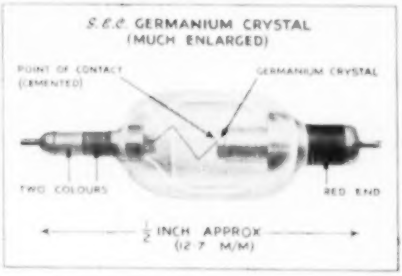

The General Electric Company Ltd. welcomes, and will give sympathetic consideration to enquiries to meet specialised requirements and specific circuit applications. Write and ask for particulars of types available to Osram Valve and Electronics Dept., Magnet House, Kingsway, London, W.C.2.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2.

Photograph by courtesy of Hollick and Taylor Recording Studio Birmingham

From the comprehensive range of Painton faders, types are available to meet all the exacting requirements of modern recording technique. From B.B.C. studio to home recorder you cannot do better than rely upon . . . . . .

Control by PAINTON

Agent in Belgium:
Monsieur Paul Grimmeyke
41, Avenue Jean Stobbaerts,
Bruxelles

PAINTON & CO LTD · KINGSTHORPE NORTHAMPTON

Sit back and enjoy the NEW—

'CONCERT MASTER'!

This latest high fidelity amplifier has all the features which you have asked for. Of impeccable performance, it is of compact size and includes a detachable control panel which is quite unique. It contains no valves, and has no H.T. or L.T. voltages. It is instantly removed by snap fasteners and makes the amplifier eminently suitable for fitting into a cabinet, the main amplifier being placed at the bottom and the control head on its six feet cable can be placed just where you want it. This last word in amplifier design will take high or low output pick-ups and has provision for radio and microphone inputs.

PRICE
£29.10.0
TWO YEARS' GUARANTEE

Write for your copy of our fully illustrated catalogue today!

DEFERRED TERMS AVAILABLE ON ALL MODELS

R.A. TUNING UNIT

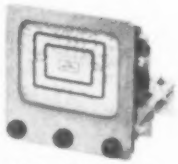

A really fine design with lasting high performance. R.F. stage on all wave bands. High fidelity superhet or T.R.F. performance. Suitable for any amplifier. Price **10 gns.**, plus £2 6 8 tax. With escutcheon plate as shown 5/- extra. (2 years' guarantee).

THE K.1 AMPLIFIER

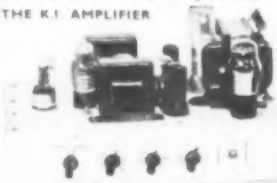

A seven-valve amplifier especially designed for the 'light-weight' high-fidelity type pick-up. Independent bass and treble controls. Price complete, **17 gns.**, or in kit form, **13 gns.**

Blueprint available separately 2/6

THE TRICORNE SPEAKER CHAMBER

For optimum acoustic performance with any good 12-in. speaker. Labyrinth construction, walnut veneered and cross-braced.

Price **11 gns.** plus 20/- deposit (returnable) for crate.

Phone: WESTern 1350

Charles
AMPLIFIERS
(SALES) LTD.

Our equipment can also be seen at
Webb's Radio, Soho St., W.1
University Recording Co., 16, Burleigh Place, Cambridge
Ernest Buchan, 28, Belmont Street, Aberdeen
Farmer & Co., 81 George St., Luton

181 KENSINGTON HIGH STREET LONDON · W.8

FOR THE UTMOST REALISM FROM RECORDS & RADIO

this indicating instrument accuracy

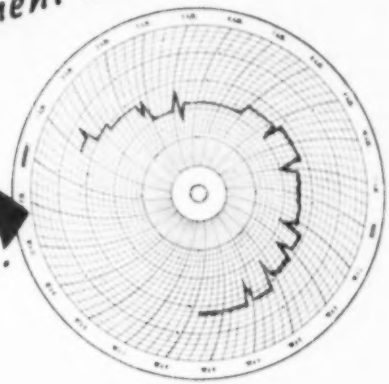

reproduced on this chart . . . .

by the

Fielden

Servograph

Movements available from 50 micro-amps. or 15 millivolts upwards.

Prices (British Isles) from

£65

SERVOGRAPH OPERATES DIRECTLY FROM VERY LIGHT CURRENT SOURCES, consuming but a few Micro-watts for full scale deflection. Its working principle is unique and sets up a new high standard of accuracy and robustness for graphical recording meters. SERVOGRAPH's accuracy is to *BSS.89 for Grade 1 Indicating* Instruments—because its servo-driven pen arm removes all load from the instrument movement, admits a robust and trouble-free pen, and maintains this accuracy with full or empty ink reservoir. Needing no levelling, it operates correctly in any position and can be connected directly to tachometers, thermocouples, resistance thermometers, CO_2 indicators, pH meters and so on, repeating their accuracy on the chart. Equally useful, too, as an ammeter, voltmeter, etc., it may embody a moving iron, moving coil, dynamometer or electrostatic movement.

Please write for technical leaflets 100 M.

FIELDEN (ELECTRONICS) LTD.

FASTON ROAD WYTHENSHAWE MANCHESTER

FIELDEN ELECTRONICS (Australia) PTY. LTD.
409 COLLINS STREET - MELBOURNE - AUSTRALIA

Specialists in Industrial Electronic Equipment

SOUND & VISION KIT

21 Valves. Suitable for 9in., 10in. and 12in. Magnetic Tubes. Less Tube, tube holder and Mask. Chassis all stamped out. State whether for Sutton Coldfield or Alexandra Park. Complete with booklet, instructions, etc. **£31 12s. 6d.** carr. paid.

Pre-Amplifier de Luxe. Consisting of power pack and two R.F.s. Built up and enclosed in case. **£7 12s. 6d.** carr. paid.

MAINS TRANSFORMERS, FULLY INTERLEAVED, SCREENED AND IMPREGNATED. ALL PRIMARIES ARE 200/250 v. Half Shrouded.

MSM63. (Midget) Output 250/0/250v. 60 m/a. 6.3v. at 3 amps. 5v. at 2 amps. ... 15/-
MS63. Output 250/0/250v. 60 m/a. 6.3v. at 3 amps. 5v. at 2 amps. ... 15/6
MS40. Windings as above. 4v. at 4 amps. 4v. at 2 amps. ... 15/6

Output
MS2. 250/0/250v. 80 m/a. ... 17/6
MS30. 300/0/300v. 80 m/a. ... 17/6
MS3. 350/0/350v. 80 m/a. ... 17/6
MS2X. 250/0/250v. 100 m/a. ... 19/6
MS30X. 300/0/300v. 100 m/a. ... 19/6
MS3X. 350/0/350v. 100 m/a. ... 19/6

Fully Shrouded

Output
FSM63. (Midget) Output 250/0/250v. 60 m/a. 6.3v. at 3 amps. 5v. at 2 amps. ... 15/6
FS2. 250/0/250v. 80 m/a. ... 19/6
FS30. 300/0/300v. 80 m/a. ... 19/6
FS3. 350/0/350v. 80 m/a. ... 19/6
FS2X. 250/0/250v. 100 m/a. ... 21/6
FS30X. 300/0/300v. 100 m/a. ... 21/6
FS3X. 350/0/350v. 100 m/a. ... 21/6
All the above have 6.3/4/4v. at 4 amps., 5/4/4v. at 2 amps.
FS43. Output, 425/0/425v. 200 m/a. 6.3v. 4 amps. C.T. 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded ... 42/6
FS50. Output, 450/0/450v. 250 m/a. 6.3v. 2 amps. C.T. 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded ... 62/6
FS30X. Output, 300/0/300v. 80 m/a. 6.3v. 7 amps. 5v. 2 amps. Framed, Flying leads ... 26/6
FS35X. Output, 350/0/350v. 250 m/a. 6.3v. 6 amps. 4v. 8 amps., 4v. 3 amps., 0-2-6.3v. 2 amps. Fully shrouded ... 59/6
FS160X. Output, 350/0/350v. 160 m/a. 6.3v. 6 amps. 5v. 3 amps. Fully shrouded ... 37/6
FS43X. Output, 425/0/425v. 250 m/a. 6.3v. 6 amps. 6.3v. 6 amps. 5v. 3 amps. Fully shrouded ... 57/6
HS6. Output, 250/0/250v. 100 m/a. 6.3v. 6 amps. C.T. 5v. 3 amps. For receiver R1355. Half shrouded ... 24/6
HS150. Output, 350/0/350v. 150 m/a. 6.3v. 3 amps. C.T. 5v. 3 amps. Half shrouded ... 25/9
FJ6. Output, 250/0/250v. 100 m/a. 6.3v. 6 amps. C.T. 5v. 3 amps. Half shrouded ... 25/9
FS120. Output, 350/0/350v. 120 m/a. 6.3v. 2 amps. C.T. 6.3v. 2 amps. C.T. 5v. 3 amp. Fully shrouded ... 27/6
The above have inputs of 200/250v.

FILAMENT TRANSFORMERS

F4. Output, 4v. 2 amps. ... 7/6
F6. Output, 6.3v. 1 amp. ... 7/6
F66. Output, 6.3v. 6 amps. ... 5/3
F6X. Output, 6.3v. 3 amps. ... 5/-
F12. Output, 12.6v. tapped 6.3v. at 3 amps. ... 15/6
F24. Output, 24v. tapped 12v. at 3 amps. ... 21/6
F12 and F24 framed with Flying Leads.
FU6. Output, 0-2-4-5-6.3v. at 2 amps. ... 9/-
F29. Output, 0-2-4-5-6.3v. at 4 amps. ... 15/-
FU6 and F29 clamped with Flying Leads.
F5. Output, 6.3v. at 10 amps. 5v. at 10 amps. 12.6v. at 5 amps. 10v. at 5 amps. ... 31/6
F6/4. Output, four at 6.3v. tapped at 5v. at 5 amps. per winding, giving by suitable series and parallel connections 24v. at 5 amp., 20v. at 5 amp., 18v. at 5 amp., 15v. at 5 amp., 12.6v. at 10 amp., 10v. at 10 amp., 6.3v. at 20 amp., 5v. at 20 amp. ... 47/6
F5 and F6/4 framed with Flying Leads.

OUTPUT TRANSFORMERS

MOP1. Ratios 26, 46, 56, 66, 90, 120-1 50 m/a. max. current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel and clamped ... each 5/-
OP1. Midget Power Pentode, ratios 30, 60, 90-1, 40 m/a. Secondary 2/3 ohms. ... each 3/2
OP2. Midget Pentode, ratios 45-1. Secondary 2/3 ohms. 40 m/a. ... per doz. 33/-
OP10. 10/15 watts output. 20 ratios on Full and Half primary ... 16/3
OP30. 30 watts output. 20 ratios on Full and Half primary ... 23/9
Williamson's O.P. Transformer to Author's specification ... £3/12/6
Chokes for Williamson's Amplifier. 30H at 20 m/a., 15/6; 10H at 150 m/a. ... 29/6
C.W.O. (add 1/- in £ for carriage), all orders over £2 carriage paid.

H. ASHWORTH
(Dept. W.W.)
676 GT. HORTON ROAD
BRADFORD, YORKS.

SDK.22G

The best
HIGH
and
LOW

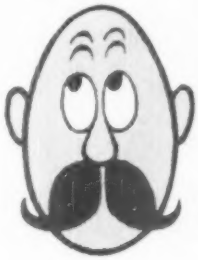

Exide AND **Drydex**
LOW TENSION ACCUMULATORS HIGH TENSION BATTERIES
for better battery radio reception

ISSUED BY CHLORIDE BATTERIES LIMITED

DIE PRESSED *Ceramics* FOR GENERAL ELECTRICAL PURPOSES

Die Pressed Ceramics for the hundred-and-one problems of the Electrical Industry are a speciality of the 'T.T.' organisation and as such you are assured of the keenest co-operation to your individual requirements.

T.T. Ceramics, by reason of their close tolerance and general accuracy save your assembler's time and minimise breakages, yet in spite of their high quality, are by reason of our experience still supplied at competitive prices.

Our technicians are 'At your Service.'

Taylor Tunnicliff & Co LTD

Head Office: EASTWOOD HANLEY STAFFS *Stoke-on-Trent* 5272-4

London: 125 HIGH HOLBORN, W.C.1. *Holborn* 1951.

Factories at: Hanley, Stone and Longton, Staffs.

The better they are made

the more outstanding the results

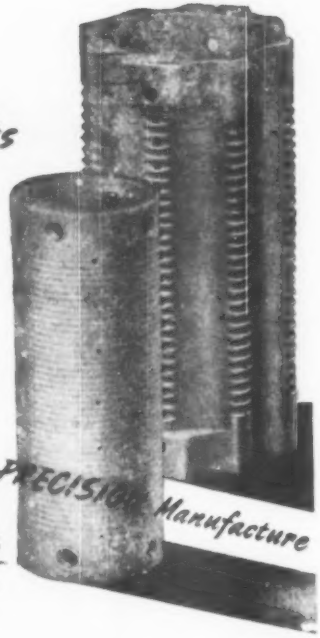

MADE IN THREE PRINCIPAL MATERIALS.

FREQUELEX. An insulating material of low Dielectric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX. A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX. A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

Bullers

Specialize in PRECISION Manufacture

BULLERS LOW LOSS CERAMICS

BULLERS LTD., 6, Laurence Pountney Hill, London, E.C.4. Phone: Mansion House 9971 (3 lines)
Telegrams: "Bullers, Cannon, London"

VALVES For SPECIAL PURPOSES

20A3

Miniature tetrode thyratron

The 20A3 is a miniature indirectly heated tetrode thyratron designed for use in relay application. It has a high control ratio, low grid/anode capacitance and passes a very low grid current. Used in conjunction with a high resistance circuit the 20A3 can be operated directly from a high-vacuum photo-cell.

RATING	
Heater Voltage	6.3 volts
Heater Current	0.6 amps.
Arc Voltage Drop	8 volts
Max. Forward Anode Voltage	650 volts
Maximum Peak Inverse Anode Voltage	1300 volts
Max. Shield Grid Voltage	—100 volts
Max. Control Grid Voltage	—100 volts
Max. Peak Cathode Current	500mA
Max. Average Cathode Current	100 mA
Control Grid Circuit Resistance	0.01—10.0 MΩ
Control Ratio G1	250*
,, ,, G2	1000†

BASE B7G MINIATURE

LIST PRICE £1 . 10s. 0d. (provisional)

NOTE:—All maximum ratings are absolute values not design centres. Heater to cathode voltage must never exceed 25 volts peak. The heater must be switched on for a minimum of 10 seconds before the anode voltage is applied.

*$V_{g2}=0$; $R_{g1}=0$
†$V_{g1}=0$; $R_{g1}=0$; $R_{g2}=0$

EDISWAN

MAZDA

RADIO VALVES AND CATHODE RAY TUBES

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2

The ANTIFERENCE "Antex"

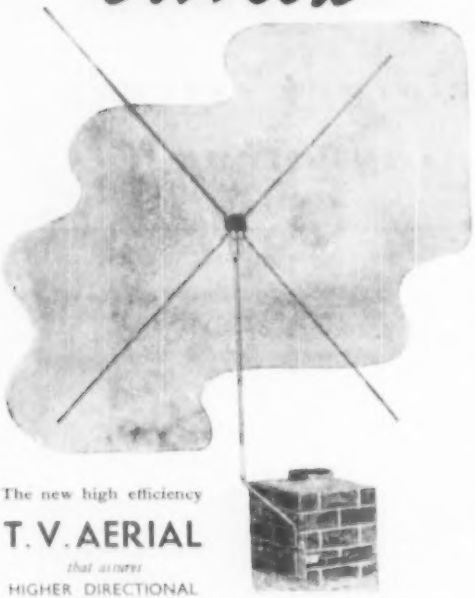

The new high efficiency

T.V. AERIAL

that assures

HIGHER DIRECTIONAL PROPERTIES

*

STRONGER SIGNALS

*

GREATER REDUCTION OF INTERFERENCE ON SOUND AND VISION

*

The "Antex" sets an entirely new and higher standard in television reception. An increase of gain approximately 2 db is obtained when compared with a standard 'H' array. Ask your dealer for full particulars.

MODEL XL for London
,, **XL/B** for Birmingham
including 7ft. mast and chimney lashing equipment as illustrated **£3.15.0**

MODEL XW for London
,, **XW/B** for Birmingham
including 7ft. mast and wall m'ting bracket **£3.0.0**

BRIEF TECHNICAL DATA

Input impedance	70-80 ohms
Forward gain	5.0 db
Back/Front Ratio	22.0 db
Weight (less mounting)	1½ lbs.

Better performance at less cost

ANTIFERENCE LIMITED · 67 BRYANSTON STREET · LONDON W.1

Stop worrying about that metal work problem—there's always Ritherdon's!

This old established firm make Instrument Cases, Amplifier Racks, Fuse Boxes, Busbar Chambers, etc. to customers' specifications.

Experience has taught them that it costs no more to work to individual requirements than to produce standard lines. Bring that problem to Ritherdon's, all enquiries are welcome and will receive prompt attention.

RITHERDON & CO LTD

LORNE STREET, DARWEN, LANCS. Phone: Darwen 1020

Specialists in fine sheet metal work since 1895.

FOR QUICK DELIVERY
AT
REASONABLE PRICES
OF
RADIO & ELECTRONIC PRODUCTS
(Wholesale Only)

Write or phone:—

S. Szymanski
(pronounced SHE-MAN-SKEE)

ELECTRONIC ENGINEER & STOCKIST
95 STRODES CRESCENT
STAINES, MIDDLESEX

Staines 3971

VALVES are our speciality—Probably the Largest Actual Stockist in England

EXPORT ENQUIRIES WELCOMED

CINTEL

TIME CHANGES...
accurately measured

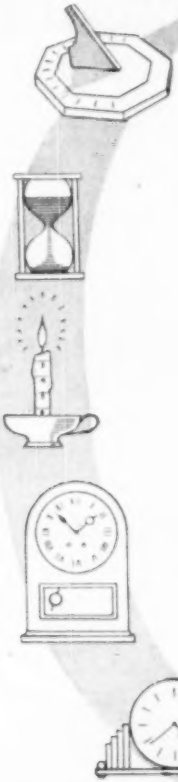

The 'CINTEL' Microsecond Counter Chronometer

Will measure very short time intervals in the range 1 Microsecond to 1 Second with an accuracy of $\pm 1\mu S$, $\pm 0.005\%$ and 10 Microseconds to 10 seconds with an accuracy of $\pm 10\mu S$, $\pm 0.005\%$.

The instrument has many other applications apart from Time measurement including Random Counting, Frequency Measurement, Frequency Division etc.

For further particulars please write for Leaflet No. MCC1/1.

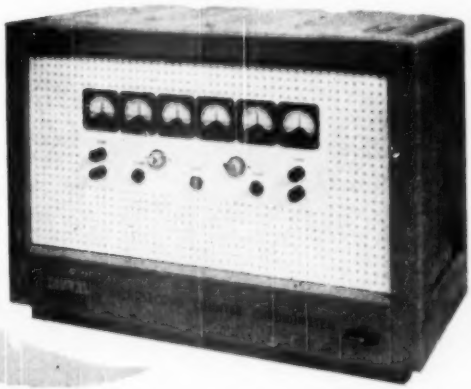

BIF 1950
MAY 8-19
EARLS COURT & OLYMPIA
SEE OUR EXHIBIT
OLYMPIA
Stand C.16

CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

FOREMOST IN THE MANUFACTURE OF

• Counters & Chronometers • Metal Detectors • Oscilloscopes • Photo-Electric Cells • Cathode Ray Tubes • Geiger-Muller Tubes • Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S·E·26

Telephone: HITher Green 4600

Northern Agents:
F. C. ROBINSON & PARTNERS LTD
287 Deansgate, Manchester 3

Scottish Agents:
ATKINS, ROBERTSON & WHITEFORD LTD
100 Torrisdale Street, Glasgow, S.2

CINTEL
REGISTERED TRADE MARK

a step in the right direction

In this new Ambassador Console we have put quality reproduction before anything else. Its six valve A.C. superhet circuit possesses unusual features which contribute to the receiver's most outstanding fidelity of reproduction. The response of the whole L.F. system to the L.S. terminals is flat within 1 D.B. limits from 50—12,000 c.p.s. Push-pull output via a high quality output transformer feeds a 12" high flux density loudspeaker.

PRICE £36 · 0 · 0 TAX PAID

DESIGNED AND PRODUCED BY—

AMBASSADOR OF GREAT BRITAIN REGD

RADIO WORKS, HUTCHINSON LANE, BRIGHOUSE, YORKS

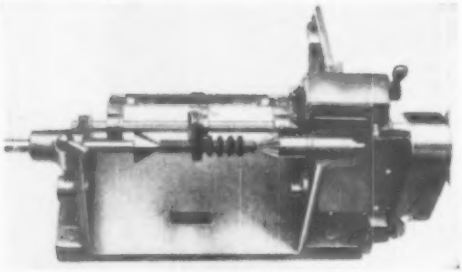

MODEL WX

AUTOMATIC COIL WINDING MACHINES

AND HAND WINDING MACHINES

Wave winding machines for single or multiple coils 1/16" to ¾" wide for power drive.

SOLE AGENTS ABROAD

K. G. Khosla & Co., 22 School Lane, New Delhi, India.
Etablts Octave Houart, 14, Quai de l'Industrie, Sclessin-lez-Liege.
J. P. Fielding Co. (Canada), P.O. Box 35, Station "H" Toronto, Canada.

R. H. Cunningham P.T.Y. Ltd., 61 Stanhope Street, Malvern, Victoria, Australia.

ETA TOOL CO (LEICESTER) LTD

29a, WELFORD ROAD, LEICESTER

Phone—5186

Three new arrivals . . .

Baby—Minor—Major —all doing fine

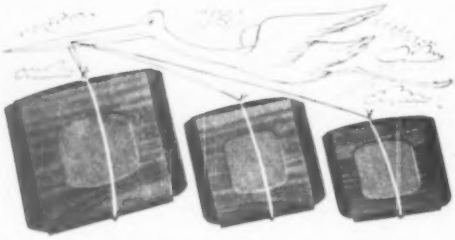

Another step forward in Extension Speaker Design is taken with these new models. Bafflette Baby 39/6, Bafflette Minor 52/6, Bafflette Major 65/-, all fitted with out of sight volume control. Finished in walnut veneers.

Transformers extra. Baby and Minor 6/-, Major, 8/6.

Supplies are now reaching distributors.

Richard Allan

RADIO LTD · BAFFLETTE HOUSE · BATLEY · YORKS

Spire Speed Nuts cut assembly time to a minimum; they're so easy and quick to fix, even in really difficult blind assemblies and awkward locations. They will not "clog" with paint or enamel. They eliminate a retapping operation. And once home, Spire Speed Nuts lock tight as long as they're wanted (regardless of any number of bolt removals) their unique double-spring action sees to that. If you're worrying right now over a fastening problem, why not send for more news of Spire — fastest thing in fastenings.

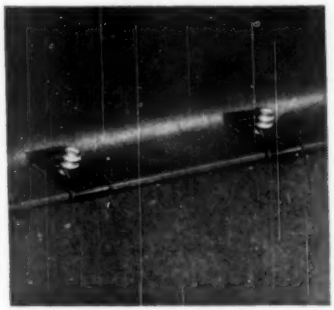

Spire
Real
SPEED NUTS

The SNU type is self-retaining, pushed into position by thumb pressure. Expensive riveting, welding or clinching operations are eliminated. If the minute gap between assembled parts is not desirable for certain applications, the SNJ type ensures a close seal.

THAT'S FIXED THAT

Enquiries to
Simmonds Aerocessories Ltd., Byron House, 7-8-9, St. James' Street, London, S.W.1.
HEAD OFFICE AND WORKS: TREFOREST, GLAMORGAN

54

Simon

Can you give Service?

- Outdoor functions in the coming Summer months will provide many opportunities for the recording engineer.
- How many times have you refused assignments because there was no available power supply at the site? A portable power supply unit will make your service really mobile and independent.
- A converter need not be an expensive, bulky and noisy piece of machinery. The unit illustrated here has been designed expressly for the battery operation of recording equipment and all applications demanding a readily portable and stable source of A.C. power.

VC12 CONVERTER

Housed in steel case finished in blue stove enamel and fitted with chrome carrying handles. Equipped with voltmeter and output frequency control.

Input:	12 volts D.C.
Output:	230 volts, 50 cycles.
Rating:	150 watts
Dimensions:	13in. x 6½in. x 8in.
Weight:	26lb.

SIMON SOUND SERVICE

Recorder House, 48 50 George Street, Portman Square, London, W.1, England

Telephone: Welbeck 2371 (4 lines) Telegrams: Simsale, Wesdo, London Cables: Simsale, London

High Fidelity Reproduction.

TYPE "K"

The S. G. Brown Type "K" Moving Coil headphones, with the following outstanding characteristics, supply that High Fidelity Reproduction demanded for DX work, monitoring and laboratory purposes, etc.

CHARACTERISTICS.

D.C. RESISTANCE. 47 Ohms.

IMPEDANCE 52 Ohms at 1,000 c.p.s.

SENSITIVITY, 1.2 x 10⁻⁷ Watts at 1kc. = .0702 Dyns/cm

Descriptive literature on request

PRICE £5.5.0 PER PAIR

Your Local Dealer can supply

For details of other S. G. Brown Headphones (prices from 30/- to 77/6) write for illustrated Brochure "W.W."

HEADPHONES WHICH UPHOLD BRITISH PRESTIGE

Telephone: Watford 7241

S.G.Brown, Ltd.

SHAKESPEARE STREET, WATFORD, HERTS.

IDEAL BARGAINS FOR CONSTRUCTORS

Assemble your own

Table Electric Gramophone or Record Player.

CABINETS

Beautifully polished Walnut with Rumanian Birch grille and feet. Lid interior felted. Top plate cut out for gramophone unit. Recessed escutcheon plate fitted in side for volume control. Access trapdoor in base. Rubber non-scratch feet. Sub-baffle for 6½in. loudspeaker. External 16 x 14 x 12in. deep. Internal 15 x 13 x 7in. below top plate, 4in. above to lid. Solid and finely built.

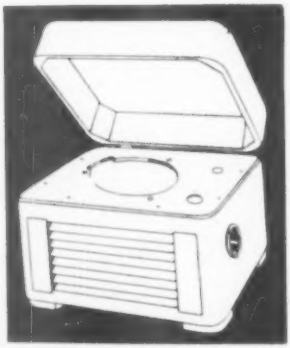

£3. 10. 0.

Each, incl. Purchase Tax. Packing and carriage 7/-

GRAMOPHONE UNITS for top plate. Constant speed. Modern high output, perfect tracking angle pickup. Superb quality. A.C. Mains. £3/10/8, including Purchase Tax.

3w AMPLIFIER KITS On chassis 11½in. x 4in. Less valves £3/15/-

6½in. high Flux **LOUDSPEAKERS 17/6**

GROUP HEARING AIDS We designed and installed the famous equipment at the National Institute for the Deaf (see "W.W." Sept., 1948), and those of many Institutes and Public Buildings. Consult us for the BEST and CHEAPEST communal hearing aids.

N. MIERS & CO. LTD., Telephone: EUSton, 7515.

115, Gower Street, London, W.C.1.

S.A. 3848

SEI serves

THE INSTRUMENT MANUFACTURER

PHOTOCELLS

Illustrated here are three standard types, but S. E. I. Photocells can be supplied mounted or unmounted in other sizes to meet special individual specifications.

Make sure you always use S. E. I. Photocells.

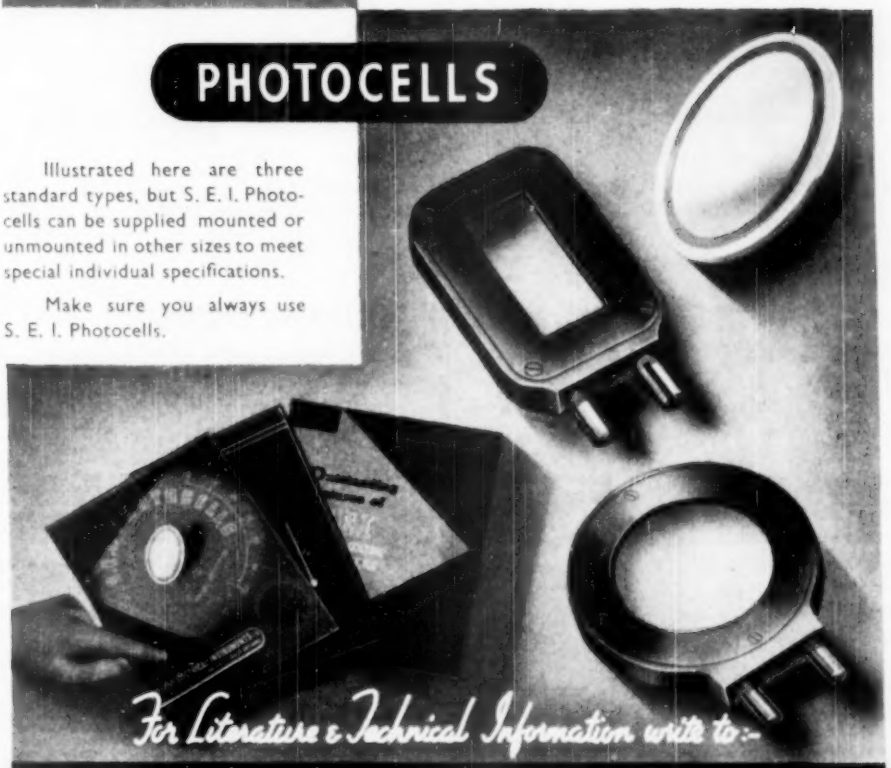

For Literature & Technical Information write to:-

SALFORD ELECTRICAL INSTRUMENTS LTD.

PEEL WORKS · SILK STREET · SALFORD 3 · LANCS · ENGLAND

A subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

A CAPACITOR...

Actual photograph

for the tightest of TIGHT CORNERS

TYPE W99 MOULDED METALLISED PAPER

(HUNT'S PATENT)

STANDARD DIMENSIONS
3/16" dia. x 7/16" long

RANGES 150v D.C. : 0.004uF to 0.01uF
350v D.C. : 50 pF to 3000 pF

(Additional capacitances at higher working voltages will be available shortly).

TEMP. RANGE: −15° C to + 71° C.
I.R. Better than 20,000 megohms.
SELF-HEALING

TRULY MINIATURE. There are more than two hundred Type W99 Capacitors piled on this standard match box! Another new development by Hunts to meet the increasing needs of designers and manufacturers for a quality capacitor for use in light weight, compact equipment employing miniature valves and for T.V. equipment.

SPECIAL NOTE. Now available in the W99 range and in the same standard dimensions—1000 pF 300 v. A.C. wkg. at 71° C. As a decoupling capacitor, this is suitable for a frequency range of 50 c.p.s. to 100 mc's

Full details of all Hunts types, samples and advice on any capacitor application, gladly supplied on request.

REGISTERED TRADE HUNTS CAPACITORS MARK

THE TRADE MARK OF RELIABILITY

DRY ELECTROLYTICS · FOIL AND PAPER · METALLISED PAPER · STACKED AND SILVERED MICAS · ETC.

A. H. HUNT LTD., WANDSWORTH, LONDON, S.W.18 TELEPHONE: BATTERSEA 3131 ESTD. 1901

Instruments for Research and Industry

Model 44 SUBSTANDARD

MULTI-RANGE METER

A self-contained precision instrument for general laboratory use and for calibrating first grade single or multi-range meters. The accuracy on the 44 range is **Substandard** on D.C. and within ± 0.5% on A.C.

★ *These meters are made with the greatest care and have been supplied for a number of years to the leading laboratories at home and abroad.*

ELECTRONIC INSTRUMENTS LTD.
17, PARADISE ROAD · RICHMOND · SURREY · ENGLAND

ICS

HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following:

Complete Radio Engineering · Radio Service Engineers · Radio Service and Sales · Advanced Short-Wave Radio · Elementary Electronics, Radar and Radio · Television Technology

And the following Radio Examinations:

British Institution of Radio Engineers · P.M.G. Certificates for Wireless Operators · City and Guilds Telecommunications · Wireless Operators and Wireless Mechanics, R.A.F.

Write today for our FREE "**Radio**" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need of and the means of instruction.

International CORRESPONDENCE SCHOOLS

Dept. W.L.18, International Buildings, Kingsway, London, W.C.2

MORGANITE

The Deaf Aid instrument illustrated is by Amplivox, Ltd.

New Midget TYPE D.A. POTENTIOMETERS
SUITABLE FOR ALL DEAF AID AND MIDGET APPLICATIONS

This Potentiometer is available with two sizes of knob, with or without cam-operated Single Pole Switch, and has the usual low noise track as in our larger types of controls. The power dissipation is $\frac{1}{10}$ watt when uniformly loaded; sealing is essentially dust-proof; the silver-plated tags provide easy soldering; and single nut mounting is a feature. The switch is designed for battery operation up to $\frac{10 \text{ volts, } \frac{1}{4} \text{ amp.}}{150 \text{ volts, } 25 \text{ milliamps.}}$ and the contact resistance is less than ·05 ohms. Switch insulation is over 100 megohms at 100 volts. The larger of the Control Knobs is available in black only, and the smaller knob in black or coloured (red and ivory standard). Other colours to B.S.I. standard, can be supplied by arrangement. (A leaflet giving fuller details, together with scale diagrams of both midget sizes will be sent on request.)

Dimensions shown in Black on White apply to the smaller knob.

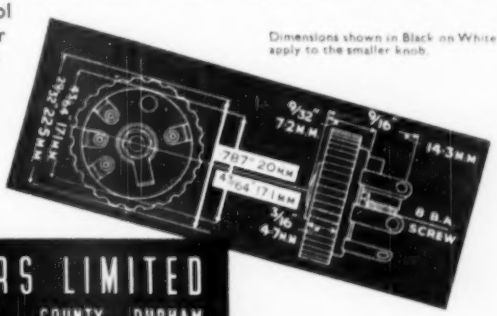

MORGANITE RESISTORS LIMITED

BEDE TRADING ESTATE, JARROW, COUNTY DURHAM.

TELEPHONE: JARROW 67136 TELEGRAMS: "MORGANITE" JARROW.

Wharfedale

LOUD SPEAKER W.12

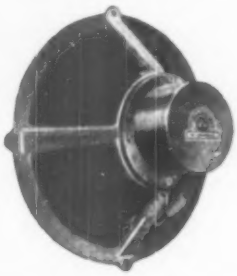

Die Cast Non-resonant Chassis with accurate rear suspension. Impedance, 15 ohms. Diameter, 12". Weight, 11½ lbs. Peak input 15 watts. 13,000 lines flux density. **Price 140/-.**

Now fitted with new type of cone with improved H.F. response. Available with cloth surround, type W.12/CS, at 150/- for domestic use and reflex loading.

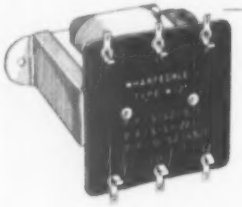

W.12 TRANSFORMER

Designed for use with speakers up to 15 ohms impedance where the output does not exceed 10 watts.

Ratios: 45, 22 and 15 to 1 all centre tapped. Max. D.C. 80 m/amps:
Inductance 50 Henrys, no D.C.
Inductance 5 Henrys, 75 m/a.
Leakage Induction .07 Henry.

Weight 2 lbs. Price 21/-. *Special Ratios to order at 4/- extra.*

Made and Guaranteed by

WHARFEDALE WIRELESS WORKS
BRADFORD ROAD, IDLE, BRADFORD

'Phone: IDLE 461 'Grams: "WHARFDEL, IDLE, BRADFORD"

M.R. SUPPLIES Ltd

(Established 1935)

Selected material only—full and fair descriptions—all prices nett.

VOLTAGE CHANGING TRANSFORMERS (portable). 100/110 v. 200/240 v. (110 v. taps) and vice versa, auto wound, loading 1.35 kva., in steel cabinet 9½" × 8" × 8", with carrying handle. Just right for mobile cine work. Exceptional offer **£4 15/-** (dis. 2).

PUBLIC ADDRESS SPEAKERS. Real opportunity for brand new G.E.C. model 1488 10 watt Pressure Units, P.M. model, 15 ohms, with built-in line transformer in weatherproof casing. **£6** model up only **65/-** (dis. 1/6). Or complete with all metal disc. Projector Horn **£5 12 6**, or with 42in all metal true exponential horn with non-hygroscopic fibre. Complete speakers carr. paid England and Wales (2 extra Scotland and Ireland).

STEEL TRIPODS to suit all P.A. Speakers. Well-known as the best type of P.A. tripod, strong and rigid under all weather conditions. Extend to 10 feet with ample height selection. **55/-** (dis. 5/-).

TELEPHONE SETS. Type 11 Mk. III with semi-improved Handset—**no battery required.** Magneto ringing compactly housed in metal case with hinged lid (8½ × 6½ × 6½ approx.). Easily installed—two wire connection from one set to the other—an ideal outfit and a sensational bargain. **21/-** per set (dis. 1/6) or the pair for **39/6** (dis. 3/-).

GEARED MAINS MOTORS (Squirrel induction) 220/240 v. A.C. Size 7in. long by 4in. dia. (approx.) with 2½ gearbox fitted giving final shaft speed of 200 r.p.m. at great torque. These are substantially built to a precise standard for continuous duty and full load starting. Reversible. Supplied with capacitor and diagram (new). **£4 10/-** (dis. 1/6).

"FUZIT" WIRE JOINTERS apart from their normal use the value of this offer lies in the New portable transformer. Price 200/250 v., use 240 volts 5 amps (approx.). The complete equipment with carbon-electrode Hand Tool for electrically welding wire, copper or resistance, 50/56 S.W.G. (Last £6/6/-). Brand new, with instructions. **32/6** (dis. 1/6).

THERMOSTATS, water cooled, 60/70 deg. F. "Cuthy" range 50/70 deg. F., differential 4 deg., capacity 15 amps. **25/-** (dis. 1/-). "Tellington," range 40/80 deg. F., diff. 4 deg., capacity 10 amps. **30/6.** Capillary type (ex Govt. new). Range 55/70 deg. F. Price (no compensator) 30/- long, capillary tube 39/- long, **17/6** (dis. 1/-).

HOT-WIRE AMMETERS for L.F. or L.F. currents. 50/-, 60/-. Brand new Admiralty instruments with magnetic damping and fuse. Two models, 0/1.2 amp. and 0/3 amps. Either **7/6** (packing 1/6).

HIGH-DUTY VANE PUMPS. Made to top specification in Bronze throughout for Admiralty. Power required to drive approx. 1 h.p. Will pump up to 5,000 g.p.h. Head 75ft. Suction 27ft. **£6.** Industrial concerns will be supplied with photograph giving dimensions on request. Brand new. **£6 15/-** (dis. 1/6). Also the reliable **STUART CENTRIFUGAL PUMPS** from stock. Self contained Motor/Pump Units for 220/250 v. A.C. (No. 10 250 g.p.h.) **£5 15/-** (dis. 1/6). No. 12 3,000 g.p.h. **£8 10/-** (dis. 1/6).

HIGH DUTY SELENIUM RECTIFIERS. Industrial formal sealed type. D.C. delivery up to 10 volts for amps. full wave (List price £5 each). Brand new. **72/6** each (no. 2/-). A pair of these in bridge will deliver up to 20 volts **10 amps.** full wave. **£7 the pair** (carr. 2/6).

OUR NEW MULTI-PURPOSE TRANSFORMER. Primary tapped 200/220/240 v. Secondary tapped 0/6/12/20/30 v. 2 amps. This ingenious transformer provides the following secondary voltages: 6, 7, 8, 9, 10, 12, 14, 16, 18, 20 and 30 at 2 amps., with further adjustment by side-tailing primary. **27/6** (dis. 1/-).

Further details of any item, with sketch or photograph sent on receipt of stamp. The diligent and enthusiastic service.

M. R. SUPPLIES Ltd., 68, New Oxford Street, London W.C.1

Telephone MUSeum 2958

PLEASE tell us of OTHER applications

Drayton 'Hydroflex' Metal Bellows are an essential component part in Automatic coolant regulation . . Movement for pressure change . . Packless gland to seal spindle in high vacuo . Reservoir to accept liquid expansion . . Dashpot or delay device . . Barometric measurement or control . . Pressurised couplings where vibration or movement is present . . Dust seal to prevent ingress of dirt . . pressure reducing valves . . Hydraulic transmission . . Distance thermostatic control . . Low torque flexible coupling . . Pressure sealed rocking movement . . Pressurised rotating shaft seals . . Aircraft pressurised cabin control . . Refrigeration expansion valves . . Thermostatic Steam Traps . . Pressure amplifiers . . Differential pressure measurements . . Thermostatic operation of louvre or damper.

for HYDRAULICALLY FORMED

Seamless, one-piece, metal bellows combining the properties of a compression spring able to withstand repeated flexing, a packless gland and a container which can be hermetically sealed. Made by a process unique in this country, they are tough, resilient, with a uniformity of life, performance and reliability in operation unobtainable by any other method.

Drayton METAL BELLOWS

Write for List No. N800-1 DRAYTON REGULATOR & INSTRUMENT CO. LTD., WEST DRAYTON, MIDDLESEX. West Drayton 2661 B.8

designed ....

with your specific needs in mind

MODEL 1035

The Cossor general purpose Oscillograph is designed and built by electronic engineers who are themselves familiar with the every-day problems which technicians have to face. The instrument consists of a Double Beam Tube operated at 2kV., a Time Base, Y Deflection Amplifiers and Internal Power Supplies. The 90mm. screen is flat, and traces are presented over the full area. Signals are normally fed through the Amplifiers, and the calibrated Y-Shift controls provide a measurement of the applied voltages. The Time Base operates repetitively, or by external trigger (for single stroke operation), or at trigger pulse repetition frequency for continuous scanning. A calibrated X-Shift Control is provided for the measurement of Time.

Model 1428 CAMERA

Specially developed for use with Cossor Oscillographs, it provides the simplest means of recording stationary or non-recurrent waveforms and slow transients by the moving film method on standard perforated 35 mm. film or paper. Of robust construction, it has provision for power drive by the Cossor Three-Speed Motor Attachment, Model 1429.

COSSOR

Double Beam OSCILLOGRAPH

Further details obtainable on application to:—

A. C. COSSOR LTD., INSTRUMENT DIVISION, HIGHBURY, LONDON, N.5

THE RADIO TELEPHONE YOU CAN TUCK UNDER THE DASH

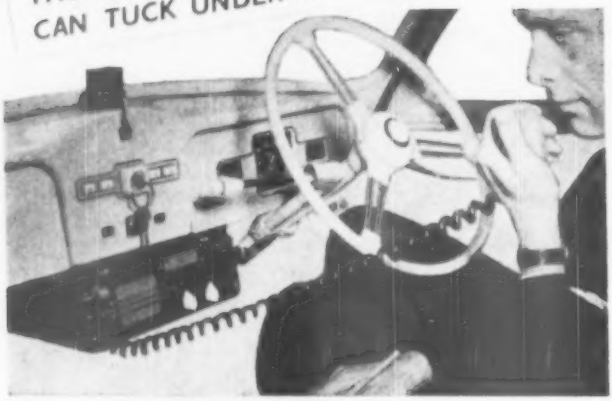

B.C.C. V.H.F.

RADIO TELEPHONE EQUIPMENT

The B.C.C. Mobile Radio-Telephone illustrated here will give two-way communication with the Fixed Station up to a distance of 25 miles or with the portable Pack-set up to 5 miles.

This B.C.C. equipment sets a new standard in V.H.F. Communications Technique and has been approved by the G.P.O. The complete range consists of:

Fixed Stations	Models L111 & H111
Mobiles	Models L67 & H67
Pack Sets	Models L45V & H45V
Hand Portables	Models L45AV & H45AV

This equipment can be supplied to cover any spot frequency in the 75-100 Mc/s or 150-185 Mc/s bands.

Write now for full details and outstanding features of this remarkable equipment.

NOTE THESE FEATURES

Size T/R. 11½in. × 8in. × 4in. (30 cm × 21 cm × 10 cm.) Power Pack 8in. × 5½in. × 3½in. (21 cm. × 14 cm. × 8 cm.) Weight T/R 15½ lbs. (7kg.), Power Pack 9½ lbs. (4.2kg.)

The Transceiver is easily installed below the instrument panel with the small power pack in any convenient place. The remarkably low battery drain permits connection of the set to the car batteries, obviating the cost and weight of auxiliary accumulators or larger dynamo.

BCC

BRITISH COMMUNICATIONS CORPORATION LTD. Gordon Avenue, Stanmore, Middlesex. Tel. GRImsdyke 1455

DESIGNERS — MANUFACTURERS — AMATEURS —

For EFFICIENCY & RELIABILITY INSIST on —

'Cyldon' VARIABLE CAPACITORS

All standard laws, capacity ranges, & voltages up to 15kV.

AIR-SPACED TRIMMERS

MICA DIELECTRIC COMPRESSION TRIMMERS

VARIABLE TRANSMITTING CAPACITORS

SYDNEY S. BIRD & Sons, Ltd.
Cambridge Arterial Rd., Enfield, Middx.
Phone: Enfield 2071-2

TRANSFORMERS AND CHOKES

SPECIALLY DESIGNED FOR ALL ELECTRONIC EQUIPMENT

SOUND CONSTRUCTION — EFFICIENT DESIGN

INDUSTRIAL TYPES UP TO 25 K.V.A.

STEWART TRANSFORMERS Ltd.
1021 FINCHLEY RD., LONDON, N.W.11
Tel.: SPEdwell 3006 and 3533

Mullard

REVIEW OF NEW AND CURRENT VALVES

MULLARD MINIATURES. The Mullard range of miniature valves on the B7G (7-pin button) base includes both mains ("D") and battery ("E") types, and meets most requirements for miniature telecommunication receivers, industrial electronic equipment and light-weight miniature measuring instruments. The present range includes the following :—

EY91 Half-wave Rectifier
EC91 V.H.F. Grounded-grid Triode
EF91 High Slope, Sharp Cut-off R.F. Pentode (6AM6)
EF92 Vari-mu, R.F. or I.F. Pentode
EAC91 Diode Triode for frequency-changing up to 300 Mc/s
EB91 Screened Double Diode (6AL5) (separate cathodes)
EL91 Output Pentode (6AM5) (1.4W Output)
ECC91 V.H.F. Double Triode (6J6) (physical common cathode)
DK91 Vari-mu Heptode Frequency Changer (1R5)
DF91 Vari-mu R.F. or I.F. Pentode (1T4)
DF92 Sharp Cut-off R.F. Pentode
DAF91 Single Diode Pentode (1S5)
DL92 Output Pentode (3S4) (0.27W Output)
DL93 A.F. or R.F. Output Pentode (3A4)
DL94 Output Pentode (3V4) (0.27W Output)
DA90 R.F. Diode (1A3)
DCC90 R.F. Double Triode (3A5)
2D21 Gas-filled Tetrode (Vh—6.3V)

A RANGE OF INDUSTRIAL PHOTOCELLS. The Mullard range of all-glass photocells finds a particularly wide range of applications in industry and research. The types with caesium/silver-oxide cathodes (type C), have a high sensitivity to incandescent light and near infra-red radiation and are particularly recommended for applications where a high output is required. For colour matching and photometric applications, photocells with caesium/antimony cathodes (type A) are available, with a particularly high sensitivity to daylight and radiation throughout the visible colour spectrum. The end-view photocell 58CV, is intended for use in compact photometric units where conservation of space is of utmost importance.

No.	Type	Cathode Surface	Base	Sensitivity (μA/l)
20CV	Vacuum	C	B8G	25
20CG	Gas-filled	C	B8G	150
90CV	Vacuum	C	B7G	20
90CG	Gas-filled	C	B7G	125
20AV	Vacuum	A	B8G	45
90AV	Vacuum	A	B7G	45
58CV	Vacuum	C	Wire-in	15
58CG	Gas-filled	C	Wire-in	85

MULLARD DISC-SEAL TRIODES FOR U.H.F.

For applications such as U.H.F. links, local oscillators, and wide band applications such as multi-channel communication systems, radar altimeters, etc., the use of frequencies up to 1500Mc/s or even 3000Mc/s is often required. The Mullard Disc-Seal Triodes have been designed specifically for such purposes.

In the ME1001, adequate cooling and low inductance are combined in the design of the anode and grid discs to give an anode dissipation of 10 watts and an upper frequency limit (as an oscillator) of 3750-3500Mc/s (8-8.5cm).

The ME1003 is basically similar in design to the ME1001, but the larger electrodes permit an anode dissipation of 25 watts. However, the larger clearances necessary to obtain this value, limit the upper frequency to 2500Mc/s.

PRINCIPAL CHARACTERISTICS

	ME1001	ME1003
Heater Voltage (V)	6.3	6.3
Heater Current (A)	0.4	1.0
Max. Anode Voltage (V)	350	500
Max. Anode Dissipation (W)	10	25
Max. Anode Current (mA)	50	200
Max. Peak Anode Current (mA)	150	500
Power Output (W)	0.5 (at 3000 Mc/s)	6 (at 1500 Mc/s)
	3.5 (at 500 Mc/s)	10 (at 430 Mc/s)
Mutual Conductance (mA/V)	6	20
Amplification Factor	30	30

B.I.F.

We are Exhibiting in the Scientific Instruments Section at Olympia.

STAND C69

MULLARD ELECTRONIC PRODUCTS LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2.

MV176

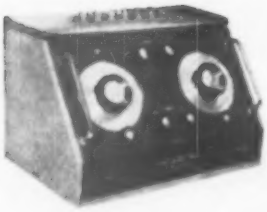

Balanced, unbalanced and three terminal measurements between 15 Kc/s and 5 Mc/s.
Capacity: 0.01 pfd. - 0.02 mfd.
Resistance: 10 ohms - 10 megohms.
Inductance: 0.5 microhenry - 0.05 Hy.
Accuracy: ± 1% to 3 Mc/s. ± 2% to 5 Mc/s.

Radio Frequency Bridge Type B.601

Balanced and unbalanced measurement between 1 and 100 Mc/s.
Susceptance: Equivalent to ± 80 pfds.
Conductance: 0 to 100 millimhos.
Accuracy: ± 2%, ± .5 pfd., ± .05 millimho.

V.H.F. Admittance Bridge Type B.701

Wayne Kerr

V.H.F. Admittance Bridge Type B.901

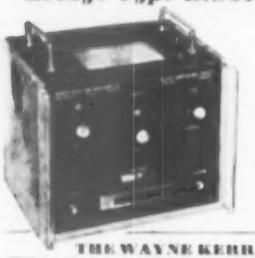

Unbalanced measurement between 75 and 250 Mc/s.
Susceptance: Equivalent to ± 80 pfds.
Conductance: 0 to 100 millimhos.
This bridge will be available soon.

V.H.F. Admittance Bridge Type B.801

Balanced and unbalanced measurement between 1 and 100 Mc/s.
Susceptance: Equivalent to ± 250 pfds.
Conductance: 0 — 100 millimhos.
Accuracy: ± 2%, ± .5 pfd., ± .1 millimho.

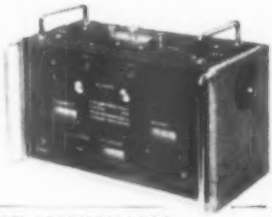

THE WAYNE KERR LABORATORIES LTD., NEW MALDEN, SURREY. MALDEN 2202

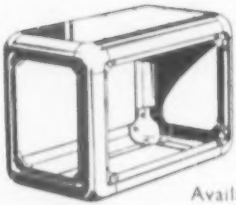

Widney and DORLEC CABINET SYSTEM

Available now in two gauges★, this prefabricated method of building practical cabinets without elaborate tools is proving more popular than ever. Fully illustrated and dimensioned lists are available on request.

★ "Standard" gauge Outside Radius 1 1/16" (List R2)
"Small" gauge Outside Radius 11/16" (List R3).

Technical & Sales Agent
C. H. DAVIS
59, BROMPTON RD., LONDON, S.W.3
Telephone: KEN. 4201

Widney PRODUCT
ESTABLISHED 1898
MANUFACTURERS
HALLAM SLEIGH & CHESTON LTD
WIDNEY WORKS · BIRMINGHAM · 6

HUGE DEMAND FOR THE MURPHY T.V. PATTERN GENERATOR ★

The demand for the Murphy T.V. Pattern Generator continues to grow, and although substantial deliveries are being made, our waiting list is still a very considerable one.

EARLY APPLICATION IS ADVISABLE AS WE ARE RECEIVING MANY REPEAT ORDERS.

For those who are still unaware of the outstanding excellence of the Murphy T.V. Pattern Generator we invite you to make application for a demonstration.

★ The Murphy T.P.G.11 provides in a small, portable equipment the complete synchronising waveform, as used by the B.B.C., in the test signal, essential for correct alignment of T.V. receivers. A pattern generator which does not give such a waveform is of very limited use, so pay the extra cost—and have a Murphy T.P.G.11.

For full specifications write to:

F. LIVINGSTON HOGG

65, BARNSBURY STREET, LONDON, N.1.
or Telephone TUDor 5277 for a demonstration

F. LIVINGSTON HOGG, SPECIALIST IN HIGH GRADE INSTRUMENTS FOR THE COMMUNICATIONS INDUSTRY.

NITROGOL *Capacitors*

QUALITY has always been the basis of Dubilier technical supremacy and in the television field too, this factor has confirmed Dubilier's lead in the international field.

Thus it is natural that only components of tested quality and worth will satisfy television engineers. Experience has proved that Dubilier Nitrogol Capacitors, acknowledged by technicians throughout the world for their reliability, are best suited to the manufacturer of television apparatus.

In such applications as radar, amplifiers, undersea cable repeaters and industrial electronic applications, Nitrogol Capacitors are again a prime necessity.

Comprehensive catalogues giving detailed information of capacitors and technical service are available upon request.

DUBILIER
CONDENSER CO. (1925) LTD.

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, N. ACTON, LONDON, W.3
'Phone: Acorn 2241 (5 lines). 'Grams: Hivoltcon, Wesphone, London. Cables: Hivoltcon, London. Marconi International Code

D38A

New Two Speed-motor....

At the turn of a switch you have two speeds, 33⅓ or 78 r.p.m. The Turntable is a full 12" diameter; its main spindle precision ground and lapped, runs in phosphor bronze bearings. The synchronous motor is virtually vibrationless and is suitable for playing standard, transcription and microgroove recordings. Guaranteed mechanically perfect. New super light-weight pick-up available with the interchangeable heads for microgroove and standard recordings.

A Connoisseur PRODUCT

Manufactured by

A. R. SUGDEN & CO. (ENGINEERS) LTD. WELL GREEN LANE BRIGHOUSE YORKS.

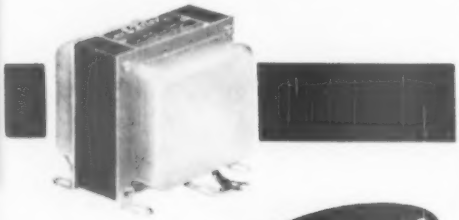

MAINS TRANSFORMERS & CHOKES

Varley REGD. TRADE MARK

All "Varley" products are manufactured from the highest quality materials.

Transformers, etc., are individually wound and have interleaved windings with ample insulation, ensuring freedom from breakdown.

The comprehensive range of Shielded and Open type Transformers available meets the requirements of every circuit. Write for list, etc.

MADE BY

OLIVER PELL CONTROL LTD
CAMBRIDGE ROW · WOOLWICH · S·E·18
Telephone: WOOLWICH 1422

THE NEW B.P.L. SUPER RANGER

20,000 OHMS PER VOLT.

D.C. VOLTS: 100 mV to 5 kV

D.C. CURRENT: 1 μA to 1 Amp.

A.C. VOLTS: 0·5 V to 5 kV.

A.C. CURRENT: 10 mA to 10 Amps

RESISTANCE: 1 ohm to 2 megohms

OUTPUT: 0 to 62 db

METER: 5-inch Long arc, fitted with knife-edge pointer and mirror scale.

LIST PRICE: £22 - 15 - 0.

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS, RADLETT, HERTS.

Tel: Radlett 5674-5-6

Your career in **RADAR** starts in the R.A.F

First in the field with Radar, Britain still leads the nations in research into its future. That is why the Air Force is the finest Radar School in the world and offers such a wonderful opportunity to make Radar your career. You earn while you learn. You get an important job at the end of your training—as Radar fitter, mechanic, assistant.

And Radar is only one of the many skilled trades open to men between the ages of 17½ and 33 who sign on for **five years** in the R.A.F.

Learn your trade in the

ROYAL AIR FORCE

and be trained for life!

TO:—AIR MINISTRY
DEPT W.D.3 VICTORY HOUSE,
KINGSWAY, LONDON, W.C.2

Please send full details of R.A.F. careers.

NAME .....

ADDRESS .....

AGE .....

EX-AIRMEN SHOULD ASK FOR DETAILS OF £125 BOUNTY SCHEME

TELCON TELEVISION AERIAL DOWNLEADS

For Improved Picture Quality and Maximum Efficiency

TELCON have recently introduced a new 80 ohm balanced screen twin feeder for fringe area operation. This coupled with our well-known K.12.SM. covers all possible requirements for screened twin television aerial feeders.

CABLE CHARACTERISTICS

Area	Local	Fringe
Code	K.12.SM.	BA.24.PSM.
Attenuation db/100 ft. at 45 Mc/s	5.9	2.5
Overall diameter	0.232"	0.297"

Further details of these and other R.F. Cables on application.

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO LTD

Head Office: 22, OLD BROAD STREET, LONDON, E.C.2 *Telephone:* LONdon Wall 7181

All enquiries to TELCON WORKS, GREENWICH, S.E.10 *Telephone* GREenwich 3291

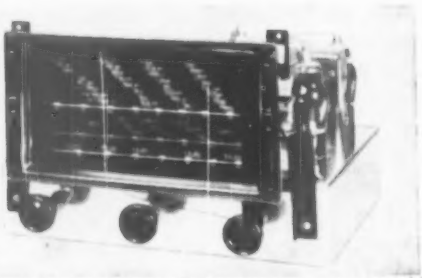

YOUR CHASSIS, SIR!

YOU can build the handsome SUPERHET pictured above! It's so SIMPLE, failure is IMPOSSIBLE!

Yet the performance equals that of commercially built units at double the price. You can be PROUD of your achievement—since the cost is **well** within your pocket!

How is it done? As thousands of our delighted friends know the secret lies in the use of the pre-aligned **MODEL 30 TUNING UNIT** comprising the famous 3 waveband model 30 superhet. Coil pack, pair of "MM" I.F. Transformers, dial (with new station names) and 2 gang Condenser—the WHOLE ALIGNED AND SEALED AS A UNIT! Price **54/9** (inc.) or **76/6** with J.B. S.L.B. spin-wheel Tuner. We supply **COMPLETELY** punched chassis 12in. x 9in. x 2½in. at **11/6** ea. "Easy-as-A.B.C." construction sheets at **3/6** per set AND all Components for 30 Feeder Unit, 40 Feeder Unit (with R.F. stage), 5v. A.C., 5v. A.C./D.C., 6v. A.C. and 10 watt quality Amplifier. For further details, and a host of valuable circuits, data, etc., send **1/6** NOW for NEW EIGHTH EDITION of "The Home Constructor's Handbook" and **Catalogue**. This book has now been greatly enlarged. All standard Radio and Television lines are available, of course, at the KEENEST prices!

RODING LABORATORIES

(Mail Order Dept.)

70, LORD AVENUE, ILFORD, ESSEX

Phone: WAN. 5486

You are offering

***PEAK PERFORMANCE**

with the

GRAMPIAN D.P.I.

THE IDEAL MICROPHONE FOR P.A. WORK, BROADCASTING AND RECORDING

Here is a wide range high fidelity moving coil type Microphone which combines good sensitivity with a level response curve. Equally suitable for Auditorium or Outdoor Work, and its use can confidently be advised for Amateur as well as Professional use. Housed in modern streamlined die cast alloy case of great strength and finished in hammered metallic lacquer with chromium plated grille. Delivery from stock. List price £8.8.0

Dimensions 3" diam. 3¾" back to front. Net weight 2 lb. Frequency response 60-9,000 c.p.s. Output impedance 15 ohms. Fitting 5/16" B.S.F. Connection 2-pin plug.

GRAMPIAN

P.A EQUIPMENT

Grampian Reproducers Ltd., Hampton Road, Hanworth, Middx.

'Phone: Feltham 3657.

An entirely new development . . .

THE METROVICK UNIVERSAL METER

This latest Metrovick product in the field of electronics gives the Electronic and Radio Engineer all he needs in a multi-range instrument for the measurement of current, resistance and voltage. In addition, provision for R.F. Voltages is made by the inclusion of a probe which employs a diode valve for rectification. All sections give indication on the same moving coil instrument, and a multiplier switch enables all the A.C. and D.C. ranges, except the 1000 volt scales to be trebled if required.

Though so compact, the instrument is robust enough to be used constantly under average conditions. It weighs only 17 lb., and is contained in an attractive steel case in cream or blue hard stoved enamel, fitted with leather carrying handle.

TYPE 214

Send for further details contained in leaflet 652/2-1

METROPOLITAN-VICKERS ELECTRICAL CO. LTD.

TRAFFORD PARK, MANCHESTER 17

E.E. 901

New Moving Iron Meters

Taylor moving iron meters are repulsion type instruments of an improved and patented design, noteworthy is the almost linear scale shape from 20% to full scale. Available in round flush and semi-flush rectangular types, many ranges are "ex stock"

Illustrated catalogues of all Taylor products gladly sent upon request

SERIES 400

TAYLOR ELECTRICAL INSTRUMENTS LTD

419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND

Telephone SLOUGH 21381 (4 lines) • Grams & Cables TAYLINS, SLOUGH

Other products include: MULTIRANGE A.C. D.C. TEST METERS • SIGNAL GENERATORS • VALVE TESTERS • A.C. BRIDGES • CIRCUIT ANALYSERS • CATHODE RAY OSCILLOGRAPHS • HIGH AND LOW RANGE OHMMETERS • OUTPUT METERS • INSULATION TESTERS • MOVING COIL INSTRUMENTS

Stars for Sale!

SPECIFIED T.V. PARTS from stock

T.C.C. CONDENSERS

12pF 20%	ceramic	ACT4	1/-
18pF 10%	do.	ACT1	2/6
12pF 20%	do.	ACD2	1/3
40pF 10%	do.	ACT1	2/6
40pF 20%	do.	ACT1	1/9
47pF 20%	do.	ACT1	1/9
500 pF	mica disc	CM30	1/6
.0001	mica	CM20	1/2
.0002	do.	CM20	1/2
.001	do.	CM20	1/9
.001	Metalclad	CP110W	2/2
.002	do.	CP100	1/9
.002	do.	CP100	1/10
.01	do.	CP100	1/10
.01	do.	CP100N	1/8
.015	do.	CP100N	2/-
.02	do.	CP100N	1/9
.03	do.	CP100N	2/1
.1	do.	CP100N	2/3
.1	do.	CP200H	2/2
.25	Metalpack	CP400N	2/8
.01,500v	Tubular	S43	11
.1,500v	do.	S43	1/3
.001KV	Unbushed	CP500Q	4/6
.001/.15KV	do.	CP500Q	7/6
.01KV	do.	CP500Q	7/6
.1/TKV	do.	CP500Q	15/-
.1/500v.	Pinpack	CE100N	2/6
.2/500v.	do.	CE100N	2/6
.25/12v.	do.	CE100N	2/6
.5/500	Lockpack	CE200L	4/9
.5/250	do.	CE200L	6/6
2/450	do.	CE2FP	10/-
8+8/450	do.	Transvor	12/-
.05/500	do.	CE100L	7/6
.05/500	do.	CE100LE	11/6
.05/50	do.	CE100A	10/-
.05/50	do.	CE100A	8/9
.05/50	do.	CE100A	13/6
.05/50	do.	CE100A	6/9

MORGANITE RESISTORS

Type T midget (± 20%)	4/-
Type T midget (± 10%)	6/-

MORGANITE RESISTORS—Cont.

Type R midget (± 20%)	6
Type R midget (± 10%)	9

RELIANCE POTENTIOMETERS

Type TW wire-wound 100, 500, 1K, 2K, 2.5K, 5K, 10K, 25K, 50K 4/6
Type TW 100K 5/-
Type SG Carbon 100K, 1 Meg. 5/-

TALLON CONSOLE TV CABINETS

12in. Viewmaster £12 10 0
12in. Electronic Eng. £13 10 0
(Both carr. pd. packed flat.)

WHITELEY Table Cabinet for 9in. Viewmaster, complete with mask, glass and engraved knobs £6 17 6
12in. conversion parts for Viewmaster 17 6
Elac PM focus units £17
21 v., 8/9; 22 6; R16 25/-
Rim White masks for round or flat ended tubes 11 3
12in. do. round or flat 21 6
All parts for the 9in. or 12in. Lord or Bermondsey Viewmaster can be supplied from stock in either single parts, stages (in 7 or 9 make) Kits.

Valves—EF91, 21/4; EB91 8/7; EB91 11/7; EL91 17/1; EA76, 12/10

CRTS MW22/16, CRM 22, £11 6 10 MW31/74, CRM 32, £13 5 9; MW36/44, CRM36, £15 2 5; CRM151A, £18 1 4.

Satisfaction guaranteed. All goods post free over £1.

PHONE: SOUTH 5977

Fifth RADIOCRAFT Ltd

69-71 CHURCH GATE SLOUGH

Slough Grev 6281

CO-AX AIR-SPACED ARTICULATED R.F. CABLES

BASICALLY BETTER

IMMEDIATE DELIVERIES FOR HOME & EXPORT

FOR RADIO FREQUENCIES

LOW ATTEN TYPES	IMPED OHMS	ATTEN db/100 ft at 100 Mc/s	LOADING Mc/s	O.D. "
A 1	74	1.7	0.11	0.36
A 2	74	1.3	0.24	0.44
A 34	73	0.6	1.5	0.85

HIGH POWER FLEXIBLE

FOR VIDEO and SPECIAL APPLICATIONS

CAPAC mmf/ft	IMPED OHMS	ATTEN db/100ft 100 Mc/s	O.D."
C1	7.3	150	2.5	0.36
PC1	10.2	132	3.1	0.36
C11	6.3	173	3.2	0.36
C2	6.3	171	2.15	0.44
C22	5.5	184	2.8	0.44
C3	5.4	192	1.9	0.64
C33	4.8	220	2.4	0.64
C44	4.1	252	2.1	1.03

PHOTOCELL CABLE

VERY LOW CAPACITANCE CABLES

Write for data sheets to the originators of air spaced R.F. Cables

TRANSRADIO LTD. 138a CROMWELL ROAD LONDON S.W.7

CONTRACTORS TO H.M. GOVERNMENT

FREQUENCY SHIFT EQUIPMENT

now available!

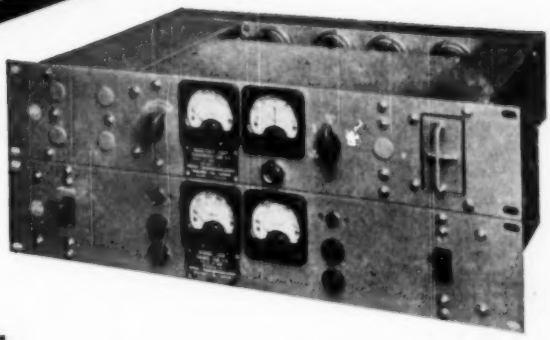

FREQUENCY SHIFT RECEIVING TERMINAL

Type FSR1. For the conversion of radio communication receivers to frequency shift operation.

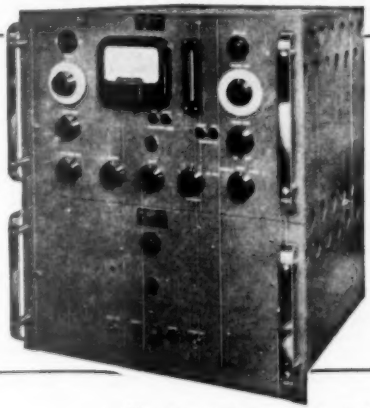

FREQUENCY SHIFT KEYING UNIT

Type FSK2. For the conversion of radio transmitters to frequency shift keying.

The above equipment can be fitted on site by Station Engineers. Modification of the radio equipment, if required, would be of a minor nature.

AUTOMATIC TELEPHONE & ELECTRIC Co. Ltd.

(RADIO & TRANSMISSION DIVISION)

Strowger House, Arundel Street, London, W.C.2

Telephone: TEMple Bar 9262. Telegrams: Strowger, Estrand, London

STROWGER WORKS, LIVERPOOL, 7

A.14011-B.34

CERAMICS by U.I.C

UNITED INSULATOR COMPANY LTD. TOLWORTH SURBITON SURREY ENGLAND

Cables: Calanel, Surbiton. Telephone: Elmbridge 524

TELEVISION from 50 OR 110 VOLT D.C. SUPPLIES

BUILT TO MEET THE NEEDS OF THE MOMENT BY **VALRADIO**—THE CONVERTER PEOPLE.

This Power Unit is designed for driving

THE PYE UNIVERSAL AC/DC TELEVISION RECEIVER

from Low Voltage D.C. supplies of 50 or 110 volts.

The output is D.C., with less than a ½-volt ripple, resulting in an exceptionally steady picture. The conversion efficiency is 80% with a current consumption of 1·4 amps on 110-volts or 2·8 amps on 50-volts supply.

TYPE No. 240 125 110-A or
TYPE No. 240 125 50-A.

PRICE £16-0-0

Literature upon request to

VALRADIO LIMITED

57 FORTESS ROAD, LONDON, N.W.5

GUlliver 5165

"You're CERTAIN to get it at ARTHURS!"

★ **VALVES:** We have probably the largest stock of valves in the country. Send your enquiries.

AVO METERS IN STOCK

Avo Model 7	£19 10 0
Avo Model 7, high resistance	£19 10 0
Avo Model 40	£17 10 0
Valve Tester	£16 10 0
Test bridge	£11 0 0
Avo Minor, AC/DC model	£8 10 0
Electronic Test Meter	£35 0 0
Signal Generator	£25 0 0
Valve characteristic meter	£40 0 0

TAYLORS METERS. List on request

DECCA PICK-UPS	£3 15 5
DECCA HEAD for Garrard	£2 19 2
Adaptors	3 8
COSSOR DOUBLE BEAM OSCILLOSCOPE	£85 10 0

"Viewmaster" Television Kits in stock for Birmingham and London area. Please state which required.

LATEST VALVE MANUALS
Mullard - 5/- ea.
Mazda - 1/- ea.
Brimar - 2/6 ea.
Brimar Teletube & Radio - 4/-
Post 4d. each extra

LONDON'S OLDEST LEADING RADIO DEALERS

Arthurs

EST. 1919

PROPS: ARTHUR GRAY, LTD.

Terms C.O.D. or cash with order

Our Only Address: **Gray House, 150 152 Charing Cross Rd., London, W.C.2** TEMple Bar 5833/4 and 4755

ELECTRICAL, TELEVISION & RADIO ENGINEERS.

AIRMEC

SIGNAL GENERATORS

A RANGE from 30 c/s to 30 Mc/s is covered by the Signal Generators illustrated here. One or other of these will be found to meet the requirements of most laboratories, workshops and experimental departments engaged on audio or radio frequency measurements.

The particular features of these instruments are their accuracy, stability, wave form and constancy of output combined with a robust construction suitable for bench use or for forward mounting on the standard nineteen-inch rack. Pamphlets 11 & 12 give further details

TYPE 701 H.F. SIGNAL GENERATOR

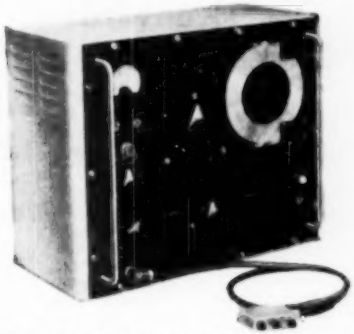

Range: 30 kc/s to 30 Mc/s in seven stages.
Frequency Calibration Accuracy: ±1%.
Output Level: Variable from 1μV to 1 volt. Additional output terminal at 5 volts.
Modulation: Internal at 1 kc/s. External 30 c/s to 10 kc/s. Depth variable 0 - 80%.
Frequency Modulation: Negligible.
Output and Frequency: Unaffected by load conditions and output constant over frequency range.

TYPE 702 L.F. SIGNAL GENERATOR.

Range: 30 c/s to 30 kc/s in three stages.
Accuracy of Calibration: ±1% ± 1 c/s.
Stability: ±0.5% ± 0.5 c/s.
Distortion: Less than 2%.
Output Meter: Calibrated in db and open circuit volts.
Attenuator: Standard output impedance with steps of —20db, —40 db, —60 db.
Output: 100mW into 600 ohms or 15V open circuit.

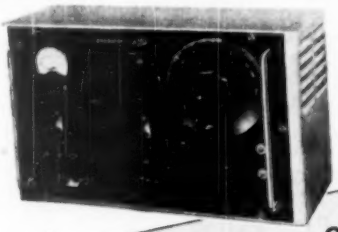

OSCILLOSCOPES
VALVE VOLTMETERS
SIGNAL GENERATORS
RADIATION INSTRUMENTS
BRIDGE OSCILLATORS
ELECTRONIC COUNTERS
INSULATION TESTERS
COMMUNICATION TEST GEAR
INDUSTRIAL ELECTRONIC APPARATUS

The Quality of an AIRMEC *product is outstanding*

AIRMEC LABORATORIES LTD

HIGH WYCOMBE · BUCKINGHAMSHIRE · ENGLAND

TEL. HIGH WYCOMBE 2060 *CABLES: COMMLABS HIGH WYCOMBE*

DESIGNERS AND MANUFACTURERS OF SCIENTIFIC AND INDUSTRIAL ELECTRONIC EQUIPMENT

Serving the Four Corners of the World

The need for reliable Radio communication is being met throughout the world by Redifon equipment for many civil, commercial, marine and aeronautical services. The G.41, illustrated, is a typical example of a 5-7½ KW Transmitter for world wide, high speed Telegraphy, Teleprinter, Telephony and Broadcast purposes.

COMMUNICATIONS

Redifon Radio

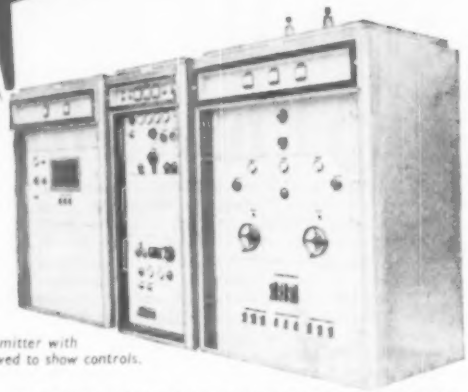

G.41 Transmitter with doors removed to show controls.

Radio Communications Division

REDIFON LIMITED, BROOMHILL ROAD, WANDSWORTH, S.W.18

DESIGNERS & MANUFACTURERS OF RADIO COMMUNICATION & INDUSTRIAL ELECTRONIC EQUIPMENT. Phone: VANdyke 5691

"REPRODUCTION OF RECORDS—I"

by J. H. Brierley

Booklet. Price 3/6 (by post 3/11).

This booklet is the first of a series of practical booklets dealing with specialised high fidelity equipment.

After touching on some aspects of fundamental design, a preamplifier is described incorporating all necessary equalising, variable tone control and filter circuits, which requires 5 mV. at the grid of the input for an output of 2 v., the hum and noise level not being higher than 60 dbs.

Twenty-one drawings and photographic illustrations are employed in giving precise wiring and constructional details; in addition the reasons why certain things must be done are fully discussed so that the reader is left with a knowledge of how to do things rather than an ability to copy slavishly some standard design.

The scope of this booklet covers also the connecting of pick-ups to pre-amplifiers, the connecting of pre-amplifiers to amplifiers, the construction of a "Rumble Filter" and advice on general layout.

Order from your local radio or book shop or direct.

J. H. BRIERLEY (Gramophones & Recordings) LTD.

46, Tithebarn Street, Liverpool, 2

BALDWIN

MOVING-COIL for d.c.

RECTIFIER for a.f.

THERMAL for h.f.

4-INCH SQUARE FLUSH-MOUNTING INSTRUMENTS

especially for electronic test-gear

MAY HAVE ILLUMINATED DIAL — FIRST-GRADE ACCURACY TO BS. 89

Other instruments include Visual Null Indicator Resistance Boxes, Potentiometer, etc.

BALDWIN INSTRUMENT Co. Ltd.

DARTFORD, KENT *Dartford 2989*

LONDON CENTRAL RADIO STORES

Government Surplus — Immediate Delivery from Stock

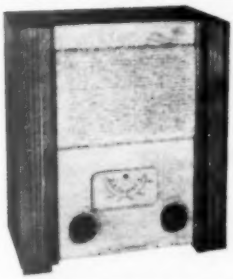

UNREPEATABLE OFFER

4-VALVE USED SUPERHET UTILITY RECEIVER

Every one guaranteed to be in working order. Medium Waveband only.

Four valves, P.M. Speaker, complete in pinewood cabinet size 13½ × 12 × 6½in. A.C. mains 200/250 volts. In good condition.

PRICE

£3.19.6

Plus 5/- carr. and pkg.

PHILIPS 6-VALVE COMMUNICATIONS RECEIVER

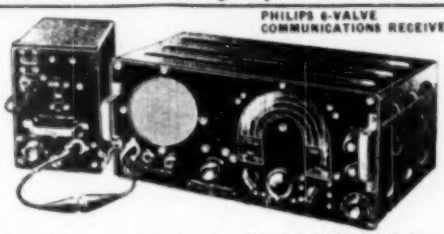

16-50, 200-550 and 800-2,000 metres. R.F., F.C., 2 I.F.s D.D.T. Pentode Output. Spin-wheel tuning. In black metal case with built-in speaker. Complete with power pack, A.C. 200/250 v. Can also be supplied with 12 v. D.C. power pack if required. BRAND NEW—EX GOVT.

£17.10.0

CATHODE RAY TUBES

12in. VCR140 Blue Screen, Magnetic deflection, magnetic focus maximum 6 Kv., heater 4 v., international octal standard connections **90/-**, carr. and pkg., 5/-. New VCR97 6in. tube, **37/6**, carr. and pkg., 5/-.

R.A.F. 6-VALVE SUPERHET RECEIVER UNIT No. 25

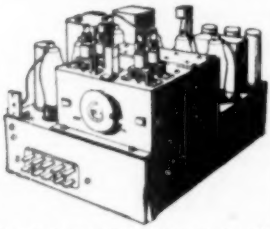

All valves guaranteed. This unit is easily adapted for Short-wave reception for home use. In addition to two EF36, two EF39, one EK32 and one EBC33 valves, it contains 1 pr. 480 Kcs iron dust I.F. Transformers, Mic. and phone output transformers, a number of resistances and fixed condensers of useful values, two 1 mfd. 500 v. wkg. and four .1 tubular condensers, pot'meters, Int. Octal Valve holders, Tuning Coil, etc., mounted on steel chassis 8½ × 6½ × 2½in. FREE circuit diagram 9in. × 19in. showing all components, supplied with each set. In new condition.

22/6

FRACTIONAL H.P. A.C. MOTORS, converted from ex-Govt. Generators. Brush type 220-250 v. 50 cycles, approx. 5,000 r.p.m. Overall diam. 10 × 4in. ⅜in. spindle extends 1in. both ends. **21/-.**

HEADPHONES. American lightweight, 200 ohms, suitable for Deaf Aid, **7/6** pair.

BRAND NEW ACCUMULATORS

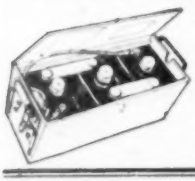

Complete in strong case, as illustrated. British made, 6v. 80a. Size 12x9x7 in. Weight 45 lb.

£3.10.0

Carriage and pkg., 5/-.

1/30th H.P. MOTORS. Constant speed. Double ended spindles. 220-250 v. These motors are new, not surplus conversions and are suitable for 16 mm projectors and many other purposes. **A.C. D.C., 37/6.**

VISION UNIT, Type 182. Complete with 6in. 517 C.R. Tube, 2in. 139 C.R. Tube, one 807, three VR65, one 6J5 valves. 0-5 milliammeter, condensers, etc. Suitable for television, **55/-.**

CO-AXIAL CABLE for T.V., 75 ohms. 12 yard lengths, **8/-.**

2-VOLT VIBRATORS, Type R79C. 7-pin self-rectifying. Output 200 v. at 60 mA. Made by Electronic Laboratories Inc., **7/6.**

UNI-SELECTOR SWITCHES with complete wipers. 4-bank, **37/6**; 6-bank, **37/6**; 3-bank, **22/6.**

FIVE-WAY RUBBER COVERED CABLE. Suitable for lighting and other purposes. Per doz. yds. **6/-.**

MOVING COIL HAND MICROPHONE. Complete. **5/6.**

BALL MICROPHONE

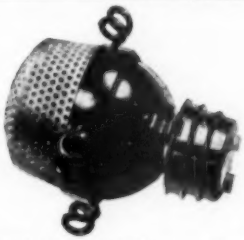

Manufactured by Standard Electric. All in perfect condition. Suitable for broadcasting and recording. Moving Coil (Dynamic). Omni-directional. No energising necessary. High Fidelity. Coil Impedance 15 ohm and will work very well in conjunction with an ordinary speaker transformer. Is of the type used by many leading bodies, such as the B.B.C. and G.P.O. for high fidelity reproduction.

£4.17.6

PLEASE NOTE

● All carriage paid unless otherwise stated. ● Carriage charges relate to British Isles only. ● We do not issue lists or catalogues. ● We have hundreds of items in stock too numerous to list, including Special Admiralty Transmitters, Receivers, etc., so when in Town pay us a visit.

PHOTO-ELECTRIC CELLS, Type G817. These cells are the gas-filled type with caesium Cathode. Made by Cintel. Minimum sensitivity 100 μA lumen, working volts 100 D.C. or peak A.C. Projected cathode area 16 sq. cm. Suitable for 16 mm. Home Cinema Talkie equipment, Safety Devices, Colour and Photo Matching, Burglar Alarms, Automatic Counting, Door Opening, etc. Brand new. In original cartons.

42/6

MAP READING TORCH

Powerful magnifying lens, 3in. diam. in bakelite case. Fitted with dimmer switch. Takes 2 U2 cells. With bulb, less batteries.

22/6

WALKIE-TALKIE Transmitter and Receiver CHASSIS, Type 38 Mk. II

Including four ARP12 valves. In metal case. Complete with components, except the Send/Receive switch and the ATP4 valve. With wiring diagram. Price

20/-

EX-R.A.F. TUNING UNIT TYPE 207A. BRAND NEW. Includes Clystron valve, 5 Neon tubes CV71, 1 5Z4G and other useful components. As illustrated, plus metal cover.

21/6

PHOTO ELECTRIC CELLS, Type CV143 Small infra-red image, glass converter tube, 50/100 v. Suitable for all purposes. Guaranteed New. N.B.—We cannot enter into correspondence regarding these cells.

14/6

SELF-ENERGISING TABLE MICROPHONE AND HEADSETS Sound Power. The microphone is mounted on a fully adjustable stand with on/off switch. No batteries or current required to operate. UNUSED IN CARTONS.

10/6

ELECTRO MAGNETIC COUNTERS

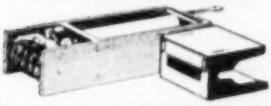

Ex G.P.O., every one perfect, electro magnetic, 500 ohm. coil, counting to 9,999, operated from 25 v.-50 v. D.C., many industrial and domestic applications.

7/6

LONDON CENTRAL RADIO STORES, 23, LISLE ST. (GERrard 2969) LONDON, W.C.2.

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.

Recognised as the Most Reliable Valveholders

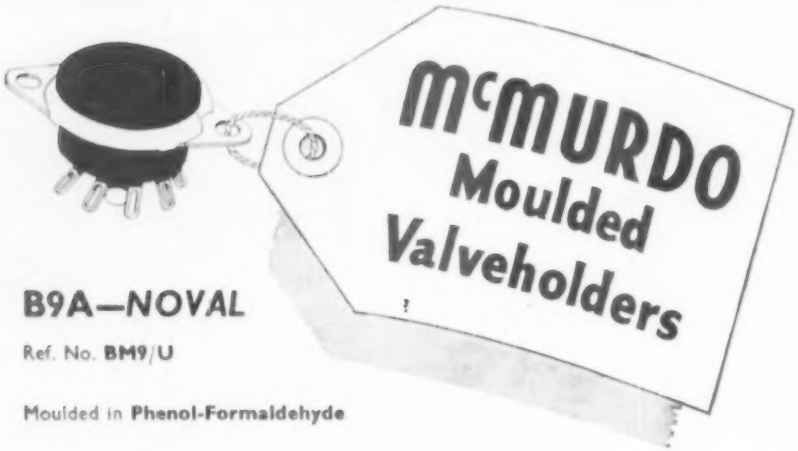

B9A—NOVAL

Ref. No. **BM9/U**

Moulded in **Phenol-Formaldehyde**

* *Also supplied with various saddle assemblies to meet customers' requirements.*

THE McMURDO INSTRUMENT COMPANY LTD., VICTORIA WORKS, ASHTEAD, SURREY · ASHTEAD 3401

TELE-RADIO (1943) LTD.

177, EDGWARE ROAD, LONDON, W.2

COMPONENTS FOR QUALITY AMPLIFIERS.

Chassis punched and drilled	£1	7	6
Partridge mains transformer 425/150 mA	£2	17	0
Partridge mains transformer 425/200 mA	£4	8	0
Partridge smoothing choke 25H 60 mA		16	0
Partridge smoothing choke 13H 200 mA	£1	11	0
Partridge Williamson output transformer (wire ends)	£5	0	0
Partridge Williamson output transformer (Tag Board)	£5	13	0
Wharfedale L.S. W10/CS 10in. cloth suspension	£7	5	0
Wharfedale L.S. Golden 10in. Unit 2/3 & 15 ohms	£4	0	0
Wharfedale L.S. Super 8/CS. 2/3 and 15 ohms	£4	0	0
Goodman's single cone loud speakers Audio 60	£6	15	0
Goodman's double cone loud speakers Axiom 12	£8	8	0
Vitavox K 12/10 loudspeaker	£7	0	0
Partridge output transformer PPO/O 6,000 ohms A-A. Sec. 3·75 & 15 ohms	£2	12	6
Partridge output transformer PPO/1 8,000 ohms A-A. Sec. 3·75 & 15 ohms	£2	12	6
Partridge output transformer PPO/2 10,000 ohms A-A. Sec. 3·75 & 15 ohms	£2	12	6
Matched KT66 valves per pair	£1	16	6
Matched 6V6 valves per pair	£1	5	8
Matched 6F6 valves per pair	£1	5	8
Matched PX4 valves per pair	£1	13	0
Matched PX25 valves per pair	£2	14	10
Matched 6B4 valves per pair		18	4
Matched 2A3 valves per pair	£1	5	8

Williamson quality amplifier can be seen and heard at our premises in Edgware Road. When ordering please include sufficient for postage and packing.

Shop Hours: Mon.-Sat., 9 a.m.-6 p.m. Thursday, 9 a.m.-1 p.m.

Phone: PAD 6116 or 5406

RUCO PRODUCTS

GLASS DIALS
for the
NEW WAVELENGTHS
are now available
for all our units

RUCO PRODUCTS
Crown Works,
197, Lr. Richmond Rd., Richmond,
Surrey

Phone: Prospect 7463

MINISCOPE

displays Audio Grid overload

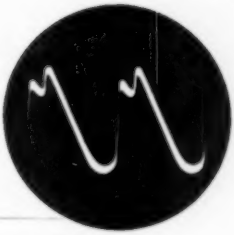

A.F. amplifier test. Test signal to input. Miniscope probes across speech coil. Trace shows grid overloading of output valve due to excessive input voltage.

INPUT to amplifier under test—Undistorted sine-wave, generous amplitude.

The M.861B "Miniscope"—the most compact of all oscilloscopes—weighs only 7½ lbs and measures only 6¾" in height—yet is a thoroughly reliable portable instrument of immense value to the serious radio engineer—and at a reasonable price.

Specification

"X" plate sensitivity 50 v/cm. "Y" plate sensitivity 60 v/cm. Time Base frequency sweep 10 - 50,000 c.p.s. **Price £21.0.0**

"Add-on" Units available

M.862B Double Beam Unit **Price £12.0.0**

M.863B I.F. Alignment Unit **Price £8.10.0**

DELIVERY—AT ONCE

Send for leaflets Nos. X. 9832, X.365 and X.475

minimise

trouble shooting with a

MINISCOPE

A G&C PRODUCT

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2

MAGNAVISTA DOES IT AGAIN!

Two more winners from the Magnavista production line!

A Trolley Table with lens incorporated which solves the problems "where to put the set and how to fix the Lens" and a Console Stand which, for design and finish, is in advance of anything that you have seen to date.

TROLLEY TABLE MODEL.

Simply designed tubular steel table with telescopic and swivel Lens adjustment, fitted with large wheels for easy movement. Finished in polychromatic bronze suitable for 9in. 10in. or 12in. Receivers. Price £7.17.6 (incl. Pur. Tax). Magnavista Lenses for this Model at usual list.

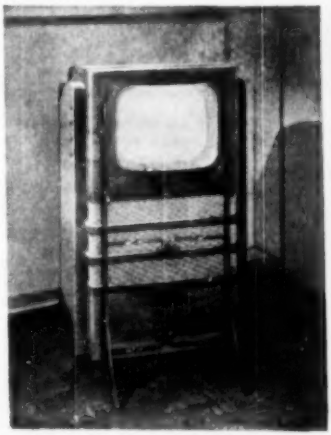

CONSOLE STAND MODEL.

Beautifully designed hand-forged wrought iron, finished in polychromatic bronze which, although unobtrusive, enhances the finest cabinet. This is the aristocrat of Television Stands and is available complete with Magnavista Television Lens, suitable for 9in., 10in. or 12in. Receivers. Price £7.7.-.

The MAGNAVISTA TELEVISION LENS

There are Magnavista Lenses for all receivers. Available from good dealers.

The MAGNAVISTA TELEVISION LENS Leaflet from

METRO PEX LTD.

38, Great Portland Street, London W.1.

King's Heath Stn., Birmingham 14.

A GREAT NAME
rests on public trust

The name Marconi is a household word all over the inhabited world. It has come to mean in people's minds all that is most modern in wireless and communications. In fact, wherever the English language is spoken, the words Marconi and wireless are interchangeable. The Marconi Company is justifiably proud of the universal confidence its name inspires.

Marconi

the FIRST and GREATEST name in Wireless

MARCONI'S WIRELESS TELEGRAPH COMPANY LIMITED — MARCONI HOUSE — CHELMSFORD — ESSEX

The Revolutionary

GOLDRING

Headmaster

HYPERFIDELITY

PICK-UP

With an interchangeable Pick Up Head for every type of record

Supplied in attractive Display Carton complete with Goldring Tonaliser and Transformer

★

Goldring Products include

PICK-UPS, PICK-UP HEADS, SAPPHIRE JEWEL POINT NEEDLES, AND RADIOGRAM ACCESSORIES.

Write for full Descriptive Lists and Technical Information

ERWIN SCHARF

49-51a DE BEAUVIOR ROAD, LONDON, N.1

Telephone: CLISSOLD 4431

ACRU

neon indicator lamps

ONE-HOLE FIXING

In handsome Black Bakelite holder complete with series resistance and leads, to show Pink, Red, Amber or Green, on 230v or 400v AC or DC. Specially designed for easy assembly in ¾-inch mounting hole.

Send now for full details, prices and terms.

For
SWITCHBOARDS,
INDICATOR PANELS,
MACHINE CONTROLS,
HEATING APPLIANCES, ETC

THE ACRU ELECTRIC TOOL MFG. CO. LTD.

123, Hyde Road, Manchester, 12.

Ardwick 4284.

NL

talk you down

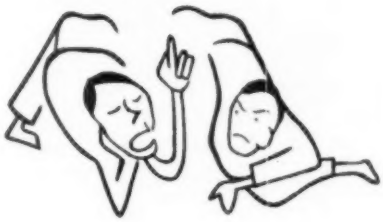

Continuous pressure is the raison d'etre, but such efficiency is more usefully applied in the 'Talk-you-down' system bringing aircraft safely on to the runway. It is but logical that this important work demands Transformers which are the result of specialised development and manufacture, and it is surprising how often they bear the name Parmeko

PARMEKO *of* **LEICESTER**

Makers of Transformers for the Electronic and Electrical Industries

12½ mA Subminiature Amplifier Pentode

XFW20

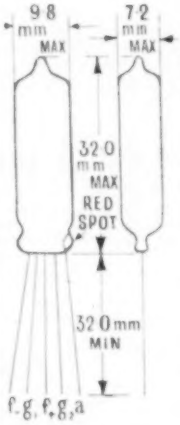

The XFW20 is a sub-miniature voltage amplifier pentode with a filament current of only 12½ mA.

It is a robust, reliable valve having a high gain and very low microphony.

Its principal use is in the early stages of hearing aids, but it has applications in many small instruments.

TYPICAL OPERATION

Filament Voltage	**0.625v**
Filament Current	**12½mA**
H.T. Supply Voltage	**22½v**
Anode Load	**1 to 2 MΩ**
Screen Resistance	**3 MΩ**
Stage Gain	**32**

HIVAC
THE SCIENTIFIC VALVE
BRITISH MADE

GREENHILL CRESCENT, HARROW-ON-THE-HILL, MIDDLESEX

Telephone: HARrow 2655

SPLENDID

ISOLATION

SIGNAL GENERATOR TF867

Because its superiority is unchallenged, Signal Generator type TF 867 stands alone, in splendid isolation. Beautifully designed and finished, its behaviour is impeccable over the range 15 kc/s to 30 Mc/s. Especially noteworthy are an expanded wide-view scale and a concentric terminating unit which, while showing exact circuit conditions on an animated diagram, is also a dummy aerial and impedance source of 75Ω or 13Ω. Other facilities of the Signal Generator include crystal standardisation, freedom from unwanted frequency modulation, deep amplitude or carrier shift modulation and stabilised output control. Output is variable from 4V to 0.4μV and calibration indicates true artificial signal e.m.f. irrespective of load. For further information please apply:

MARCONI INSTRUMENTS LIMITED

ST. ALBANS, HERTFORDSHIRE · Telephone: St. Albans 6161/5

Northern Office: 30 Albion Street, Hull. **Western Office:** 6 Portview Road, Avonmouth. **Southern Office & Showrooms:** 109 Eaton Square, London, S.W.1. **Midland Office:** 19 The Parade, Leamington Spa.

Please ask for folder "SUMMARY OF COMMUNICATIONS TEST GEAR"

LONDON

OR

BIRMINGHAM!

Here is an opportunity worth grasping, build your own Television Receiver at a price you can afford.

- No technical knowledge required.
- Designed around common types of valves.
- No unusual types to obtain.
- Will suit 9", 10" or 12" Tubes.
- The most competitive price on the market.

CAN BE BUILT FOR £20 (C.R. Tube Extra)

Instruction books PRICE 5/- *post free.*
Write today for further details.

PRE-AMPLIFIERS NOW AVAILABLE

One Valve Model, completely aligned and tested 30/-
Two " " " " " 40/-

PERM. MAGNET FOCUS RINGS — For all makes of C.R. Tubes. Type FR1 21/-; Type FR2 22/6; Type FR3 25/-. Quote type no. Ion Traps 3/6 each.

HOUGHTON & OSBORNE LTD.

Electron Works, Thame, Oxon.

Telephone: Thame 182.

THE HOUSING PROBLEM

WE HAVE THE ANSWER

We can supply attractive and well-built cabinets to your design for housing sound equipment.
Almost any finish can be supplied and a wide range of veneers enables us to match existing furnishing schemes and styles.
Why not send us a sketch of your requirements, or better still call and see us.

A fully illustrated leaflet describing our range of Loudspeaker Cabinets will shortly be available.
May we put your name on our mailing list, to receive this and future leaflets to be issued.

ROGERS DEVELOPMENTS Co.,
106, HEATH STREET, HAMPSTEAD,
LONDON, N.W.3

Tel.: HAMpstead 6901

GOODMANS INDUSTRIES LTD.
Lancelot Rd., Wembley, Middx.
Tel.: Wembley 1200 (8 lines). 'Grams: Goodaxiom, Wembley.

MORE FLUX DENSITY—GREATER EFFICIENCY—IMPROVED PERFORMANCE.

A single cone medium heavy duty reproducer with an outstanding smoothness in response and performance. The magnet assembly using anisotropic material provides a total flux of 158,000 maxwells on a 1¼in. pole, the back centring device being a dustproof linen disc with concentric corrugations. Functional in design and of robust precision construction, this 12in. unit meets the most modern needs in the field of Public Address Installations, small cinemas, high power radio-gramophones, etc.

Also available ready mounted in a strongly constructed mahogany cabinet (Model AL.5).

Overall Diameter	12 5/16in. (31.3 cms.)
Overall Depth	6 15/16in. (17.6 cms.)
Voice Coil Diameter	1¾in. (4.4 cms.)
Fundamental Resonance	75 c.p.s.
Voice Coil Impedance	15 ohms.
Power Rating	15 Watts Peak A.C.
Flux Density	14,000 gauss
Total Flux	158,000 maxwells
Nett Weight	12lb. 13oz. (5,810 gr.)
Finish	Grey Rivelling Enamel

For use with this model we recommend Goodmans High Fidelity Heavy Duty Output Transformer, Type H.4 or Multi-Ratio General Purpose Output Transformer, Type T.4.123 (5,000, 8,000, 10,000, 14,000 ohms push-pull). Nett Weight, 5lb.—2,265 grammes.

GOOD NEWS *for the discriminating gramophone enthusiast*

GREAT REDUCTION IN PRICES

of

ROTHERMEL

CRYSTAL PICK-UPS

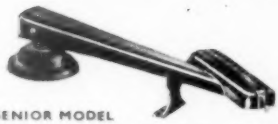

SENIOR MODEL

This has a handsome bakelite tone arm with offset head to facilitate tracking. The performance is superb and will give you new pleasure from your favourite recordings.

Old price, including Purchase Tax, 65/-.

NEW PRICE 28/-

Purchase Tax 12/6

MODEL S.12

A perfectly straight tone arm fitted with the improved Rothermel Cartridge head which minimises breakage of the crystal element under ordinary use. The S.12 gives a very high performance over a wide frequency range.

Old price, including Purchase Tax, 60/8.

NEW PRICE 26/-

Purchase Tax 11/6.

To bring the more expensive models within the reach of the most slender purse, the famous Rothermel Crystal Pick-ups have been greatly reduced in price. Now, the superb performance of these high class instruments can be enjoyed by all.

(This price reduction came into force on January 1st, 1950.)

CONCERNING CRYSTALS

ROCHELLE Salt Crystals lend themselves admirably for use in the construction of High Fidelity Electrical Pick-ups. The chief characteristics of these instruments are clearness of attack and extreme sensitivity, giving a large output voltage for direct connection to the domestic Radio Receiver. The Pick-up Cartridge consists of a bimorph crystal element coupled to a light stylus chuck. Due to the flexibility of the crystal, very little mechanical damping is required, resulting in an element having excellent characteristics with a rising low frequency response to compensate for recording deficiencies.

JEWEL TIPPED NEEDLES

These give hundreds of playings, and improve reproduction with negligible wear on records. Straight, Trailer and Miniature types are available. *If your retailer cannot supply, write direct to the pioneers of Crystal Pick-ups.*

MODEL S.8

The well-known popular Pick-up embodying the improved Rothermel Cartridge head. Although moderately priced, it gives a very high performance and is thoroughly recommended for all-round use.

Old Price including Purchase Tax, 60/8.

NEW PRICE 26/-

Purchase Tax 11/6.

MODEL U.48

This has been expressly designed to bring high fidelity crystal reproduction within the reach of all. Although the price is low, it nevertheless possesses many of the features found in the more expensive models. A thoroughly sound instrument with a remarkable performance.

Old Price, including Purchase Tax, 36/2.

NEW PRICE 19/6

Purchase Tax 8/8.

N.B. Inadvertently the positions of the S.12 and U.48 illustrations were reversed in our April announcement.

R. A. ROTHERMEL LTD., Canterbury Road, Kilburn, London, N.W.6. *Phone* Maida Vale 6066 (3 Lines)

WESTINGHOUSE BRAKE & SIGNAL CO., LTD., 82, YORK WAY, KING'S CROSS, LONDON, N.1

QUALITY TUNERS
and
HI-FIDELITY
AMPLIFIERS

TRF Tuners	from £10-10-0	Plus Tax
SUPER-HET	" £15-15-0	" "
AMPLIFIERS	" £14-14-0	No Tax
PRE-AMPLIFIERS	" £7-7-0	" "

Full details in illustrated leaflet.

GOODSELL LTD., 40, GARDNER ST.,
BRIGHTON, Sx. *Tel.* 26735

Easy Terms:
LONDON RADIO SUPPLY CO., BALCOMBE, SX.

The Quality of old Craftsmanship in Modern form

Furzehill

INSTRUMENTS

d.c. coupled cathode ray oscilloscopes
oscilloscope cameras
valve voltmeters
a.f. attenuators
beat frequency oscillators
stabilised power supply units
high dissipation resistance boxes

Please write for our catalogue

FURZEHILL LABORATORIES LIMITED

BOREHAM WOOD · HERTS · Tel: ELStree 1137

ROLA

A name which ten million speakers have carried to the uttermost parts of the earth. A range which provides a unit to meet all normal requirements. Brief details are given below.

MODEL	Overall Diameter	Magnet Pole Diameter	Flux Density	Total Gap Flux (Maxwell)	Peak Power Capacity
B3KO	3" (sq.)	.57"	7,500	14,000	.5w.
B4KO	4" (sq.)	.57"	7,500	14,000	.75w.
B5K	5"	.57"	7,500	14,000	2w.
K5Q	5"	.75"	8,500	21,000	2.5w.
K5G	5"	.75"	10,000	25,000	3w.
K6D	6.5"	.75"	6,500	16,500	2.75w.
K6Q	6.5"	.75"	8,500	22,000	3w.
K6G	6.5"	.75"	10,000	26,000	3.5w.
K46D	6.25" x 4.25" (Oval)	.75"	6,500	16,500	2.5w.
K46Q	6.25" x 4.25" (Oval)	.75"	8,500	22,000	3w.
K46G	6.25" x 4.25" (Oval)	.75"	10,000	26,000	3w.
F6JO	6.5"	6"	9,000	18,500	3w.
Z8D	8"	1"	6,500	25,000	4w.
Z8M	8"	1"	8,000	31,000	4.5w.
Z8R	8"	1"	9,500	37,000	5w.
Z10D	10"	1"	6,500	25,000	6w.
Z10M	10"	1"	8,000	31,000	6.5w.
Z10R	10"	1"	9,500	37,000	7w.
P44	12.2"	1.5"	10,000	60,000	10w.
G.12	12.2"	1.75"	13,000	146,000	12w.

Voice Coil Impedance is 3 ohms in the case of all the above models except the G.12, where the impedance is either 15 or 8 ohms.
Write for details—enquiries are invited for Cones, Laminations and Output Transformers.

BRITISH ROLA

Ferry Works, Summer Road, Thames Ditton, Surrey. Phone: Emberbrook 3402-6

ROLA *THE SPEAKER YOU KNOW BY EAR*

Leaders in their field

BM40—30-watt Portable Battery Mains Amplifier.

An attractive appearance and unique construction combined with first-rate performance gives this instrument a hall-mark of distinction.

- Designed for both A.C. Mains and 12 volt battery operation.
- Provision for independent electronic mixing of two microphones and one gramophone channel.
- Built-in vibrator.
- Special tone control circuit, with independent bass boost and cut, and treble boost and cut.

These and many other features make the BM40 the most up-to-date amplifier on the market.

Write for further details of this and other portable amplifiers.

Mixer Amplifiers Type FA30 and FA60.

Designed in two self contained sections comprising an electronic mixing panel and power amplifier. The FA30 incorporates a 30-watt, and the FA60 a 60-watt power amplifier.

The electronic mixing unit has five inputs, three microphone and two gramophone, with individual controls.

Separate tone controls for Mic. and Gram. channels are included.

A master gain control for mic. channels enables complete balancing to be easily accomplished.

The mixing unit has two additional 600 ohm. outputs to sub. feed other power units should greater power be required.

The quality, high standard of perception, engineering and performance make these units ideal for use in Theatres, Pavilions, Political Meetings, Conferences and indeed anywhere where perfect control and balancing of microphone and gramophone points is essential.

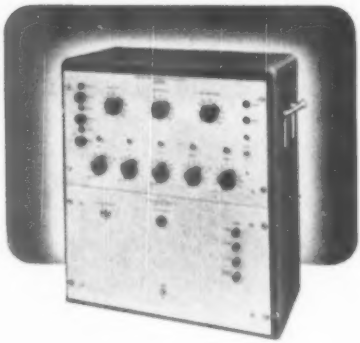

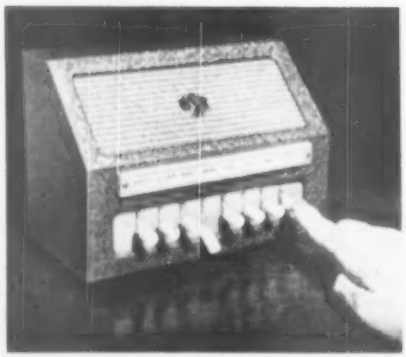

Telemaster Inter-Office Communicating Equipment.

The most up-to-date equipment available.

Adds new dignity to every business establishment, be it office, shop, restaurant, factory or indeed anywhere where there is need of rapid and simple means of communication.

Models available to suit every possible requirement. De Luxe multi-point models allowing communication between any or all stations, and executive control models for simple two-way conversation between master and extension.

Birmingham Sound Reproducers Ltd.
Claremont Works, Old Hill, Staffs., Eng.

Wireless World

RADIO AND ELECTRONICS

May 1950

40th YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK M.I.E.E.

Editor: H. F. SMITH

PUBLISHED MONTHLY. Price 2/- (last Thursday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Ethaworld, Sedist, London."

ANNUAL SUBSCRIPTION:
Home and Overseas, £1 6s. 0d.; U.S.A. and Canada, $4.50

BRANCH OFFICES:

Birmingham: King Edward House, New Street, 2
Coventry: 8-10, Corporation Street.
Glasgow: 26B, Renfield Street, C.2.
Manchester: 260, Deansgate, 3

In This Issue

EDITORIAL COMMENT 161
TELEVISION CAMERA TUBES 162
TRANSIENTS AND LOUDSPEAKER DAMPING. By *J. Moir* .. 166
SHORT-WAVE CONDITIONS. By *T. W. Bennington* 170
PHYSICAL SOCIETY'S EXHIBITION 171
DEFLECTOR COIL CHARACTERISTICS—3. By *W. T. Cocking* .. 176
WORLD OF WIRELESS 180
THE "OHM'S LAW" OF ELECTROSTATICS. By "*Cathode Ray*" 183
OLIVER HEAVISIDE AND HIS LAYER. By *Sir Edward Appleton* 187
MORE ABOUT SPOT WOBBLE. By *T. C. Nuttall* 189
TELEVISION INTERFERENCE. By *A. L. Parsons* 192
UNBIASED. By "*Free Grid*" 194
MANUFACTURERS' PRODUCTS 195
LETTERS TO THE EDITOR 197
RANDOM RADIATIONS. By "*Diallist*" 200

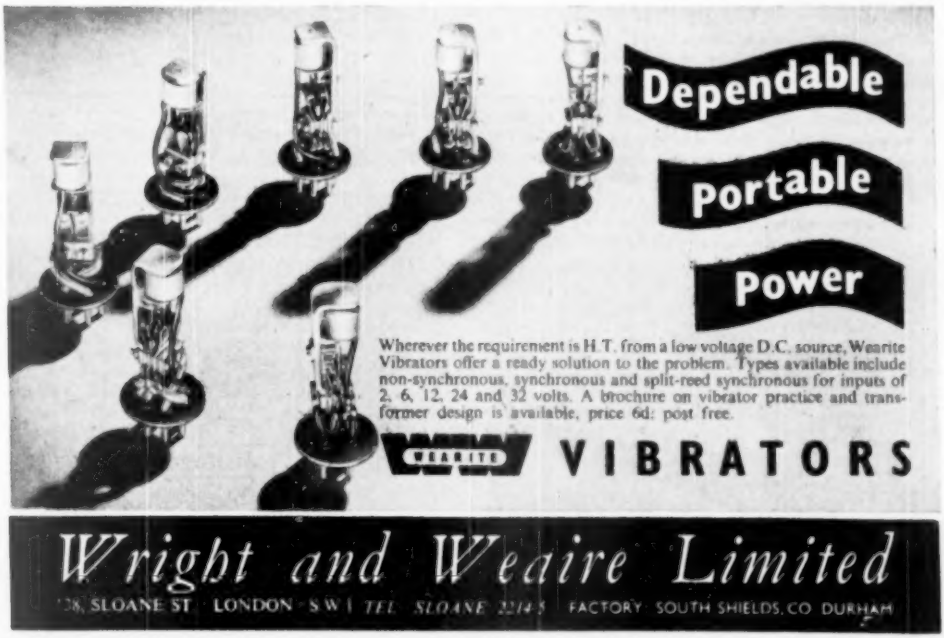

No. 2

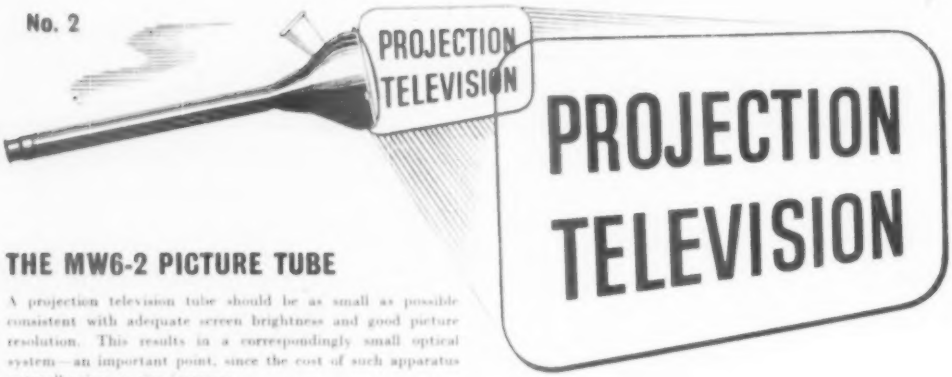

THE MW6-2 PICTURE TUBE

A projection television tube should be as small as possible consistent with adequate screen brightness and good picture resolution. This results in a correspondingly small optical system—an important point, since the cost of such apparatus naturally rises as size increases.

Tube size, however, is governed by spot size, and this in turn depends upon the value of the beam current, which should be low, and the anode voltage which should be high for minimum spot size. Limitations to these values are set by such practical considerations as tube life, safety, and manufacturing difficulties. All these requirements are satisfied by the MW6-2 picture tube which has a simple triode electrode construction and a 2½" diameter screen. Operated at an anode voltage of 25KV and the recommended beam current of 100 μA, the spot diameter is 0.0023 in., and the I_a - V_g curve is sufficiently steep to allow the tube to be driven by a normal video output valve.

The luminescent screen is backed by a very thin aluminium coating which reflects outwards much of the emitted light which would otherwise be directed to the rear of the tube. The increase in the output of forward-going light due to this feature may be as much as 75% to 80%. The metal backing also eliminates internal reflections, thus enhancing picture contrast, and also serves as an efficient ion trap.

A ring-shaped electrode situated between the anode and grid, and connected to one of the base pins (which should be earthed) forms

an effective spark trap, safeguarding the cathode from damage by intercepting any discharge resulting from, say, the release of a small quantity of gas under unintentional over-load conditions.

The anode terminal is surrounded by a glass shield to obviate risk of flash-over or leakage from the E.H.T. connection.

The external surface of the tube is coated with a graphite composition and must be earthed. This coating, with the

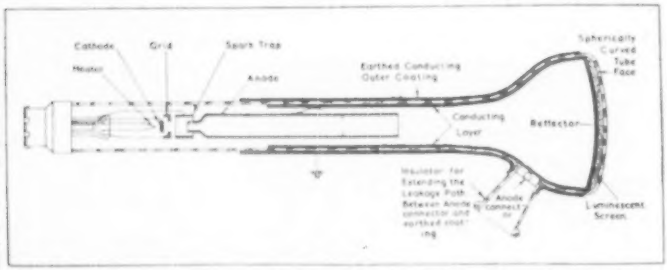

glass envelope and internal aluminium metallising, form a capacitor of approximately 450 μμF which, with a 1 MΩ resistor in the 25 KV lead, serves as the final smoothing of the E.H.T. supply.

TUBE DATA

HEATER suitable for parallel or series operation	V_h	6.3 V
	I_h	0.3 A
TYPICAL OPERATING CONDITIONS		
V_a		25 KV
I_a (av.)		100 μA
$V_{drive\ (pk)}$ excluding synchronising pulses		65 V
V_{g1} for beam cut-off		−40 to −90 V

Spark trap must be at earth potential

Mullard

Equipment manufacturers are invited to submit their enquiries to the following address:—

MULLARD ELECTRONIC PRODUCTS, LTD., SETMAKERS DEPARTMENT, CENTURY HOUSE, SHAFTESBURY AVE., W.C.2

(MVM 127)

Wireless World

VOL. LVI. No. 5. MAY, 1950

Television Standards for Europe

AT the risk of wearying our readers, we feel impelled to return to a subject that is fundamental to the healthy growth of television: the standardization of European transmission systems. It is generally admitted that the cost of good television programmes is high; obviously, without good programmes, the service cannot grow, and so any country embarking on television is in danger of the vicious circle. In Europe, a continent of relatively short distances, there is a real technical possibility of exchanging programmes between countries and so the high cost can be shared. Up to a point, exchanges of "canned" film programmes can be made without regard to the technical standards adopted by the various nations, but the exchange of living "actuality" items becomes impracticable unless there is uniformity of transmitting systems.

The present time is particularly opportune for again drawing attention to this matter. As reported on another page, an international study group of the C.C.I.R. is now visiting this country with the object of investigating our television practices from many different aspects. We hope and think the members will gain a favourable impression of the practicability of our 405-line system as an international standard. The arguments in favour of it are already well known; economy in bandwidth and economy in receivers are the principal factors. It happens that the bandwidth required is just within the capacity of existing European telephone cables, which could, therefore, be used for programme exchanges at off-peak hours. Receivers for a 405-line system can be produced cheaply by manufacturing methods that do not differ in essentials from those used in making broadcast sound receivers.

As to whether the picture quality produced by our system is good enough is a question for the members of the study group themselves to decide, but it may be pointed out that the quality at present obtained, good as we believe it to be, does not represent the ultimate possibilities of 405-line transmission.

Another argument in favour of 405-line transmission is presented in a letter, printed elsewhere in this issue, from a Dutch reader who is out of sympathy with the present European devotion to the idea of 625 lines. He contends that the next development will be in the direction of colour rather than in increase of definition, and so any monochrome system is to some extent a temporary expedient. Therefore, he argues, it behoves the war-impoverished continent of Europe to make a start with the cheapest practicable system.

A similar plea was recently made by O. S. Puckle, Chairman of Council of the Television Society, who went so far as to urge that "at least the Benelux countries" should adopt our standards. An official statement of the Radio Industry Council also stresses the advantages of standardizing on 405 lines. At first sight, this British advocacy of the British system may, to our continental neighbours, savour of commercial propaganda. Of course, British television firms would stand to gain from the rapid international growth of television, and to that extent would doubtless welcome the adoption of that system which, as many of them believe, would be most suitable. But this advantage would be shared by their continental competitors: further, British manufacturers have proved that they can design and make both transmitting and receiving equipment of any standard that their customers may require, and on this score it hardly matters to them what system may be chosen.

So far at least as *Wireless World* is concerned, there is nothing sinister, subtly propagandist or nationalistic in our advocacy of 405 lines: for reasons we have given, it is thought to be the best compromise between conflicting requirements for use as a European standard.

Television Camera Tubes

The Manufacture of Image Orthicons

ONE of the outstanding advantages of the Image Orthicon is its ability to operate under conditions of very low light intensity. It is even possible to obtain a reasonably good picture by the light of a single candle.

Since the Marconi Company first decided to rely mainly on these tubes for use in television cameras, considerable improvements in performance and manufacturing technique have been made. The latest type of tube is now being manufactured by the English Electric Valve Company at Chelmsford.

The electrode arrangement is shown diagrammatically in Fig. 1 and it consists of four basic sections—photo-cathode and image section, target group, electron gun and electron multiplier.

The optical image is focused on to the semi-transparent photo-cathode which is deposited on the optically-worked flat face of the tube. The resulting electron emission from the photo-cathode may be considered as constituting an electron picture which in turn is imaged by means of a longitudinal magnetic field on to the target plane. (This electron imaging is of the long-field unity-magnification variety.)

The target consists of an extremely thin sheet of glass of definite conductivity. Electrons bombarding the target (at a velocity of approximately 300 V) cause the release of secondary electrons. The secondary-emission coefficient being greater than 2, a net gain is achieved at this stage as well as a reversal of "polarity"; that is to say, illuminated picture points *lose* electrons and so appear on the image side of the target as a *positive* charge. All the secondary electrons are collected by the "target screen" which is an extremely fine gauze located parallel to and extremely close to the glass target on the image side.

The finite resistance of the glass target allows it to function as a two-sided target; that is, it can be scanned on the side remote from the image. As always in an Orthicon the electron velocity of the scanning beam is reduced substantially to zero at the plane of the target. This process involves a number of problems all of which had, however, previously been solved for the case of the straight Orthicon. The principal problem is to arrange for orthogonal landing of the scanning beam in a sharply focused condition. This is achieved by use of magnetic deflection fields superposed on a long focusing field and

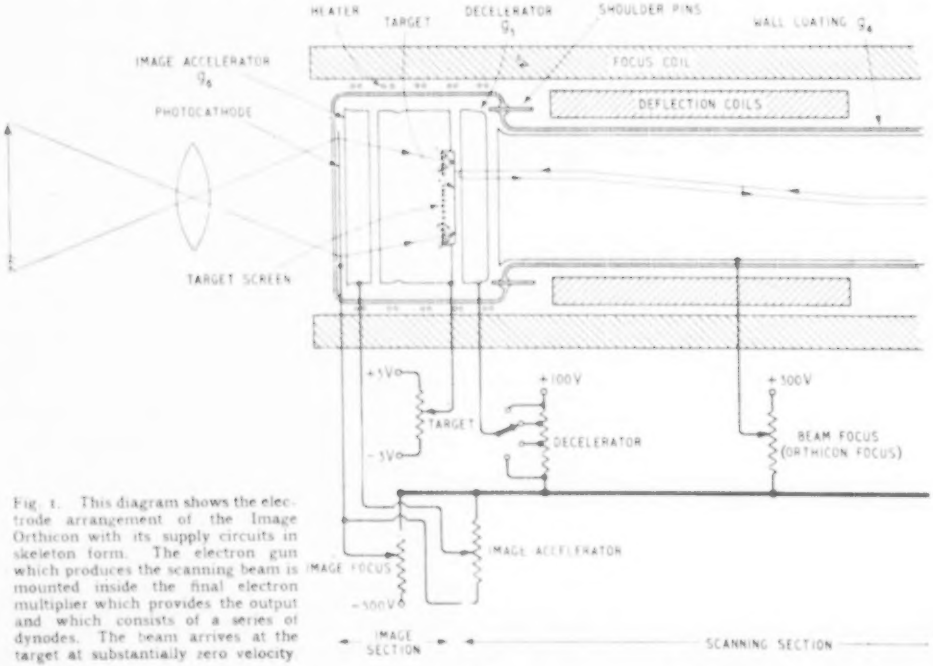

Fig. 1. This diagram shows the electrode arrangement of the Image Orthicon with its supply circuits in skeleton form. The electron gun which produces the scanning beam is mounted inside the final electron multiplier which provides the output and which consists of a series of dynodes. The beam arrives at the target at substantially zero velocity.

Component parts of the Image Orthicon with the completely assembled tube shown on the extreme right.

by the use of auxiliary electrostatic lenses constituted by the various electrodes g_1, g_2 and the target screen.

The mode of operation of the tube can conveniently be illustrated by considering the case of a picture consisting of a single white picture-point on a uniformly black background. In this case only one picture-point of the target is electron-illuminated. When the scanning beam scans the target, electrons will land on the dark portions until a target potential is established (near to zero or cathode potential) for which no further landing is possible. The whole

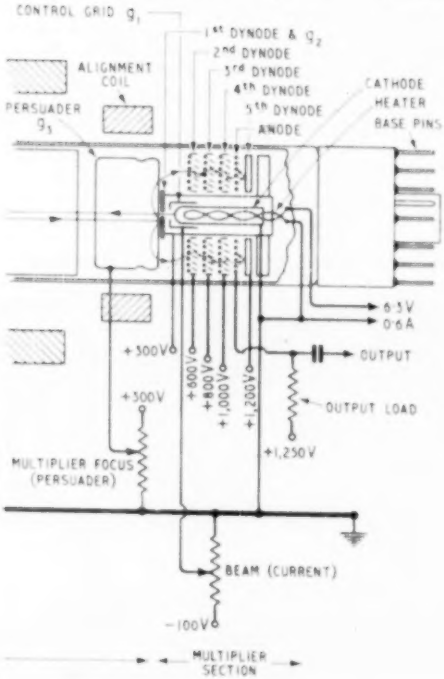

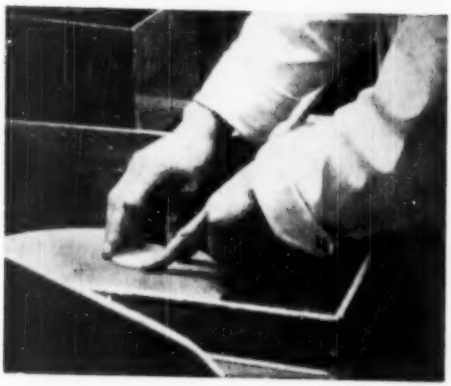

Two of the processes involved in manufacture. Optically working the flat face of the tube and (below) assembling the gun mount and electron multiplier on a jig.

Assembling the image mount and stem tube on a jig.

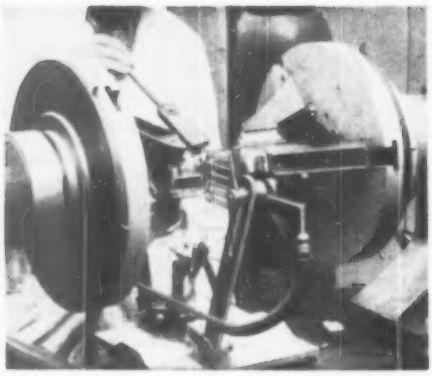

Sealing the bulb to the stem on a glass-working lathe.

of the scanning beam is returned, and does in fact return to the gun structure in the immediate vicinity of its starting point, which is the "defining aperture" in electrode g.

In the case of the white picture-point, however, electrons are continuously being lost on the image side of this part of the target and electrons are deposited to neutralize the resulting local positive charge. If the resistivity of the glass target were infinite, this situation would be a transient one and an equilibrium condition would be built up in which the scanning beam became non-cognizant of the white picture point. However, owing to leakage through the target, the landed electrons on the scanning side leak through to the positive charge on the image side so that a fresh landing is made on every scan. This results in the reduction of the return-beam current which constitutes the signal from the tube.

To realize the full potentialities of this scheme it is necessary to apply a considerable amount of electron multiplication to the return-beam current before taking it as signal to the normal amplifier. This is accomplished by a series of annular multiplier discs of the pin-wheel variety (dynodes d_1, d_2, d_3 and d_4) which are built concentrically around the electron gun structure. The role played by the target screen must now be clarified. It is normally set some 2-V positive of the "non-landing potential." Now it is impossible for a white-picture point to go substantially more positive than this 2-V value because, if this were to happen, the secondary electrons would be unable to reach the target screen and have literally no where else to go. This voltage defines the range of linear operation of the tube and it would be expected that if the illumination were sufficient to allow a white-picture point to reach this voltage in a time less than the picture repetition time this would result in "saturated whites." In fact this phenomenon is not observed. On the contrary, a new regime sets in which may be described as "electron redistribution." The white picture points proceed to rain electrons on to the darker picture points and so maintain picture contrast. This phenomenon plays at least three very useful roles:

1. It allows the tube to operate over an extraordinarily wide range of illumination.

2. It produces a desirable reduction in the gamma of the picture.

3. It reduces the effective storage time of the tube and so eliminates the appearance of "smearing" on moving objects.

As can be seen from Fig. 1, the scanning beam originates from the cathode and emerges through a hole in the centre of the electrode labelled 1st dynode and g. The latter is its initial role for, being 300-V

Vacuum r.f. heating is used in the preparation of the target mesh.

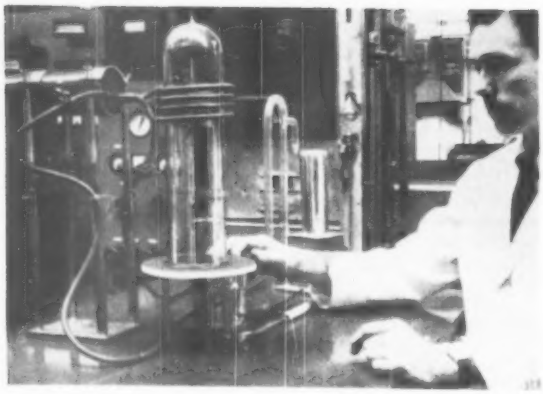

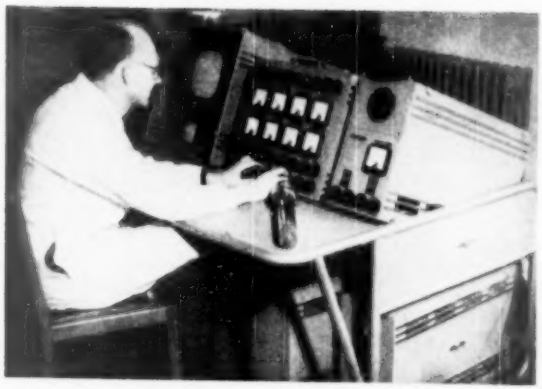

Test gear used for checking the characteristics of the finished tube.

positive to cathode, it acts as the anode of the electrode gun. The return beam lands on it away from the hole, being persuaded to do so by the deflecting system g_1, which is aptly termed the "persuader," since its object is to ensure that the return beam lands on the electrode clear of the emergent beam.

To the return beam the electrode acts as the first dynode of the electron multiplier. Secondary emission is produced and the paths of the secondaries are to the so-called pin-wheel 2nd dynode at which more secondary electrons are produced, and thence to d_1, d_2, d_3 and the anode from which the output of the tube is taken. These pin-wheel dynodes are mounted concentrically with and outside the electron gun and comprise inner and outer rings holding a series of radial slats—somewhat like a radial Venetian blind.

Manufacturing Problems

Not the least of the difficulties of tube manufacture arises from the fact that the tube comprises virtually four distinct sections, so that a fault in any one renders the complete tube useless. This is, of course, unavoidable since all four sections must necessarily be in a common evacuated envelope.

The parts of the tube which have produced the greatest manufacturing problems are:—

The Photo-cathode. A cæsium cathode is used and the difficulties arise because some of the processes needed for obtaining the best cathode conditions are in conflict with other requirements, notably that of avoiding leakage to other electrode surfaces.

The Target Mesh. In order to avoid limiting the resolution of the tube the target screen has to be of extremely fine mesh; in the present instance 500 per linear inch. Also a high degree of "transparency" is required. These screens are made by an electrolytic process from a ruled-glass master. This master is sputtered with palladium which is then wiped off the high spots to leave a palladium grid in the troughs of the rulings. The electroplating deposits copper on the palladium which is peeled off under water to form a copper mesh.

The Target Proper. This is a sheet of glass approximately 0.0002-in thick and 1½-in diameter. To obtain the necessary rigidity of mounting and high degree of flatness it is stretched in drumhead fashion on a metal ring. Natural surface tension processes of a delicate character are involved in producing this unit.

The Target Assembly. The problem here is to obtain highly uniform target to mesh spacing of the order of 0.001 in. In view of the extremely delicate nature of both elements this calls for special technique.

Electron Gun. This is in many respects of normal construction but involves the use of a defining aperture which is of the order of 0.001-in diameter.

Electron Multiplier. This structure, which is realized in magnesium-silver alloy, consists of five stages of multiplication and has to show a gain in the region of 200 total.

Under good conditions, the standard 3-in Image Orthicon can do justice to a 500/600-line picture resolution. Its contrast reproduction is also entirely satisfactory under proper lighting conditions.

The unique feature of the tube is its sensitivity and it is this, taken in conjunction with a number of important practical features, which renders it an outstanding camera tube for outside broadcast work.

British Industries Fair

MORE than fifty radio and electronic manufacturers are among the 3,000-odd exhibitors at this year's B.I.F. which opens simultaneously at Castle Bromwich, Birmingham, and Earls Court and Olympia, London, on 8th May. Generally speaking the "heavy engineering" side of radio is concentrated at Birmingham, where B.T.H., G.E.C., Marconi's, Westinghouse, B. I. Callenders, British Electric Resistance, Brush Electrical, Chloride, English Electric, Londex, Morganite Resistors, Plessey and Telegraph Construction & Maintenance are exhibiting.

Radio is well represented at Olympia where some forty stands in the Radio and Scientific Instrument Sections are occupied by manufacturers of domestic receivers, valves, test and measuring equipment, communications gear, sound reproducing equipment and hearing aids. The exhibitors at Olympia include:—

Atmos Laboratories	Lee Products
B.T.H.	M.S.S. Recording
Baldwin Instruments	Magnetic
British Electronic Products	Measuring Instruments
British Vacuum Cleaner	Megatron
Brown, S. G.	Metro Pex
Cinema Television	Mullard
Compton Organ	Osmaside
Cooper Telephones	Pilot
Dallas, John F.	"Q Max"
Dawe Instruments	Sangamo Weston
Ekco	Scophony Baird
Electronic Developments	Shipman, E.
Elliott Bros.	Simon Sound Service
Extract Telephone	Southern Instruments
G.B. Equipments	Standard Telephones & Cables
General Acoustics	Taylor Electrical Instruments
Hallen Sound Equipments	Tinsley Engineering
Inbelt	Twentieth Century Electronics
Johnson, Matthey	Whitley Electrical
Lectron Hearing Aid	Wolter Transformer

The Fair, which lasts until 19th May, will be open each day except Sunday, from 9.30 to 6.0. Admission is by Trade Buyers' Badge which is obtainable at the entrances price 2s 6d on presentation of a trade buyer's business card. The public will be admitted on the 14th and 17th on payment of 2s 6d.

Wireless World and *Wireless Engineer*, with the technical books in each of the specialized fields covered by sixteen of the thirty-two journals in the Iliffe group, will be featured on a stand at Castle Bromwich.

Transients and Loudspeaker Damping

Experimental Investigation of Some Conflicting Theories and Beliefs

By J. MOIR, M.I.E.E.

VERY widely divergent opinions appear to be held among high-quality reproduction enthusiasts on the subject of amplifier output impedance, and after hearing a recent discussion the writer decided to try to produce some experimental evidence on the problem. First, let us attempt a recapitulation of the views of both (or is it three?) sides. Those "in favour" claim that a low output impedance increases the magnetic damping of the motion of the moving coil and thereby improves the transient response, while those "against" claim that low output impedance definitely impairs the h.f. response of the speaker and therefore degrades the transient response. A sub-section of the "against" claim that no improvement is to be obtained by reducing the output impedance below, say, 10% of the voice coil impedance. These viewpoints will be examined, first to see what might be expected and then to see what actually happens.

As a typical transient, a square pulse of voltage will be applied to the speaker, in the expectation (ill founded) that a square wave of air pressure will result. A square wave of this kind can be a severe test for a loudspeaker, or indeed any mechanical device, and it can be assumed that if it deals faithfully with this pulse, speech and music will not represent a serious problem. A square pulse also has the advantage that one can visualize the result without much difficulty.

Before proceeding further it is probably advantageous to clear the air a little over the meaning of amplifier output impedance, and magnetic damping.

The output impedance is the value of Z given by applying E volts (a.c.) to the amplifier output terminals, the amplifier being alive and working, and obtaining a current of I amps flowing through the amplifier output circuit, Z being E/I. This can be measured with a voltmeter and ammeter or more elegantly by a bridge method. Z varies with frequency, a typical sort of result, obtained on an amplifier employing two Ph 44 valves in push pull, being shown in Fig. 1. Without feedback the value of Z obtained over the middle frequency region, say 250/1,000 c/s, would generally be about half the "optimum load" for the amplifier, but given the freedom of applying feedback, the designer can make the output impedance almost anything he requires without altering the "optimum load" to which the amplifier must be connected if maximum undistorted power is to be obtained. Given a "perfect" output transformer without losses, the impedance that is measured is that of the output valve divided by n^2 where n is the ratio of the output transformer, and it is a pure resistance at all frequencies. A practical transformer introduces additional losses and also introduces various reactances that make the impedance change with frequency as shown in Fig. 1; but for simplicity the amplifier impedance will be assumed to be a pure resistance.

It should also be noted that it is the ratio of speaker impedance to amplifier impedance and not the absolute value of output impedance that is of consequence; a speaker of 100 ohms and amplifier of ten ohms will produce (to a first approximation) the same results as a speaker of 10 ohms

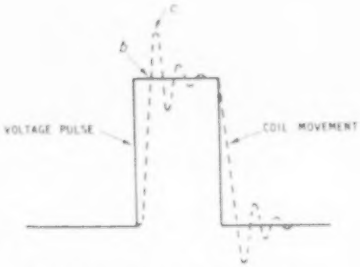

Fig. 2. Applied voltage and coil motion.

Fig. 1. Variation of output impedance with frequency in a typical amplifier.

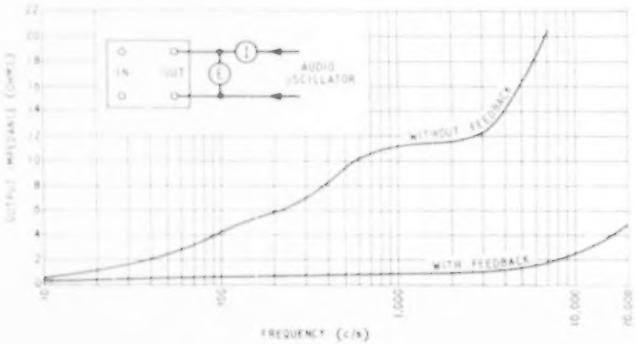

fed from an amplifier of 1 ohm, i.e., the damping factor is 10/1 in both cases.

$$\text{Damping Factor} = \frac{\text{Loudspeaker Impedance}}{\text{Amplifier Impedance}}$$

Now for magnetic damping. If a coil of wire, or even a single turn is moved in a magnetic field, a voltage is induced into the coil, and if the ends of the coil are connected to a resistance, current will flow through the coil and resistance, power will be dissipated and extra effort will have to be exerted to move the coil through the field, or if the coil is swinging freely in the magnetic field it will be brought rapidly to rest.

With this preliminary excursion let us consider how the coil and cone might be expected to move when a square wave of voltage is applied, Fig. 2.

As the coil (and cone) possess mass they move off slowly from the position of rest, lagging behind the voltage, but on reaching the position *b*, corresponding to the applied voltage, they overshoot to a point *c* where they are brought to rest by the restraining influence of the surround, and the kinetic energy stored in the moving mass becomes potential energy stored in the "springiness" of the surround. The coil then reverses direction, swings back through the mean position, oscillating about its final position until the energy stored in the moving mass is dissipated in frictional losses, and the coil comes to rest displaced from the unenergized position by an amount corresponding to the applied voltage. When the voltage pulse is removed, the coil returns to the "off" position lagging behind the current, overshoots, oscillates several times just as before, finally coming to rest ready for the next pulse.

Without any doubt it will be agreed that as the oscillations were not part of the original waveform they should not be inserted by the loudspeaker. The energy appearing in the oscillation was part of the signal energy, the loudspeaker only acting as a frequency converter and rearranging the frequency spectrum of the square pulse to emphasize the frequency corresponding to the natural frequency of the mass of cone and coil on the "springiness" of the surround.

After each pulse the coil is finally brought to rest due to the energy stored in the moving mass being dissipated by the various losses in the cone and surround, the air friction (viscosity) losses due to the air trapped in the narrow gaps between coil and pole pieces, the energy dissipated as sound, and, most important of all from our point of view, the electrical losses in the moving coil—amplifier output circuit. When the coil overshoots its final position the voltage generated in the coil exceeds the driving voltage, circulating a current back through the amplifier output impedance and introducing an I^2R loss.

The reality of these oscillations is indicated by Fig. 3(a) an oscillogram of the voltage across the voice coil terminals when a d.c. voltage pulse is applied. The rate of rise and fall of voltage is too great to be shown on the photograph but the oscillation at the top of the pulse and end of the pulse is clearly shown. In this case the effective resistance of the amplifier feeding the speaker was roughly twelve times the d.c. resistance of the coil.

It will be appreciated that though these are records of the transient voltage across the coil; this voltage is produced by the motion of the coil and they are therefore records of the coil motion.

The effects of amplifier output resistance on the coil damping were directly measured in the following way. A small piece of aluminium foil was fixed to the voice coil and provided with a thin flexible connection. Across the speaker frame, a micrometer was supported so that it could be screwed in to touch the foil strip on the voice coil, contact being indicated by the flashing of a small neon lamp in series with the foil and micrometer head. The voice coil was deflected inwards by passing a direct current through the coil and on switching this "off" the coil

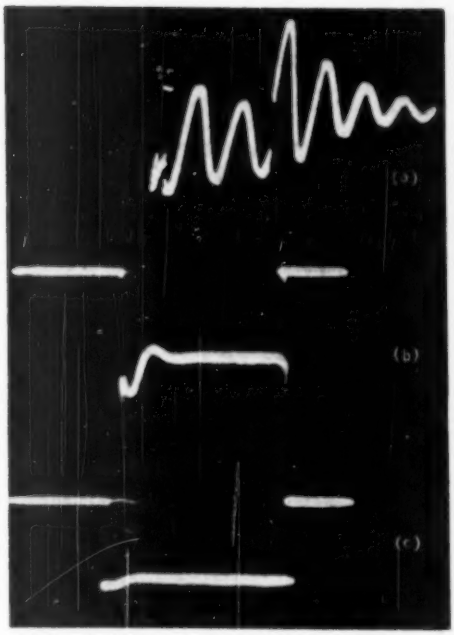

Fig. 3. Oscillations of voice coil supplied from source of adjustable resistance, (a) 100 ohms, (b) 10 ohms, (c) 2 ohms.

Fig. 4. Amplitude of first overshoot as a function of resistance across the moving coil.

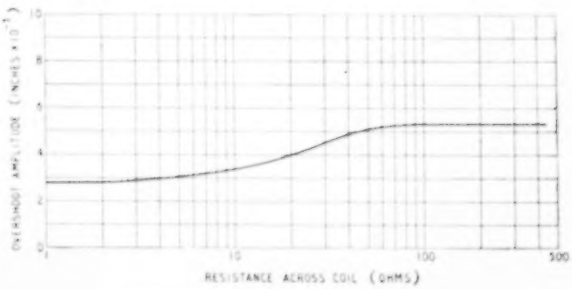

and cone swing out, pass through the unenergized position, overshoot, oscillate about the mean position, and finally come to rest in the centre. The micrometer served to measure the amplitude of the first overswing and this was checked for a range of values of resistance shunted across the coil. The results are shown in Fig. 4. It will be seen that the overswing continuously decreases with decrease of R down to a value of about 2 ohms and then becomes constant. This is significant as it indicates that in this case there is no advantage in using an amplifier having an output resistance less than half that of the loudspeaker.

It was believed that a direct mechanical measurement of the overshoot would perhaps be a more convincing indication of the results than would a measurement of the voltage across the voice coil, but it is simpler to make the electrical measurement. By making the applied pulse repetitive and using a variable resistance across the voice coil, the oscillation of the voice coil can be adjusted to the point at which no overshoot is observable on the oscilloscope. In this instance, a resistance of 3 to 4 ohms was necessary to obtain a unidirectional return to the central unenergized position, but the actual value is not highly critical. Figs. 3(b) and 3(c) indicate the voice coil motion for values of 10 ohms and 2 ohms respectively and it will be observed that a resistance equal to the voice coil impedance produces a marked reduction in the amplitude of oscillation when compared to the result shown in Fig. 3(a). The circuit used to provide the repetitive pulses for Figs. 3(b) and 3(c) leaves the coil connected to the battery (of very low resistance) at the peak of the inward swing effectively removing any trace of oscillation of the voice coil at the top of the pulse.

Fig. 5. (a) Practical amplifier circuit, (b) Equivalent circuit with resistor substituted for valve, (c) Values referred to transformer secondary. Leakage inductance L_L, and moving coil inductance and resistance L_c and R_c. Loudspeaker assumed "perfect" with no resistance or static inductance. (d) Primary inductance of transformer and static inductance of coil removed. (e) Equivalent circuit (including loudspeaker) at frequencies below 100 c/s.

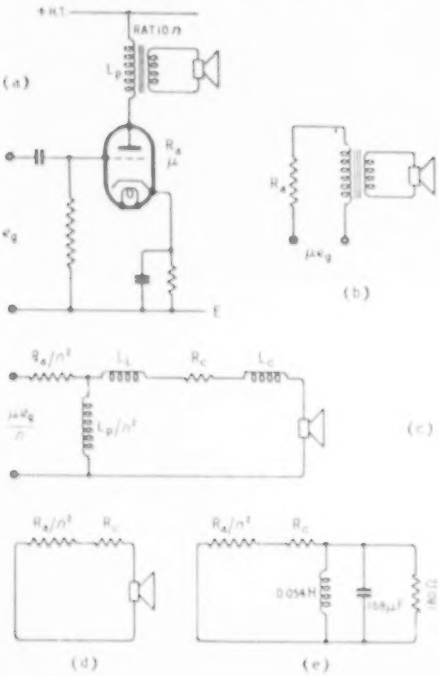

The effects to be expected from shunt resistance on the voice coil can best be decided by considering the equivalent electrical circuit of the loudspeaker and driving amplifier. In Fig. 5(a) is the practical amplifier circuit and in 5(c) the equivalent circuit with all values referred to the secondary. In the low frequency region the transformer leakage inductance and moving coil inductance (measured with coil held stationary) are too small to be of significance and can be ignored. The transformer primary inductance L_p is too high to be of interest if the transformer is a good one and of no interest if it is a poor one because no quality enthusiast would use it. The circuit as seen by the moving coil thus becomes that of Fig. 5(d). To define the equivalent electrical circuit of the moving coil itself the impedance/frequency characteristic was obtained using the measuring circuit of Fig. 6(a). This produced the curve shown, characteristic of a parallel resonant circuit from which it may be deduced that the coil in motion is equivalent to a perfect inductance of 0.054H in parallel with a condenser of 168 μF and a resistance of 180 Ω. The values may appear somewhat surprising, but L and C have no physical existence, the effect of L and C being produced entirely by the motion of the voice coil in the magnetic field. The frequency of resonance, 52.5 c/s, is that of the mechanical system comprising the mass of the cone and coil supported on the "spring" formed by the cone surround and centring. The shunt resistance represents the energy loss due to internal friction in the cone and surround, the viscosity loss is the air in the narrow gaps between the voice coil and magnet and the regrettably small amount of energy dissipated as sound.

These values can now be added to the equivalent circuit of Fig. 5(d) to give 5(e). Over the low frequency range considered the performance of this LCR combination will be exactly the same as that obtained from the circuit of Fig. 5(a) with the actual speaker, but the equivalent circuit has the great advantage (at least to an electrical engineer) of rendering the performance more susceptible to calculation.

For a circuit of this type there is a critical value of shunt resistance below which the circuit is non-oscillatory. This is given by $R = \frac{1}{2}\sqrt{L/C}$. Substituting the values of L and C obtained from the electrical circuit it is found that R = 9 ohms.

Let us see just what is meant by the expression "a critical value of resistance which will make the circuit completely non-oscillatory." In Fig. 7 the equivalent circuit of Fig. 6(c) is redrawn to add a battery, high resistance and switch. In the position shown the battery charges the condenser through the high resistance and on closing the switch the condenser is discharged through the parallel combination of L and R. With values of R well above

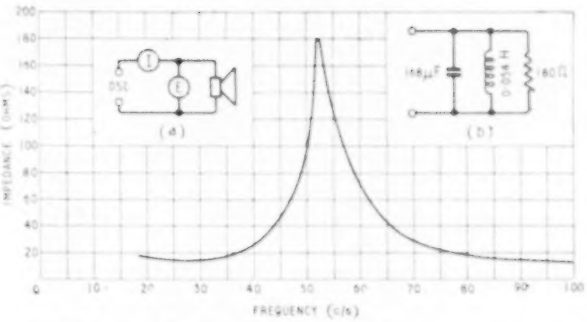

Fig. 6. Impedance-frequency characteristics of a moving-coil loudspeaker measured with circuit (a). The curve approximates to the response of a parallel resonant circuit with the values given at (b).

the critical value the voltage across the circuit will oscillate for several cycles as shown in Fig. 7(d), the amplitude of oscillation gradually decreasing as the energy, originally stored in the charged condenser, is dissipated in the resistance R. If the process is repeated with a decreased value for R the number

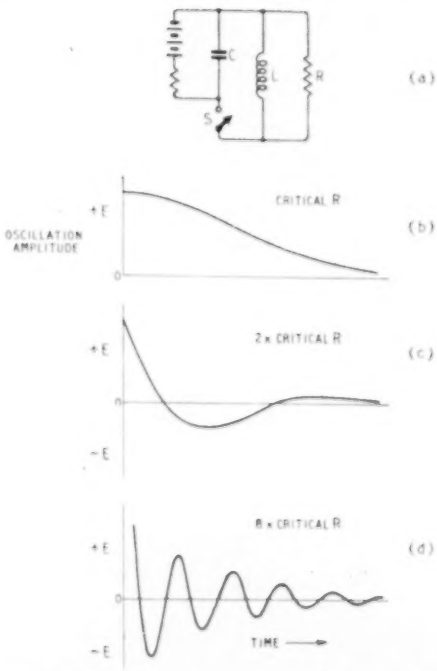

Fig. 7. Equivalent electrical circuit of moving-coil loudspeaker with the addition of a battery. Voltage fluctuations on closing the switch S are shown at (b), (c) and (d).

Fig. 8. Effect of field current on voice coil oscillation.

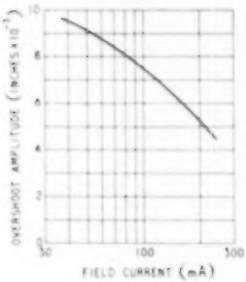

of cycles of free oscillation will decrease as R is decreased. For the critical value of R no oscillation will take place, the voltage falling to zero without overshooting. Further decrease in R will merely make the voltage fall to zero more quickly. The critical value of resistance is that value which just prevents the current reversing in direction, i.e., the current approaches its final value from one side only.

The process is identical with the mechanical motion of the coil and cone; above a critical value for the damping the coil will oscillate several times before coming to rest; at a critical value of damping it will just not oscillate at all, but return to the final position without overshoot; below this value it will merely return more quickly than for the critical value.

In this particular speaker it will be seen that the critical value of resistance is calculated to be 9 ohms whereas the value below which no overshoot (oscillation) occurs is about 2.5 ohms, the difference being due to the 8 ohms effective resistance of the voice coil below which the damping circuit resistance cannot be reduced *because the external resistance is always in series with the voice coil's own resistance.* Short of introducing an amplifier having a negative output resistance there appears to be little or nothing to be gained by reducing the output resistance below 10-20 per cent of the d.c. resistance of the voice coil.

Something can, however, be achieved in a different direction; if the damping current that flows cannot be further increased by decreasing the circuit resistance, it may still be increased by increasing the voice coil circuit voltage. The voltage generated by the voice coil moving in the field is given by $E = vlB$, where B = gas flux density, l = length of wire, and v = coil velocity.

For a given gap volume l the length of wire cannot be increased, v, the coil velocity, is fixed by the frequency of the oscillation, leaving only the gap density B to be increased. This is a parameter that is at the designer's disposal (though gauss cost money), and Fig. 8 is a plot of the measured amplitude of oscillation of the voice coil for a fixed shunt resistance of 10 ohms (plus coil resistance) and a range of field currents known to be below the saturation value. It will be seen that, roughly speaking, a fourfold increase in gap density (field current) reduces the amplitude of overshoot oscillation by a factor of two.

This would appear to dispose of the suggestion that feedback amplifiers can introduce too much damping

as it will be seen that the obtainable damping is severely limited by the voice coil resistance. Incidentally, the suggestion that too much negative voltage feedback can make an amplifier unable to deal with fast transients is also unsound. Excluding tricks, the addition of feedback makes the characteristics of an amplifier approach more and more closely to the characteristics of the components of the feedback network, i.e., the two resistors which determine the amount of feedback, and resistors at least are like Cæsar's wife.

Finally, the question of "too much feedback reducing the h.f. response and thereby degrading transients." This is a point so obscured by side issues that no precise answer can be given, but some indication of the result may be helpful. The voice-coil impedance of almost all speakers increases with increase of frequency due to the coil inductance, thus reducing the driving current and the acoustic output at high frequency. If the speaker is driven from a high-impedance source, this current decrease, being a function of total circuit resistance, is not so serious as when a low-impedance source is used. Thus it can be said that the relative h.f. output will always be greater when a high-impedance source is used. However, if the overall response is "flat," with the usual sort of "non-feedback" output impedance ratio of amplifier/speaker = $\frac{1}{4}$, increasing the output impedance will increase the transient distortion by over emphasizing the h.f. components of the pulse. Whether change of output impedance improves or degrades the transient response always depends upon where you start from, but it has been shown that an increase in output impedance always makes the transient "overshoot distortion" more troublesome, whatever it does to the high-frequency components of the transient.

Finally, do these oscillations really produce noticeable degradation in quality? Does an amplifier with a signal applied to its output really behave like a decent clean-living resistor? Can the loudspeaker be made to produce a good square acoustic signal, and if it can, what does it sound like? These and other questions must be left for later discussion.

SHORT-WAVE CONDITIONS

March in Retrospect : Forecast for May

By T. W. BENNINGTON
(Engineering Division, B.B.C.)

DURING March the average maximum usable frequency for these latitudes decreased very slightly during the day, and increased considerably during the night. These are the normal seasonal variations.

Daytime working frequencies remained high; in fact, higher on the average than had been expected. U.S.A. stations on frequencies over 30 Mc/s were not often heard, but the 28-Mc/s band held on remarkably well. 11 Mc/s was about the highest regularly usable night-time frequency.

Sunspot activity was, on the average, higher than during the previous month. The giant sunspot of February 20th (now much reduced in size) crossed the sun's central meridian again on March 18th, and further ionospheric disturbances followed.

Though the early part of the month was ionospherically "quiet," the latter part was subject to much ionospheric storminess, and the month as a whole must be classed as a disturbed one. The most disturbed periods were 6th-7th (minor), 13th (minor), 19th-22nd, 24th-25th and 27th-28th. Strangely enough, no Dellinger fadeouts were reported during the month.

Forecast.—Daytime m.u.fs in these latitudes should continue to decrease during May, whilst night-time m.u.fs should continue to increase.

Daytime working frequencies on east-west circuits should therefore be considerably lower, and those on north-south circuits somewhat lower, than during April. It is unlikely that 28 Mc/s will be usable over east-west circuits at any time during the month, though it may occasionally be usable in southerly directions. Moderately high frequencies will, however, remain of use for longer periods than during April, because of the longer duration of daylight at this end of the circuits. Frequencies as high as 14 Mc/s should remain regularly usable until after midnight, and the lowest frequency really necessary at any time of night should be of the order of 12 Mc/s.

Daytime frequencies for medium-distance communication should be somewhat higher than during April because such communication will take place via the E or F_1 layers for several hours daily. There is likely to be a big increase in the rate of incidence of Sporadic E, and transmission up to 1,400 miles may be frequently possible, perhaps on exceptionally high frequencies.

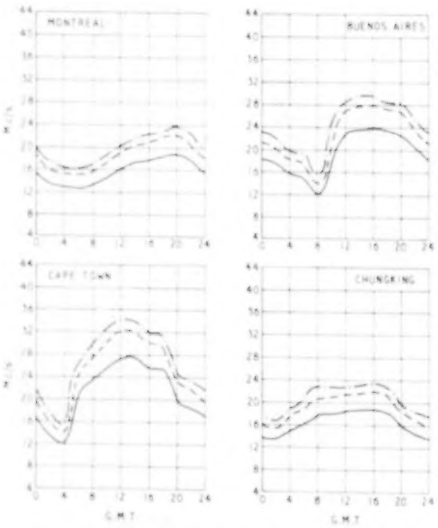

The curves indicate the highest frequencies likely to be usable over four long-distance circuits from this country during the month.

These Valves make News!

NEW TYPES FOR V.H.F. OPERATION

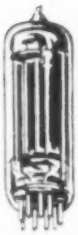

B9A (Noval) Base
Seated Ht. 2 1/8in. max.
Diameter 7/8in. max.
Retail price 20/-.

TYPE 5763 Miniature Beam Power Amplifier

Specially designed for use as frequency multiplier to 175 Mc/s., type 5763 will give considerable output for very small driving power. As a Class C power amplifier it will operate efficiently at frequencies exceeding 100 Mc/s.

RATINGS

Heater Voltage	6.0 v.	
Heater Current	0.75 a.	
Heater Cathode Potential	100 v. max.	
Anode Voltage	300 v.	Absolute maximum values
Screen Voltage	250 v.	
Anode Dissipation	12 w.	
Screen Dissipation	2 w.	
Bulb Temperature	250° C.*	

* At the hottest part of bulb surface.

Operation as Class "C" amplifier or oscillator at 50 Mc/s.

Anode Voltage	300 v.
Screen Voltage	250 v.
Driving Power	0.35 w.
Output Power	8.0 w.

Operation as Frequency Multiplier to 175 Mc/s.

	Doubler	Tripler
Anode Voltage	300 v.	300 v.
Screen Supply Voltage	300 v.	300 v.
Driving Power	0.6 w.	0.6 w.
Output Power	3.6 w.	2.8 w.

Octal Base
Seated Ht. 3 1/8in. max.
Diameter 1.5/16in. max.
Retail price 25/-.

TYPE 2C26A Power Triode

This valve will function efficiently as oscillator or power amplifier at 150 Mc/s and is particularly suitable for pulse operation.

RATINGS

Heater Voltage	6.3 v.
Heater Current	1.1 a.
Anode Voltage	400 v.
Anode Dissipation	10 w.

PULSE RATINGS*

Peak Anode Voltage	3,500 v.	Absolute maximum values
Peak Anode Current	6.0 a.	
Peak Grid Voltage	700 v.	

* For Pulse length 10μS. Duty Cycle 1 per cent.

BRIMAR

WRITE NOW TO DEPT. 4530
for data sheets on the above valves.

TECHNICAL ADVICE SERVICE

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.

The following is an independent report by
J. C. G. Gilbert, F.R.S.A., Assoc. I.E.E., M.Brit. I.R.E.,
reprinted from the *Music Trades Review*, March, 1950

THE ACOS G.P.20 MICRO-CELL PICK-UP

Manufacturers: Cosmocord Ltd., Enfield, Mddx.

Price: £2 10s. plus £1 1s. 5d. purchase tax.

In the interesting realm of gramophone pickups, the crystal types have always been capable of producing excellent results when designed correctly and when operated with the correct circuit constants. The *Cosmocord* organisation' have specialised in this type of pickup for many years, and the unit now under review must be the nearest approach to perfection yet reached for this crystal type.

Construction

The pickup head is a really diminutive size, being about one inch high, half inch wide and five-eighths of an inch deep. The sapphire needle employed is mounted on a flat stiff torsion arm that freely accommodates vertical movement, and conveys the modulated track to the crystal without any lost motion. To prevent damage to the armature and needle a more rigid spring finger takes up the shock if the pickup is accidentally dropped on the record. The head is mounted in a neat moulding with an attractive chromium motif. The head is detachable from the carrying arm and contact is made via two small spring contacts. The arm is a cream moulding with an offset head in order to reduce the tracking error, and at the rear end is a beautifully smooth bearing, incorporating a counterweight so that the pickup pressure on the record is between 12 to 14 grams. The base for mounting the pickup to the motorboard is adjustable between 1 ⅛ to 2 ⅝ inches, thus accommodating all types of motor heights above the motorboard. An extremely thin screened lead from the head to the base is housed in a slot in the moulding, and due to its lightness it reduces drag to an absolute minimum.

The unit is supplied with a baseboard template for correct mounting and a moulded support for the pickup when not in use.

Test Report

The pickup was mounted according to the instructions, and the adjustable height of the arm greatly facilitated the correct position of the pickup head relative to the record. A series of tests were done with various constant frequency records, with (*a*) an open circuit valve voltmeter, and (*b*) a wide range amplifier and Voigt domestic loudspeaker. The valve voltmeter test confirmed the published graph under this condition being 1 at from 30 cps. to 300 cps. followed by a gradual drop by 3db. to 1,000 cps. and remaining within 1 db. to above 10,000 cps. With an amplifier having a grid leak of 500,000 ohms input, the bass register fell below 100 cps. to 30 cps. by 8 db. By the inclusion of a simple resistance capacity filter in parallel with the pickup, the whole of the response above 300 cps. can be raised to that below and then the pickup response is sensibly constant throughout the recording range. On some of the full amplitude cut constant frequency records one always expects to hear much direct radiation from the pickup itself, but one of the most remarkable points of the *Acos* pickup is the almost complete absence of noise. On standard recordings of wide dynamic range, the direct noise is so small that it can be heard only when the amplifier is shut off.

Compared with other types of pickups that possess a similar wide band characteristic, the output is extremely high, for it exceeds a half volt on normal records, and can therefore be used with the majority of commercial radio receivers without the need for a pre-amplifier. Modern high fidelity magnetic moving coil and ribbon types usually have outputs in the order of millivolts or even less, and therefore it is essential to use a fair amount of pre-amplification before connecting the signal to the main amplifier. This point alone should encourage many potential customers to purchase this pickup. The vertical flexibility of the needle armature motor rumble, that is noticeable on more rigidly mounted armatures, virtually disappears. Due to the very low downward pressure of 12-14 grams coupled with the freedom of movement, the sapphire should last for many hundreds of playings before any noticeable wear is experienced. During the period of this test the needle was inspected before using it on an Adams and Hilger Shadowgraph that enlarged the needle by 50 times. After nearly two months' use, during which some 150 records were played, no measurable wear was found. The pickup was purposely dropped several times from two inches on to the record, and due to the efficiency of the spring protector no damage was suffered by the sapphire.

On musical records the results are truly outstanding. The delicacy of the violins, the sourness of the oboes, the snare of the timpani, and the pureness of the flute are all reproduced as near to the original as I have ever heard. Due to the lack of resonance within the recording range, the reduction of needle-scratch is most noticeable, giving a gentle "shush" in place of the normal "hiss." Transients are fully reproduced and the piano suffers none of the added damping that many pickups provide. Truly this is a remarkable pickup, and even more so when one considers the extremely low price of 50s. plus purchase tax. I am aware only of two other pickups that can compare in performance with the *Acos Microcell*, and both of those handsomely exceed £20. To the engineers who have developed such a remarkable crystal pickup with its low noise, high output and negligible record wear every praise is due, and although the U.S.A. was the home of the crystal pickup, and it still enjoys high popularity, they have nothing to compete with this unit.

It is understood that supplies of this pickup are now becoming more plentiful, and from now on they should be available in small quantities.

COSMOCORD LIMITED • ENFIELD • MIDDLESEX

Telephone: ENFIELD 4022

Physical Society's Exhibition

Electronic Research and Measuring Equipment

The fifth post-war exhibition of the Physical Society, held in London from 31st March to 5th April, included many items of radio and electronic interest. This report opens with a description of some of the exhibits concerned with research and development rather than routine production.

RESEARCH

THE applications of germanium are no longer confined to the diode. The crystal triode, or transistor, is on its way to practical use. The G.E.C. Research Laboratories demonstrated its characteristics on an oscilloscope and showed experimental equipment embodying it. A three-stage a.f. amplifier with a gain of 66db and an input impedance of 1kΩ was shown.

Germanium also forms the basis of a method of measuring magnetic field strength by the Hall effect, shown by both G.E.C. and B.T.H. If a magnetic field is applied at right angles to a conductor carrying a current, a p.d. is developed across the conductor which is proportional to both the field and the current and which is at right angles to both. The effect is relatively large when the material is germanium, and a sensitivity of 10A per 1mA per 1,000 gauss is obtainable. The germanium can be physically very small and so can be used for exploring magnetic fields.

Synthetic piezo-electric crystals were shown by Standard Telephones. Ethylene diamine tartrate is easily grown and produces crystals suitable for use in line filters.

A method of transmitting telegraph signals over narrow bandwidths was shown by Marconi's W.T. Company. Signals of 66 w.p.m. can be transmitted over a bandwidth of 10c/s, using a 5-unit code. Pulse-amplitude modulation is used with 32 levels; the noise level must be 36db below the peak signal level.

The Royal Aircraft Establishment showed an electronic curve follower for feeding recorded information to a computer. The curve is drawn on transparent film and is scanned by a c.r. spot oscillating at 3kc/s with an amplitude of 1mm. A photo-cell and amplifier is used with a phase-sensitive rectifier and gives an output proportional to the displacement of the centre of oscillation from the line. This is fed back to the deflector plates and locks the centre of the spot to the line. The deflector-plate voltage forms the output of the device.

The Telecommunications Research Establishment showed locked-oscillators of the sine-wave type giving frequency multiplication in steps of 10:1, and the Signals Research and Development Establishment exhibited a number of balanced-T bridges built for impedance measurements in the 50-100-Mc/s region. One model includes a decade resistance standard.

GENERAL ELECTRONICS

AMONGST the exhibitors of power supply units, one of the highest claims for stability was made by Cawkell, who demonstrated a model giving 200V at 50mA with stabilization of 0.003 per cent for mains or load variations of 15 per cent. The valve-heaters in the instrument are connected in series across the stabilized h.t. line, and a thermal-delay switch allows them to reach full temperature before the stabilizing action commences. A 300-mA current-stabilized power supply by W. G. Pye gave 0.01 per cent stability for 12½ per cent mains variations and ±100Ω variation on the normal load of 300Ω. Here again the valve heaters are in series across the stabilized line, and tappings are taken from the potentiometer thus formed to provide h.t. voltages, thereby saving extra resistors. Cinema-Television, Dynatron and E. K. Cole had stabilized e.h.t. units for nucleonic work, whilst Tinsley showed an a.c. stabilizer using a thermistor-bridge detector. A constant-current source for supplying valve heaters or filaments, using a transductor, was shown by the British Scientific Instrument Research Association, and a constant-voltage 12 V supply by Advance Components.

Several firms have been concerned with the problem of producing stable d.c. amplifiers. Southern Instruments showed a drift-corrected d.c. amplifier in which an oscillating relay continuously compares input with output so that any variation in gain is made to operate an automatic correcting circuit. Another self-balancing method was demonstrated by Electronic Instruments, for use in an electrometer, but here the correcting process was set in motion periodically by a cam-operated switching system. Two alternative methods of d.c. amplification were on view. Nagard used the d.c. to modulate a carrier frequency of 14Mc/s in an amplifier which had a flat frequency response up to 1Mc/s and a maximum gain of 15,000. Tinsley and Sunvic, on the other hand, modulated the d.c. by means of a mechanically operated "chopper," then amplified the result by normal methods and finally rectified the output.

Demonstrations of various applications of magnetic amplifiers were confined mainly to two firms. Elliott used them for amplifying signals from thermo-couples, for driving a uniselector and for speed control of a 1-h.p. motor, whilst Electro Methods showed several applications, including the integration of small signals by a low-inertia integrating motor driven by a magnetic amplifier. Thermionic amplifiers with special uses were shown by E. K. Cole, de Havilland, T.R.E. and Cawkell. The latter's exhibit was a demonstration amplifier for schools, with

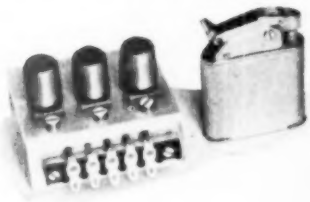

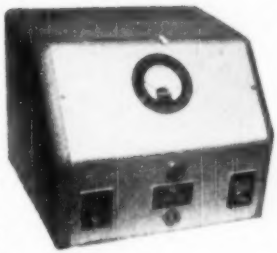

G.E.C. 3-stage amplifier using transistors compared in size with a cigarette lighter.

(Right) W. G. Pye current-stabilized power unit, designed for supplying a hydrogen lamp

Electronic apparatus for counting the red corpuscles in human blood, developed by Metropolitan-Vickers

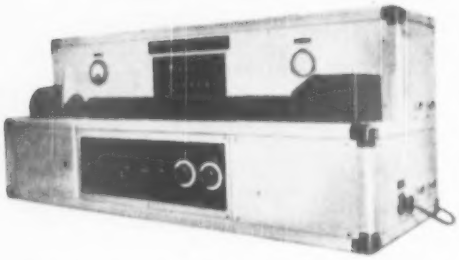

controls brought out on the front panel to enable circuit constants to be altered whilst the effects at the output are studied on a c.r.o.

In the field of computing, for those who find it difficult to convert decimal to binary numbers, Elliott showed a machine that will do the job automatically. An analogue computor for solving twelve simular linear equations was exhibited by de Havilland, and the N.P.L. had on view a junior model of their automatic computing engine, which is still in process of development. To reduce the tedium of designing directional aerial arrays by the trial-and-error method, E.M.C. have produced an experimental apparatus in which the trial radiation pattern is traced instantaneously on the screen of a c.r.o.

Counters and scalers were very much in evidence this year. In general they followed the conventional form of an electronic system providing either scales of two or scales of ten, together with a mechanical register to give the total count. An interesting application demonstrated by Metropolitan-Vickers was the counting of blood corpuscles. The blood is diluted by a known amount and passed down a capillary tube, an image of which is formed by a microscope on to a photo-cell; thus, the passing of a corpuscle causes the photo-cell to produce a pulse which in turn actuates the counter. Other exhibitors of counters were Airmec, Dawe Instruments, Panax, Dynatron, E. K. Cole, Lydiate Ash, Marconi Instruments, and the Atomic Energy Research Establishment, many of the instruments being designed for counting the random pulse outputs of Geiger-Muller tubes and ionization chambers.

Several portable radiation monitors and detectors worked by batteries were on view, the principal exhibitors being Baldwin Instruments, Ediswan, E. K. Cole and Panax. For determining the strength of radiation in particles per minute, rate of count meters were shown by E. K. Cole and Panax.

INDUSTRIAL ELECTRONICS

ESTABLISHED methods of applying variation of resistance, capacitance, inductance or photo-emission to the control of industrial processes or production were, as usual, well represented, and some interesting new principles of control were shown for the first time.

In the radioactive thickness gauge, developed by the Electronics Division of E. K. Cole, the absorption of emanations from a radioactive source is used to indicate the thickness of sheets and films, e.g., paper, plastics or even steel. A tray containing the radioactive element is placed below and an ionization chamber above the moving strip, and no mechanical contact is necessary. The output from the ionization chamber is converted to a.c. by a vibrating-reed electrometer, amplified and compared with the output from an identical reference source in which a normal specimen of the material under examination has been inserted. Assuming that the density of the material remains constant, the output indicated by the differential meter gives a measure of the variation of thickness to an accuracy of 1 or 2 per cent at speeds up to 5 or 6 ft/sec for materials such as paper and plastic. The strength of the source required under these conditions is perfectly "safe" from the point of view of health; for higher speeds and denser materials some shielding may be necessary.

Measurement of the temperature of flue and furnace gases in the region of 1,000° to 2,000° F presents many difficulties, particularly when the average temperature across a furnace 20 or 30ft wide and a few inches above the fuel is required. A solution has been provided by Lydiate Ash Laboratories, in which the velocity of propagation of supersonic waves is the underlying principle. The output from a stable l.f. oscillator, variable over a limited frequency range, provides a circular trace on a c.r. tube after passing through a network giving two signals spaced 90° in phase. It also provides pulses for firing a Trigatron which discharges an e.h.t. circuit in a spark gap with peak pulse energies of 600 kW. The sound energy of the spark is concentrated in a beam by a reflector, and is picked up by a transducer, amplified, and a suitable h.f. component above the ambient furnace noise is filtered and applied to the trace. The pulse repetition frequency is adjusted according to the length of the sound path, and a scale-of-two ensures that the received pulse coincides with the transmitted pulse at normal temperatures after two revolutions of the trace. In this way the temperature scale is expanded to give better resolution. The spot travels anti-clockwise, and as the temperature rises the received pulse arrives after shorter intervals of time and progresses clockwise under a calibrated graticule. The transducer

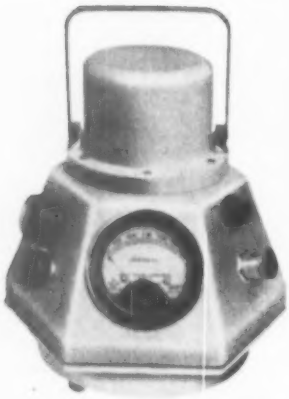

Ediswan portable gamma radiation monitor type 1030C, for indication of integrated dose up to 0.125 roentgens, and (right) de Havilland moving-coil vibrator for fatigue testing. Alternating thrust 250 lb and frequency range 0 to 1,000 c/s.

(a)

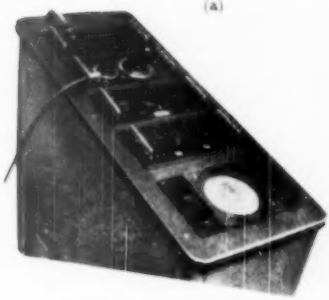

(b)

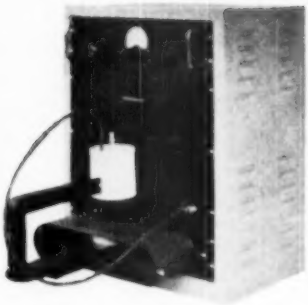

(c)

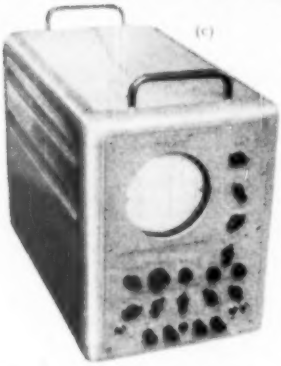

(a) Control and display unit of Lydiate Ash Laboratories' electronic high temperature indicator.

(b) Ekco thickness gauge, showing external radioactive source and ionization chamber.

(c) Portable automatic curve tracer made by Industrial Electronics, Ltd.

cannot be inserted directly in the furnace gases, and an end correction is applied electrically. Compensation is also provided for changes in the gas composition.

Fatigue testing at low and sub-audio frequencies is gaining in importance, and regenerative amplifiers are being used as self-drive units in conjunction with vibration pickups and filters to select the natural frequency at any required mode of vibration. Complete equipment for this type of work, shown by de Havilland Propellers, included a large moving-coil drive unit with many features—including cloth-loaded synthetic resin centring spiders—reminiscent of conventional loudspeaker design. The Type 1/D1 vibrator, as it is called, has an energized field taking 1 kW, and at full load exerts an alternating thrust of 250 lb with amplitudes up to 0.25 inch over a range of 0 to 1,000 c/s; the natural frequency of the unloaded assembly is 5 c/s.

Instantaneous visual indication of frequency is given by the Type 1204 "strobotuner" shown by Dawe Instruments. Twelve stroboscopic rings revolving at speeds proportional to semitone intervals on the equally-tempered scale are driven by a synchronous motor energized from a valve-maintained tuning fork. The normal fork frequency is 440 c/s, but it can be varied a semitone on either side by sliding loading weights, if pitches other than the international standard are required. The revolving discs are illuminated by neon lamps, connected in the output of a microphone amplifier so that the frequency of the sound under investigation causes the appropriate disc to appear stationary. Seven rings of segments on each disc are marked at octave intervals and the total frequency range of indication is 32 to 4,070 c/s. The equipment is designed primarily for manufacturers of musical instruments, and considerably reduces the time of adjustment and testing.

Another useful aid to the production testing of audio-frequency components such as loudspeakers, transformers, filters, amplifiers, etc., is the Type 1900 portable response curve tracer which was demonstrated by Industrial Electronics. One of the r.f. oscillators in a beat-frequency generator is controlled through a reactance modulator by a linear sweep generator giving a scanning rate variable between 3 sec and 1 minute. The output of the b.f.o. is divided, and part is fed through an R.C. network, rectified and amplified in a push-pull d.c. amplifier to give, on a c.r. tube, a horizontal deflection which is proportional to the logarithm of frequency. Feedback is applied between the deflector system and the reactance modulator, gives a reasonably constant rate of deflection on the spot. Vertical deflection from the input amplifier is normally linear, but a logarithmic compression circuit, depending on the characteristics of a contact rectifier, can be switched in when desired. Special precautions have been taken to ensure the stability of frequency calibration and the scale is checked at one end against mains frequency, and at the other against a stable resonant circuit.

Many industrial control devices depend on the accurate measurement of displacement, and the proximity switch and proximity meter shown by Fielden (Electronics) are examples of the sensitivity obtainable when using balanced capacitances for this purpose. The principle has been extended to graph recorder mechanisms in which the movement of the pointer of a 0-50 μA meter is followed at a distance, depending on capacitance, by a servo-operated moving vane to which the pen mechanism is connected.

OSCILLOSCOPES

THE cathode-ray oscilloscope is as ubiquitous as ever and many different types were shown. The Duddell string oscillograph is still used, however, and the Cambridge Instrument Co. showed 6- and 12-channel models having a frequency response up to 1,400 c/s. Clifton Instruments also showed an electromagnetic type.

Mullard wideband oscilloscope.

A. R. Cawkell Electronic Engineers had a c.r. type for 0.5-100c/s with a sensitivity of 50mV/cm. It is a double-beam type with an electronic switch.

The Industrial Electronics A.F. Response-Curve Tracer is designed for checking a.f. apparatus and draws a frequency-response curve on a long-afterglow screen.

On oscilloscope with an amplifier calibrated to 5 per cent in volts was shown by Nagard. It is in two units and covers zero to 10Mc/s. Furzehill Laboratories showed general-purpose oscilloscopes. The 1084D has an amplifier providing a sensitivity of 7mV/cm over the range 0.1-2Mc/s or 21mV/cm up to 3Mc/s. The time-base has a range of 20c/s to 150 kc/s. The 1684N is designed for low-frequency use and has an upper limit of about 50kc/s. It includes 10:1 sweep expansion.

Airmec Laboratories had an oscilloscope with a Y amplifier operating from zero to 5Mc/s and a timebase giving sweeps from 0.5sec to 1μsec. Mullard showed a wideband oscilloscope with X and Y amplifiers with a response from zero to 20Mc/s for −3 db. The sensitivity is 100mV/cm and a probe input is available.

An elaborate oscilloscope was exhibited by Metropolitan-Vickers. It is of the continuously evacuated type and operates at 100kV.

Cameras for recording oscilloscope traces are available in many types, but a special display was made by Avimo. This firm showed continuous film-recording cameras. With a film capacity of 200ft and film speeds between 2.5in/sec and 30in/sec operation is from a 24-V power supply.

SIGNAL SOURCES

AN interesting feature of the newest types of signal generator is the provision of both frequency and amplitude modulation from internal sources. The Marconi Instruments Model TF995 typifies the trend as it provides internal f.m. at 1,000c/s with deviations variable from 25kc/s to 600kc/s, and a.m. up to 50 per cent. The r.f. oscillator is variable over 4.5 to 9Mc/s only, but by using cascade harmonic multipliers an effective frequency range of from 14.5 to 216Mc/s is obtained. Included also is a crystal calibrator. A more ambitious model is the TF948, covering 20-80Mc/s, and with internal modulation by four frequencies with f.m. deviations up to 600kc/s and a.m. up to 80 per cent. It has a crystal check circuit, f.m. and a.m. monitoring and a tuning scale giving about 7 feet for each of the two frequency bands.

An f.m. signal generator intended primarily for testing receivers in the 90-Mc/s region was shown by Mullard. Known as the Model E7572, the final f.m. signals are obtained by mixing the output from a fixed frequency f.m. oscillator with that from a variable c.w. oscillator and using high- and low-pass filters to select the difference and summation frequencies. Ranges of 3-15Mc/s and 80-100Mc/s are thus obtained with a single variable oscillator. Two forms of modulation are provided, a 500-c/s sine wave with variable deviation up to ±100kc/s and a 100-c/s repetition saw tooth.

A new Advance audio generator (type H1) is notable for its wide coverage, 15c/s to 50kc/s, and the provision for either sine-wave or square-wave output. Heavy negative feedback ensures low distortion and the output is variable from 2000V to 20V.

METERS

TYPICAL of the modern trend in design of mirror galvanometers is the Pye "Scalamp," a new self-contained model with galvo unit, scale and lamp in one case. In addition to other novel features it has switchable shunts to vary the sensitivity and a shock-proof mounting to absorb bench vibration.

A number of new models with shortened suspension, to reduce the height of the case, were shown by Tinsley, and further examples were seen among the exhibits of Hilger, Pullin and Turner.

Pointer instruments have undergone little change, save that meters with a sensitivity of 100μA full scale are now more plentiful. A meter of this sensitivity was included in a new Series 30 (3-in scale) made by Pullin.

A tropical version of the Avo Electronic Test Set is now available, and there is also a valve-voltmeter conforming to B.S. standards for first-grade moving-coil instruments. It is the Model 26, made by Electronic Instruments, and is usable up to 200Mc/s.

BRIDGES

WIDE RANGE self-contained bridges for the measurement of small values of inductance and capacitance figured among the exhibits of Cinema/Television. One, covering 0.005μH to 50mH in 12 ranges, gave direct readings of mutual and self-inductance with an accuracy of ±1 per cent of the half-scale reading on all ranges, and this also had facilities for measuring resistance of from 0.05mΩ to 5kΩ in 12 ranges also. Another covered, in 36 ranges, 0.5×10⁻¹²F to 100μF and 1Ω to 50,000MΩ.

A feature of these bridges is the employment of inductively coupled ratio arms and circuits that cancel out the inductance, capacitance and resistance of external connecting leads, thereby enabling measurements to be taken with the components in situ.

Wayne Kerr showed some bridges of exceptional interest; the B401 impedance bridge, for example, gives in situ measurements of capacitance, resistance and inductance over the ranges 0.1pF to 10,000μF respectively. Measurements can be made at either 5kc/s or 50.5kc/s

(a)

(b)

(c)

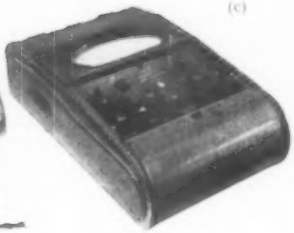

(a) Marconi Instruments f.m.-a.m. signal generator, type TF948, having very long frequency scales; (b) Pye "Scalamp" self-contained mirror galvanometer; (c) Laboratory valve-voltmeter made by Electronic Instruments.

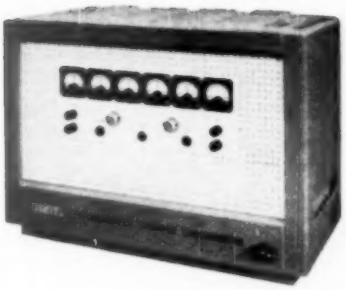

(a)

(b)

(c)

(a) Cinema-Television electronic stop-watch (microsecond counter chronometer). (b) Standard Telephones push-button h.f. attenuator; (c) 20th Century Electronics c.r. tube.

from an internal oscillator or with an external generator over 50c/s to 20kc/s. The accuracy is ±1 per cent. Another, the type B001, is designed primarily for measurements of susceptance and conductance of v.h.f. aerial systems over the frequency range 50 to 250Mc/s.

MISCELLANEOUS TEST EQUIPMENT

AN instrument for measuring very short intervals of time, described as the Millisecond Counter Chronometer, was shown by Cinema-Television. Its range is 1 sec to 1 sec, calibration being in steps of 1μ sec. A starting pulse activates circuits which continue to record the number of cycles of an internal oscillator until the arrival of a stopping pulse. Another microsecond counter, the Chronotron, was included among the exhibits of Electronic Instruments.

A wavemeter of unusual accuracy, 1 part in 10^6, was shown by Plessey. It incorporates several reference oscillators, one being crystal controlled, and covers a range of 15 to 10,000Mc/s.

For analysing complex waveforms Muirhead have developed a high-precision type wave analyser, Model D189A. Resistance-capacitance tuning is employed, and the exploratory range is 19c/s to 21kc/s. It is not a heterodyne type.

Dawe had a v.h.f. "Q" meter, range 30 to 200Mc/s, and an improved sound level meter, the new model being about half the size of the older, but providing the same facilities.

VALVES AND C.R. TUBES

AN unusually small number of valves and tubes were shown at this year's exhibition. Standard Telephones had a reflex klystron for 6–7cm with an output of 0.65–1W, and capable of being frequency modulated 0.8–1Mc/s per volt. A frequency shift of 400Mc/s is possible by mechanical tuning.

20th Century Electronics exhibited precision c.r. tubes. There are two single-beam types, 4in and 5in, and a 6-in double beam, all with flat faces. The last has two separate guns, and it is claimed that there is no interaction between them; the X-plates are common.

A range of cold-cathode valves and electrometer valves was shown by Ferranti.

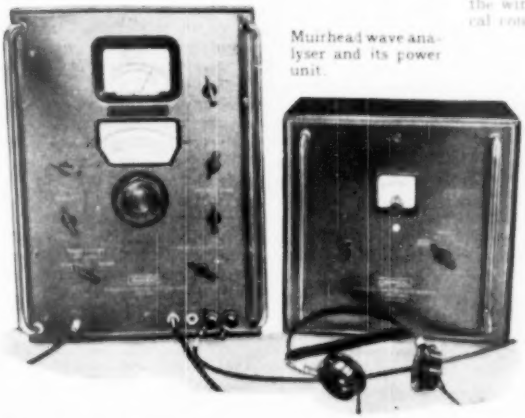

Muirhead wave analyser and its power unit.

COMPONENTS

STANDARD TELEPHONES showed a range of swaged-seam capacitors for tropical purposes. Both paper and mica-dielectric types are made, and the terminals and mounting are on the same face of the component.

Variable transformers and wire-wound resistors were exhibited by Zenith, while Gambrell showed 50-MΩ standard resistors and had an interesting precision slide-wire, comprising 50ft of wire wound as 100 turns on a drum.

Westinghouse, in addition to the well-known ranges of metal rectifiers for h.t. and e.h.t., were showing new types designed for use as "clamping diodes" in television line-scan circuits. They range up to the 1N136 with a rating of 3.47kV peak inverse and a mean current of up to 150mA. Types with cooling fins can be supplied for higher currents.

Standard Telephones also showed selenium rectifiers and have an e.h.t. type rated for 40V r.m.s. per plate or 80V peak inverse in television fly-back circuits.

Breeze connectors for coaxial cables operating at 7.10kV were exhibited by Plessey, who also had a range of microwave components. Variable resistors, of both the wire-wound and carbon types, fully sealed for tropical conditions, were also shown.

MATERIALS

FURTHER advances in the performance of permanent magnets are foreshadowed by a new process developed by the Permanent Magnet Association, though it will be some time yet before magnets will be commercially available. Using an alloy similar in chemical composition to Alnico, it has been found possible to grow columnar crystals internally in a direction favourable to the magnetic circuit, and magnets formed by this method have given figures for BH_{max} of the order of 7 to 8 × 10^6 gauss-oersteds compared with the previous best of 5.5 × 10^6 for the anisotropic heat-treated Alcomax III.

A new ceramic material, K3,000, was shown by Mullard Electronic Products. Developed for use in r.f. bypass capacitors, it has a permittivity of the order of 3,000 in the temperature range 10° to 70° C.

Deflector Coil Characteristics

3. *Performance of Frame Coils*

(*Concluded from p. 151 April 1950*)

By W. T. COCKING, M.I.E.E.

So far as the field efficiency is concerned all the conclusions reached about line coils apply equally to frame coils with only one exception; it is not possible to reduce LI^2 appreciably by using copper screening around core-type coils at frame frequency. With the ring-type iron circuit and normal forms of construction the LI^2 figure for the frame coils is normally higher than for the line. There are two reasons for this; on the one hand the frame coils must necessarily be shorter than the line because the bent-up ends must fit inside the ends of the line coils, and on the other hand the bent-up ends of the frame coils must be longer because they have to pass over the side wires of the line coils. As an example, with the assembly used for the measurements of Table 2 and with ring 2, the line coils have $LI^2 = 1.06$ and the frame coils $LI^2 = 1.32$. For ease of comparison both figures are for the same deflection.

However, at frame frequency the LI^2 figure is not always of the first importance. The energy lost in the resistance of the windings is no longer negligible compared with the energy stored in the inductance but actually greatly exceeds it. The real figure for the deflection power is now proportional to $RI^2 = LI^2 \times R/L$.

Because of this it is theoretically possible to adopt quite different methods of improving frame-coil efficiency. For instance, if the window area of the iron circuit is increased the field efficiency decreases (LI^2 increases) but the winding area increases and so larger wire can be used and the resistance decreases (R/L decreases). If R/L decreases more than LI^2 increases, RI^2 decreases and the efficiency is improved.

In some cases this occurs to a marked extent and low RI^2 figures are possible in spite of very poor LI^2 values. As an example, one commercially-produced core-type coil has $LI^2 = 6.08$ and $R/L = 0.185$ so that $RI^2 = 1.12$, whereas the coil referred to just above with $LI^2 = 1.32$ has $R/L = 1.88$ and $RI^2 = 2.48$. The commercial coil is actually not quite as good as it sounds for its resistance has been reduced so much that it is no longer permissible to ignore the energy stored in the inductance. It is necessary to use the accurate expression $RI^2(1 + 0.103L/R)$ which equals 1.74 in this case. Using this expression also for the bent-up end coil we get a figure of 2.61 instead of 2.48.

Although the commercial coil has only 1/4.6 of the field efficiency the resistance losses are so low that it needs only 1/1.5 of the input power of the other coil.

Although the RI^2 figure, modified if necessary by using the full expression, indicates the power input needed by the coil for deflection it is necessary to be very careful in using it. In practice, the important factor is really the power which must be provided by the valve which feeds the coil, not the power which must be fed to the coil. Under ideal conditions the two are proportional to each other, and then the lower RI^2 the better. In practice, however, it is not always possible to match valve and coil and when this happens a decrease of RI^2 may be of no benefit; it may merely increase the mismatch and leave the power supplied to the valve from the h.t. supply unaltered.

This is not the place to enter into a discussion of methods of feeding the deflector coil, but it is necessary to realize that in some cases improvements in the efficiency of a frame deflector coil confer little or no practical benefit. The true utility of a frame coil can only be assessed by considering it in conjunction with the valve and coupling circuit.

Even if RI^2 were a direct measure of the practical goodness of a coil when connected in circuit there is not a great deal that can be done to reduce the figure. With a given form of construction RI^2 can be reduced only by increasing the winding area. This can be usually done only by increasing the window area of the iron circuit, which increases LI^2 but reduces R/L more. However, the iron circuit is common to the line and frame coils in most cases and the increase of window area reduces LI^2 of the line coils. The magnitude of the power involved in line deflection is so much greater than in frame that the net result is likely to be an increase in the total power required.

Coil Inductance

So far little or nothing has been said about the actual number of turns on the coils. This is a minor matter with little or no effect on the efficiency, for it affects neither LI^2 nor R/L. If the coils are not fed through transformers, the turns must be chosen to suit the requirements of the valves which supply them with the saw-tooth current; in other words, they must be chosen to match the valves. If transformers are used the number of turns is not at all important because the transformer ratios can be chosen to suit.

Transformers are usual in commercial practice and for the line scan a coil inductance of some 5–10 mH is common. This usually needs 150–200 turns in each coil of the pair. The wire gauge is from No. 26 to No. 32 s.w.g. and is convenient whether the coils are wound to shape or bent after winding. Frame coils have the same order of inductance but they are often a little higher—up to about 25 mH.

In cases where transformers are not used higher inductances are necessary. For the line scan the inductance needed is of the order of 70 mH and something around 500 turns per coil is required. For the frame an inductance of up to about 2 H is desirable in many cases and this will call for something approaching 3,000 turns per coil.

A practical limitation occurs here because it is not

possible to reduce the wire size indefinitely. With the winding area often available 3,000 turns would require No. 46 gauge wire and this is much too weak mechanically for a deflector coil. It is undesirable to use any wire smaller than No. 42 s.w.g. and a limit of No. 40 is preferable. With this last gauge the limit to the turns is around 1,000 per coil in many cases.

To a large extent it is this which limits the possibility of matching the coils to the valve. If it were possible to reduce the wire size without limit it would be possible to wind on turns until the voltage drop across the resistance of the coils reached the limit set by the valve and h.t. supply. The current would then be a minimum and optimum matching would be obtained. As it is, the voltage drop across the coils is often well below that permissible in the valve circuit and the current must be correspondingly increased.

The same factor arises, but in a different way, even when transformer coupling is used. It is no longer in the deflector coil but is transferred to the transformer. It becomes much more complicated to investigate, however, because the matching then becomes tied up with questions of the size, weight and cost of the transformer as well as its efficiency and power of distorting the scan.

There is one form of deflector-coil construction which must be mentioned here because it does permit an unusually large winding space for the frame coils. It has already been briefly referred to and is based on a lamination which acts as a split iron ring for the line coils, while the two halves of the ring form poles for the frame coils. The iron circuit is built from a stack of laminations of the form shown in Fig. 3*. The advantages of this form of construction are two; the winding space for the frame coils is increased and so R/L can be reduced, and the laminations, if earthed, provide screening between the side wires of the line and frame coils. The disadvantages are a relatively low field efficiency for the frame coils, for an appreciable amount of field closely encircles the side wires, and a field distribution within the c.r. tube which is controlled by the shape of the poles and, therefore, not readily changed.

An experimental assembly was constructed on a 1¼-in stack of 0.02-in G. L. Scott type S.31 motor-stator laminations. The line coils occupied nearly 60° for each side limb instead of the usual 45° and had bent-up ends. The internal diameter of the split ring formed by the poles was 42 mm. The frame coils were simple slab coils of circular section with a simple bend to clear the tube neck. They did not fully occupy the winding space available and so the R/L figure obtained was not so low as would be possible. The winding distribution in the line coils was also not quite right in this first attempt and there was some barrel distortion of the raster.

The line coils gave $LI^2 = 0.94$, $L = 18.8$ mH, $R/L = 1.56$. The frame coils gave $LI^2 = 2.19$ (for the same 7.5-in deflection), $L = 30.3$ mH, $R/L = 0.81$ and $RI^2 = 1.76$. Although LI^2 is considerably worse than for a bent-up end frame coil, R/L is much lower and the true efficiency is better.

Constructionally, the frame coils are much easier to make than the bent-up end type. The line coils are slightly more difficult than usual, because one end must be bent-up with the iron circuit in place. In addition to the partial screening afforded by the iron, the line coils can be rotated relative to the frame while the assembly is in operation so that it is easy to adjust the assembly for a rectangular raster and minimum magnetic coupling between the two sets of coils.

One disadvantage is that the raster shape is seriously affected by any imperfections of the lamination assembly. It is necessary to take great care to obtain a true stack and it was found to be only too easy to stack the laminations so that they had a slight twist. A more serious drawback is the lack of control over the frame field distribution. This means that it is not possible with a single type of lamination to make deflector-coil assemblies which are suited to all types of cathode-ray tube. It is mainly this last point which has made the writer view this form of construction with some disfavour, but the difficulty of obtaining a sufficiently true stack to avoid raster distortion is another factor. It is also one which applies to all core-type coils. He has concluded therefore, that the bent-up end coils with a ring-type iron circuit is the best form of construction.

Effect on Focus

So far deflector coils have been considered only in respect of their efficiency. It is, however, necessary that a deflector coil shall produce a rectangular raster evenly focused over its surface even if this entails a sacrifice of efficiency. This matter has to be discussed in rather general terms because actual measurements of defocusing are rather difficult.

With a ring-type iron-circuit, the shape of the raster is governed by the disposition of the side wires of the coils. The focus is also affected by this but also by the end connections. Referring to Fig. 8(a), the diagram shows a section though the middle of an assembly of line coils only. It can be shown that to produce a uniform magnetic field within the tube the turns density should vary as cos θ, so the total turns

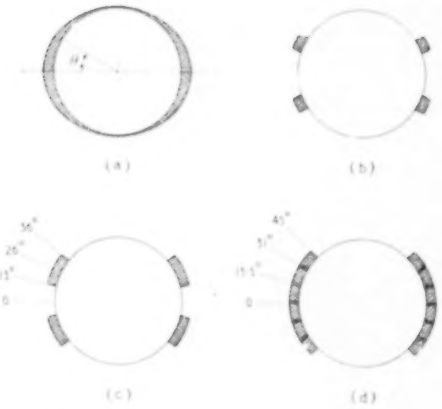

Fig. 8 (a). Shows a graded winding of varying thickness and (b) a small uniform winding. The latter must be centered on a 26° angle (c) for a curved-face tube. A 45° winding with the turns centered on 26° is shown at (d), the turns are distributed by changing the wire size in steps.

* March 1950, p. 97.

as sin θ. This calls for a winding of varying thickness and is consequently an inconvenient construction.

In practice, the grading of turns is usually made in steps. One way of doing this is to change the wire gauge at intervals during winding; another is to wind the coil in a number of identical sections which are spaced at varying intervals; still another is to wind the coil in evenly spaced sections and to vary the number of turns in each section.

As the number of sections is reduced so the approximation to the gradual distribution decreases and it is at its worst when each side limb degenerates to a single uniformly-wound section as shown in Fig. 8(b). A rectangular raster is easily secured with all these arrangements, but the focus improves as the turn distribution approaches the gradual.

Although it is commonly said that a uniform deflecting field is needed, this is not actually the case. The radius of curvature of the tube screen is greater than the deflecting radius and a suitable non-uniform field is necessary if the raster is to be rectangular; the departure from uniformity is greatest for a flat-face tube. Strictly speaking a deflector coil should be designed for a given tube and each tube type should have its own design of coil. In practice, this is not necessary and one design is usually satisfactory for all curved-face tubes and another for all flat-face types. Because a less uniform field is necessary with the latter it is more difficult to secure good focusing with them.

A uniform field gives pincushion distortion of the raster with all tubes. To obtain a rectangular raster the field must be made increasingly of pincushion shape as the radius of curvature of the tube screen increases, for a pincushion field tends to give barrel distortion of the raster. A coil assembly designed for a flat tube will therefore give barrel distortion on a curved screen and, conversely, one designed for a curved screen will give pincushion distortion with a flat.

The field becomes of the pincushion type as the bulk of the turns shift to small angles in Fig. 8. This means that the sin θ distribution must be weighted so that more turns appear for small values of θ and less for large. With the small ungraded coils of Fig. 8(b) the spacing between the adjacent limbs must be decreased.

When both line and frame coils fit around the tube neck, as in the bent-up end type of coil, θ is limited to 45°, for there are eight sets of side wires to fit around the tube neck. It is found that a rectangular raster requires that 50% of the turns lie between 0 and 26° and 50% between 26° and 45°. If the side wires are in one uniformly distributed section, the easiest to make, they must then extend from 13° to 39° as shown in Fig. 8(c). Such a coil can give very good results with a curved-face tube, such as the MW14C. There is some defocusing in the corners but not a serious amount. This distribution was used in the *Wireless World* Television Receiver.

Better focusing and efficiency are obtainable with the full 45° occupied by a distributed winding. A suitable distribution is shown in Fig. 8(d). The first 15.5° section contains 25% of the total turns, the middle section of 31-15.5 = 15.5° contains 36.5% and the third of 45-31 = 14° the remaining 38.5%. Note that this last section is the inside one of the coil as wound. The distribution is obtained by changing the wire gauge. This winding gives a better focus, and is somewhat more efficient because there is less waste space. It is more difficult to make, however.

The major defocusing troubles in a deflector coil usually come from the end connections. The field produced by these ends is chiefly in the form of loops encircling the end wires. Some field is necessarily produced in a direction acting along the electron beam and so having a defocusing action.

If the ends are bent-up well away from the tube neck the field which they produce within the tube, where it can affect the electron beam, is relatively weak and very little defocusing occurs. However, such ends take a greater length of wire and so produce a greater total field and the efficiency suffers.

Apart from the end connections, the field produced by the side wires extends beyond the ends of the assembly; it bows outwards from the ends. This is inevitable for it is not possible to terminate a magnetic field abruptly in a uniform medium. This bowing field itself has components acting along the electron beam which affect the focus. The only way of mitigating the curvature of the field is by increasing the diameter of the assembly, but this has a big effect on efficiency.

It is found, in practice, that the end bowing of the field is not serious for an assembly of 30-mm inside diameter. When the end connections are taken as closely as possible around the tube neck some defocusing in the corners does occur and it is desirable to keep these end connections further from the tube. Assemblies giving a rectangular raster and very little defocusing are possible with an LI^2 figure of the order of 1.3 or better.

The effect of the end fields is more serious at the front of the coil assembly where the beam emerges from the field than at the back where it enters it. This is because the beam enters the field on the axis of the tube in the most uniform region of the field and at the greatest possible distance from the end connections. At the front, the beam emerges from the field anywhere over a relatively large area and at full deflection is not greatly separated from the wall of the tube.

It is clear, therefore, that the front end of the assembly is more critical for the avoidance of defocusing than the back end. Consequently, it is permissible to bend up the back end connections less than the front, and it is advantageous to do so because it reduces the amount of wire needed and improves efficiency slightly.

Iron Losses

Nothing has so far been said about iron losses in the ring or core. Such losses inevitably occur but have no effect at all on the efficiency of the deflector coil as we have been considering it. They can, however, have a big effect on the efficiency of the circuit which feeds the deflector coil.

The importance of iron losses depends on the type of circuit. If critical, or slightly under critical damping is used, as in the *Wireless World* Television Receiver, the iron losses are unimportant. Indeed, a fairly high iron loss is an advantage since it reduces the power that must be dissipated in resistances. In addition, it provides distributed, as distinct from lumped, damping of any subsidiary resonant circuits which may be formed between sections of

Fig. 9. The line output stage modified as shown at (a) can be used to measure overshoot. The picture seen on a c.r. oscilloscope is shown at (b).

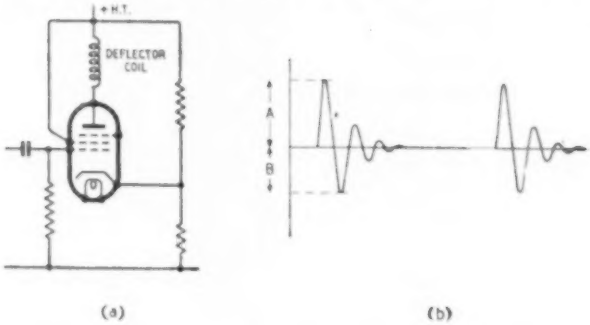

windings and their self-capacitances. In this case laminations as thick as 0.02 in are quite satisfactory and are often to be preferred to thinner ones.

Matters are quite different when the circuit is of the type using a damping diode. It is then desirable to let this valve provide as much as possible of the damping and iron losses should then be kept to a minimum. The inherent total losses are easily measured in terms of the overshoot and from them figures for the Q can be computed. This is unnecessary, however, in many cases for it is the overshoot itself which is important.

The easiest way of measuring overshoot is to include the coil directly in the anode circuit of the line time-base output valve, removing all damping circuits and increasing the bias on the valve so that it remains cut off for, say, a third of the scan period. The input wave should cut the valve off very sharply on fly-back. The circuit is shown in Fig. 9 (a) and in (b) the anode voltage waveform as seen on an oscilloscope. It is usually sufficient to place the oscilloscope input lead near the anode of the valve; if it is connected directly to it, the voltage is usually much too great.

The fractional overshoot is the ratio B/A. It cannot exceed unity and if the measured value is greater, something is wrong with the equipment—probably the oscilloscope amplifier is overloading! An overshoot much over 0.9 is unlikely in practice.

The writer has not so far made many measurements of overshoot, but as an indication of what to expect he has obtained a figure of 0.9 for a deflector coil without iron. The same coil with a 1-in stack of 0.02-in laminations forming a 42-mm diameter ring gave an overshoot of 0.625 only. With a damping diode the circuit efficiency varies very roughly as the square of the overshoot, or in this particular case, in the ratio $(0.9/0.625)^2 = 2$. The deflector coil efficiency itself varies in a 2 : 1 ratio with and without the iron, so that in this case considering coil and circuit together the overall efficiency would be the same whether the deflector coil had an iron circuit or not.

In practice, of course, a transformer is needed and the iron losses in its core have a marked effect on the overshoot. This modifies matters and makes the deflector-coil efficiency of more importance than the losses in its iron circuit. Nevertheless, when a damping diode is used it is desirable to minimize the core losses. The laminations used should, therefore, be as thin as possible and of a high grade material with minimum hysteresis loss.

It is usually difficult to obtain thinner laminations than 0.014 in and although these are really much thicker than is desirable, they are appreciably better than 0.02 in. The quantity of iron used must obviously have an effect on the iron losses and it is reasonable to suppose that the use of, perhaps, one-half of the number of laminations needed for a full stack and spacing them out to occupy the full space would appreciably increase the overshoot.

It was shown earlier that this reduces the coil efficiency by only a small amount, so that it would probably be advantageous to adopt this form of construction. This lies in the future, and at the time of writing no measurements have been made to show the possibilities. The matter is complicated by the transformer. This component not only has itself high core losses, but is inefficient on a field basis. Because of the need for high insulation and low self-capacitance the leakage inductance tends to be large. This means that the transformer itself has a large waste field and stores a good deal of energy. Its efficiency is often no more than 50%.

The transformer efficiency does not directly influence the deflector coil but its core losses do, for if the core losses are large the overshoot will be small no matter how small the losses in the deflector-coil iron circuit are made. It will usually be advantageous to try to reduce core losses in one component only when those of the other are of the same order of magnitude. Of course, if the losses in one are very heavy and in the other very small, it is always useful to improve the poorer one, but a big improvement may be needed to be worth while.

Club News

Birmingham.—The first of a series of d.f. tests will be undertaken by members of the Slade Radio Society on 14th May. At the meeting on 12th May the first of a series of discussions on television fundamentals will be opened by R. T. Turner and will deal with time bases. On 26th May D. Symmas will describe the construction of a television receiver using ex-Government equipment. Meetings are held at 7.45 in the Parochial Hall, Broomfield Road, Erdington. Sec.: C. N. Smart, 110 Woodmore Road, Erdington, Birmingham, 23.

Sheffield.—The morganized Sheffield Amateur Radio Club now meets on the second Wednesday of each month at Albion's Works, Lydgate Lane, for technical lectures and on the fourth Wednesday at the Dog and Partridge Inn, Tuppett Lane. Sec.: E. Walker (G2LT), 114 Welwyn Close, Intake, Sheffield, Yorks.

Sunderland.—The last of the lectures in the series on valve manufacture, which have been given by members of the staff of Ediswan's to the Sunderland Radio Society, is on "Testing and Inspection" and will be given by H. Booth on 17th May at Prospect House, Prospect Row, Sunderland. Sec.: C. A. Chester, 38 Westfield Grove, High Barnes, Sunderland, Co. Durham.

British Amateur Television Club.—The note on this club in our February issue was a little ambiguous. The purpose of the club is to encourage amateur activity in television transmission. Sec.: M. Barlow (G3GVO), Cheyne Cottage, Dukes Wood Drive, Gerrards Cross, Bucks.

WORLD OF WIRELESS

Europe's Wavelengths • International Video Standards • Component Standardization • Audio Exhibition

Copenhagen Observations

FROM observations made at both the B.B.C. checking station at Tatsfield and the measuring station of the new European Broadcasting Union at Brussels it appears that all the 25 countries who were signatories to the Copenhagen Broadcasting Convention have conformed to it in most respects.

There have, however, been departures from the Plan by some of the non-signatories. Although Spain was not represented at the Copenhagen Conference—because she is not a member of the United Nations—she was allocated new frequencies but has, so far, continued to use the old wavelengths. As many of these come between the frequencies allocated at Copenhagen to other countries there has been considerable interference in certain parts of the Continent. Luxembourg also continues to operate on its old long wavelength as well as on the new medium-wave one.

Some stations in Palestine, Egypt, Andorra, Malta, Austria and Trieste, have not conformed to the Plan and the stations in the American Zone of Germany, for which three frequencies were allocated, are said to be operating on twenty-five. The American Forces Network is using five—Frankfurt, 593 kc/s (10 kW); Stuttgart, 1,061 kc/s (50 kW); Munich, 1,554 kc/s (100 kW); Beyreuth, 548 kc/s (10 kW); Berlin, 611 kc/s (1 kW).

To assist stations in calibrating their transmitters the B.B.C. recently placed the long-wave transmitter at Droitwich at the disposal of the European Broadcasting Union so that details of measured variations could be broadcast throughout the early hours of the morning in English, French and Russian. Stations in Brussels and Paris were also used for this purpose.

Television Standards

MEMBERS of the Television Study Group of the International Radio Consultative Committee (C.C.I.R.)—one of the four permanent committees of the International Telecommunication Union—are visiting countries on both sides of the Atlantic for demonstrations of television preparatory to meeting to discuss international standards. They will have seen American, French and Dutch equipment prior to seeing demonstrations in this country from 26th April to 5th May. On the following day the committee will open its meeting in London which is scheduled to last eight days.

Plans have been made for the 30 or so members of the committee representing the governments and radio industries in fifteen countries to visit research establishments of the B.B.C., G.P.O. and the industry.

News in Morse

A REVISED schedule of the London Press Service morse transmissions from Post Office stations has been secured in response to requests from readers and is given below. The material broadcast in this service is not copyright and may be used for personal information, distribution or "house" newspapers. The speed of transmission is from 20 to 25 w.p.m. We are advised that preparations are being made to replace the morse transmissions to the Near and Middle East by a Hellschreiber service.

The number in the fourth column of the table indicates the zone of reception (1, Europe; 2, Near and Middle East; 3, Africa; 4, N.E. Asia; 5, Australasia; 6, India; 7, S.E. Asia; 8, N. America; 9, S. America).

G.M.T.	Call	Freq. Mc/s	Zones
0015-0045	GFX	11.845	8
0100-0104	MHz	9.725	6
0100-0115§	GIN	10.860	9
0130-0135	GSJ	6.085	1, 2
	GHB	11.980	2
0445-0545*	GBJ	10.885	3
0945-1045*	GCV	19.705	4
1100-1200*	GIM	12.875	1, 2
	GCV	19.705	4, 5
1115-1215	GFA	20.100	6, 7
1200-1300*	GCT	19.095	3
1215-1315*	GFA	20.100	6, 7
1330-1430*	GIM	12.875	1, 2
	GDZ	15.010	4, 5
	GCT	19.095	3
1445-1545*	GFE	16.130	7
	GFA	20.100	6, 7
1600-1700*	GIM	12.875	1, 2
	GSH	10.885	4, 5
	GCE	19.095	3
	GAO	17.160	6, 7
1700-1800*	GAO	17.160	6, 7
1730-1830*	GBJ	10.885	3
1845-1945	GHB	11.980	2
	GBJ	10.885	4
1900-2000*	GAU/3	12.455	1, 2
1945-2045*	GHB	11.980	6, 7
	GBJ	10.885	4
2100-2200*	GCI	8.730	1, 2
	GAH	8.065	4, 5
	GAO/4	14.901	3
2215-2315*	GCX	9.020	6, 7
2330-0100	GIT	6.085	1, 2
	GAH	8.065	4
	GHB	11.980	5
	GCX	9.020	6, 7
2330-0045*	GAV	14.430	9

* Weekdays only.
† Alternate Fridays.
‡ Terminates at 0030 on Mondays.
§ From 0100-0145 on Mondays.
‖ Mondays excluded.

R.E.C.M.F. Report

THE seventeenth annual report of the Radio and Electronic Component Manufacturers' Federation records that nearly one-third—approximately £4,000,000—of the total value of the radio industry's exports during last year was of components and associated products exported direct.

The question of standardization has again been considered at some length by the Technical Panels of the Federation. From the component makers' viewpoint, standardization—particularly dimensional—has much to commend it since it simplifies tooling and production, but it is pointed out that it is not a matter for the component manufacturer alone. The principal difficulty in the way of introducing greater standardization is the reluctance of many manufacturers to restrict their individuality of design. Moreover, the "modern radio and electronic component is a mind of all work" being used in equipment ranging from domestic receivers to electro-encephalographs.

At the annual general meeting on 20th March the representatives of the following firms were elected to the Council for 1950-51: Belling & Lee, British Centralab, British Electronic Condenser, Bulgin, Garrard, Long and Hambly, T.C.C., Westinghouse and J. & H. Walter.

B.S.R.A. Exhibition

PLANS for the exhibition of recording, reproducing and audio equipment, which is being organised by the British Sound Recording Association for 20th and 21st May, include space for some twenty exhibitors and demonstrations of manufacturers' equipment in a separate hall. Mobile recording equipment provided by the B.B.C., E.M.I., Pathé Pictures and M.S.S. Recording, will also be on view.

The exhibition will be held at the Waldorf Hotel, Aldwych, London, W.C.2, from 2.30 to 6.0 on the 20th and from 10.30 to 6.0 on the 21st. Admission will be by catalogue, price 1s.

I.A.R.U. Jubilee

TO mark the 25th anniversary of the formation of the International Amateur Radio Union, a congress is being held in Paris from 17th to 20th May under the auspices of the Réseau des Emetteurs Français.

Two committees will be selected

from the delegates; one will deal with licensing regulations and the other with technical matters such as interference and propagation and with the proposal that amateurs should co-operate with the International Scientific Radio Union (U.R.S.I.) in undertaking scientific observations. The R.S.G.B. is submitting a paper on the latter subject.

Indexes

It is regretted that there has been some delay in producing the index to the 1949 volume of *Wireless World*. It will be available this month, price 1s 1½d by post, from our Publishers. Cloth binding cases for the volume are also obtainable, complete with index price, 4s 1ld including postage. Our publisher can undertake the binding of readers' issues; the cost, including binding case, index and postage on the bound volume, is 14s 3d.

Copies of the 56-page index to the Abstracts and References Section of our sister journal *Wireless Engineer* are still available. The index includes subject and author sections and a list of the names and addresses of the 180-odd journals regularly scanned for abstracting. The index is obtainable from our Publishers, price 1s 8d.

Pioneer Craftsman

A LIST of the jobs on which E. F. Hills (see photo) has worked since he joined Marconi's W.T. Company in 1903 as a tool and instrument maker reads like a potted history of radio. He started with the ten-inch spark coil, which formed the heart of early transmitters like the one shown in our Marconi Marine Jubilee photo last month. Mr. Hills made one of the first facsimile transmitters; he worked on Navy arc sets in the 1914-18 war and on radar in the last war. In 1918 he transferred to the near-by English Electric Valve Company's works, and is now making jigs for assembling television camera tubes (see page 162).

OBITUARY

It is with regret that we record the death on 23rd March of **Daniel Bonney**, head of the External Relations Division of the English Electric and Marconi group of companies and director of nine overseas associated companies. He had been with Marconi's for 24 years having joined the company when he was 22.

We also regret to record the death at the age of 49, of **F. A. Cobb**, M.I.E., Assoc.I.E.E., who, for the past three years has been managing director of Electronic Tubes, Ltd., of High Wycombe, Bucks. He was on the engineering staff of 2LO in the early days of the B.B.C. and from 1926 to 1929 was chief engineer of the Indian Broadcasting Company at Calcutta.

The death is also announced of **G. H. Nash**, C.B.E., M.I.E.E., at the age of 69. From 1911-1928 he was Chief Engineer of Standard Telephones and Cables, and was a director of the company from 1927-1935. He also held a number of executive positions in international telegraph and telephone concerns. From 1942-1945 he was Deputy Director of the Ministry of Aircraft Production.

PERSONALITIES

Sir Edward Appleton, who prior to his appointment as Principal of Edinburgh University was Secretary to the D.S.I.R., has had a further honour conferred on him. He has been awarded the Sir Devaprasad Sarvadhikary Gold Medal for 1949 by the University of Calcutta. The medal is awarded biennually to "one of the most honoured scientists of the age."

Major Gen. L. B. Nicholls, C.B., C.B.E., M.I.E.E., who retired from the Army in 1947 to become a director of Cable and Wireless, has been appointed managing director of the company in succession to **John Innes**, C.B., B.Sc., A.M.I.E.E., who has retired. After commanding the Second Divisional Signals in France in the early months of the war, he served as Chief Signals Officer successively in the Middle East, North Africa and Europe.

Prof. E. B. Moullin, M.A., Sc.D., president, and **W. K. Brasher**, M.A., secretary, of the Institution of Electrical Engineers, are representing the Institution at the second Commonwealth conference of representatives of engineering institutions being held in Johannesburg in April.

P. G. A. H. Voigt, B.Sc., A.M.I.E.E., has gone to North America to explore the high fidelity position in Canada with a view to introducing in the Dominion the Voigt loudspeaker produced by Voigt Patents, Ltd., of which he is a director.

FROM SPARK COIL TO IMAGE ORTHICON.—E. F. Hills, with 47 years of wireless service to his credit, at work in the English Electric Valve Company's factory at Chelmsford

H. J. Leak, M.Brit.I.R.E., director of the firm of manufacturers bearing his name, is visiting the Continent to arrange for an exhibition of the company's equipment at the Milan Fair.

Oswald F. Mingay, editor of the Australian *Radio Electrical Weekly*, who has been in this country for some months, is leaving on April 29th for the United States where he will continue his study of the world's radio and television industries. He is due back in Sydney at the end of July having been away 13 months.

B.B.C. APPOINTMENTS

A. R. A. Rendall, B.Sc., M.I.E.E., who joined the B.B.C. Lines Dept. in 1935 and has since successively held the positions of Asst. Head of the Lines Dept. and Asst. Head of the Design Dept. has been appointed Head of the Designs Dept. in succession to H. R. Kinnison who recently resigned to join the United Nations Organization. Mr. Rendall was with the International Standard Electric Corp. prior to joining the B.B.C.

E. G. Chadder, who, since joining the original B.B.C. in 1923, has successively held the posts of Engineer-in-Charge at Aberdeen and Washford, Asst. Supt. Engineer (Transmitters) and Studios and, since 1939, Supt. Engineer (Studios), has been appointed Senior Supt. Engineer (Sound) in succession to L. Hulme who recently resigned.

F. Williams, B.Sc., M.I.E.E., has been appointed Supt. Engineer (Studios), B.B.C., in succession to E. G. Chadder. He joined the Corporation in 1925 and after successively being Engineer-in-Charge of the studio centres at Cardiff, Birmingham and Manchester, was appointed Asst. Supt. Engineer (Studios) in 1946. He became head of the Corporation's Engineering Secretariat last year.

A. P. Monson has been appointed Superintendent Engineer (Recording) in succession to **M. J. L. Pulling**, who was recently appointed Senior Superintendent Engineer (Television). Mr. Monson joined the B.B.C. in 1933 and became head of the Transcription Recording Unit in 1941 and Assistant Superintendent Engineer (Recording) in 1943. Prior to joining the B.B.C. he was with Cossor & Co.

H. W. Baker, for the past four years Engineer-in-Charge of the B.B.C.'s television station at Alexandra Palace, has been appointed Asst. Supt. Engineer (Television). He left Marconi's to join the B.B.C. in 1926 and held the post of Asst. Engineer-in-Charge at Alexandra Palace from 1937 until the television service closed down in 1939. During the war he was Engineer-in-Charge of various B.B.C. transmitters including the high-power long- and medium-wave station at Ottringham.

H. Walker, O.B.E., A.M.I.E.E., has been appointed Engineer-in-Charge of the London television station in succession to H. W. Baker. He has been with the B.B.C. since 1931 and joined the staff at Alexandra Palace just before the station opened in 1936. After serving in the R.A.F. during the war he returned to A.P. as Asst. Engineer-in-Charge when the television service re-started in 1946.

W. Balfour, who, prior to joining the B.B.C. in 1934, was at the G.P.O. station at Portishead, has been appointed Engineer-in-Charge of the B.B.C. studio centre and transmitter at Aberdeen. He succeeds **W. W. Inder** who has retired after seventeen years' service.

IN BRIEF

Licences.—Although the total number of receiving licences (sound and vision) in the United Kingdom decreased by 1,800 during February, the number of television licences increased by 31,200. The figures are: sound, 11,891,200; vision, 316,700.

Amateur Exhibition.—The R.G.S.B. is planning to hold the fourth Amateur Radio Exhibition at the Royal Hotel, London, W.C.1, from 22nd to 25th November.

Radio Officers.—The casualty rate among Marconi Radio Officers during the 1939-45 war was higher than in the Fighting Services—one man in six in the company's war-time staff of 6,000 radio officers lost his life. This fact was given by Sir George Nelson, chairman of the Marconi International Marine Communication Co., at the company's Jubilee banquet which was attended by some 200 guests, including representatives of State and the shipping and radio industries.

"British Plastics," our associate journal, is organizing a plastics exhibition and convention, in co-operation with the British Plastics Federation, to be held at Olympia early in June, 1951.

Television Society.—Attendances at the meetings of the Television Society have increased to such an extent that it has been decided to limit the number of visitors. Admission of visitors will in future be by ticket only, obtainable from the Lecture Secretary, 180 Bromley Road, Beckenham, Kent.

"B.B.C. Television Service" is the title of a 32-page booklet issued by the Corporation giving a short history of the development of television and a technical description of the present system. This 2s booklet is obtainable from the B.B.C., The Grammar School, Searle Road, Wembley.

FROM ABROAD

819-Line Television transmissions have begun from the new 300-watt station erected at Lille by Radiodiffusion Française. The frequencies are 181.25Mc/s. vision, and 174.5Mc/s sound. Horizontal polarization is employed.

German Amateurs.—A 28-page list of German amateur transmitters is included as a supplement to the 21st January issue of CQ, the official organ of the Deutscher Amateur Radio Club. The list includes German nationals only (DL1, 3 and 7) and not members of the occupying powers.

Television and the Cinema.—The growing affiliation between these two forms of entertainment in the United States is exemplified by the announcement that the American Society of Motion Picture Engineers, has changed its name to the Society of Motion Picture and Television Engineers.

Athens—New York direct photo-telegraph service was recently opened by Cable and Wireless.

EXPORTS

British-Made Discs, with the trade name "London," are being marketed in North America by the London Gramophone Corp., which is a subsidiary of the Decca Record Co. In addition to the standard 78-r.p.m. records the company is also marketing long playing microgroove discs which are recorded, processed and pressed in this country by Decca. A recent report of the U.S. Dept. of Commerce states that the London Gramophone Corp. is importing 50% of all records going into the U.S.A.

Uruguayan Enquiry.—Tenders for three communications-type receivers covering all broadcasting bands—with characteristics similar to the Hammarlund Super Pro 400X—two all-wave table models with bandspread tuning on short waves and two s.w. and m.w. battery portables with telescopic aerials, are called for by the Servicio Oficial de Difusion Radio Electrica, Montevideo. Tenders for six communications-type receivers are also being sought by the Direccion General de Comunicaciones, Montevideo. Tenders must be presented in Spanish by accredited local agents. The specifications in Spanish are available for inspection at the Commercial Relations and Exports Department, Board of Trade, Room 1080, Thames House North, Millbank, London, S.W.1 (references: CRE(B)/47105/50 and CRE(B)/47857/50).

Industrial Enquiry.—An Indian firm, intending to embark on the local manufacture of broadcast receivers, amplifiers, loudspeakers, and a few other accessories and components, wishes to hear from British firms willing to collaborate. Letters addressed under cover to the Editor, enclosed in a stamped air-mail envelope, will be forwarded.

Belgian Congo.—Under the Belgian Congo Ten-Year Plan provision is made for the establishment of a wired wireless distribution system in the native city of Leopoldville for which a sum of Fr.8,675,000 has been provided. Catalogues, specifications and prices covering the supply and installation of the central receiver and erection of distribution wires should be sent without delay to the Gouvernement General, Bemo, Direction Générale, Kalina, Leopoldville, Belgian Congo.

BUSINESS NOTES

Capacitors.—The production of trimmer capacitors by A. H. Hunt has been discontinued, and the tools and jigs for their manufacture have been acquired by Sydney S. Bird & Sons, of Enfield. The firm of A. H. Hunt is concentrating on fixed capacitors, and has opened a new factory at Wrexham, Denbighshire.

RCA Radar.—A lightweight radar set for small craft and an improved direct-reading Loran equipment, both recently announced by the Radio-marine Corporation of America, are to be distributed in this country by RCA Photophone, of 36 Woodstock Grove, London, W.12. The radar set has 30kW peak power, works on 3 c/m and has 4 range scales (max. 20 miles).

Scope Laboratories.—Australian manufacturers of the 6-second Scope soldering iron—notify us that their factory has been moved to 417, Keilor Road, North Essendon, Melbourne, W.6, Victoria, Australia.

Corner Ribbon loudspeaker described in our January issue is being demonstrated by Peter Hildesley, 73 Grosvenor St., London, W.1. (Tel.: Mayfair 6914).

"Testoscope."—Through a printer's error the voltage and price of the new popular model of the Rimbaken "Testoscope" tester were incorrectly given in the advertisement on page 80 of our January, 1950, issue. Voltage should be 100/400, a.c. or d.c., and price 12s 8d.

Telegraphic Address of A. H. Hunt, Ltd., of Wandsworth, London, S.W.18, has been changed to "Capacitors, Pat, London."

MEETINGS

Institution of Electrical Engineers

Commemoration of the Centenary of the birth of Oliver Heaviside on May 18th. "Heaviside, the Man," by Sir George Lee, O.B.E., M.C., at 3.0; "An Appreciation of Heaviside's Contribution to Electromagnetic Theory," by Prof. Willis Jackson, D.Sc., D.Phil.; "Heaviside's Operational Calculus," by Prof. B. van der Pol, D.Sc.; "Fifty Years' Development in Telephone and Telegraphy Transmission in Relation to the Work of Heaviside," by W. G. Radley, C.B.E., Ph.D., and "Some Unpublished Notes of Heaviside," by H. J. Josephs at 5.30.

Radio Section.—"A Million-volt Resonant-cavity X-ray Tube," by B. Y. Mills, B.Sc., B.E., at 5.30 on May 19th.

The above meetings will be held at the I.E.E., Savoy Place, London, W.C.2.

Northern Ireland Centre.—Faraday lecture on "Radar" by R. A. Smith, M.A., Ph.D., at 7.30 on May 2nd at the Wellington Hall, Belfast.

South Midland Radio Group.—"Some Electromagnetic Problems," by Prof. G. W. O. Howe, D.Sc., LL.D., at 6.0 on May 1st at the James Watt Memorial Institute, Great Charles Street, Birmingham.

British Institution of Radio Engineers

London Section.—"Multi-station V.H.F. Communication Systems Using Frequency Modulation," by E. G. Hamer and W. P. Cole, B.Sc., at 6.30 on May 25th, at the London School of Hygiene and Tropical Medicine, Keppel Street, London, W.C.1.

Merseyside Section.—"History and Development of Rediffusion Systems," by M. Fawcett, at 7.0 on May 3rd, in the Accountants' Hall, Derby Square, Liverpool.

South Midlands Section.—Visit to Sutton Coldfield television station May 17th.

Institute of Navigation

Symposium of papers on "Marine Radio Position Fixing Systems" at 4.0 on May 19th, at the Royal Geographical Society, 1, Kensington Gore, London, S.W.7.

British Kinematograph Society

"Motion Pictures for Television," paper prepared by the American Society of Motion Picture and Television Engineers at 7.15 on May 2nd at the Royal Society of Arts, John Adam Street, London, W.C.2.

Hull Electronic Engineering Society

"Electronic Counting Equipment" by Cinema-Television, Ltd., at 7.30 on May 12th, at the Electricity Showrooms, Ferensway, Hull.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

Aircraft interference with television reception.

This interference is not electrical but is caused by the television wave being reflected from the aircraft. As the aircraft is moving the result is most disturbing, if the aircraft is circling the result may be intolerable.

We had a letter from a reader of this page who is situated near an R.A.F. airfield and who was using an aerial in his loft, not a true dipole nor one of our inverted "V" type, and he complained that reception was intolerable; what should he do?

We recommended a simple dipole L.501/L. Here is his reply:—

"I wrote to you a little while ago regarding low flying aircraft interfering with television; at the time I was using an aerial in the loft. I have now fitted one of your dipoles L.501/L outside and am using balanced feeder. The difference in signal strength is amazing. With the old aerial the aircraft absolutely spoilt the picture, with the new outside one the aircraft only causes a flutter on the screen.

One of our inverted "V" type "Veeriod" would have been little better than his original aerial. Any aerial with one or more elements other than perpendicular is very sensitive to reflections from aircraft and should not be used near an airfield nor on a busy route.

Field strength survey.

The "Belling-Lee" mobile research unit has completed its first tour, and we are indebted to the press for the interest which they showed in the results. Manufacturers and Official Bodies asked for additional copies to supplement their own results, and in general the interest shown proved the usefulness of the service.

As this work can hardly be classed as true research and, as true research cannot be carried out when the unit is away, it has been found necessary to equip a second unit which should be on the road by the time this goes to press. The first tour was within the 60/70 mile radius of Sutton Coldfield; the next tour will probably be carried out between the 50/60 mile radius.

"SCREENECTORS."

A new range of lightweight plugs and sockets. Housings take coaxial, 2-pole and 3-pole plug and socket assemblies. Wide choice of mounting arrangements.

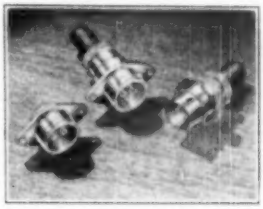

Characteristics and list numbers of "Screenectors"

Assembly	Coaxial	2-pole	3-pole
Flex plug	L722/P	L615/P	L715/P
Chassis socket	L722/S	L615/S	L715/S
Through chassis socket	L723	L699	L716
Flex socket	L724	L690	L717

Type	Characteristic impedance ohms *	Contact Resistance	Capacitance * Conductor to conductor	Conductor to screen
Coaxial	75	Less than 5 milliohms each	—	—
2-pole	100		1 pF	2.5 pF
3-pole	—		—	—

* At 1 Mc/s

This new range of screened light alloy connectors is based upon the draft R.E.C.M.F. specification for a non-reversible screened twin plug and socket to load cables up to 0.2 in. diameter over the braid. At the same time the design has been made versatile so that single and multipole contacts may be assembled into the common housing.

This housing is machined and therefore possesses an appearance in keeping with modern instrument finish.

Although a "quick" thread locking ring forms part of the assembly the screen skirt is resilient, thereby maintaining excellent contact should the locking ring inadvertently be left loose.

The contact assembly insulator is moulded from low loss nylon filled bakelite X.17163 or equivalent grade, and the design includes lengthened leakage paths between contacts in order to maintain high insulation resistance.

Both the connections to the silver plated contacts are by soldering to wedge slotted spills, while the screen connection is based upon the well-known split cone method of clamping. A reinforcing rubber sleeve is also included to decrease insulation wear at the point of flexing.

The housing is designed so that various applications may be employed, e.g., line connector, flex plug and chassis socket and vice versa, through-chassis (bulkhead) connector, all varieties with either one, two or three pins or sockets, and each part interchangeable in its appropriate position in the assembly.

"Multirod" feeder.

It is natural that we have had a number of enquiries as to what to do when connecting a "Multirod" to a receiver, the maker of which insists on the use of say screened balanced feeder. Well, you must use the feeder specified by the maker, even when we emphasise that semi air-spaced coaxial* is our first choice. There will be losses in the system, but the signal provided by the "Multirod" will still be better than that on an "H" or any other array we know of, provided it is used with the same feeder. In view of the conflicting situation, it is highly desirable that the television receiver industry gets together and standardises receiver input impedances and the basic type of feeder to be employed.

Incidentally, a length of coaxial feeder (used as a ¼ wave matching transformer) is provided with the "Multirod." We wish to emphasise that this should not be altered or omitted when installing the aerial.

"Multirod" Masts.

As the "Multirod" is invariably used for fringe reception, height is of utmost importance.

It has been found desirable to supply it complete with an additional 36 foot mast, making a total height of 50 foot, effectively guyed and capable of being rotated.

An alternative "Multirod" with an additional 12 foot mast, making a total 26 foot erection, with chimney lashings and roof guys is also being made available.

*L.688 semi-airspaced coaxial feeder for use with "Multirod" aerials in fringe areas. Price 2/3 per yard.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND

The TWIN assembly of the NEW miniature H.T. RECTIFIERS

SELENIUM SenTerCel RECTIFIERS

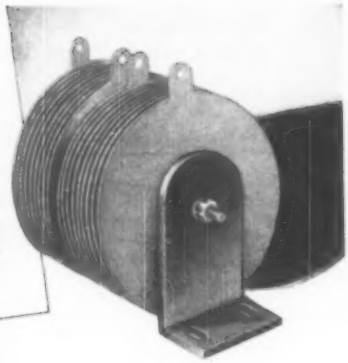

The new range of **SenTerCel miniature H.T. Selenium rectifiers** have these unique features:

- No limit to size of reservoir capacitor.
- Withstands overloads such as charging current of deformed electrolytic condensers
- Low price.
- Small size and light weight.
- Simple mounting.
- Outlast life of equipment.
- Instant starting.
- Low heat dissipation.

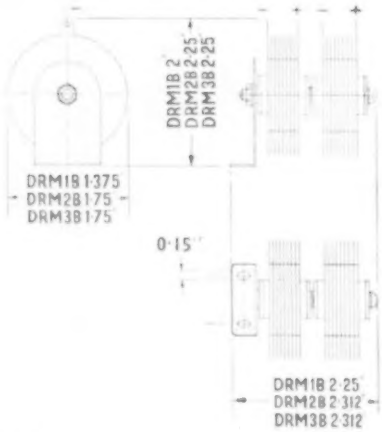

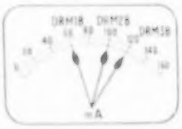

Maximum Output Current (at 35°C)

Maximum Input Voltage (1 m.s.)

Maximum Instantaneous Peak Current—unlimited

RATINGS

TYPE	DRM1B		DRM2B		DRM3B	
Maximum continuous dissipation	[illegible]	[illegible]	[illegible]	[illegible]	[illegible]	[illegible]
Maximum output current (mean)	[illegible] mA	[illegible] mA	[illegible] mA	[illegible] mA	[illegible] mA	[illegible] mA
Maximum peak voltage (r.m.s.)	[illegible] volts		[illegible] volts		[illegible] volts	
Maximum peak inverse voltage	[illegible] volts		[illegible] volts		[illegible] volts	
Maximum instantaneous peak current	Unlimited		Unlimited		Unlimited	
Weight	[illegible] oz		[illegible] oz		[illegible] oz	

SELENIUM SenTerCel RECTIFIERS

Standard Telephones and Cables Limited

(Registered Office: Connaught House, Aldwych, London, W.C.2)

RECTIFIER DIVISION, WARWICK ROAD, BOREHAM WOOD, HERTS. *Telephone: Elstree 2401. Telegrams: Sentercel Borehamwood*

THE

"Ohm's Law" of Electrostatics

Apparent Paradox of the Electrostatic Voltmeter

By "CATHODE RAY"

PEOPLE who teach electricity to those who intend to mess about with bells and lamps and kettles and even with motors usually rely heavily on water pipes and pumps for their illustrations, and fight shy of electrostatics. But if the instruction is with a view to radio, that won't do. For radio is full of capacitors, and people who have learnt to think of electricity only as currents can't cope with it. To them, a capacitor is just a break in the circuit.

So we radio people have to go through electrostatics—charged bodies, pith balls, and all. And if that seems too cobwebbed to be worth serious attention—well, perhaps that is why the behaviour of electronic circuits is sometimes perplexing. Although many people go along quite usefully for a time on a hazy idea of these fundamentals, sooner or later they get stuck. So I hope nobody will think the subject of the following discussion is out of place in *Wireless World*.

One of the first things we are taught in electrostatics is "Like charges repel; unlike charges attract." The pith balls and gold-leaf electroscopes are brought in to demonstrate the truth of these statements, and (provided the teacher has had the supreme good luck to hit on a nice dry day for it) the repulsion and attraction are duly demonstrated. Irrespective of whether the demonstration was a success or not, however, we are faced with the unanimous ruling of the wise men that two charges, q_1 and q_2, concentrated at points separated by a distance d, repel one another with a force equal (if the right units are used) to $\frac{q_1 q_2}{d^2}$

(To avoid unnecessary complications we shall assume the permittivity is 1 every time.)

If q_1 and q_2 are like charges—both negative or positive—the result is positive; but if they are unlike charges it is obviously negative, and of course a negative repulsion is an attraction.

Although charges concentrated at points are impossibilities, so that nobody can demonstrate the above law accurately by direct experiment, indirect methods of proof have been quite successful.

So far so good. We go ahead and draw imaginary lines coming out of positive charges and ending on negative charges to represent the electric field with its attractive force, and learn that there is a continuous fall of potential along them. We also learn that if the opposite charges are on parallel metal plates the plates attract one another, with a force proportional to the square of the voltage between them, and that this is the principle on which the electrostatic voltmeter works. An electrostatic voltmeter is really just a small variable capacitor, with one set of plates so delicately mounted that even the very small attractive forces that arise in practice make the plates move and indicate the voltage. Since the force is proportional to V^2, it makes no difference whether the voltage is $+V$ or $-V$.

The first feelings of uneasiness may occur when one hears it explained that it is only the *difference* of potential that counts, and that although $+100$ volts is a high potential relative to -100 V or even 0 V, it is at the same time a low or negative potential relative to $+200$ V. If, then (we say to ourselves) the potential difference and hence the attractive force between any two bodies is the same, regardless of whether their respective potentials are -50 V and $+50$ V, 0 and $+100$ V, or $+100$ V and $+200$ V, what happens to the doctrine that "like charges repel"? Or, sticking to that doctrine, so convincingly demonstrated, what about the electrostatic voltmeter? Can it be used to measure the voltage across the anode resistor in Fig 1, which has both its ends positive? Or will its pointer move backwards off the scale because its plates, bearing "like charges," repel one another? If so, what happens when the earth is disconnected? And does the voltmeter still refuse to work properly if one terminal is at $+0.001$ V and the other at $+600.001$ V? If not, why not? And are you still perfectly clear about the whole affair? If you are not, you may care to read on.

What is meant by an electric charge? There are various ways of defining or describing it. One may think of charges as the things which, when in motion, are an electric current. Electrons are (or carry) small negative charges. But the mere presence of electrons is not enough to charge anything. Generally there are equal numbers of positive particles, which cancel out the external influence of the electrons, so that no electrical effects can be detected. A single electron by itself is a very minute negative charge, and behaves in the special ways which we describe as electrical. So does a unit composed of

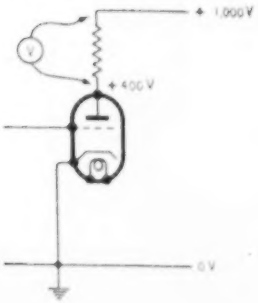

Fig. 1. Can an electrostatic voltmeter be used to measure the voltage between two points of the same sign?

1,000,001 electrons and 1,000,000 positive particles—except, of course, that its greater mass prevents it from moving about as nimbly as an unattached electron." Similarly, one positive particle (such as an ion), or a combination of 1,000,000 positive particles with 999,999 electrons, is a minute positive charge.

The important fact about charges is that there is a force of attraction between opposite kinds, tending to bring them together again into the neutral or unelectrified state. Hence the attraction between oppositely-charged pith balls, or plates of an electrostatic voltmeter. If you want to charge anything—that is to say, to separate negative from positive particles—you have to use an electromotive force, reckoned in volts, to do it, and in doing it you set up a back voltage tending to discharge. This back voltage is generally called the difference of potential between the two places where the separated opposite charges have been made to go, and the routes along which the attractive force between them acts are called lines of force.

The difficulty about really fundamental things like electric charges is that there is nothing more fundamental that can be used to describe them. If you have to give a detailed description of a building, it is quite easy. You can say how many bricks or stones compose it, and how they are arranged, and what materials are used for decoration, and so on. You can take for granted people know what bricks and paint and paper are. But it is more difficult to describe the raw materials, and the difficulty increases the farther back the inquiry is pressed. When it comes to describing electrons, we can say a lot about what they do, but really nothing at all about what they *are*. For us to do that, they would have to be made of still more elementary parts, and so far as we know they aren't. So fundamental things can only be discussed in terms of mental pictures, analogies, mathematical "concepts," etc., such as "lines of force." This is very helpful in enabling people to make practical use of things they really don't understand. The fact that nobody knows what electrons are has not prevented millions of people from making use of them in most complicated and ingenious ways—in radio sets, for example. Usually all concerned manage to agree to use the same mental pictures when they discuss these fundamental things or perform the calculations necessary to exploit them to the best advantage.

Although these concepts are so helpful, and it is difficult to see how we could carry on engineering and other applied sciences without them, they are dangerously liable to mislead us into accepting them as realities. It is rather like a clerk at some head office, whose life is so bound to his figures of manpower and output that he forgets that they are only artificial symbols of the real things in the factory.

Lines of force, for example. We know by experiment that exceptional things happen in the space around what we are pleased to call "electrically charged bodies." We just don't understand why or how these things happen, but it has been found by careful study that they always happen in certain definite ways and with certain numerical relationships. So scientists have defined various quantities such as charge and potential, and have enunciated various "laws" connecting them, and to help you and me to grasp these they have imagined such things as lines of force. Owing to the care with which these things have been defined, they make up a consistent system, and one can work about with them and design electrical appliances and predict their performance with confidence. But they are quite arbitrary. If there are beings in Mars who have studied these things they may have quite a different way of thinking about them, yet leading to the same results.

So with this in mind, let us look into the charge and potential question.

We had got as far as the basic fact that we can't have one without the other. Suppose you have a light tinfoil-covered ball suspended in the room by an insulating thread. To charge it, you have to apply an e.m.f., as in Fig. 2. What the e.m.f. of the battery does is to remove electrons from the ball and transfer them to earth. These electrons still maintain their mysterious bonds of affinity with their positive partners left on the ball, and calling these bonds "lines of force" helps us to visualize them but doesn't actually explain anything. What we do know is that they show up as a voltage—a "potential difference"—between ball and earth; and when enough electrons have been transferred to make this p.d. equal to 1,000 volts (in this case) the current ceases, because the battery can't hold back a greater voltage than its own. We say the ball is charged to + 1,000 V. It would be equally true to say that the earth is charged to − 1,000 V (relative to the ball); but nobody *would* say so, because it has been agreed, for general convenience, to refer all potentials to earth, whose potential is arbitrarily called zero. Except with this understanding, it is meaningless to say anything has a certain potential. All we can

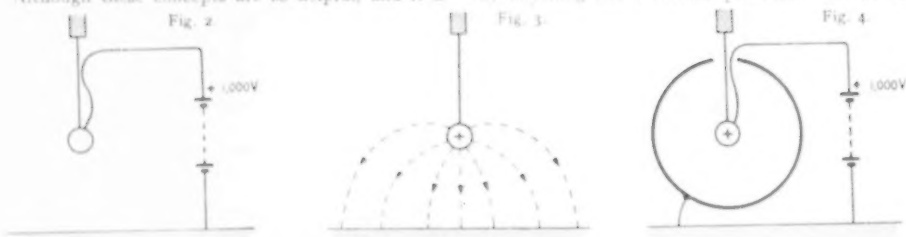

Fig. 2. First stage in a charging experiment. An insulated ball is charged to + 1,000 volts. Fig. 3. Second stage: the charging battery is removed. Fig. 4. First stage of second experiment: an earthed globe surrounds the ball while it is being charged.

Fig. 5. Second stage, corresponding to Fig. 2. Fig. 6. First stage of third experiment: the globe is at + 1,000 V. Fig. 7. Second stage: the globe is charged, but the ball is uncharged *although it is at a potential of + 1,000 V.*

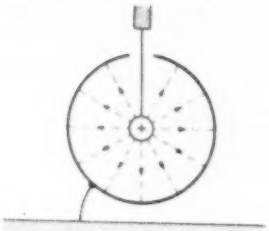

Fig. 5.

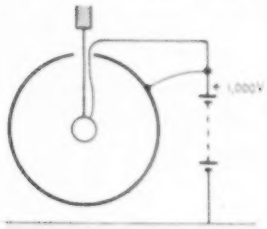

Fig. 6.

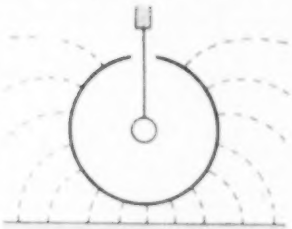

Fig. 7.

know is that there is a certain potential difference between it and earth or any other specified location.

By taking note of the amount and duration of the charging current, we could measure the charge needed to cause the p.d. of 1,000 V. The amount of charge needed to set up a given p.d. is very important in practice, and has been given the special name "capacitance." If the 1,000-V battery transferred 24,000,000,000 electrons (= 0.004 microcoulomb), the capacitance would be 0.004/1000 microfarad, or 4pF. The bigger the ball, and the closer to earth, the greater the capacitance. That part of the story is likely to be familiar to all readers; in fact, people who work much at radio and kindred arts soon find themselves able to visualize capacitance and estimate its magnitude far more readily than the potentials and charges themselves. It is therefore a particularly valuable "concept." The relationship which expresses it, $C = Q/V$ (where Q is the charge and V the p.d.) is about as important in electrostatics as $R = E/I$ in current electricity.

In Fig 3 the battery has been removed; and as the connection to earth has gone with it the electrons have been unable to get back, and the ball remains charged to + 1,000 V. To emphasize this, a few lines of force have been dotted in. They show the paths electrons would take if they were free to fly across the space from earth to ball. (Unfortunately the conventional plus-to-minus arrows point in the opposite direction.)

Next, suppose the experiment to be repeated with the ball at the centre of a hollow metal globe connected to earth (Fig 4). The result (Fig 5) will be very much the same, except that all the lines of force will end on the globe. They could not go through it to earth, because a line of force between globe and earth would indicate a p.d. between them, and that is impossible so long as there is a connection of negligible resistance between the two, making the potential of the globe the same as that of earth. Exact measurement would show that the charge was greater this time, indicating a greater capacitance. That is a well-known result of shortening the lines of force.

Lastly, after having taken care to discharge the ball by earthing it, repeat the experiment with the globe connected to + 1,000 V. (Fig 6). This time it will be found that the ball won't charge at all. No charging current flows through the connection to it from the battery, though of course a comparatively large current will have flowed into the globe to charge it to 1,000 V. But since the ball and the globe are at the same potential, there can be no lines of force between them, so no charge on the ball. This agrees with our "law," $C = Q/V$, in the form $Q = VC$, which indicates that zero V between two things with capacitance to one another (such as the globe and the ball) necessarily means zero charge. Looked at another way the ball has no capacitance to earth (because screened by the globe), so that even when there is a V to earth there can be no Q.

Charge and Potential

So we see that being at a high potential (to earth) doesn't necessarily mean being charged. If the surroundings are at the same potential there can be no charge, and so no forces. For example, the fact that both sides of the electrostatic voltmeter in Fig 1 are positive to earth need not mean that they are both positively charged. With a little care in arrangement, any question of repulsion and consequent errors in readings can be kept out of it, without limiting the use of the instrument to points that are of opposite potential to earth.

Suppose we have two parallel plates, with a p.d. of 100 V between them. This will cause a certain attractive force, tending to pull them together. What we want to be quite clear about is what difference it makes if the plates are at, say, + 50 and − 50 V, + 100 and 0V, or + 200 and + 100 V.

Fig 8 shows the first of these. The battery main-

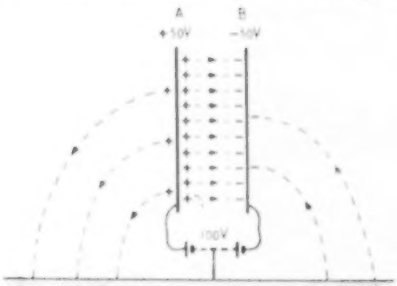

Fig. 8. State of charge when two plates, with a p.d. of 100 V, are respectively positive and negative to earth. A is assumed to have a larger capacitance to earth than B.

tains the 100-V p.d., and if we know the capacitance between the plates the charge follows from Q = VC. Suppose it is 10 units, each represented in the diagram by a + and − sign with a dotted line of force linking them.

So much for the internal situation. Externally, A has a certain capacitance to earth, and is being held at + 50 V with respect to it; so it must have received an additional charge. If the capacitance of A to earth is, say, 0.6 times its capacitance to B, this charge will be 3 units, as indicated. (Remember the p.d. to earth is only half that to B.) Similarly, if the capacitance of B to earth was 0.4 times its capacitance to A, it would have an additional negative charge of 2 units. These external capacitances are larger than would be likely in practice, in order to make the diagrams clearer. But the principle is the same whatever the values. So besides being attracted to one another, A and B will be attracted to earth (in its widest sense). The net attraction between A and B is reduced by the capacitances to earth. If A and B were the plates of an electrostatic voltmeter, such counter-attractions would cause variable errors unless precautions were adopted.

Fig 9 shows the plates with the same p.d. between them, but the potentials to earth are 100 V and zero respectively. So there is no extra charge on B, but A has to carry twice as much as before. Considering only the "internal" charges, the fact that B carries as many units as A, although it is at zero potential while A is at + 100 V, may seem rather strange. But the capacitance between B and earth, when they are short-circuited, is infinitely great, so any charge on B is possible without p.d. to earth.

In Fig 10 both plates are positive; but as there is the same p.d. between them as before, the internal situation is unchanged. Compared with Fig 9, the external charge on A is doubled, owing to the doubled voltage; while now the external charge on B is positive! The net charge on B is therefore only 6 negative units; the remaining 4 needed for internal affairs are derived from a separating-out of the electrons and positive ions composing B.

If A were the moving plate of a voltmeter, it would be attracted more strongly to the surroundings than to B, so would read lower than zero! If, on the other hand, it were the fixed plate, the external attraction wouldn't matter. Making B the moving plate would be all right so long as it was earthed, as in Fig 9. But at any other potential, as in Figs 8 and 10, there would be error due to the counter-attraction of earth. This can be overcome, however, and the instrument made suitable for use under conditions such as Fig 1, by surrounding the moving plate with a metal screen connected to the fixed plate. This makes the counter-attraction always the same at any scale reading, so that it can be allowed for in the calibration.

Just to complete the series we might add Fig 11 showing the situation with zero p.d. between the unscreened plates. Here all the lines of force have external destinations, so the plates tend to be drawn apart.

When considering the experiment illustrated in Fig 6, we noted that connecting the globe to + 1,000 V put the previously earthed ball in such a condition that no charge moved on to it when it was connected to + 1,000 V. Seeing that the ball has appreciable capacitance, this can only mean that connecting the globe to + 1,000 V also raised the potential of the entirely insulated ball from zero to + 1,000 V. This, of course, is one of the most popular uses of capacitance—to alter the potential of some part of a circuit without any conducting path.

Yet another deduction from V = Q/C may be of some interest even though it is not often used. Suppose you charge a capacitor and then take it to pieces by pulling the plates apart; what happens to the charge? Well, assuming the insulation remains perfect, so that the charge cannot escape, the only possible result of forcibly decreasing C is for V to rise. So if you want a higher voltage than any you have got, charge a capacitor and then remove one side of it into mid-air!

In any event, put V = Q/C alongside Ohm's Law in your primary kit of mental tools; it is a great help in all these problems.

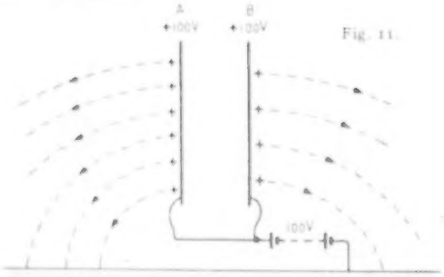

Fig. 11.

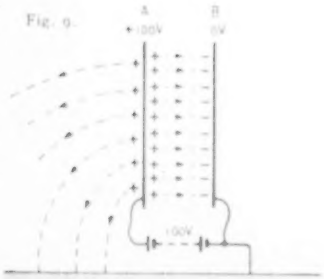

Fig. 9.

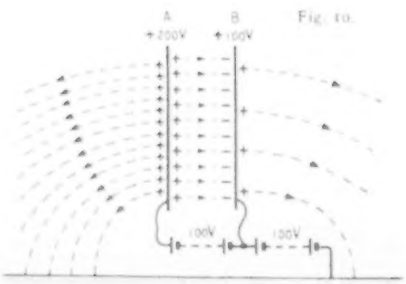

Fig. 10.

Fig. 9. Same p.d. between plates as in Fig. 8, but one plate earthed.

Fig. 10. Same p.d. between plates, but both positive to earth. Part of the negative charge on B is derived from itself.

Fig. 11. No p.d. between plates; both positive to earth.

HIGH QUALITY REPRODUCTION

"FIFTY and THIRTY WATT" CINEMA AMPLIFIERS as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required.
PRICES range from **34½ gns.** to **42½ gns.**

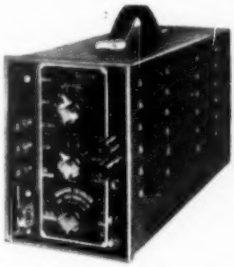

TYPE C.P. 20A AMPLIFIER
For A.C. Mains and 12 volt working giving 15 watts output, has switch change-over from A.C. to D.C. and "Stand-by" positions. Consumes only 5½ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.
PRICE **£28 . 0 . 0.**

FOUR-WAY ELECTRONIC MIXER
This unit has 4 built-in balanced and screened microphone transformers, normally of 50-30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less, and any impedance can be supplied to order. PRICE **£24 . 0 . 0.**

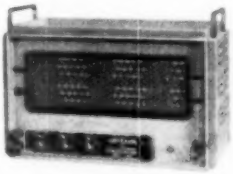

OTHER MODELS IN OUR RANGE OF AMPLIFIERS
"SUPER-FIFTY WATT" - - - - - PRICE **36½ gns.**
"THIRTY WATT" - - - - - - - - - " **30½ gns.**
"10-15 WATT RECORD REPRODUCER" - " **25½ gns.**

These are fitted in well ventilated steel cases with recessed controls, as illustrated.

Full details upon request.
EXPORT ENQUIRIES INVITED.

VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19
Telephones: LIB 2814 and 6242-3 Telegrams: "Vortexion Wimble, London."

the user —

"I must congratulate you on your product which I think is one of the best I have heard. It compares favourably with much more expensive speakers."

the trade —

"I do agree with you when you state it to be the best speaker in domestic use. Quite candidly I will say it is the first time I have been satisfied with a speaker for quite a while . . . . I can now say to my friends and customers 'There, that's the type of speaker *you* want.'"

the technical press —

"On a plane baffle the Concentric Duplex gives a clean and full-bodied bass response of surprisingly good quality for a 10 in. diaphragm. The diaphragm suspension is also of a type well suited for use in conjunction with a cabinet of the 'bass-reflex' type if this is preferred."

Wireless World February 1950

Leaflet on request

a chorus of praise for

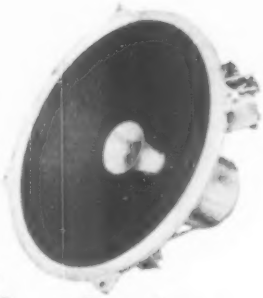

Stentorian
Concentric Duplex

HIGH FIDELITY REPRODUCER

SPECIFICATION: Series Gap magnet of Alcomax 3. Flux in LF gap 12,000 gauss on 1" pole
" " HF " 13,000 gauss " " "
Power handling capacity, 6 watts. Frequency range 50-14,000 c.p.s. Fundamental bass resonance, 65 c.p.s.

Complete with matching transformer and filter condenser. **£6 - 6 - 0**

WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS · ENGLAND

Somerford and Miniford

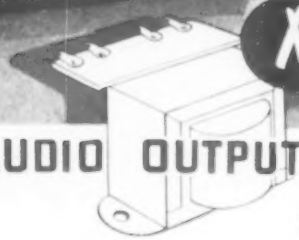

AUDIO OUTPUT TRANSFORMERS

These two standard ranges of Output Transformers will meet all the normal needs of the home constructor. They provide a degree of accuracy, quality and dependability which cannot be surpassed.

SOMERFORD. A range of Output Transformers designed to ensure high quality and reliable performance. Suitable for single ended or push-pull circuits, they cover the widest limits of the audio frequency band. May be used with confidence for the most exacting circuits.

MINIFORD. A range of high quality transformers of economical design which provide excellent reproduction for domestic purposes, but over a more restricted range of audio frequencies than the Somerford Transformers. 2, 4 and 8 watt types suitable for all outputs.

★ **CHARACTERISTIC CURVES** of Somerford Transformers showing frequency response between 20 cycles per second and 25,000 cycles per second are available upon request.

Write for our latest Folder giving complete details of the SOMERFORD and MINIFORD Transformers

GARDNERS RADIO Ltd

SOMERFORD · CHRISTCHURCH · HANTS

Phone: CHRISTCHURCH 1025

Oliver Heaviside and His Layer

An Appreciation of His Work

By SIR EDWARD APPLETON, F.R.S.

THIS month the world of science and engineering is celebrating the centenary of the birth of Oliver Heaviside, mathematical genius and one of the pioneers of electrical communication. It is therefore fitting that some reference to Heaviside's contributions to radio science should be made in *Wireless World*, Britain's oldest wireless journal. Oliver Heaviside was born on May 13th, 1850, at 55, King Street, Camden Town, and died in Torquay on February 4th, 1925. His aunt was married to Sir Charles Wheatstone, the pioneer of electric telegraphy, while his brother was a divisional engineer of the British Post Office, stationed at Newcastle-on-Tyne; so that Oliver, as a youth, was stimulated by a scientific atmosphere of electrical interest. Until fairly recently there was some obscurity concerning the record of Heaviside's doings in his early twenties, but it now seems clear that he actually served as a telegraph operator in the Great Northern Telegraph Company, working at the Newcastle station of the company which operated a cable to Denmark. It was during the four years of his service with the telegraph company (1870-1874) that Heaviside began to publish papers on telegraph theory. He was associated during the same period with his brother in conducting experiments on duplex telegraphy, first over an artificial line and later between Newcastle and Sunderland. But his interests were more theoretical than practical and, in 1872, he started the publication of a stream of papers, mainly fairly short and appearing principally in *The Electrician* and *Nature*, which continued for forty years. These papers were concerned with the propagation of variable currents through wire circuits and the propagation of electric waves through the ether of space, as well as with the development of his own new and vigorous methods of solving differential equations, especially those representative of electrical circuits.

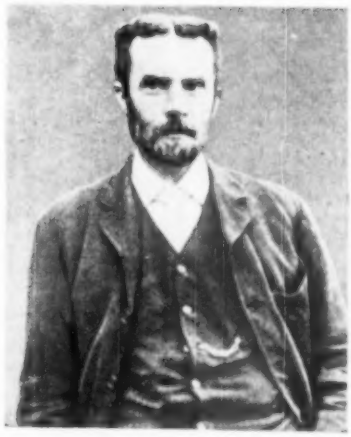

Oliver Heaviside, 1850-1925.

When Heaviside was 38 years of age Heinrich Hertz in Germany succeeded in generating and detecting electric waves. We know that the two men corresponded on scientific matters in a most friendly manner though it seems that they never met in person. Heaviside, of course, lived through the heroic age of the birth and early development of practical radio communication and doubtless pondered a great deal about the question of the propagation of radio waves round the spherical shape of the earth. Indeed, we know that a mathematical friend, G. F. Fitz-Gerald of Dublin, actually put the problem directly to him in 1899 when people were actively discussing whether Marconi's success in communicating over short distances might yet be crowned by the achievement of trans-Atlantic radio transmission. It is not, however, known whether or not Heaviside worked mathematically at this problem of electric wave diffraction round a conducting earth. All that is available at present in the way of record in this connection is Heaviside's famous suggestion concerning the possible existence of an electrical conducting layer in the higher atmosphere which would facilitate round-the-earth transmission. This occurs in his remarkable article entitled "Theory of Electric Telegraphy," written in June, 1902, and published in the tenth edition of the "Encyclopædia Britannica." The significant passage reads: "There may possibly be a sufficiently conducting layer in the upper air. If so, the waves will, so to speak, catch on to it more or less. Then the guidance will be by the sea on the one side and the upper layer on the other." In the language of to-day it would appear that Heaviside pictured the space between the spherical surface of the earth and the lower surface of the upper atmospheric conducting shell as a wave-guide, which, as we now know, will transmit all wavelengths of value less than $2h_0$, where h_0 is the distance between the conducting ground and the conducting layer.

Heaviside was not alone in postulating the existence of an upper-atmospheric conducting layer which facilitated long-distance radio propagation. A similar suggestion was made by Professor A. E. Kennelly of the United States about the same time, and, now that we know such a layer actually exists, it is known as the Kennelly-Heaviside Layer. Its existence was proved directly by observing the succession of signal interference maxima and minima produced at ground level by the direct and reflected rays when the wavelength of a transmitter was gradually varied through a known amount. The height of the Kennelly-Heaviside Layer (or E Layer, as it is often termed) was found to be of the order of 100km above ground level. It should, however, be pointed

out that it was Heaviside's suggestion rather than the even more detailed formulation of Kennelly that prompted in this country all the early radio work on the ionosphere, as the complex of ionized layers is now termed. Especially important in stimulating my own interest in the subject was the theoretical work of Dr. W. H. Eccles who gave precision to Heaviside's suggestion by expressing it in a modern form, accounting for the layer conductivity in terms of electrons and ions. Also, so far as I am aware, Eccles was the first to use the term "Heaviside Layer."

Nowadays the ionosphere is subjected to an hourly sounding of its characteristics at many places all over the world; for, over the last quarter of a century, we have learned how to find the electron concentrations in the various ionized layers, and also how to relate such results to the processes whereby radio waves are reflected and refracted at different ionospheric levels. As a result of this work the subject of ionospheric forecasting has developed, whereby it is possible to indicate in advance to the radio communication engineer the range of radio frequencies likely to be most effective in transmission from one place to another, in any part of the world, at any time and over any distance.

But the original stimulus to all these developments came, as I have said, mainly from Heaviside. As also in the case of his work on operational mathematical methods, Heaviside said the first word about something that many others later developed and extended. That is characteristic of a genius.

Economical Battery Set

For High Quality Reception of Local Stations

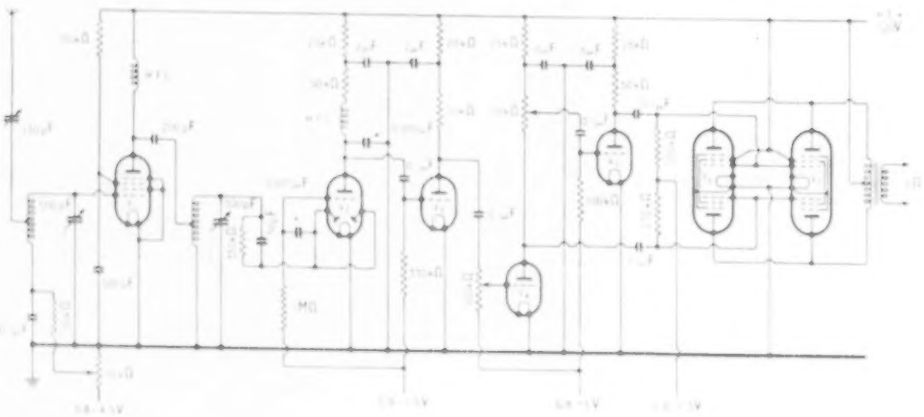

DESIGNED by L. Thomas, this straight receiver will give a maximum power output of 3.4 watts for an average h.t. consumption of under 10 mA and an l.t. consumption of 1 amp. Decoupling is sufficient to maintain stability until the h.t. battery voltage falls from 120 V to 90 V.

Since reception of only a few local stations is required, the selectivity given by the two tuned circuits is ample, provided that the series aerial capacitor is adjusted for optimum results. The diode detector plus amplifier, using a double-diode triode (V_2), was adopted because it was found to give better quality than a leaky grid detector, for the same filament consumption.

The triode phase splitting circuit does not contribute to the gain of the receiver, but gives markedly better quality than the usual q.p.p. driver transformer. No correction circuits for attenuating high frequencies are used on the two double-pentodes, because these valves are in parallel, and consequently have a low joint impedance which automatically reduces loudspeaker resonances. In any case, a certain amount of top accentuation is desirable to balance the extended bass response given acoustically by the loudspeaker. This is a 12in dual suspension model by Sound Sales, Ltd., in a "phase inverter" cabinet. The output transformer is the *Wireless World* model, marketed by M.R. Supplies, Ltd.

A list of the valves used is given below. Unfortunately these have now become "obsolete" or "replacement" types, so in case there should be any difficulty in obtaining them, the "current" types in brackets are suggested as suitable alternatives.

V_1	Mullard VP2B	(Cossor 210VPA or Marconi VP2A)
V_2	Mullard TDD2A	(Marconi HL23DD)
V_3	Mullard PM2HL	(Marconi HL2)
V_4, V_5	Tungsram LD210	(Marconi HL2)
V_6, V_7	Cossor 210QP	(Marconi QP25)

More About Spot Wobble

Removing "Lininess" from Television Pictures

By T. C. NUTTALL (*Cinema-Television, Ltd.*)

THOUGH I am fully in agreement with R. W. Hallows as to the benefits arising from television "spot wobble," in the March *Wireless World*, I cannot entirely agree with the explanation given in that article. What I regard as the correct explanation involves some unusual conceptions, and it is hoped this article will clear up misunderstandings.

Spot-wobbling is an old idea, but in recent years three important applications have been found for it. These are:

(1) To cover up some faults liable to occur with certain methods of recording television pictures on film.

(2) To reduce screen saturation effects in high power c.r. tubes for large-screen projection systems, and

(3) To remove objectionable line structure effects from large, bright, directly viewed television pictures of high quality. It is this third application which has, naturally, excited the widest general interest, and is the one with which we shall be mainly concerned in this article.

Before we can hope to understand how spot-wobble works, we must have a clear idea of the nature of the defects which we intend to correct. I am going to start, therefore, by showing that the simple explanation of interlacing, as normally given, is insufficient to describe all that actually takes place in practice.

In an interlaced system, as we all know, the odd-numbered and even-numbered lines are scanned in separate frame traversals, spaced in time by one-fiftieth of a second; the process is repetitive, so that the full complement of lines will be scanned in any two consecutive traversals. If our circuits and apparatus are working properly the scanned lines will be accurately interlaced on the c.r. tube screen. This, however, is by no means the whole story; accurate interlacing in the observer's eyes involves the two further factors of persistence of vision and fixation of the eyes.

The odd and even lines are presented to the observer as two flashes separated in time by one-fiftieth of a second. He can get the impression of an interlaced set of lines only if his persistence of vision is sufficient to "store" the visual information for the required time.

Now the persistence of vision is very much affected by the brightness of the object being observed, as is shown very clearly by the relations between brightness, frequency and flicker. The earliest television systems used a frame frequency of 12½ per second, but that was when the pictures were very dim. As the brightness was increased it became necessary to raise the frame frequency to 25 per second and later to 50 per second to avoid flicker. C.r. tubes have improved so much in the last few years that the limit to the brightness we can now use is once more determined by considerations of flicker. (The Americans can use more brightness than we can because their frequency is 60 instead of 50).

Enlarged sections of a television screen picture; one with and one without spot wobble.

We are obviously working in a range of brightness where persistence of vision is no longer sufficient to give the observer the impression of a set of interlaced lines. Instead, he gets the impression of a set of lines (only half of the full number) which *change their position* at each flash. If he allows his eyes to follow the movement he will see this half-set of lines crawling up or down the picture at a rate which will cause them to travel the full height of the picture in about 7½ seconds. This is what I shall refer to as the "crawling line" effect. Even if persistence of vision does not fail us we must still recognize that the observer must keep his eyes still if he is to see the odd and even lines in their correct relative position. But the observer will not keep his eyes still—he will want to follow the movements of objects in the picture. Whenever the observer's eyes are moving up or down he will lose the effect of the interlace, and if the rate of movement approximates to the crawling rate he will become acutely aware of the crawling line pattern. This effect is probably seen at its worst when the B.B.C. wind their titles and captions slowly up the picture, often at the most objectionable speed!

These effects may not appear very serious on a c.r. tube with a poor focus, but then, of course, the general definition will be poor. It is only when we have taken some trouble to produce a bright, sharply focused picture that we realize the seriousness of the crawling line effect. With a good focus, the black-to-white contrast in the crawling line pattern is greater than any contrast in the picture details.

The B.B.C. pictures contain, nominally, 377 active lines, or, say, 188 per frame. When we complain of "lininess" we can be reasonably sure that

the 188 crawling lines are to blame—the 377-line pattern is too fine to be objectionable—so we must concentrate our attention on removing the effects of the 188-line pattern.

We may expect that any method of removing the 188-line pattern must also cause a reduction in the picture definition. This generalization is true only in a qualitative sense, for we shall find that the possible methods differ considerably in the extent to which they spoil the definition. We are, obviously, seeking the method which does the least damage.

We might consider the use of c.r. tubes with elliptical or rectangular spots, or astigmatic focusing systems, etc., but we can reject all these on various grounds. The size and shape of c.r. tube spots are very ill-defined quantities which vary with brightness, and any attempt to put tight limits on them would produce enormous difficulties in design and manufacture. In any case we should find that these solutions do not satisfy our "minimum damage" condition. The required solution must be more cunning than these.

Heterodyne Whistle Analogy

At this stage I would like to introduce a useful analogy with the 9 kc/s heterodyne whistle in an ordinary radio sound receiver. The whistle is unimportant in a poor set, but it comes into prominence when we take steps to improve the "top" response. When this happens, the designer puts in a "whistle filter," and if the filter is sufficiently selective the whistle is cut out with only a small degradation of the sound quality. Our 188-line pattern is a rather close analogue of the heterodyne whistle. It is a pattern, with a clearly defined spacing, which is interfering with our enjoyment of the picture. The first clue which we get from this analogy is that we should take advantage of the regularity of the pattern to use some device which operates to remove this particular pattern in a selective manner.

Suppose that we could produce a c.r. tube with a double spot, so that each line scan would draw two lines, and 188-line scans would draw 376 lines. If the spots were the right distance apart (half the normal pitch of the 188 lines) the 376 lines would be equidistant and all signs of the 188-line structure would have disappeared (see diagrams A and B).

This is obviously a selective system, and it can be shown that it is the most selective system which is theoretically possible. (Our selectivity is limited, compared with the "whistle filter," by the fact that we cannot produce "negative light" on the screen corresponding to the negative half cycles of ripple which can be produced in an electrical circuit).

This theoretically ideal system cannot be used in practice because we cannot make the c.r. tube with the required double spot. At this point we introduce the idea of spot-wobbling. If we could take a tube with a single spot and wobble this spot with a *square* wave wobble so that the spot occupied one position for half of the cycle and another position for the other half, and if, further, we could make the frequency of the wobble sufficiently high, then the tube would behave in all respects as though it had a double spot (see diagram C). This idea avoids the difficulty of making a special c.r. tube, but it is still not practicable, since there is no possibility of producing a square wave deflection at the frequency required (say about 10 Mc/s). All we can expect to obtain at this frequency is a sine-wave deflection.

In a sine-wave wobble, the spot is travelling slowly at each end of its travel and is not actually at rest for any appreciable part of the cycle, also it wastes some time, compared with a square wave, in crossing from one side to the other. Nevertheless, the sine-wave wobble gives us a close approximation to a double spot and accurate calculation shows that it is not far short of the ideal. The sine-wave wobble is therefore both practical and a close approximation to the ideal (see diagram D).

The required amplitude of wobble is of considerable interest. It is easy to see that with a square-wave wobble the peak-to-peak amplitude should be half the 188-line pitch, and we would expect the sine-wave wobble to require a somewhat greater amplitude. Accurate calculation (see Appendix) shows that the correct peak-to-peak amplitude is 0.7633 (or, in round figures, say three quarters) of the line pitch.

The correct amplitude is a well-defined quantity, there is nothing arbitrary or empirical about it. If we use a whistle filter in a sound receiver we obviously tune the filter to the whistle frequency. Similarly, if we spot-wobble there is no point in using any other than the correct amplitude. Note that the correct amplitude depends only on the line pitch; it is not affected in any way by the size of the unwobbled spot.

The spot-wobbler can use any frequency between 8 and 10 Mc/s (there is nothing to gain by exceeding 10 Mc/s) but from a practical point of view care should be taken to avoid frequencies likely to produce harmonic interference (e.g., 9 Mc/s, whose fifth harmonic at 45 Mc/s might interfere with the radio receiver). Power requirements are very low, and one very small oscillator valve should be adequate. The biggest practical difficulties arise in connection with screening and decoupling to prevent the whole frequency finding its way to places where it is unwelcome. It is important to avoid any brightness modulation which might destroy the brightness equality of the two "equivalent spots," and so pro-

These diagrams represent a small portion of a single frame (188 lines) of a picture two feet in height. The coarse line structure in A is eliminated in B by the use of a double spot. The same result is achieved in C by the use of a square wave wobble. The practical sine-wave wobble shown in D is a close approximation to the ideal. Viewed from a suitable distance (remembering that the picture height is two feet!) these diagrams give a reasonable indication of the reduction of "lininess". It must be recognized, however, that *stationary* diagrams of this kind cannot adequately represent what is seen in practice, where the continual shifting of the lines and the phase of the wobble on successive scans produce a blurred appearance compared with the diagrams.

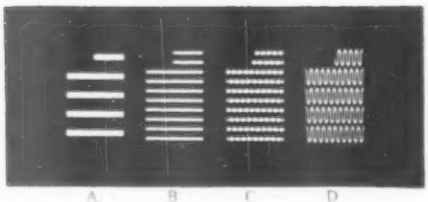

A. B. C. D.

vent the accurate balancing-out of the 188-line pattern.

Major Hallows wrote enthusiastically about the results produced by spot wobbling, and his reactions are typical of observers who have seen pictures on a 20-inch tube supplied for demonstration purposes with the Cintel film scanner installed at Alexandra Palace in May, 1949. When the liminess is removed, observers voluntarily reduce their viewing distance in a ratio of about two to one, which far more than compensates for the slight theoretical loss of definition produced by the spot wobble. The 405-line system is then found to give a very satisfactory degree of definition. It seems probable that the advocates of the so-called "high definition" systems (say 800 lines or so) are expressing their desire for less liminess rather than for more definition. With only a fraction of the complication and expense, spot-wobbling goes a long way towards satisfying this desire.

"Canned" Television Programmes

The other applications of spot-wobbling, although not, perhaps, of such wide general interest, are worthy of brief mention. In recording television pictures on continuously moving film (which method is used, for example, by the B.B.C.) it is often difficult to ensure accurate interlacing, on the film, of the two sets of lines forming each complete picture. The problem is primarily one of optical and mechanical accuracy in chasing the moving film, but is complicated by the rather unpredictable dimensional shrinkage of the cellulosid base of the film. Any inaccuracy will result in a "pairing" of the recorded lines. (This will not be discovered until the film is developed, when, of course, it is too late to make any correction!) This defect is shown clearly in the photograph used to illustrate Major Hallows' article. If such a picture were scanned again for re-transmission serious "beat" patterns would result from interference effects between the original and the new scanning lines. Spot-wobbling can be used to avoid this trouble, and the small loss of definition which results is less objectionable than the beat patterns.

The other photograph was intended to show the effect of spot wobbling, but on examination it will be found that definition is lacking in both *horizontal and vertical* directions. Now a spot-wobble can cause loss of definition in *only one* direction, so it must be concluded that the loss of definition in this photograph was not caused by spot-wobbling. I would like to emphasize that this photograph is definitely misleading, as the loss of definition which would be produced by a correctly adjusted spot-wobbler would be so small as to be almost undetectable in a photograph of this size.

In high-power c.r. tubes used for projecting cinema-size television pictures the current density in the scanning spot is more than one hundred times greater than in an ordinary c.r. tube, and produces considerable saturation effects in the fluorescent material. This gives rise in turn to variations in brightness and colour; the latter, in particular, can be rather objectionable. These troubles can be largely overcome by the use of spot-wobbling which has the effect of reducing the current density and making it less critically dependent on exact focusing conditions, in addition, of course, to its normal effect of reducing or eliminating liminess. However, the non-linear nature of the saturation effects rules out any simple mathematical analysis of the problem so that, in this case, the optimum amplitude of wobble is determined by a process of judicious trial and error.

These modern applications of spot-wobbling were developed, in 1947-48, in the laboratories of Cinema-Television, Limited, who had acquired the patent rights in 1946. So far, spot-wobbling has been used mainly for high-quality demonstrations; as far as I am aware it has not yet been applied to any commercial television receivers, though this may be expected to follow in due course. A word of caution is perhaps not out of place here—spot-wobbling will not cure all television troubles. It will not turn a mediocre picture into a good picture, but it can and does turn a good picture into an excellent picture.

APPENDIX

As the line spacing is regular, the screen brightness is a periodic function of distance measured across the lines and may be expressed as the sum of a mean brightness plus a fundamental (188-line) cosine component plus harmonic components (376 lines, 564 lines, etc.). We are interested in making the fundamental (188-line) component disappear; i.e., we want to make it have zero amplitude. The amplitude of any component may be found by the standard method of Fourier analysis, i.e., we multiply the brightness distribution by the appropriate cosine wave and integrate over one cycle to determine the mean value of the product. If we perform this operation on the brightness distribution of a wobbled spot we find that the integral turns out to be a standard form of the Bessel function $J_0(x)$ where x, in our case, is the ratio of the peak-to-peak wobble to the line spacing. The fundamental (188-line) component will disappear when $J_0(x) = 0$. On referring to published tables of the Bessel functions we find that $J_0(x) = 0$ when $x = 0.765$.

Television O.B. Links

At a recent discussion meeting of the Radio Section of the Institution of Electrical Engineers, it was emphasized that developments in television outside-broadcast technique were continually calling for new types of equipment. Also, increasing demands were being made for means whereby the vision signal could be passed to the transmitter. Before the war some 17 miles of low-loss balanced-pair cable had been laid in the London area; this has since been supplemented by 33 miles of coaxial cable. Connections to this 50-mile cable network can be made, up to distances of a few miles, through ordinary telephone circuits fitted with equalizers and amplifiers. This cable system is now used by the B.B.C. for about half the outside broadcasts, the remainder being passed by a radio link, which has a range of about 30 miles; this range could be extended by using links in tandem. The idea of "breaking in" to intermediate stations of the London-Birmingham radio relay link, though technically practicable, was not envisaged.

To reduce setting-up time, a certain amount of permanent wiring has been installed at places from where outside broadcasts were regularly relayed. Camera cables, however, could not be permanently fitted, as there was danger of deterioration.

As to the outside broadcast equipment itself, it was agreed during the discussion that it could undoubtedly be reduced in size, but the opinion was expressed that this would not greatly shorten the time needed for setting up. The link to the transmitter remained the most important factor.

The author operating the interference tracer.

Television Interference

Tracing an Unusual Source

By A. L. PARSONS, Grad.I.E.E.
(Murphy Radio)

THE writer was recently concerned with a most perplexing case of television interference, the symptoms, causes and tracing of which may be of general interest.

The television receiver screen was sometimes cut in two by a very wide white horizontal band. This might have been diathermy since the interference appeared to be modulated at 300 c/s. However, this band would sometimes vary in width and brightness and sometimes the whole picture would break up into a series of white bands moving up and down the screen. Also, these latter symptoms were always accompanied by peculiar vibrations, which seemed to emanate from different components on the television receiver chassis.

It was also noticed that the vibrations bore some similarity to speech and music. Closer observation showed that the vibrations and picture variations were in fact inter-related and eventually it was proved, beyond doubt, as a result of making comparisons with the loudspeaker output from a broadcast receiver, that these vibrations and variations were in direct sympathy with the B.B.C. Light Programme. Photographs of the interference patterns produced, one corresponding with orchestral music and the other with a steady note, are reproduced on this page.

Several different types of television receiver were tried on the same aerial, but in spite of the fact that they employed different intermediate frequencies and, too, that some of them were of the "straight" type, similar interference patterns and vibrations were produced. It should be mentioned here that none of the sets showed any signs of interference on the sound channel. Tuning the oscillators of the superhet receivers over a small range caused no noticeable change in the interference.

With the aid of a Murphy Interference Tracer, Type TS17, the interfering frequency was found to be 44.8 Mc/s, and the source was finally traced to a house 40 yards away. The TS17, which Murphy is supplying to the Post Office, is essentially a highly sensitive eight-valve radio receiver, using miniature components throughout. Power supplies are from self-contained dry batteries, supplying 1½ volts l.t. and 120 volts h.t. An "S" meter and headphones are incorporated. The meter circuits have quick charge and slow discharge characteristics, which are extremely useful when checking impulsive interference. A rod aerial and small loop aerial are provided, and these can be used as required.

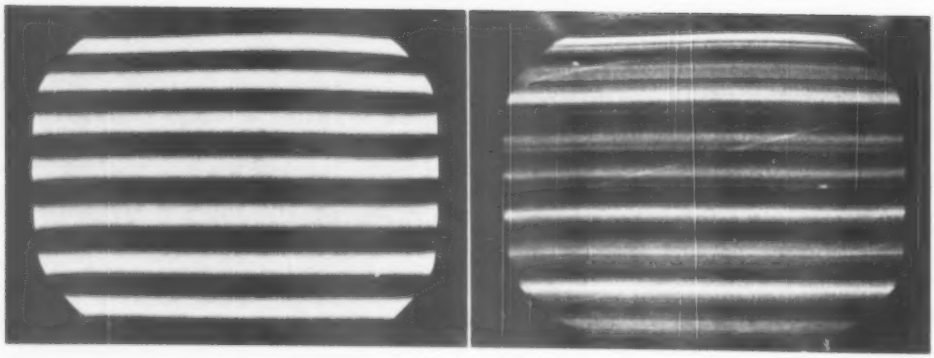

(a) (b)

Interference patterns produced with a steady note (a) and by mixed high- and low-frequency modulation (b).

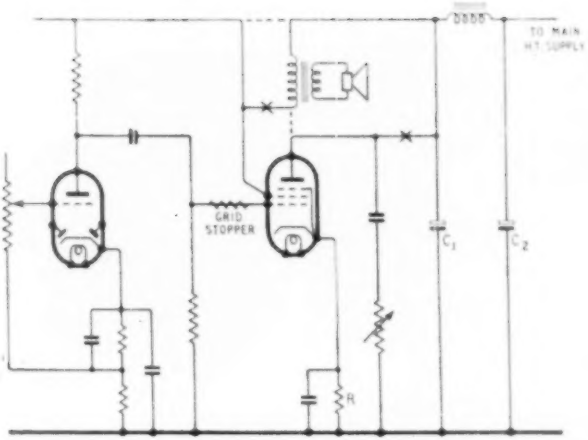

The offending output stage. The leads which were disconnected are marked with a cross and the new connections and grid stopper are shown dotted. R was 100Ω instead of 320Ω and both C_1 and C_2 defective.

The interference source was eventually found to be an ordinary universal mains, superhet, broadcast receiver of approximately 1934/35 vintage, and tests showed that while the local oscillator and the i.f. amplifier were in no way to blame, movement of leads in the output stage altered the interference frequency. Also, placing a finger on the grid cap of the output valve was found to stop the radiation completely. The rather obvious conclusion was that the output stage was oscillating parasitically at 44.8 Mc/s and that the received programme was modulating these oscillations. The programme was, in fact, heard quite plainly on the headphones of the interference tracer.

More detailed examination of the receiver showed that a "dabbler" had been at work. The output valve was non standard, the wiring incorrect (as shown in the diagram), the cathode resistor value low and the h.t. smoothing capacitors of low capacitance. The defective capacitors, with the resultant 50c/s ripple from the half-wave rectifier circuits, accounted for the horizontal band on the television screen during breaks in the Light Programme. However, correction of all these faults did not remedy the parasitic oscillations. A remedy was eventually provided by the insertion of a 20,000-ohm grid stopper, as shown in the diagram.

There was still one query: why was the modulation always the Light Programme? The radio set owner soon answered that one when he explained that he "had no time for the Home Service."

NEW BOOK

Recent Advances in Radio Receivers. By L. A. Moxon, B.Sc. (Eng.), A.M.I.E.E. Pp. 178+v, figs. 92. Cambridge University Press, Bentley House, 200, Euston Road, London, N.W.1. Price 18s.

THIS book is the latest to be issued in the "Modern Radio Technique" series and, to quote the publishers' note, "is intended for readers familiar with the technique of designing radio receivers in 1939 and concentrates particularly on those advances which were made during the war years." This is a more accurate indication of the scope and content of the book than the title.

The book is short and, of the 178 pages of text, nearly one-half is devoted to considerations of noise in receivers of the radar type. Wide-band i.f. stages are also covered in some detail, including the design of multiple stagger-tuned amplifiers. The remainder of the work covers the recent trends in commercial and communication receiver design with some reference to f.m. and television receivers, including "some new circuit tricks."

As we might expect from the authoritative nature of the source, the chapters on noise and i.f. amplication are more detailed than the rest of the book, and much of the material has not appeared under a single cover before. The chapter on noise measurement is particularly commendable and should give the reader the information required to put the subject on a quantitative practical basis.

In treatment and presentation of the subject the book is not, however, all that could be desired; there is a tendency to use the concepts and jargon of this special field which is hardly in keeping with the declared objectives of the book. Mathematical proofs are studiously, almost laboriously, avoided, whilst condensation of argument has been carried to lengths which, only too often, make the final conclusions appear almost as unsupported statements. There is also a noticeable lack of the explanatory notes and references to establish concepts which make a textbook stimulating and interesting to read. Nor does the author always define his terms or set out his symbols very clearly; for example, on the same page (p. 13) we find the same symbol used for temperature and for pulse-length. Again, on p. 90, we are given a diagram of the response of a multiple stagger-tuned amplifier in which the symbol "a" appears, to find what this particular "a" is (a slightly different "a" has appeared on the previous page) it is necessary, first, to turn up the Appendix, where it appears in an expression, and then look back through the text until it is found, defined implicitly, in another expression!. Furthermore, the symbols used are not always in accordance with the B.S.I. recommendations. The book is, however, notably free from errors and misprints whilst the diagrams are always clear.

In short, apart from method of presentation, the major portion of this book is of great value for the useful information it gives in a new specialized field; the later portion, however, tends to be a tantalizing collection of snippets and its main purpose should be to interest the reader sufficiently to turn up the original references.

E. J.

UNBIASED

By FREE GRID

Bloody but Unbowed

MY recent plea (W.W., March, 1950), for the jettisoning of outworn nomenclature by substituting the terms cathode and anode for the misleading negative and positive for batteries and the like, has brought, as I expected, a deluge of protests from the diehards. One of the strongest supporters of the old + and − school of thought is the respected chief engineer of one of our great storage battery makers.

As is fitting, his words are as weighty as the products he fathers but unfortunately his arguments are not. The chief plank in his platform seems to be that the + and − signs have been "a British standard for over 50 years." I do not doubt it, but I would remind him that the

horse represented the British standard of transport for far longer than 50 years and had it not been displaced by the internal combustion engine there would have been far less demand for his products.

In addition he rails against the use of terms of Latin and Greek origin in articles dealing with any aspect of wireless technology. Does he not know that the words "plus" and "minus," which he champions so strongly, belong to one of these two detestable languages?

Other objectors point out that when a cell is supplying power its negative terminal will be its anode but this will become the cathode when the cell is being charged. I can only suggest that they look up the words κατά and ἀνά in a good Greek lexicon.

The B.B.C. Forsaw It

BUT enough of such matters for I want to say a few words about the plight in which the Americans now find themselves, having foolishly ignored the vast store of television engineering experience accumulated in this country since 1936. According to one of their radio trade journals, *Successful Servicing*, Feb., 1950, nemesis has overtaken them because they overlooked a measure which the B.B.C. foresaw over fifteen years ago. As you know, the Americans, "puffed up with pride and armed with arrogance"—to quote the words of one of their most famous sons—sniffed disdainfully at vertical polarization and the upright television aerial which we use; instead they adopted horizontal polarization and bird-perch aerials.

Needless to say such an open challenge to American prowess was accepted. Unfortunately birds are no less stupid than human beings in failing to "pass along the car, please," but gregariously congregate on one limb of the aerial. Even if their weight does not always bend it their ill-distributed body capacitance upsets its electrical constants.

The result is that all the technical talent of the U.S. radio industry is now being diverted from more vital channels into finding a cure for this menace. Heating the aerial elements by eddy currents has proved a cure worse than the disease; while using electric motors to rotate the perches about their own axis is complicated. The most successful device, I should imagine would be to instal a loudspeaker near every aerial to belch forth recorded catcalls.

Radar to the Rescue

SCARCELY a day passes that we do not hear of some new radio application, more especially in the realm of radar. I do my best to keep you *au fait* with these but one development is now brewing which is of such importance that I wonder if I can reveal it to you without inviting the attention of MI5. At any rate, here goes.

I hear on high authority that the Government is much concerned at the number of road accidents involving very ancient cars. The reason for many of the accidents is said to be the drivers' inability, especially when reversing, to see through the dense clouds of smoke which the cars emit. Operations like reboring or reseeving can cure some of them, but in many cases the patient is too far gone to respond to such treatment.

It is therefore proposed to make an order in Council to make it compulsory for these modern Elijah's chariots—for some of them emit flames, too—to carry radar so that the drivers can see through the smoke clouds. This government order will, of course, mean great activity in the radio factories and I am told it will be given high priority.

A greater diversion of new cars to the home market would seem to my untutored mind a simpler way of solving the problem. But it ill behoves me or any of us radiomen to urge this point on the Government. Let the automobile industry do its own work. For my own part I feel this scheme should be made applicable to all cars and every motorist be made to drive blind, as indeed, so many of them appear to do at present.

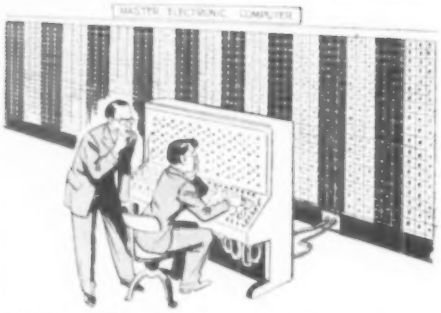

"Wrong answer again, Bellamy; it's obviously the time constant of R531 and C672."

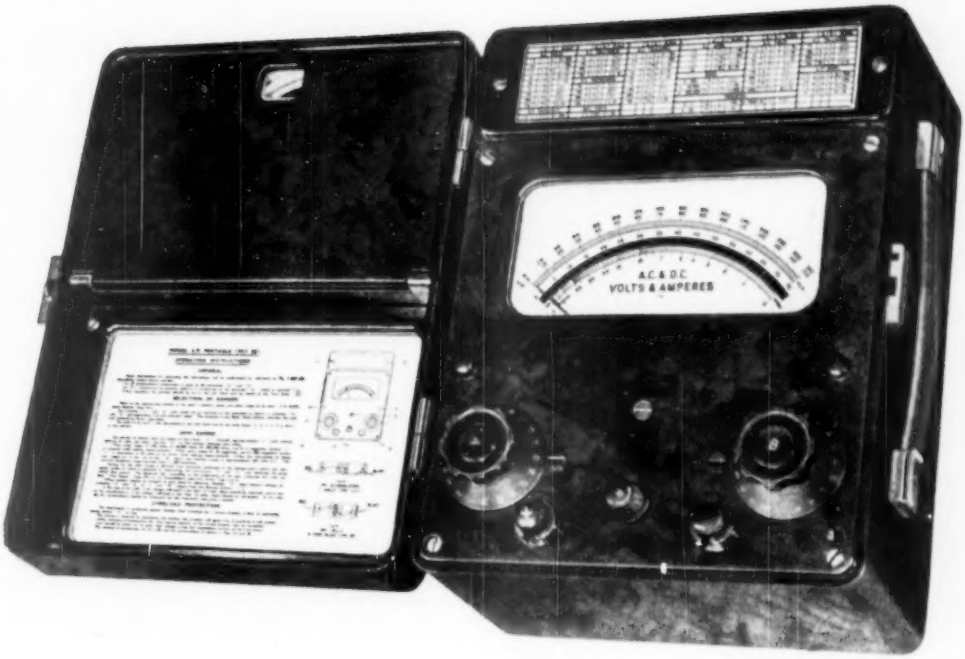

The WESTON S.75 Multi-Range Test Set

53 Ranges with Rotary Switch Selection

This uniquely comprehensive Test Set has 53 ranges for measuring AC and DC current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500 v. Selection is carried out by two 20-position switches. A fully protective safety device is fitted and is operative for forward or reverse overload. The 150 division 6" scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89 covering first grade instruments. Full details of this, and other Weston electrical measuring instruments will gladly be supplied on request.

SANGAMO WESTON LIMITED

ENFIELD, MIDDLESEX

TELEPHONE: ENFIELD 3434 (6 LINES) AND 1242 (4 LINES)
TELEGRAMS: SANWEST, ENFIELD

AREA DEPOTS:

201 St. Vincent Street, Glasgow.	Central 6208
Milburn House, Newcastle-on-Tyne.	Newcastle 26867
22 Booth Street, Manchester.	Central 7904
33 Princess Street, Wolverhampton.	Wolverhampton 21912

ESSENTIALS

FOR THE BEST PRODUCTION!

THE PHASE INVERTER SPEAKER

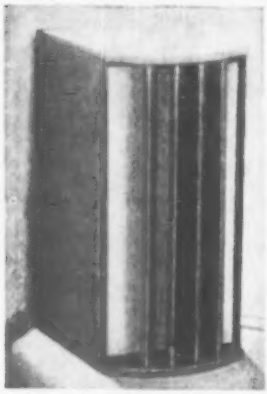

Beloved by its numerous users and flattered by imitation. Measuring only 29" high x 14" square, this instrument provides the music lovers' perfect answer to the "Baffling" problem. Response 25 to 13,000 cps; fitted with the famous Sound Sales dual suspension auditorium unit. Input impedance 6 ohms.

Price £12 10 0

HEAVY DUTY OUTPUT TRANSFORMER TYPE 038,
characteristic ... ldb. from 20-20,000 cps.
Price £2 6 8

WEBB'S RADIO, 14, Soho St., London, W.1
supply all SOUND SALES products on Deferred Terms

ALLOY CORED SCRATCH FILTER CHOKE

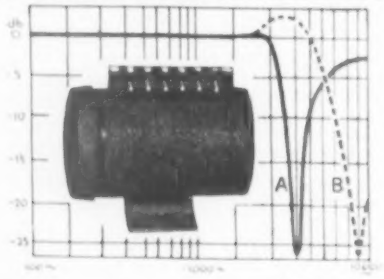

TYPICAL RESPONSE CURVES

A
B

WHERE SURFACE NOISE IS THE LIMITING FACTOR TO SUPREME QUALITY OF REPRODUCTION, fit a Sound Sales alloy cored steep trough tuneable filter. We know the problem of removing Surface Noise or Heterodyne whistle is not easy to solve, but the steep trough filter has so far produced the most encouraging results we have encountered when using a compact component which can be incorporated in existing apparatus.

CHOKE TYPE C.SF. Dia. 2½", length 3½" **PRICE £1.8.9** each

Obtainable directly from Sound Sales Ltd., appointed Agents and the best Resellers

SOUND SALES LIMITED

MANUFACTURERS OF ELECTRONIC PRODUCTS SINCE 1931

Showrooms & Offices—

125, OXFORD STREET, LONDON, W.1

GERrard 8782

Works: **West Street, Farnham, Surrey** Tel: Farnham 6461/2/3

Contractors to the Admiralty, Air Ministry, Ministry of Supply G.P.O., B.B.C., etc. On A.I.D. List

PLAN YOUR CAREER

RADIO - TELEVISION and other INDUSTRIAL ELECTRONIC subjects

ELEMENTARY & ADVANCED COURSES

DAYTIME

- Principles and Practice of Radio—1 year.
- Telecommunication Engineering—2 years.
- Electronic Engineering—3 years (*including one year's practical training in E.M.I. Factories*)—leading to C. & G. full Technological Certificate.
- Marine and Air Radio Officers' Course (*for P.M.G. Licence*).

also **HOME STUDY**

- Radio
- Television
- Industrial Electronics
- Maths.
- Physics.

Write for FREE BOOKLET to Dept. 16

E.M.I. INSTITUTES

10 PEMBRIDGE SQUARE, NOTTING HILL GATE, LONDON, W.2
Telephone: BAYswater 5131/2

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.

E.1008

THE THREE 'R's

3", 3½", 6" RECTANGULAR INSTRUMENTS *by* PULLIN

Series 30

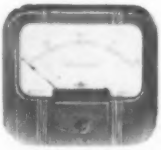

Series 35

These three rectangular instruments are designed on symmetrical lines, thus giving a distinctive clear open scale and pleasing appearance. Each size available in all standard ranges. The Series 65 and 35 can be fitted with dial illumination.

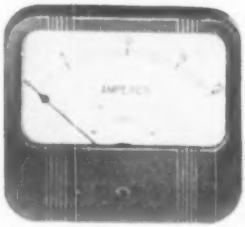

Series 65

MIP

MEASURING INSTRUMENTS (PULLIN) LTD.

Electrin Works, Winchester Street, Acton, London, W.3.
Telephone ACOrn 4651/3 & 4991

Manufacturers' Products

New Equipment and Accessories for Radio and Electronics

Neon Indicators

A RANGE of miniature neon indicator tubes is now available from the General Electric Company, Magnet House, Kingsway, London, W.C.2. They are designed for use on 200-250 V mains supplies, when connected in series with a 0.25 to 0.5 MΩ resistor (1 watt).

Current consumption and other details are given below:—

Type	Supply	mA	Cap	Price
[illegible]	[illegible]	[illegible]	[illegible]	[illegible]
C	[illegible]	0.5	[illegible] Edison screw	[illegible]
G	[illegible]	0.35	Miniature bayonet, centre contact	[illegible]
"Jewel"	[illegible]	0.5	[illegible] Edison screw	[illegible]

Radio-Television Console

IN the new Model TRC124 "Electrovision" console (Model TRC1124 for the Midlands), a pre-set radio receiver giving three alternative stations on medium waves and one on long, is combined with an 18-valve television circuit operating a 12in c.r. tube (picture size 10in × 8in). Basically the design of the television receiver follows that of the TSC102. Focus is fixed with an auxiliary pre-set adjustment for mains voltage fluctuation, the operating controls are "Brightness" and "Contrast." Interference suppression circuits are provided for both vision and sound channels.

The radio receiver comprises three valves, a frequency changer (UCH42), i.f. amplifier and detector (UAF42) and output (UBC41). Station selection is by rotary switch and illuminated indicator panels show the name of the station being received.

Made by E. K. Cole, Southend-on-Sea, Essex, the Model TRC124 costs £75 12s including tax.

New Auto-Radiogram

AN interesting feature of the six-valve superhet circuit of the Model ARG23AF radio-gramophone, made by the Marconiphone Company, Hayes, Middlesex, is the employment of an earthed-grid triode in the signal-frequency amplifying stage.

On the gramophone side the latest lightweight type pickup is used in conjunction with a new record-changer mechanism handling ten 10in or 12in records, unmixed. A two-position switch gives normal or extended frequency range to suit all types and conditions of record.

The "double-console" type cabinet includes a compartment for record storage, and both the radio tuning panel and record changer compartment are provided with doors. A 10in permanent-magnet loudspeaker is fitted and the rated power output of the amplifier is 5 watts.

Dimensions are 38in × 35½in × 17½in and the price is £108 7s 3d including tax.

New Television Valves

THE range of Mullard valves for use in television equipment has recently been extended to include two new types on the "Noval" (9-pin) base. These valves are a triode-pentode (ECL80) and an r.f. pentode (EF80). Both offer special advantages in the design of television equipment.

The EF80 is characterized by a particularly high slope and is primarily intended for use as an r.f. amplifier, or mixer valve, in television receivers. Its general performance corresponds with that given by the Mullard high-slope pentodes EF50, EF42 and EF91. It has the distinct advantage over these valves, however, in that it can be operated with an h.t. voltage of 170 only as against the usual 250 volts. This makes the EF80 a particularly useful valve for the transformer-less type of television receivers.

Having separate triode and pentode sections, the ECL80 has a wide number of uses. It enables sets to be designed with the fewest number of valves and thus reduces the size of the equipment. Three straightforward ways of using this valve in television receivers are as follows:—(a) pentode section as synchronizing pulse separator, triode section as line oscillator; (b) triode section as frame oscillator, pentode section as frame output; (c) triode section as a.f. amplifier, pentode as audio output valve.

The makers are Mullard Electronic Products, Ltd., Century House, Shaftesbury Avenue, London, W.C.2.

Dielectric Heating Oven

A NEW 5-kW r.f. heating oven for thick plastic pellets and rubber preforms has been introduced by the General Electric Company, Magnet House, Kingsway, London, W.C.2. The salient feature of the design is the large area of the electrodes (24in × 18in) and the continuously variable spacing (up to 6in) which can be adjusted while the set is in operation. The lower earthed electrode slides out on a drawer for ease of loading.

A pre-set matching inductance

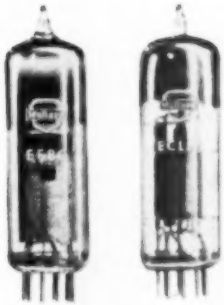

Mullard Noval-base (9-pin) valves, EF80 and ECL80 high-slope pentode and triode-pentode respectively for use in a.c./d.c. television receivers.

The earthed electrode in the G.E.C. 5-kW dielectric heating oven pulls forward for ease of loading.

gives wide latitude in adjusting the coupling to the electrical characteristics of the work.

Sound Amplifying Equipment

SEVERAL additions have been made recently to the range of sound amplifying equipment made by Ardente Acoustic Laboratories, Compton, nr. Guildford, Surrey, and many well established products have been redesigned.

Of chief interest among new products are the Type 360 and 660 amplifiers for a.c. mains. These have outputs of 30 and 60 watts respectively for distortion levels of less than 2%. In both types a low-noise, high-gain input stage (EF37) is followed by a double triode (ECC33) in which one section is used as a phase-splitter to feed the push-pull output stage (two EL37s). In the Type 360 a single GZ32 rectifier supplies h.t. and bias is automatic; in the Type 660 there are two GZ32 rectifiers and a separate selenium rectifier supplies fixed bias. A relay is fitted for h.t. switching, and a guard circuit prevents the application of h.t. until the output plug is connected. The frequency response is 3 db down at 30 and 10,000 c/s and 3 db down at 20,000 c/s. Bass and treble cut controls are included.

The amplifiers are available in cabinet and rack-mounted form, and suitable radio tuners and mixer units can be provided. Prices are £36 and £45 for the rack types and £45 and £58 for the cabinet models.

Other recent additions to the Ardente range include the new "Black Prince" moving-coil microphone, the redesigned Type PMB6 labyrinth loudspeaker, Types PMDC, PMCH and PMDW diffusion loudspeaker units and the Type PMDH marine loudspeaker in corrosion resistant silicon aluminium alloy.

Versatile V.H.F. Transmitter

DESIGNED originally to meet certain local requirements at airports, the PT10 transmitter has a wide field of application as a fixed station transmitter for a short-range v.h.f. radio telephone service.

Rated at 12 watts output the equipment consists of separate r.f. and modulator units, which can be assembled for either rack or desk mounting and can be combined with a receiver to form a complete radio telephone installation.

For airport use the coverage is 118 to 132 Mc/s and operation is on a single spot frequency in this band, the desired channel being selected merely by plugging in an appropriate crystal and making a few minor tuning adjustments.

Operation of the equipment has been simplified considerably by the use of wide-band inter-valve couplings wherever possible so that tuning adjustments are reduced to a minimum, while pre-set circuits in the audio part of the transmitter check any tendency to overmodulation. Grid, anode and cathode current metres are included for routine servicing and for tuning whenever a new channel is required.

The whole equipment is very compact and economical to operate; the supply required is 230 volts, 50 c/s. It is made by The Plessey Co., Vicarage Lane, Ilford, Essex.

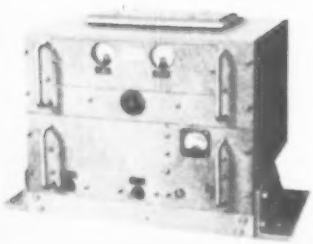

Plessey 12-watt v.h.f. radio telephone Type PT10, assembled for desk mounting

Miniature Relays

RELAYS play an important part in all kinds of radio and sound amplifying equipment, but for economic reasons and the fact that remote control is not often needed, they are rarely found in broadcast sets. "Business radio" and the many kinds of mobile v.h.f. radio-telephones rely to a great extent on relays for their operation, and the latest miniature types produced by Engel and Gibbs, 98A-5, Finchley Road, Golders Green, London, N.W.11, should find applications for these purposes.

The normal patterns measure 1 5/8in high; the base is 3/4in × 1 5/8in and the weight is 1.4 oz only. There is an hermetically sealed model with the same base dimensions, but 1 1/2in high, and this weighs 1.6 oz. Normal operating power is 1 watt at d.c. voltages up to 50. If higher voltages have to be used, a series resistor must be included. A.C. models are not available, but a simple rectifying circuit will supply the low current needed.

The relay contacts are mounted on a ceramic block and, while designed for relatively low d.c. voltages, they will handle up to 500 mA at 240 V a.c. On d.c., an external quenching circuit is needed for control of voltages in excess of 50.

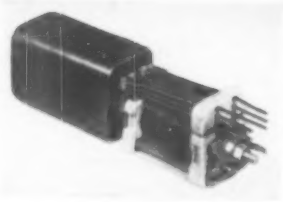

Midget relay suitable for use in mobile and business radio-telephones, made by Engel and Gibbs.

Apart from loading considerations, the relay is eminently suitable for a.f. and r.f. circuit control, aerial switching from send to receive in low-power sets being one such application. The normal contact arrangement is double-pole change-over. Contacts are of either pure silver or palladium-silver mounted on nickel-silver or beryllium-silver blades as required, and each blade has two contact tongues accurately aligned.

Hospital Radio

A VERSATILE new radio equipment (Type E1011) for hospitals has been introduced by the Amplifier Department of Philips Electrical, Century House, Shaftesbury Avenue, London, W.C.2.

It consists of a compact enamelled metal ensemble in which a radio tuner for short, medium and long waves is mounted above a ventilated amplifier compartment which can be fitted with an interchangeable amplifier, of 15, 25, 50 or 100 watts output. A pilot loudspeaker is provided for tuning, and input terminals are available for gramophone and microphone inputs.

Audio Signal Generator

OPERATING from either a.c. or d.c. mains (200-250 V) the type T71 audio signal generator made by Pennine Amplifiers, 9-11, Southgate, Elland, Yorks, covers 50 to 10,000 c/s in two ranges. Maximum power output is 3 watts and alternative output impedances of 2.5 and 3,000 ohms are provided with an output voltage control calibrated for each impedance.

The instrument weighs 6½ lb, measures only 7in × 5½in × 4in, and should be useful to the serviceman for checking loudspeaker response, etc. The price is £9 9s.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

European Television Standards

WE may assume that any medium-definition European television standard, whether 405, 455, 525, 567 or 625 lines, will be temporary. The future lies in high-definition black-and-white or else in colour. Therefore, for this impoverished continent, I suggest we should start with the cheapest practicable system that will allow the mass market to be reached, and will make the best use of the metre-band wavelengths. I cannot understand the present advocacy of 625 lines for Europe.

Taking into account present possibilities and future probabilities, it is not difficult to find the right course. It is to standardize on 405 lines with the full theoretical bandwidth of 3 Mc/s. Alternatively, as a compromise, we could use 525 lines with a reduced bandwidth of 3 Mc/s.

When we become richer we can think of high definition or of colour.

C. L. ZAALBERG.

Overschie, Holland.

"Wireless World" Television Receiver

HAVING built the *W.W.* long range television receiver, I feel that my experiences might be of interest to readers in the fringe area who might be contemplating building, yet doubtful of the possibilities.

From my address you will see I am at extreme range, but in spite of this am receiving strong and steady signals.

The very slight fading that takes place is only noticeable on the sound channel, the vision remaining steady with the gain control well down.

I would mention that I have fitted separate gain controls to sound and vision receivers, having found individual control to be an advantage.

The performance is definitely at full entertainment value and the picture remains rock steady.

W. FORD

Blackburn, Lancs.

Spot Wobble

I READ with much interest the article by R. W. Hallows on spot wobble in your March issue.

The process was first brought to the notice of engineers in this country by the writer in *Wireless World* of September 4th, 1936—by the courtesy of Ferranti, Ltd.—when it was used as a method of overcoming the discrepancy in line width between the two systems of 405 lines and 240 lines when using a cathode-ray tube receiver.

It was originally the subject-matter of a patent application in 1935, which was not granted because of the prior patent of the French Compagnie des Compteurs.

There is one point I would like to stress, not only is the appearance of the picture improved without losing any definition, but the screen of the picture tube is used efficiently. By having luminescence in parts normally not excited the light output is increased.

In the current article there is mention of the use of the device in colour television. When the writer was associated with the late John L. Baird, frequent use was made of spot wobble in both colour transmitters and receivers with great advantage. The same was experienced in stereoscopic television, though to a lesser degree.

In conclusion, as the tendency seems to be towards 15 or 16in picture tubes using a very fine spot produced with accelerating potentials of 11 to 13 kV, the use of spot wobble in a receiver of this type is rapidly becoming an absolute "must."

E. G. O. ANDERSON

Television, Ltd.,
London, S.W.1.

Dark Television Screens

FROM his letter in your March issue it appears that Mr. Humphreys is either unaware that certain American cathode-ray tubes for direct viewing feature a darkened filter glass face plate, or he is hinting to tube manufacturers that there is a sound principle involved in this method of improving picture contrast.

I am not at all sure, however, that the "dark" face plate is the most satisfactory method. The highlight brightness obtainable with "daylight" aluminized tubes operated at high accelerating potentials is recognized as being more than adequate at night in a room where the normal amount of ambient illumination is provided. Such tubes provide a contrast improvement compared with non-aluminized types by eliminating reflections

Portable Model B 65 (open)

Can you provide a public address system at a moment's notice? With a B65 it is simple—just place the equipment in a suitable position and switch on. Incorporated within an easily portable case are the amplifier complete with loudspeaker, rotary transformer, 6-volt unspillable accumulator and microphone with cable. Power output is approximately 5 watts. The equipment is a most useful outfit for political meetings, religious gatherings, auctioneers, etc., and numerous other applications where no electric supply mains are available.

Price complete **£29 10 0**

An external speaker can be attached if desired.

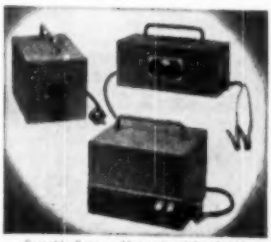

Portable Battery Mains Amplifier B 619

Operates on 12-volt battery or, by means of separate plug-in adaptor unit, on A.C. mains. Power output approximately 15 watts.

Full details of these models and others in the large Trix range of equipment available on request.

Send for latest catalogues and price list.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place, Tottenham Court Road, London, W.1. 'Phone: Museum 5817
Grams & Cables: "Trixadio, Wesdo, London."

AMPLIFIERS · MICROPHONES · LOUDSPEAKERS

within the tube (also the ion burn menace is warded off without resort to ion-traps or devices which might cause spot distortion).

The prime consideration for comfortable viewing becomes a matter of further improving the contrast in the presence of ambient illumination, which illumination, ideally, should be of the same order as that of the average picture brightness. A proposed method is to place a thin neutral-grey coloured, or "Polaroid" absorbing screen in front of the tube, preferably tilted or curved in order to avoid direct reflections from light sources in the room into the eye of the observer. An increase in contrast from 7:1 to about 30:1, equal to cinema film standard, is theoretically possible, on the assumption that there are no reflections either between the back of the filter and the front of the tube, or between the front and back surfaces of the tube face plate.

It may well be that the convenience of being able to change the filter according to the illumination outweighs the apparent additional advantage of the "dark-faced" tube in minimizing the remaining reflections. The rather paradoxical procedure of increasing accelerating voltage and scanning power, and then of reducing the maximum brightness with filters is, nevertheless, one which can yield a picture of the highest definition under viewing conditions which are the most pleasing.

G. A. PHILLIPS DALES.
Johannesburg, South Africa.

FURTHER to Alan Humphreys' letter in your March issue, I would like to point out that a projection television screen can have quite an advantage over a direct viewing tube when being viewed with light falling on the screen.

Obviously, with a direct viewing tube the black portions of the picture are nowhere near black if any light falls on the front of the screen, the "blacks" being a white screen which reflects a considerable amount of light.

With a projection system, the major portion of the extraneous light that falls on the screen is transmitted and not reflected, hence the black parts of the picture still remain black even with a considerable amount of stray light in front of the receiver.

In addition to this, the projection screen has the advantage of not reflecting any images of objects in front of the receiver as the screen face is not polished but has a matt finish.

If a projection type receiver is placed alongside a normal direct viewing receiver and both are adjusted in darkness, as soon as the light is switched on this effect is noticed considerably, the direct-viewing tube being well shown in contrast compared with the projection screen.

E. O. FRISK.
Optical Works Ltd.,
London, W.5.

Broadcast Volume Levels

"CATHODE Ray" (your December issue) evidently considers that the B.B.C. is sweetly reasonable in its technical handling of the relative volume levels of speech and music, and infers that critics of the official policy are, to a man, anti-social owners of commercial receivers manufactured before 1933. He classes complainants with the classic old lady who wanted the B.B.C. Dance Orchestra to play louder when her H.T. battery was running down. The old (and surely, dying) hobby horse is trotted out; "boom" in old receivers reduces the intelligibility of speech, volume being manually increased as an arbitrary compensation.

This does, of course, occur, but the complaint is more widespread than this, and cannot be brushed at the door of bass resonance. The controversy thrusts itself upon every citizen throughout the summer, and the B.B.C., by its appeals for "hush" on hot evenings tacitly admits that the position is serious.

The issue is simple: speech broadcasts are *not loud enough*.

The solution is equally simple. Let the B.B.C. instruct the engineers to increase the modulation level of speech. It is a procedure that should be acceptable to technician and aesthete; the volume compression system would require no modification, and music lovers who enjoy their forte *fortissimo* would be in no wise discomfited.

Surely such a palpable panacea could be granted a trial!

Yours faithfully,
JOHN and GLADYS HART.
Weybridge, Surrey.

Terminal Terminology

"FREE GRID'S" so-called "obvious" nomenclature is an unfortunate example of hopeless bringing. If the cell which he mentions is supplying power to his radio set, its negative terminal will be its anode. When the same cell is being recharged, its negative terminal will then be its cathode.

The explanation is that the terms anode and cathode are used to indicate the "in" and "out" terminals when we wish to draw attention to the direction of flow of current, while positive and negative are concerned with potential difference.

If "Free Grid" will examine the circuit of a valve rectifier he must surely agree that the cathode of the valve is the positive terminal, so far as the output connections are concerned. The cathode of a metal rectifier is always marked + rather than cathode to minimize confusion.

The more frequent association of + with anode and − with cathode arises from the fact that there are most devices absorbing power than there are producing it.

T. C. NUTTALL.
London, S.E.19.

Curious Effect

I VIEW on a television receiver built principally to *Wireless World* design. By accident, it was noticed that, after being switched off completely for about five minutes, the screen flashed.

I then watched carefully after each period of viewing. The flashes, as many as three in succession at times, appear in the bottom right-hand corner. The first one appears about five minutes after switching off, and the others follow at two-minute intervals.

The flashes always occur at the same place on the screen, all circuits are quite cold, and there was no fire in the room.

Is the flash due to energy released in the screen phosphor, and if so, could any of your readers suggest why it appears only in the bottom right-hand corner, and whether these flashes also occur during screen entertainment in the course of a programme?

ALAN E. DAVIDSON.
London, S.E.3.

Valve Types

THE statement of your correspondent, Mr. H. D. Bradshaw, that "the valve position in this country has always been notable for its confusion" is probably an all-time record in under-statement.

Besides the 4-, 5-, 7-, 9- and what-have-you pin bases, there are valves with octal bases and octal valve characteristics which bear non-octal designations, not forgetting the cunning types with bases which have all the appearance of being octal, but are not.

To further befuddle the crazy puzzle, each maker adopts his own system of designations, the meaning of which is an incomprehensible mystery, so that tables of "equivalents" are necessary to lend succour to the courageous adventurer who

would penetrate this bewildering maze.

If your correspondent hopes to see a change from this hotchpotch which has been tolerated for years by those who are oblivious of the fact that it is excluding them from many world markets, he must indeed be sanguine.

G. P. H. de FREVILLE
London, S.W.7.

"Q" Priority

YOUR contributor "P. H." says, on page 216 of *Wireless World* for June, 1949, that the article on "Q" Meters by H. G. M. Spratt in the January, 1949, issue was, to his knowledge, "the first account of this nature to be published in any English-speaking technical journal."

May I refute that statement? I myself published a comprehensive article on the "Q" Meter and its theory, including the corrections required, etc., in the *Proceedings of the Institute of Radio Engineers*, New York, as long ago as 1942. A reference to that paper is given in your own publication, "Radio Data Charts."

V. V. L. RAO
Madras, India.

MANUFACTURERS' LITERATURE

LEAFLET describing stabilised power supply unit Type SP11, giving five stabilised outputs from 200-250V a.c. input, from A. E. Cawkell, 2, Victory Arcade, The Broadway, Southall, Middx.

List of transmitting and industrial valves, neon indicators, batteries, etc. Also cards showing (a) valve equivalents, and (b) and (c) Mazda valve and c.r. tube complements for London and Midlands television receivers of many makes, from Edison Swan Electric Co., 155, Charing Cross Road, London, W.C.2.

Technical Bulletin No. 55, describing an automatic telegraph distortion monitor for use on a unit code systems from Airmec Laboratories, Ltd., High Wycombe, Bucks.

Leaflet on E.M.I. "Flexible Dipole" indoor television aerial from E.M.I. Sales and Service, Ltd., Hayes, Middlesex.

Folder on the "Cruiser 96" navigational receiver for yachts and small craft, which provides for reception of Consol signals and normal direction finding beacons, from Industrial Radio Co., 16, Devereux Road, Southend, Essex.

Leaflet describing the "Hydraclamp" hydraulically operated vice with universal joint, and adaptors for holding receiver chassis, etc., from Spencer Franklin, Ltd., 202, High Holborn, London, W.C.1.

BULGIN

REGISTERED TRADE MARK

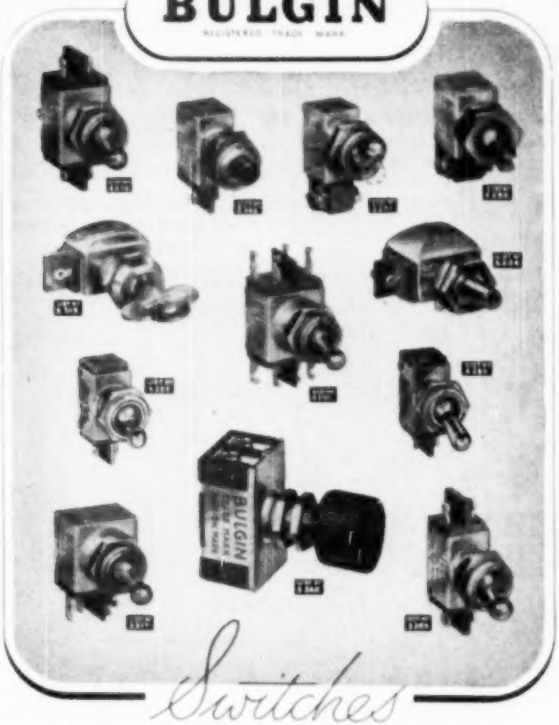

Switches

● ***OVER 200 TYPES DESIGNED***

The Famous BULGIN Range offers over 200 *Basic* types of switches, and every one in a variety of operating-levers (dollies) and finishes. Apart from Nickel-plate, Chromium-plate, Camera-black, Florentine-bronze, Polished or Matt, there are five or more plastics-coloured finishes, giving insulation of external metal parts. Combinations of every type are available, and every one guaranteed as type-tested for 25,000 operations. Better than all others, every switch embodies the EXPERIENCE OF 25 YEARS OF SWITCH DESIGN AND MANUFACTURE.

WRITE for illustrated catalogue, price 1/-, post free.

All products are now available from retail and wholesale stockists.

"The Choice of Critics"

BULGIN

A. F. BULGIN & CO. LTD.
BYE-PASS ROAD, BARKING
Telephone: RIPpleway 3474 (5 lines)

RANDOM RADIATIONS

By "DIALLIST"

Fluorescent Lamps on D.C.

A READER who has had a good deal of experience of fluorescent lamps running on d.c. has been kind enough to send me some interesting facts about their proneness to cause interference with radio and television reception. I gather that he has found interference as common on d.c. circuits as on a.c., and just as severe. The symptoms, too, are the same: the interference producing lamp develops a bright spot on one heater. I wonder whether other readers who have run these lamps on d.c. have had similar experiences? I ask because I don't feel sure that the misbehaviour described by this correspondent isn't at any rate partly due to the fact that his mains supply is very "rough," having, as he puts it, a ripple sufficient to give a reading on the a.c. range of an AVO. Has any reader found that fluorescent tubes fed by well-smoothed d.c. cause interference? If so, it seems that there may well be something in the idea that the bright spot represents a small semi-detached flake of the surface material of the heater vibrating under electron bombardment.

Television's New Look

THOUGH I'VE ALWAYS liked our 5/4 aspect ratio and still feel that it gives an image of more pleasing shape, I'm glad that the B.B.C. has decided to change over to the 4/3 ratio used in other countries. The main reason, of course, is that the 5/4 form factor doesn't fit in with standard sound track films. That's a very important consideration, for such films are bound to play an increasingly important part in the news broadcasts. For example, with the advances in making and transmitting films that are continually taking place, I can see no technical reasons why, say, next year's Grand National should not be seen on television screens that same evening. Another reason why the change is to the good is that it is one step nearer to general standardisation. On this side of the Atlantic we've now got (1) 50 frames per second interlaced and (2) the 4/3 aspect ratio accepted by everyone. The remaining trio—the number of scanning lines—is, of course, by far the most difficult. Still, it's something to have reached agreement on two points out of three.

No Great Difficulty

The majority of viewers, I take it, simply tuned up the circle on the test pattern and left it at that, making the image extend to the full height of the mask and not minding the small amount of width now sliced off by the vertical edges of the mask. Treated in this way, an image on a 12-inch tube that was previously 10×8 inches now becomes 10¼×8in., but ¼ inch is lost at either edge. Alternatively, the width may be left at 10 inches and the height reduced to 7½in. in which case there is a ½in gap at top and bottom. The handyman will probably worry off a third of an inch from each vertical edge of the mask and so obtain the full height of a larger image—85¼ square inches against the original 80.

The New Radio Channels

ON THE MEDIUM WAVES the new broadcasting channels seem, so far, to have given results that are about as satisfactory as could be expected in the circumstances. Unfortunately, a number of countries haven't signed the new agreement; and some of those that promised to come into line haven't, at the time of writing, entirely fitted themselves into their new channels. One unexpected complication has been caused by the surprising decision of our good and usually so reasonable friends, the Americans, to use many channels that were not allotted to them for their zoned Western Germany. That sort of thing will no doubt right itself in time, but I'm afraid that broadcasting conditions in Europe will never be as they should be until we have a European body armed with powers similar to those of the U.S. Federal Communications Commission.

Try it and See

THE EDITORIAL SUGGESTION in last month's W.W. that metre wave competitive broadcasts should be tried out from the Wrotham station very much appeals to me. The only sure and certain way of discovering whether competitive broadcasting can provide more acceptable entertainment than the monopolistic brand is to give it a reasonable trial. And there could be no better way of trying it out than by adopting a system which gives it full play and at the same time allows the B.B.C. to continue its own broadcasts without interruption. There's another point too. So far as I can see, if competitive broadcasting has a future in this country, that future is likely to lie on the metre waves. The reason is that the small number of our medium- and long-wave channels is hardly suited to competitive broadcasting on a national scale, and local or semi-local broadcasting of that kind would not be likely to furnish what is needed.

Pros and Cons

The most that could be done in a national way on the medium and long waves would be to use the channels now assigned to the Home, Light and Third Programmes to form three competing chains. It is doubtful whether competitive broadcasting could achieve its object unless it provided every listener with a wider choice of programmes than that. There is likely to be less congestion on the metre waves, which would give competitive broadcasting, if it comes here, a better chance of spreading itself and of showing what it can do.

How Do You Feel?

Have you ever found yourself so exasperated by the B.B.C.'s fare that you simply had to sit down and write to them about it? If so, I'm open to wager that your irritation was increased when, at length, a smug, complacent, "mother-knows-best" reply reached you. Those who have received an answer of the kind I'm thinking of must have felt that a spot of competition might do the programme side of the B.B.C. a power of good!

"Club-Model" Radio-Gramophone

FOR the overseas market G.E.C. have introduced a large automatic radio-gramophone for hotels, small dance halls, etc. The specification includes a 30-watt amplifier and alternative radio receivers can be specified. If required a 60-watt amplifier can be supplied, and there is provision for a moving-coil microphone for announcements.

CRAFTSMANSHIP

"I can most certainly say at this stage that the workmanship and finish are of a quality which I have never before encountered in the radio industry, despite the fact that my association with the industry in one capacity or another extends back over 27 years. I think you are to be congratulated all the more on this achievement in view of the increasing tendency nowadays towards inferior workmanship and design."

Part of a letter from a purchaser who is a very well-known engineer and whose identity is known to the Editor of "Wireless World."

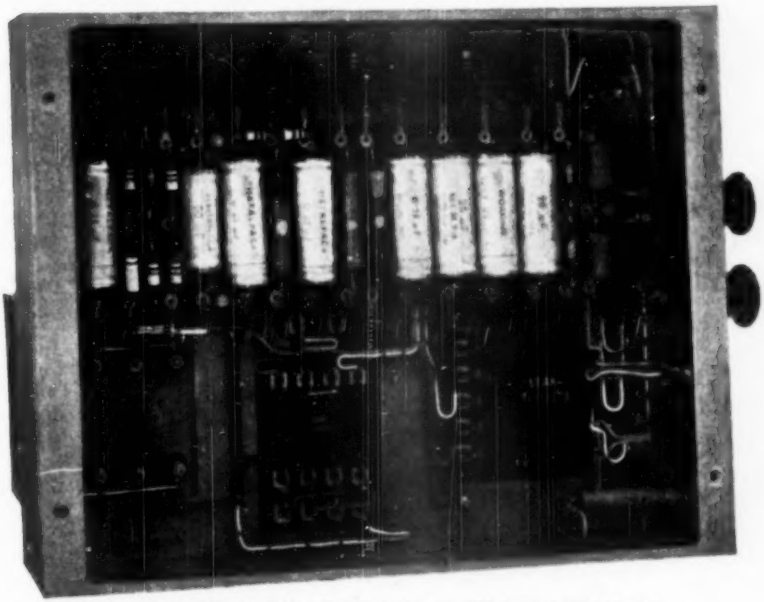

UNDER CHASSIS VIEW OF THE TL 12 POWER AMPLIFIER

LEAK equipment is built to laboratory standards in materials and workmanship by experienced men.

TL/12 TRIPLE LOOP FEEDBACK AMPLIFIER *Price* **£25.15.0** RC PA REMOTE CONTROL PRE-AMPLIFIER *Price* **£6.15.0**

The high standard of workmanship of the TL/12 amplifier is apparent on inspection. Our claimed performance figures are substantiated by a NATIONAL PHYSICAL LABORATORY REPORT on tests they have made of the TL/12. We are the only amplifier manufacturers who publish such a report.

These amplifiers are the choice of many distinguished audio engineers for high quality reproduction in their own homes.

APPLY TO YOUR LOCAL DEALER FOR FREE 16-PAGE ILLUSTRATED BOOKLET W/TL/12 OR WRITE TO US.

H. J. LEAK & CO. LTD. (Est. 1934)

BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3.

Phone: SHEpherds Bush 1173/4. Telegrams: Sinusoidal, Ealux, London. Foreign: Sinusoidal, London.

D. COHEN

RADIO & TELEVISION COMPONENTS

MAINS TRANSFORMERS

Universal. Replacement. Type. Primary 200/250 v., 280-280 v. 60 mA. 6 v. tapped 4 v. 2 amp. 5 v. tapped 4 v. 2 amp., 6 v. 0.3 amp. **10/6**, plus 1/- post and packing.

350-350 v. 130 mA., 6 v. 3 amp., 5 v. 3 amp. Primary 200/250 v. **18/6**, plus 1/- post and packing. Heater transformer 6 v. 1½ amp. Primary 230/250 volts. **6/-** plus 9d. post and packing.

Standard output transformer 5000 ohm imp. **3/3**, plus 6d. P. & P.

Midget O.P. transformer. 5000 ohm imp. **2/9**, plus 6d. P. & P.

Smoothing choke. 10 Henry 80 mA. **3/9**, plus 6d. P. & P.

Smoothing choke. Midget 40 mA. **1/11**, plus 3d. P. & P.

Line matching transformer. Pri. imp. 500 ohms. Sec. 15 ohms. **10/-**.

Mains Transformer—primary 110-250 v. secondary 350-0-350 v. 250 ma. 6 v. 4 amp. 4 v. 3 amp. quarter inch gap between laminations and bobbin, extra heaters could be easily wound. **£2/2/-**, plus 2/- post and packing.

Semi-shrouded drop through type primary 200-240 v. secondary 350-0-350 v. 80 ma. 6 v. 3 amp. 5 v. 2 amp. **15/-** plus 1/6 post and packing.

Heater Transformer. 2.4 or 3 v. 2 amps. primary 230-250 v. **7/6** plus 1/- post and packing.

Car Radio Vibrator Transformer. 6 or 12 v., **6/-**, plus 1/- post and packing.

Auto Transformer. 110-250 v. input. 70 v. 0.2 amps. and tapping for dial lamp. **5/-**, plus 1/- post and packing. Small dimensions.

ELECTROLYTIC CONDENSERS

2 mfd. 250 work. **9d.**
50 mfd. 50 work. **1/9**
16+24 mfd. 350 work. **2/11**
100 mfd. 12 v. work. **1/3**.
16+16 mfd. 450 work. **3/6**.
50 mfd. 12 v. work. **1/-**.
25 mfd. 25 v. work. **1/-**.
8 x 32 mfd. 450 work. **4/-**.
16 x 8 mfd. 450 work. **3/9**.
8 mfd. 450 v. work. **1/11**.
500 mfd. 6 v. work. **1/3**.
250 mfd. 12 v. work. **1/3**.
16 x 32 mfd. 450 v. work. **4/6**.
8 mfd. 500 v. BR 850. **2/6**.
16 mfd. 500 v. BR 1650. **3/6**.
8 x 8 mfd. 450 work. **3/3**.
30 x 30 mfd. 150 work. **3/9**.

P.M. SPEAKERS

Size	with trans.	less trans.
5in.	12/6	
6½in.	12/6	8/9
8in.	14/1	11/9
10in.	17/6	14/6

Post and packing on above items 1/- each extra.

THE HEART OF THE BURGOYNE SEVEN SECOND SOLDERING GUN. As illustrated 200/250 v. input. **13/6** plus 1/6 post and packing. Copper bit, **6d.**; automatic switch assembly, 1/-, plus 6d. post and packing.

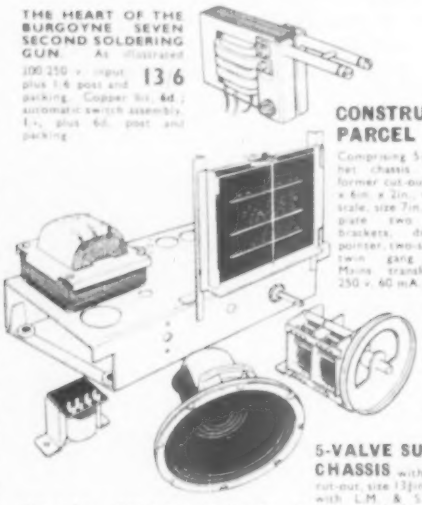

CONSTRUCTOR'S PARCEL as illustrated. Comprising 5-valve superhet chassis with transformer cut-out, size 13½in. x 6in. x 2in., with L.M.&S. scale, size 7in. x 5in. Back plate, two supporting brackets, drive drum, pointer, two-speed spindle, twin gang condenser. Mains transformer 250-250 v. 60 mA. 6 v. 3 amp. 4 v. 2 amp. and 6½in. ROLA energised speaker with O.P. transformer. Complete **27/-** Plus 2/- post and packing.

5-VALVE SUPERHET CHASSIS with transformer cut-out, size 13½in. x 6in. x 2in. with L.M. & S. scale, size 7in. x 5in. Two supporting brackets, drive drum, pointer and three pulley wheels. Complete **66/-** Plus 1/6 post and packing.

6-STATION SWITCHED SUPERHET COIL UNIT, by famous manufacturer. Ideal for Car Radio or radio set. Range coverage Pos. 1, 200-300 m.; 2, 250-360 m.; 3, 250-360 m.; 4, 320-460 m.; 5, 400-550 m.; 6, 1100-1850 m.; no oscillator required for lining up, complete with Circuit. **15/6**, post and packing 1/-.

PRE-ALIGNED MIDGET 465 Kc. MIDGET IFs, made for the above Coil Unit. **8/6** post and packing 6d.

CHASSIS TO FIT COIL UNITS AND IFs, size 11½in. x 5½in. x 1½in. **2/6**.

MAINS TRANS. TO FIT ABOVE CHASSIS. Pri. 200/250 volt. Sec. 250-0-250 v. 60 mA. 6 v. 4 amp. **13/6**, post and packing 1/-.

CONSTRUCTOR'S PARCEL, comprising chassis 10½in. x 5½in. x 2in. with speaker and valve holder cut-outs, ROLA 5in. P.M. with O.P. trans. twin gang with trimmers, pair of TRF coils, 4 International Octal valve holders wave change switch and Erie 20k pot with switch. **17/6**, plus 1/6 post and packing.

SUPERHET COIL KIT, comprising medium and short wave coils, twin gang, pair of 465 IFs, 6 pole 3 way switch, 6 trimmers, two trackers and 5-valve superhet chassis with IF and speaker cut-outs. **14/6**, plus 1/- post and packing.

BUTTON NEON INDICATOR. s.w. brass batten holder 230 v. **1/-** plus 6d. post and packing.

STANDARD 465 KC. I.F.'s. Aerialoid Q 110. **6/-** per pair.

STANDARD 465 KC. I.F.'s. Iron cored Q 120. **7/-** per pair.

MINIATURE 465 KC. I.F.'s. Type M4008. **12/6**, plus 6d. post and packing.

CERAMIC 220 pf. tolerance 10%. **£4** per thousand.

VALVE HOLDERS. Paxolin International octal. **4d.** each. Moulded insert octal. **6d.** each. EF50 ceramic **7d.** each. Moulded B7G slightly soiled **6d.** each.

LINE CORD. 3-way 0.3 amp. 180 ohm per yard. **10d.** per yard.

ENERGISED SPEAKERS

ROLA 6½in. 700 ohm field with O.P. trans. 5000 ohm imp. **11/6**. Less trans. **9/6**.

8in. 2000 ohm field with O.P. trans. 5000 ohm imp. **15/6**. Plus 1/- post and packing.

5in. Mains energised 1,000 ohms field with O.P. trans. 5,000 ohm imp. **12/6**, plus 1/- post and packing.

TUNING CONDENSERS

.0005 twin gang with feet. **4/-**.
.0005 twin gang, fitted feet, trimmers and drum. **4/7**.
Midget .00037 twin gang, fitted trimmers and Pe spex dust cover. **6/6**.
.0005 tuning condenser. **2/3**.
Post on the above items 6d. extra.

POLISHED WALNUT RADIO CABINET

15in. high, 17in. long, 10in. deep, c.w. L.M. & S. dial. Size 9½in. long x 4½in. wide, and 5 valve superhet chassis. Valve holder and transformer cut-outs. **27/6**, plus 2/- post and packing.

MAINS DROPPERS

2 amp. 1000 ohms tapped 900 ohms. **1/9**, post 3d.
2 amp. 717 ohms tapped 100 ohms. **1/6** post 3d.
3 amp. 490 ohms tapped **2/6** ea.

WAVE CHANGE SWITCHES

6 pole 3 way. **1/2**
3 pole 2 way. **1/2**
6 pole 2 way. **1/2**
5 pole 3 way. **1/2**

WHITE KNOBS

12-sided. 1½in. dia., ¾in. deep. **5d.** each.

BROWN KNOBS

1½in. dia. **4d.** each.

BLACK KNOBS

Serrated edge, brass bushed, quarter inch spindle. **£4** per thousand.

VARIABLE TRACKERS

300 x 300, 100 x 500, 100 x 220, 500 x 750, 2100, 150 x 150, 1000 x 1000, 250 x 250. Ceramic bases. **9d.** each.

METAL BRAIDED WIRE

with PVC outer insulation **6d.** per yard.

POSTAGE STAMP TRIMMERS

50pf. **4d.** each.

POST ORDERS ONLY

67 RALEIGH AVENUE, HAYES, MIDDLESEX

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

Now Ready!

PREMIER TELEVISOR KITS

FOR LONDON AND BIRMINGHAM

USING 9" OR 12" MAGNETIC C.R. TUBES

£19·19·0 *including all parts, valves and loud-speaker, but excluding C.R. TUBE*

(Carriage and Packing 15/-)

CIRCUIT DETAILS

The Vision Receiver consists of 4 R.F. stages (EF54's) which are followed by a Diode Detector and Noise Limiter (6H6) which is directly coupled to the Video valve (EF54).

Complete Kit with valves, **£3 16 0.**

Carriage and packing 2/6.

The Sound Receiver comprises 3 R.F. stages (6SH7's) followed by a Double Diode Triode (6Q7), which acts as Detector and L.F. Amplifier. A Noise Limiter (EA50) is also incorporated. The output valve (6V6) drives a 10in. P.M. Moving Coil Speaker with closed field magnet, which is included in the Time Base Kit.

Complete Kit with valves, **£3 1 0.**

Carriage and packing 2/6.

The Time Bases employ blocking oscillators on both Line (6SH7 and 807), and Frame (VR137 and 6V6). E.H.T. (Non-lethal) is taken from the Line Output Transformer through a voltage doubler employing two valves (VU111). The Sync separators are 6H6 and 6V6.

Permanent Magnet Focusing.

Complete Kit with valves, **£8 5 6.**

Carriage and packing 5/-.

The Power Supply is from a double wound mains transformer completely isolating the receiver from the mains. The H.T. Rectifier is a 5U4G.

Complete Kit with valves, **£4 16 6.**

Carriage and packing 5/-.

EACH KIT OR INDIVIDUAL PART AVAILABLE SEPARATELY

The following sensitivity figures prove that the Premier Televisor Kit is capable of reception at greater distances than any other standard commercial kit or receiver whether T.R.F. or Superhet.

VISION RECEIVER

Sensitivity : 25 μV for 15V peak to peak measured at the Anode of the Video Valve.
Sound Rejection : Better than 40 db.
Adjacent Sound Rejection : Midland Model. Better than 50 db.

SOUND RECEIVER

Sensitivity : 20μV. Vision Rejection : Better than 50 db.

CONSTRUCTION BOOK

3/-

When ordering please state "MAGNETIC" Construction Book

167 LOWER CLAPTON ROAD, LONDON, E.5

Telephone : AMHerst 4723

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

PREMIER MIDGET RADIO KIT [illegible] Due to greatly increased production we are now able to offer this Kit at a greatly reduced price. Including an attractive Brown or Ivory Bakelite case 12in. long 7½in. wide 8½in. high. The valve line-up is 6K7, 6Z7, 6V6 and a Selenium Rectifier in the A.C. model; and 6K7, 6Z7, 35A5 and a Selenium Rectifier in the A.C./D.C. model. Both are for use on 200 to 250 volt mains. The dial is illuminated, and the tuning presents a very attractive appearance. Coverage is for the medium and long wavebands.

Complete Kit of parts with valves and Diagrams £4 19 6. Inc. Purchase Tax.

Made 2 A.C. or A.C./D.C. is required.

PREMIER MIDGET SUPERHET KIT. This powerful Midget Superhet Receiver is designed to cover the short, wave bands between 16m. and 50 metres and the medium waveband between 200 and 557 metres. Two models are produced, one for 200/250 volt A.C. mains and the other for 100/250 volt A.C. or D.C. mains. Both are supplied with the same plastic cabinet as the T.R.F. Receiver. The A.C. valve line-up is 6K8, 6K7, 6Q7, 6V6 and a Selenium Rectifier. The A.C./D.C. Unit is the same, with the exception of the output valve, which is a 35A5. The dial is illuminated, making a very attractive receiver.

Complete Kit of parts with valves and Diagrams £6 19 6. Inc. Purchase Tax.

Made 2 A.C. or A.C./D.C. is required.

PLASTIC CABINETS. as illustrated above. In Brown or Ivory. 17 6.

COLLARO AUTOMATIC RECORD CHANGERS. Type RC500 Bijou-Mite. Plays one side of 12in. records. A.C. 100/250 v. with High Fidelity Magnetic or Crystal Pick-up. £10 15 -. With Sapphire Stylus. £11 8 4.

COLLARO GRAMOPHONE UNITS. High-grade Bijou-Mite Motor complete with Pick-up and Automatic Stop-Start. A.C. 100/250. With Magnetic Pick-up. £5 3 2. With Crystal Pick-up. £5 17 7.

COLLARO GRAMOPHONE UNITS AT NEARLY HALF PRICE. Noiseless Turntable and Pick-up in one unit. Auto Stop-Start, variable speed. Disc turntable. Induction Motor for 100/250 v. 50 cycles, with Magnetic Pick-up. £6 6 -. With Crystal Pick-up. £7 4 8.

CONRAD GRAMOPHONE MOTORS. A reliable Bijou-Mite Motor for A.C. 200/250 v. operation. £2 17 6. with Turntable.

GOVERNMENT SURPLUS MAINS TRANSFORMERS. All are for use on 100 volt or 200/250 Mains.

Type		Price
43	500-0-500 v. 150 m.a. 5 v. 3 a.	25 -
23	350-0-350 v. 80 m.a. 5 v. 2 a. 5 v. 2 a.	15 -
24	375-0-375 v. 80 m.a. 5 v. 2 a. 5 v. 2 a.	15 -
26	350-0-350 v. 100 m.a. 5 v. 2 a. 5 v. 2 a.	17 6

WILLIAMSON AMPLIFIER KIT. We can supply the Kit of Parts for the latest version of this famous amplifier, complete in every detail for £10 10 -, with Valves.

WILLIAMSON AMPLIFIER OUTPUT TRANSFORMERS (a speciality). 52 -.

Mains Transformers. 45 -.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. All parts for construction are available. Ideal for use in 2-valve sets. Output 2 v. 1 amp. Trickle charge for accumulator. Uses metal rectifier. 35 -.

TELEVISION AERIALS. The K.A. Tele Aerial as shown above. For the Midlands, London or Birmingham frequency. 20 -.

WALL FIXING DIPOLE. 32 6.

WALL FIXING DIPOLE with reflector. 60 -.

See our new catalogue for complete lists.

MULLARD MW36/3 Mc. MAGNETIC TUBES. We can offer a limited quantity of these new and unused Tubes at £5 15 -. TO TRADERS ONLY.

V.C.R.97. C.R. Tubes. New and tested to give full size picture. 35 - each.

The following C.R. Tubes at the above. All priced.

Type	Diameter	Deflection	Price
MT13 (VC1001)	3in.	Long	3 -
MT20 (VC1002)	5in.	Short	15 -
VCR138 (VC1003)	5in.	Short	15 -
VCR517 (VC1004)	7in.	Long	20 -
VCR97 (VC1005)	7in.	Short	15 -

All have a Blue Screen. Screen protection extra.

TRANSMITTING AND SPECIAL PURPOSE VALVES

[illegible]	10 -	[illegible]	5 -
[illegible]	60 -	[illegible]	20 -
[illegible]	10 -	[illegible]	15 -
[illegible]	6 6	[illegible]	15 -
[illegible]	40 -	[illegible]	5 -
[illegible]	17 6	[illegible]	10 -
[illegible]	60 -	[illegible]	7 -
[illegible]	60 -	[illegible]	5 -
[illegible]	80 -	[illegible]	6 6
[illegible]	7 6	[illegible]	3 6
[illegible]	5 -	[illegible]	5 -
[illegible]	20 -	[illegible]	5 -
[illegible]	5 -	[illegible]	7 6
[illegible]	6 6	[illegible]	3 6
[illegible]	6 6	[illegible]	6 6
[illegible]	6 6	[illegible]	6 6
[illegible]	6 6	[illegible]	6 6
[illegible]		[illegible]	6 6
[illegible]	40 -	[illegible]	40 -

ELECTRON MULTIPLIER PHOTO CELL TUBES. Type 931A. Brand new. Guaranteed. 30 -.

Base. 2 6.

T.V. WHITE RUBBER MASKS.

We can now supply a specially designed White Rubber Mask for the 5in. Tube at 7 6 each.

For White Masks 9 6. For White Masks. 15 -.

SUPER QUALITY TELEVISION MAGNIFYING LENS. To suit the 5in. or 7in. Tubes. Further details on request. 25 - each.

PERMANENT MAGNET FOCUS POTS. Suitable for all Tubes. 15 -. Please state Tube used.

THE NEW PREMIER 1950 CATALOGUE

contains all the newest TV Kits, Components, Aerials, Tubes etc., in addition to thousands of Radio Bargains.

Now ready — 1d.

SUPER MOVING COIL MIKE AND STAND. We have purchased the entire stock of a famous Manufacturer of PA Equipment at a very low price, and are offering a £[illegible] Super Moving Coil Mike with a [illegible] Stand complete and to match. The cost price for the stand was £[illegible]

WE OFFER THE PAIR AT 79 6. LESS THAN HALF THE USUAL PRICE.

We can supply all parts from Stock for the VIEW-MASTER Television. For Enquiries to Birmingham. Inclination Bracket. 5 - each.

LOUDSPEAKERS (a famous maker).

7in.	9 -	10in.	12 6
8in.	10 -	12in.	21 6
9in.	13 6	15in.	39 6

MOVING COIL EARPIECES.

Complete with Moving Coil Loudspeaker fitted with Cream Ebonite Moulding, rubber cord. Make excellent Music Phones or Speakers. 2 - each.

SPECIAL HEADPHONE OFFER. High grade Double Headphones, using hardened magnetic steel. D.C. Resistance 3 6 per pair. Matching Transformers required. 2 6 each.

SPECIAL OFFER OF ELECTROLYTIC CONDENSERS

[illegible]	4 11
[illegible]	4 3
[illegible]	4 11
[illegible]	2 6
[illegible]	2 6
[illegible]	3 6
[illegible]	2 3
[illegible]	2 6
[illegible]	4 11

All Capacities and Voltages available.

MOVING COIL METERS. All 2in. square mounting. [illegible] 7 6. [illegible] 8 6. [illegible] 6 -. [illegible] 7 6. [illegible] 7 6. [illegible] 5 9. [illegible] 5 9. [illegible] 7 6. All 2in. round mounting. [illegible] 15 11. [illegible] 10 6. [illegible] 8 6. [illegible] 10 6. Thermocouple meters [illegible] 5 -. [illegible] 5 -. [illegible] 8 6. [illegible] 8 6. Double-reading [illegible] 25 -.

A LARGE NEW PURCHASE ENABLES US TO OFFER AT A LOWER PRICE THAN EVER R107. ONE OF THE ARMY'S FINEST COMMUNICATIONS RECEIVERS.

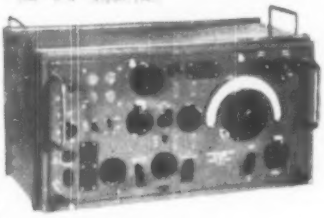

[illegible] Frequency Changer [illegible] Intermediate Frequency 1.5 Mc/s. Range 1.5 Mc/s to 18 Mc/s in 4 ranges. Mains Input 100/250 v. Complete. With valves and [illegible]. Price £12 12 -, plus 20/- carriage and packing.

SATTERT CHARGERS.

Input 100/250 v. A.C. Output 6 volts 1 amp. Continuously variable current control. Unit price £[illegible]. Two units, £10 10 - each, plus 10/- carriage.

A.C. ALL-WAVE SUPERHET CHASSIS.

Valves (plus metal rectifier) for the Radio Amateur. Uses 6A8 valve.

1 Waveband of coil (long, medium and short) included in price.

Pick-up leads. Uses 6K7, 6K7, 6K7, 6Re, 6Q7 and 6V6 in push-pull output to an output of 4 watts. Specially designed IF transformers to match output and drive the valves.

Negative feedback is applied over 3 stages giving a high fidelity output. Tone control is incorporated.

Completely new Superhet. £15 17 9d.

Also available for A.C./D.C. Mains, specification as above except that valves are 6K7, 6K7, 6K7, 6Q7, 6V6A. In kit form £13 8 10d.

ALUMINIUM CHASSIS. [illegible] made of bright aluminium with flat edges.

	Price
[illegible]	3 3
[illegible]	4 -
[illegible]	5 6
[illegible]	6 8
[illegible]	6 11
[illegible]	7 3
[illegible]	7 11
[illegible]	10 -
[illegible]	8 3
[illegible]	9 10
[illegible]	7 11
[illegible]	8 6
[illegible]	10 -

MAINS NOISE ELIMINATOR KIT.

For operation designed chokes with three smoothing condensers with full diagram. Units not all same size. Can be assembled inside existing receiver. 6 - complete.

CO-AXIAL CABLE.

Super quality cable consisting of a centre tinned core, a universal insulation, a braided screen, a weather proof PVC outer cover. For the lead-in for Television and F.M. noise cover. For the lead-in for Television and F.M. super noise cable, etc. 50 ohms impedance. Cat. No. C.200. 36 per foot.

GRAMOPHONE AMPLIFIER KIT.

Consists of complete Kit of Parts for a 12 watt Mains operated Public Address for use with any type of pick-up. A very attractive unit. Valve complement and output impedance are shown.

Cat. No. AMP12. Price complete. 65 -. For 200/250 v. mains with valves and diagrams.

SECTIONAL WHIP AERIAL. Aerial complete which plug into each other making an aerial 14ft. long. Thinner sections for fitting in the boot and for the Home. Weather proof. Length 3 6 each complete.

INSULATED BASE for above. 2 6 each.

METER KIT

A FERRANTI 500 MICROAMP M.C. METER. with diameter High Stability, High Accuracy. Resistance to operate, to, etc. for use and not sure price. Scale length 1in. diameter 1½in. 10 - the complete kit.

5 KV. ELECTROSTATIC VOLTMETER. Scale length 1in. Rod mounting. 1½in. diameter. £2 10 -.

207, EDGWARE ROAD, W.2 Phone: AMBassador 4033 **AND AT —**

All **POST ORDERS** to 167, LOWER CLAPTON ROAD, LONDON, E.5. Phone AMHerst 4723

EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

WE ARE NOW SUPPLYING

NEW LONG RANGE TELEVISOR KITS

FOR THE LONDON OR BIRMINGHAM FREQUENCIES

at the same price as the standard kit

£17 - 17 - 0

As is usual in all Premier Kits every single item down to the last Bolt and Nut is supplied. All chassis are punched and layout diagrams and theoretical circuits are included.

Five Easy to Assemble Kits are supplied :—

VISION RECEIVER with valves, carriage 2/6	£3 13 6
SOUND RECEIVER with valves, carriage 2/6	£2 14 6
TIME BASE with valves, carriage 2/6	£2 7 6
POWER SUPPLY UNIT with valves, carriage 5/-	£6 3 0
TUBE ASSEMBLY, carriage and packing 2/6	£2 18 6

This unit includes the VCR97 Tube, Tube Fittings and Socket and a 6in. P.M. Moving Coil Speaker with closed field for Television. The Instruction Book costs **2/6,** but is credited if a Kit for the complete Televisor is purchased.

Any of these Kits may be purchased separately ; in fact, any single part can be supplied. A complete priced list of all parts will be found in the Instruction Book.

20 Valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver is a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

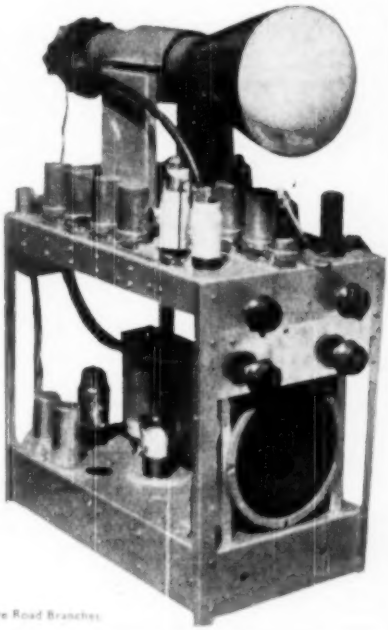

The following sensitivity figures prove that the Premier Televisor Kit is capable of reception at greater distances than any other standard commercial kit or receiver whether T.R.F. or Superhet.

VISION RECEIVER.

Sensitivity	25uv for 15v peak to peak measured at the Anode of the Video Valve.
Sound Rejection	Better than 40 db.
Adjacent Sound Rejection	Midland Model. Better than 50 db.

SOUND RECEIVER.

Sensitivity	20uv. Vision Rejection, better than 50 db.

A well-made walnut finish **PEDESTAL CABINET** is available from stock at £5/10/0 plus 7/6 carriage and packing.

Working Models can be seen during transmitting hours at our Fleet Street and Edgware Road Branches.

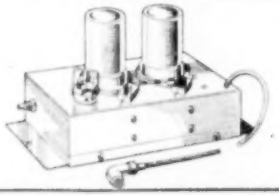

PRE-AMPLIFIER FOR FRINGE RECEPTION AREAS

We can supply the complete kit of parts to make this wide band width Pre-Amplifier, using 2 EF54 Pentodes. Powered by the TV Kit, it is completely screened. With all parts, valves, chassis, diagrams, etc., **27/6.** All parts available separately.

When ordering Televisor kits

PLEASE STATE IF THE LONDON OR BIRMINGHAM MODEL IS REQUIRED

—152-153, FLEET STREET, E.C.4 Phone : CENtral 2833

Terms of Business : Cash with order or C.O.D. over £1. Send 2d. stamp for list.

207, EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS

MORE SALE BARGAINS

Especially low prices only until May 31st.

Half As Much Picture Again

THE 6in. tube VCR97 gives a picture approx. 5in. × 4in. or 20 sq. in., a 7-in. tube would give a picture 6in. × 5in. or 30 sq. in., in fact half as much again. We can supply a 7-in. tube which has same base and same connections as the VCR97, also approx. the same working voltages, but requiring a little more frame and line amplitude—fluorescence is green. The type number of the tube is CV961, the sale price is **37/6**, plus 2/6 carriage and packing. The tubes are new and unused, the serial number will be entered on your invoice and should it give trouble within six months it will be replaced.

Power Pack Type 392

THIS is an extremely useful unit which works off A.C. without modification giving an output of 700 v. D.C. adequately smoothed. Here is a list of the components contained in the power unit: Mains Transformer for 200-250 v. 50 cycle, with secondaries of 700-0-700 v. at 70 mA., 4 v. at 2.5 amps., 12.5 v. at 1 amp. (Note these are Admiralty ratings the transformers will stand at least twice these figures). Also two rectifier valves type CV54, 10-watt resistors, three 4 mfd. 100 v. condensers, L.F. choke, 10 henry 100 mA., 2 slydlok fuses. The power pack is unused and is contained in a louvred case size 12in. × 5½in. × 8½in. Sale price **47/6**.

Receiver Type 78

THIS covers the wave band 2.4 to 13 Mc/s and it is also fitted with a 1,000 Kc/s crystal with an internal arrangement whereby its oscillator can be accurately checked with the crystal, the sets are 5 valvers and they are brand new and unused. Size is 6½in. × 8½in. × 10in. approx. Sale price is **30/-**, plus 7/6 carriage, etc.

Special Purpose Valves

WE hold a very good stock of valves of all types and for all purposes, and because we have bought in big quantities from the Ministry's most of our prices are ridiculously low when compared with others or with the original price. If you have been wanting valves for experimental purposes or to hold as spares for any equipment, this is obviously the time to buy, for instance we have 250 W. R.F. outputs for only **17/6** each.

During our sale period all prices are considerably reduced, but, of course, the quality of the valves remain the same. Unless otherwise stated all are new and unused, mostly in original cartons. As a sample of Sale Prices and types we quote from our list: VU29 2,000 v. 800 mA. mercury rect., **7/6**, VU111 5,000 v. rectifier 4 v. heater, **5/-**, VT31 250 W. R.F. output triode, **17/6**, VU508 8,000 v. 125 mA. rectifier, **12/6**, GR2 4 v. thyratron, **9/-**, 2D21 midget thyratron, **11/6**, VR91 6.3 v. R.F. pentode, **8/6**, 813 250 watts output Triode, **15/-**.

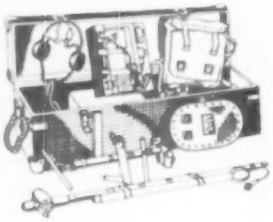

Metal (Mine) Detector

FOR the detection of ferrous or non-ferrous metals, under ground, under water or in animals, timber, chemicals, etc., etc., originally intended for detecting mines by one of our allied armies. This equipment has never been used. We have to clear the warehouse in which these are stored, and, therefore, we are offering these complete Mine Detectors for less than the cost of the transit case alone. The equipment comprises a 3-valve battery amplifier in a steel case, a shoulder haversack, and long counter balanced search coil, short search coil, headphones, function box, sensitivity measuring stick and operating instructions and circuit diagram. The original cost of this equipment was enormous, but as we have to clear our store, we will supply while they last at the very low figure of **22/6**, plus 8/6 carriage. We understand that these Mine Detectors were tested and in working order before being stored, but in view of the very low price, we can give no guarantee other than of completeness.

Radar Receiver 3084

THIS requires only the smaller modification to make it into a combined sound and vision receiver, for T.V. Main contents are: 7, EF50—2, VR136 (EF54) 1, VR135, 1, HVR2—1, R5, 1, EA50. Wire wound variable resistors, small 80 v. A.C. motors, wide band I.F. strip, brand new in original manufacturer's packing. Sale Price **49/6**, plus partly returnable packing case deposit and carriage charge of 10/-.

Indicator Unit Type 6

AS specified for the "Wireless World" oscilloscope (reprint of data 9d.), also for the inexpensive Television booklet **1/6** and our Mark I Television Constructor's envelope, **2/6**. These indicators are brand new in manufacturer's original packing, and they contain many hundreds of useful components, VCR97 6in. Cathode Ray Tube, 4—EF50 valves, 1 other valves, hundreds of wire wound pots, condensers, resistors, switches, etc. Sale Price **£3 19/6**, plus partly returnable packing case deposit and carriage charges.

Communications Receiver R1155

THIS is one of the finest communication sets ever made. Designed by leading engineers and made by one of our famous Companys, this receiver will undoubtedly give you years of good listening. Most readers well know it fairly well. The receiver covers the broadcast bands, long waves and medium waves, and short waves up to 30 Mc/s. It contains 10 valves and really brings the stations in. Sale Price **£6 10/-** for a good complete receiver. **£7 10/-** same grade receiver tested and re-aligned, etc., **£8 15/-** for unused receiver—**£9 15/-** unused receiver tested and re-aligned, all plus partly returnable packing case deposit and carriage charge of 10/-.

Crystal Substitute. TU5B

THIS very famous tuning unit has been referred to by one of radio's leading journals as an efficient crystal substitute. For instance for band spreading it has a micrometer dial which gives 2,500 divisions of the 180° of rotation of the tuning condenser. In addition the unit has a high Q tank circuit which has temperature compensated coils, a temperature compensated tuning condensers, all efficiently made up in a black crackle case. This tuning unit covers the band from 2.5 to 3 Mc/s. We will supply (where requested) a copy of the article which appeared in the radio journal showing how this can be converted into an efficient V.F.O. The total cost of the extra parts if you have to buy them all from us is less than **£1 10/-** so as the price of the TU5B is only **12/6** your V.F.O. will not be a costly item. In addition a TU5B can quickly become a transmitter or one of many other devices. Sale Price **12/6**, plus 2/6 carriage and packing.

Indicator Unit Type 162

THIS contains 2 Cathode Ray Tubes, one a 6in. type VCR517 which many constructors claim to be equal if not better than the VCR97. The other a 3in. type VCR139A which makes a very fine oscilloscope, in fact an article giving full constructional details appeared recently in a radio journal. Further, this indicator unit contains 9 very useful valves, all 6.3 v. types, a Klystron, a milliameter, a 24 v. motor, and literally hundreds of all other parts, condensers, pot meters, etc., etc. Sale Price **39/6**, plus partly returnable packing case deposit and carriage charge of 10/-.

Indicator Unit Type 182A

THIS again contains a VCR517 Cathode Ray Tube, in addition there are also eight valves as follows: 3—EF50, 1—5U4, 4—SP61's. Components include numerous pot meters, condensers, resistors, etc. Sale Price, **39/6**, plus partly returnable packing case deposit and carriage charge of 10/-.

American Type 6 Indicator

THIS indicator is virtually a copy of our Type 6 which you will remember contains the VCR97 tube, and many valves of such types as EF50's. It contains the Cathode Ray Tube type 5BP1 which is the American equivalent of the VCR97. It is a very useful unit and in addition to being useful for television work it can be converted most quickly into a 'scope. During this month the Sale Price is only **49/6**, plus 10/- carriage and packing case deposit, and to all purchasers we will present a free copy of the data showing how the 'scope can be made up. Alternatively, we will supply the data separately at **2/6** per copy.

R1355 With R.F. Unit

SUITABLE for making the Birmingham version of the "Inexpensive Televisor." This Televisor is doing good service almost all over the country. The instruction booklet is very clear and the fault-finding notes and pictures are most helpful should you get into difficulties. The Sale Price for this month only for the 1355 and the R.F. Unit together with the instructions is **55/-** complete. The receiver and R.F. unit while not being new are, nevertheless, absolutely complete and in perfect order, containing a total of 13 valves. If not calling then add 10/- as returnable deposit on packing case and to pay carriage charges. Instruction only **1/6**.

An All-Mains Three-Valver for 29/6d.

COMPLETE with filament transformer, ON/OFF switch, moving coil speaker, volume control, tuning condensers, range switch, etc., sounds a bit incredible but nevertheless it is true. Actually we supply a transmitter unit which is in new condition, you strip this down and re-build it following our instructions making a self-contained radio receiver for the broadcast band to bring pleasure to a particular friend, or to give you music while you work, study, play or rest. The price of the unit is **29/-** and this contains everything except the loudspeaker, and if it is only a little bedside receiver you want, then the miniature moving coil headphone unit type 22 is quite suitable. Alternatively, if you want the set for more normal use, then use our 3½in. speaker which costs **8/6**. The set will receive medium wave stations with reasonable strength, long waves can, of course, be added later. The set makes up into a very neat little outfit, measuring only 10in. × 6in. × 5½in. Send only **29/6** or **33/6** in full confidence because we guarantee to return your money (plus postage) in full if after making up the receiver you are at all disappointed with results, but please act quickly for these won't last long.

Receiver Type 25/73

THIS is the receiver portion of the TR 1196 and it is undoubtedly one of the most useful little receivers that has ever been offered as Government Surplus because once you have removed the tuning unit and replaced it with a standard coil pack, you have a domestic receiver. You can use almost any valves, for instance, in the first stage it needs an R.F. pentode, SP61, EF39, 6K7, etc. V2 is the frequency changer, here you can use VR55, EK32, 6K8, etc. V3 is the I.F. Amplifier, this can be the same type as V1. V4 is the detector and first A.F. Amplifier, this can be EBC33, 6Q7, VR55, etc. V5 is the output valve, say 6V6, EL32, 6L6, VT52, etc. You can see then that you will be able to make a very efficient superhet for a very small figure.

(Details of the complete circuit will be supplied gratis where requested).

Alternatively, if you don't want to build a receiver, then you have some really excellent break-down value. In the first place, there is a pair of standard 465 Kc/s dust cored I.F. Transformers. These would cost 12/6 to 15/- and, of course, in addition you will have such items as tuning condensers, coils, pre-set condensers, pot meters, etc., etc., etc. Don't waste time getting your order in for this item, the Sale Price is only **7/6** or with set of valves, **19/6**.

A Free Gift

THE famous American indicator unit APN4 uses a 5in. C.R. tube type 5CP1 and has a front panel which is most impressive, equal in fact to the most expensive 'scope. It is a double-decker unit and it is literally crammed with parts for it is a 26-valver. The parts include focus and brilliance and time base controls and hundreds of condensers, pot meters, resistors, etc., which if bought separately must cost £30 to £40. We give the unit away free if you buy the tube 5CP1 and the sale price we ask for this is only **27/6**, plus 10/- partly returnable carriage and deposit on packing case.

Receiver 1132A

THIS is a V.H.F. receiver covering 100-126 Mc/s. It uses eleven valves, it has a super tuning scale and slow motion drive and 0-5 mA. moving coil tuning meter. Totally enclosed in grey metal cabinet with plated handles. Valve line-up as follows: VR65, VR66, three VR53, VR54, VR57, VS70, VR56. Sale Price only **59/6**, carriage, etc., 7/6.

Milnes H.T. Units

RECHARGEABLE H.T. batteries, 120 volts, 600 mA. hours, rechargeable from 8 v. D.C. charger or car battery; will last for ever and show a great saving over dry batteries. Ideal for school, laboratories, boats, etc. Complete with full operating and maintenance instruction. Brand new and unused in carrying case with handle and armoured glass lid 14in. × 11in. × 8½in. Sale Price **47/6** each, carriage and insurance, 2/6.

Complete A.C. Power Pack

THIS is incorporated in the crystal monitor type 4 which is a very high grade instrument using 7 valves and providing modulated R.F. over a frequency range of 100-130 Mc/s. The size of the instrument is 19in. × 7in. × 9½in. deep. These are new but less crystals and valves, so we offer them to you for less than the value of the power pack alone. Sale Price is only **45/-** plus carriage, etc. 5/-.

Building a Car Radio?

IF so you will need a Vibrator unit. We can offer one made by the celebrated Mallory Co., of America. These work off 12 volts (you could fit a 6v. transformer) and are complete with synchronous vibrator and all necessary resistors and condensers. Slightly soiled due to storage but unused and perfect. Price **11/6** each.

Morse Oscillators

BATTERY operated Morse Oscillator, complete with modulation and interference transformers, incorporating note selector control, volume control, phone, key and interference jacks. Size 9in. × 8in. × 8½in. Power supply required, H.T. 60 v., GB4½ v., L.T. 2v. Provision for fitting batteries inside case. Supplied brand new and unused, complete with 2 valves. Sale Price **15/-**, carriage and packing 1/9.

MCR1 Power Packs

UNIVERSAL power supply to operate on any mains voltage. Designed for miniature receiver MCR1, but suitable for any small superhet. Output 120 volt H.T. 7.5 v. L.T. Size 2½in. × 3½in. × 8½in. Sale Price only **24/6**, carriage and packing 1/6.

Receiver Type 1224A

BRAND new and complete with 5 valves, ready for use as soon as batteries are connected. Frequency range 1-10 Mc/s (3 bands). Muirhead slow-motion drive giving ease of tuning. Batteries required: 2 v. L.T. 9 v. G.B. and 120 v. H.T. Sale Price, **£4 12/6**, carriage and packing 7/6 extra.

Miscellaneous Items 10/- each

MAGSLIP 3½in. transmitter. 0-1 moving coil meter 2½in. flush mounting, 1,000 Kc/s crystals double American made. P.M. speaker 8in., by very famous maker. Packard bell pre amp with valves. Filament transformer 4 v. 6 amps. Moving coil headphones with M.C. mike.

Magnetic Television

FOR 9in. or 12in. tubes, the sale price of the complete outfit is only **£18 10/-** (terms available). Call to see our demonstration model. Data for novice or technician, **2/6** only. Black and white pictures, tube is extra.

Pay Us A Visit

ON these two pages we have mentioned only a few of the many bargains which will be available during our sale. We suggest that you "Pay us a Visit" because there will be many items for callers only. Failing this you must send for our Bumper Sale List. Do not forget to enclose **6d.** in stamps, because we shall probably have to send it out in two editions.

Orders for and enquiries relating to the items on these two pages must be sent to the address below. Where your total order is £2 or more only include the specially mentioned carriage and other charges, otherwise under £2 add **1/6**, under £1 add **1/-**. Postable items can be sent C.O.D. additional charge approx. 1/-. Good stock of all items at time of going to press. Bargain list **6d.** p.f.

ELECTRON

PRECISION EQUIPMENT (2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDX.

LAWRENCES

CATHODE RAY INDICATOR UNITS TYPE APN4. This famous unit contains short persistence tube 5CP1, suitable for high definition television, also 26 valuable valves, including many 6SN7, 6SA7, etc. Front panel closely resembles an expensive oscilloscope, and is fitted with controls for focus, brilliance, time base, etc. Unused and spotlessly clean, complete with circuit diagram, **£6 15/-**. If desired, we can supply this unit with 5CP1 tube but less valves only, **67/6**.

MARCONI AMPLIFIERS TYPE 6. A really fine rack mounting job, employing two PX25 valves in push pull. Standard size panel is fitted with Anode Current Meter, Volume Control, etc. Power Unit Type 6, also on standard panel, is also supplied. Very robust construction, with delayed H.T. switching, for operation on 230 v. A.C. 50 cycles. Price only **£6**, with circuit diagram. Standard 5ft. rack by Cossor also available, for use with the above. Supplied separately, **40/-** each.

NEW AMERICAN RADAR MODULATORS TYPE MD.5B APS3. Originally employed with 3 cm. Transmitter (725A Magnetron). Contain 1 829B, 1 715B, 4 72, 3B24, 1 73 and 2 electric blowers, relays, E.H.T. oil-filled Condensers, etc. Price only **£6**.

RADAR GAS GAPS TYPE 721A. For 10 cm. equipment. **15/-** each.

NEW WESTINGHOUSE RADAR TRANSMITTERS TYPE SL1. Heavy steel case, with large motor blower 115 v. 50 cycles, **£10**. We also have available other units of this 10 cm. equipment, including Receivers, Power Units, Selsyn Amplifiers, Antenna Pedestals, Bearing Control and Indicating Units. Details on request.

NEW R.C.A. STANDARD CRYSTALS. 100 kcs. Invaluable for frequency meters, etc. Complete with special holder, **22/6**.

NEW MICROAMMETERS. Flush mounting Grade 1 movements, 500 microamps, **7/6**. Also 50 microamps, this exceptional 20,000 ohm per volt meter only **15/-**.

V.H.F. DIPOLE ASSEMBLY. Pars of Rebecca installation. Streamlined junction box. Parasitic reflector element. Suitable for mod. to TV Antenna by extending elements, **3/6**.

NEW JENSEN AUDITORIUM ENERGISED SPEAKERS. 15in. cone, with exceptional frequency response. Energisation of 16.7 watts, in the field coil. Flux density 12,980 gauss. Gap energy 7.5 million ergs. This is the famous Model A-15 Orthodynamic, listed at £89. **£7 10s.**

TELEVISION MASTS. 36ft. Made by Bendix Corp. U.S.A. Telescopic, 5in. dia. Completely self-supporting on patent tripod base. Constructed of durable resin impregnated timber. This superbly engineered product is ideal for mounting beam arrays. Erected or dismantled in 30 mins. As supplied to leading Industrial and Public concerns. Complete **£6**. Descriptive illustrated leaflet available on request.

INTERFERENCE SUPPRESSORS. Fitted in aerial lead-in to set. Small unit in screening can 1in. x 1½in. x 2½in. **3/9**.

AERIAL LIGHTNING ARRESTORS. Highly efficient, sealed in evacuated glass tube. Complete with insulated holder, **3/6**.

NEW EDDYSTONE FLEXIBLE COUPLERS. For ¼in. condenser shafts, etc. **1/6**.

NEW I.F. TRANSFORMERS. 12 cms. For TV I.F. strips, etc. Permeability tuned. With screening can, compact size, **4/-** each.

NEW AMERICAN STAR IDENTIFICATION INSTRUMENTS. Complete with charts for all latitudes in northern and southern hemispheres. Accurate in all parts of the world. In leather case, **5/-**.

R.C.A. FOCUSSING COILS. For electromagnetic tubes with neck dia. up to 1.5in. **6/6**. Deflector coil assembly to match, **6/6**.

NEW METAL STORAGE CABINETS. Of improved design, fitted with 12 sliding drawers. Overall dimensions: 10½in. x 7½in. x 6in. Extremely useful for segregation and neat storage of small parts, **17/6**.

NEW HAND MICROPHONES. Double button carbon type, with neat on-off switch on semi-spherical base. Complete with cord, **2/6**.

NEW C.R. TUBE HOLDERS for VCR97, etc., **3/6**. Discount for quantities.

NEW GUARANTEED CONDENSERS. 1 mfd. 3 kV. can type, isolated terminals, **4/-**; 2 x .075 mfd. 8 kV. oil-filled can, ceramic standoffs, **8/6**. Ditto, but 2 x .15 mfd. 8 kV. size 4½in. x 3½in. x 1½in., **12/6**. 1,000 mfd. 25 v. D.C. can, **3/6**; 4 mfd. 2 kV. can, **4/6**; .25 mfd. 1.5 kV. can, **2/-**; heavy duty twin condenser, .25 mfd. 18 kV and .25 mfd. 9 kV. large insulators, **12/6**; .01 mfd. 2.5 kV. can, **2/6**.

NEW ELECTRON MULTIPLIER PHOTO CELLS. 931A. High sensitivity, **27/6**.

SKY WAVE WHIP AERIALS. Nine-foot element. Base insulator has long leakage path for all weather operation. Mounted on roof top, this aerial provides first class results and reduces interference level. To clear, **7/-**.

GLAZED PORCELAIN 600 ohm FEEDER SPREADERS, 9d. each.

MISCELLANEOUS CLEARANCE BARGAINS. Only new material.

VARLEY 6 volt m/cycle accumulators **25/-**; Battery class B Amplifiers 2 valves (used), **12/6**; Packard Bell pre-amplifiers, 1 6SL7, 1 28D7, with manual, **13/-**; antenna tuning units, with R.F. meter, **8/6**. Airmes balloons, 5ft. dia., with special hydrogen generator, **10/-**. America: aerial kites BC357, large size, **14/-**; Blower units, 24 v. D.C., **4/9**; Resistance tag boards, 3 for **1/6**; Chokes, heavy duty, 10 h. 500 mA (used), **8/6**; Aircraft compasses, 6in. spirit filled luminous, in case, **14/-**; Co-ax cable connectors, silver plated, **2/9**. BC45): 4-5 triple control panels (used), **7/6**. Many other command equipment spares: 1 F.F. set control panels (BC966), **2/6**. Headphones, in maker's cartons, **4/6**. Magnetron magnets, **5/-**.

TERMS: C.W.O. ALL PRICES INCLUDE U.K. CARR. SATISFACTION GUARANTEED, OR MONEY IMMEDIATELY REFUNDED.

LAWRENCES,
61 BYROM ST., LIVERPOOL, 3
Telephone CENtral 4437

Henry's

RADIO COMPONENTS
ELECTRONIC & TELEPHONE EQUIPMENT

R.1355 RECEIVERS. We have been fortunate in securing a further limited quantity of these receivers. These are brand new and unused. Price **55/-** (plus 5/- carriage).

R.1355 MAINS TRANSFORMER. 200/250v. input. Outputs 250-0-250, at 120 m.a., 6.3v. at 6a., 5v. at 3a. Fully shrouded top chassis mounting and guaranteed 100 per cent. Only **28/6**.

NO. 18 SET. RECEIVER PORTION. A four-wave superhet receiver operating from 6-9 Mc/s (33 m.-50 m.). Valve line-up: 3 ARP12 (VP21), and AR8 (HL23DD). Requires only 120v. H.T. 9v. G.B. and 2v. L.T., in perfect condition, only **17/6**, plus 1/6 packing and carriage. An absolute bargain. Suitable brand new headphones can be supplied at **3/6** per pair.

N.B.—Each receiver is tested working, prior to despatch.

RECEIVER TYPE 21. The receiver portion of the W.S. 21 operating from 4.2-7.5 Mc/s. Double superhet from 18-30 mc/s. incorporating B.F.O. and crash limiter. Valve line-up 7-ARP12 (VP23), and 2-AR8 (HL23DD), plus spare valve of each type, making eleven valves in all. Only **35/-** complete.

A.M. RECEIVER UNIT, TYPE 161. Comprising 2 EF50, EF54 and EC52. Coils, relay and many condensers and resistors. The whole in metal box, size 8½ 6½ 3½in. New, a bargain at only **22/6**, carriage paid.

R1626 V.H.F. RECEIVER. Ex-A.M. Comprising 10 EF50 valves, 2 EB34, 24v. rotary generator, relays and hundreds of condensers and resistors. Complete in grey metal case. Absolutely brand new, **75/-** only.

RECEIVER TYPE 25. The receiver portion of the T.R. 1196. Covers 4.3-6.7 Mc/s., and makes an ideal basis for an all-wave receiver, as per "Practical Wireless," August issue. Complete with valves type EF36(2), EF39(2), EK32 and EBC33. Supplied complete with necessary conversion data for home use. Only **22/6**. Chassis only, **8/6**.

METER DISTRIBUTION BOARDS. Comprising 0-300v. M.I. meter, 3½in. A.C./D.C. input plug and socket, 3 output sockets, 2 porcelain fuses. Total size 12 6in. Brand new and individually boxed **17/6** complete.

POCKET VOLTMETER. Ex-Govt. Two range 0-15v., 0-250v., D.C. Brand new and complete in Web carrying case, only **10/6**.

SKY ELECTROSTATIC VOLTMETER. 0-5kV., panel-mounting, 3½in. scale, brand new, **50/-** each.

D.C. AVO MINORS. Special offer, limited quantity of these well-known instruments, brand new and boxed, but slightly soiled. Not ex-Govt. **55/-** only.

SANGAMO WESTON. Ex-Govt. 0-1 M.a. M.c. meters, 2½in. panel-mounting. Absolutely brand new, **15/-** each only.

E.H.T. TRANSFORMERS. Output 2,500v. M.a., 4v. 1.1a., 2.0-2v. 2a. (for VCR97), **35/-** only. Output 3,250v. 5 M.a., 6.3v. 1a., 2.0-2v. 2a. (for SCP1), **39/6**. Output 4,000 v. 10 M.a., 2.0-2v. 2a., **48/-**. Output 5,000v. 10 M.a., 2.0-2v., only **60/-**. All input 230v. and fully guaranteed.

MICROAMMETER. 0-500 microa., 2in. scale, moving coil, panel-mounting, **7/6** each.

OSMOR MIDGET "Q" COIL PACKS. Size 3½ 2½ 1½in. Amazing performance. Polystyrene formers with adjustable iron cores. One-hole fixing, only five connections. Factory aligned complete with full receiver circuits and instructions. 5 het for 465 kc/s., **33/-** only. I.M.S. also for T.R.F. operation M. and L.W., **30/-**. We can now offer the latest "Q" pack for 5 het battery operation. Complete with circuits incorporating either 1A7 or 1T4 series. Valves. This pack is supplied with ready-wound frame aerial. Price **37/6**.

Please note that separate H.F. Stage, for addition to the above Mains Superhet Coil Pack, can now be supplied at **15/-** only. Complete with all necessary easy-to-follow instructions.

TUFNOL SHEET. First grade, polished finish, size 21 15in. ⅛in. thick. Weight 10 lb. Drilled at intervals around the edge for 4BA counter-sunk screws. Per sheet, **15/-** only.

ALSO. 21 10½ ⅛in. Weight 3 lb., undrilled, **5/-** per sheet, plus 6d. postage.

6in. CATHODE RAY TUBES. VCR97, electrostatic, non-persistent, individually boxed, ready for transit. **35/-** each only. Postage and packing free.

Side contact base for above, **2/-**.

6in. Masks for above. Not ex-Govt. but specially manufactured to give rectangular picture. Black **6/6**. White **7/6**.

E.M.I. MARCONI AUTOMATIC RECORD CHANGERS. TYPE A.C.100. Light-weight pick-up, complete with matching transformer, **£10 10/8**, carr. paid. Latest type.

Send stamp for current Component List
Probably the most comprehensive in the trade

5, HARROW RD., LONDON, W.2
PADdington 1008 9 and 0401

UNIVERSITY RADIO, LIMITED

Offer Guaranteed Used Equipment at Attractive Prices

One only non-auto-stop Decca Deccalion, in perfect condition and working order. As new ... £20 0 0
B.S.R. Ampligram, model AG4, perfect ... £21 0 0
Eddystone 640, with Speaker, as new ... £21 10 0
Hambander, as new ... £13 0 0
BC348, converted for A.C. 200-250 volts. Perfect ... £15 0 0
MCR.1, complete with coils, power-pack, phones, etc. As new ... £8 0 0
Labgear Electronic Fault Tracer, 1948 model, as new ... £15 0 0
Taylor 65B Signal Generator, as new ... £11 0 0
Portable chrome Mike stands, brand new ... £1 11 0
Evershed's 500 volt Wee Megger in leather case, as new ... £8 10 0
Valradio D.C.-A.C. Vibrator Converter, 200 watts, in new condition and perfect working-order ... £9 0 0
Taylor model 313C Capacity and Inductance Adapter, as new ... £2 17 6
Evershed's Bridge Megger, with built-in Resistance Box, 500 volts, perfect condition ... £15 0 0

B.P.L. Signal Generator, A.C. 200-250 volts. As new ... £11 0 0
Hartley Turner (1949) P.M. Speaker, as new ... £5 10 0
Sound Sales (1949) P.M. Speaker as new ... £5 0 0
Webster Portable Wire Recorder, complete with 3 spools (2, ½ and 1 hour), microphone, modulation meter, and Auto-Transformer A.C. 200-250 volts. In perfect working order and new condition ... £75 0 0
Hallicrafter's SX16, with Hallicrafter's Speaker in cabinet (12in.) ... £25 0 0
Masteradio (1949) Car Radio, 12 volt. In perfect condition and working order. Cost over £28. Our price ... £14 10 0
Auto Transformers totally enclosed, 850 watts 1 phase, 200-250, 100-110 volts. Brand new with leads for projector or other use. A really fine job ... £6 0 0
Foster Transformers 230/240 v. 1 phase. Sec. 12 v. 30 amps. Perfect. 2 only ... £2 10 0

Latest model Collaro Auto-Changers, as new. Each ... £8 10 0
Rotary Converters, 24 D.C.—230 A.C., 100 watts, 1 phase, 50 cycles. Perfect as new. Each ... £5 0 0
As above, 12 volt D.C. input. In case. Metered ... £7 10 0
21 day Clockwork Time-Switches, 5 amp. 200-250 volt. Famous make. Totally enclosed. A few only. Cost £7 each. Our price, as new ... £3 13 0
E.D.C. Rotary Converter, 220-240 volt D.C. to 230 A.C., 90 watts. In metal case with Filter Unit. In perfect condition ... £8 10 0
Transmitter No. 12, A.C. mains. Complete with all valves. In very good condition ... £22 0 0
E.D.C. Rotary Converter, 24 volt D.C. to 230 A.C. 300 watts. Converter unit only. In perfect condition ... £8 10 0
E.D.C. Rotary Converter, 230 D.C. to 230 A.C., 200 watts. Perfect ... £8 0 0
L.D.C. as above, not ex-W.D. 150 watts. As new ... £8 0 0

WE NEED GOOD USED EQUIPMENT URGENTLY. PLEASE SEND, BRING OR PHONE FOR OFFER

Goodmans 12in. P.M. Speaker, as new ... £4 0 0
Goodmans Axiom 12, as new ... £5 10 0
Goodmans Axiom 22, as new ... £8 17 6
Vitavox 12in. P.M. Speaker, as new ... £4 0 0
Avo 1948 model Signal Generator, as new ... £10 10 0
Avo Valve-Testers (1948-49), with Roller Panel, as new ... £10 10 0
Avo Capacity and Resistance Bridge, as new ... £7 0 0
1948 model Collaro Microgram, complete and perfect in portable case ... £11 10 0
Collaro 1950 model Auto-Change Microgram, as new ... £20 0 0
Garrard RC50, mixer-changer, centre drive, A.C. 110/250 volt, as new ... £12 10 0
Collaro centre drive A.C. 'Gram Motors, with Turntables, as new ... £4 10 0
H.M.V. 10 watt A.C. 'Gram Amplifier, complete with valves (2 KT63 s.p.-p.). As new ... £10 0 0
R-1155N, with A.C. Power-pack, and Speaker in cabinet. In perfect condition and working-order ... £16 10 0
Advance Signal Generator model E-1. Complete, as new ... £15 0 0
G.E.C. Miniscope, complete and perfect ... £15 10 0
Cambridge Unipivot L Pattern 0-240 Microampmeter, 5in. scale. As new ... £7 10 0
Simon Sound Service Recording Amplifier, model EA25, complete, as new ... £20 0 0
Canadian Set VRL, complete with Power-pack, rack and valves. In new condition ... £21 10 0
Hallicrafter's S27, in new condition, complete with all valves ... £30 0 0
Another as above, with scratched case. Internally perfect ... £25 0 0
Hallicrafter's Panoramic Adapter for S27, 5 meg-1 f. as new. Complete ... £21 0 0

Voigt Corner Horn Speaker (1949-50 model). In new condition. Complete with Voigt P.M. Units. Originally cost £95. Our price ... £65 0 0
Taylor A.C. D.C. Junior Test Meter, as new ... £5 0 0
Ferguson 8 valve Floor Console (1949-50 model). Cost £45. Our price, in perfect condition as new ... £26 10 0
Wharfedale W-10-CS Speaker, as new ... £5 0 0
Wharfedale 10in. Golden Speaker. As new ... £2 10 0
Taylor model 30A 'Scope, as new, in perfect working-order ... £20 0 0
Parmeko 12 volt D.C. 10-watt Mobile Amplifier, with hand Mike. Complete and perfect ... £10 10 0
As above, 15 watt ... £11 10 0
Avo model 7, as new ... £13 0 0
Avo model 7's in leather case ... £14 10 0
Romac 25-watt A.C. Amplifier, with built-in radio, 'gram and mike inputs. As new ... £20 0 0
Baker (1948) Quality Amplifier, complete and perfect. Originally cost £27. Our price with valves ... £11 0 0
1948 Charles Amplifier ... £10 0 0
GB-LS16 Sound-on-Film or Silent Projector (one only). In new condition. A.C./D.C. Complete with valves, spools, etc. Perfect and ready to use ... £87 10 0
Marconi No. 14 Pick-up and Transformer. As new ... £2 17 6
Collaro new magnetic Pick-ups. Each ... £1 5 0
One only Leak Pick-up, latest model. With Transformer. As new ... £7 15 0
As above, without Transformer ... £6 10 0
B.T.H. ¼ h.p. D.C. Motors, 220-240 volts, perfect. Each ... £3 10 0
B.T.H. A.C. Motors, ¼ h.p. 1 phase, 50 cycles, 220-240 volts. Perfect. Each ... £6 0 0

Triplett (U.S.A.) Valve-Tester with Test-Meters in portable case. Complete with charts. As new ... £16 10 0
G.E.C. portable Tube-Checker, model TC3, with charts. As new ... £13 0 0
Taylor 45A Valve-Tester, as new ... £14 0 0
Hickock (U.S.A.) Valve-Tester in portable case, as new with all charts ... £14 10 0
Marion (U.S.A.) Flux Meter, complete and new. (One only) ... £15 0 0
Ex W.D. Type 2 Transmitter and Receiver, complete with Power-pack. As new ... £13 10 0
Jefferson Travis ultra short-wave Transceivers, complete with batteries ready to use. In new condition, with transit cases. Type UF-1. The pair ... £21 0 0
Douglas No. 3 Coil-Winder, complete with A.C.W. A.C. motor. As new ... £55 0 0
Avo Minor A.C. D.C., as new, complete with leather case ... £6 0 0
Ex-W.D. stab volt type 8 Stabilised Voltage Power-Pack. In new condition and perfect working-order ... £17 10 0
Ex-W.D. Avo model D, A.C./D.C. (As model 40.). Perfect ... £9 10 0
Radiometer's Valve-Tester, perfect. With charts ... £6 0 0
RME69, in perfect condition and working-order ... £18 10 0
Westalite Charger, 48 cells at 2 amps. A.C. 200-250 volts. As new ... £11 10 0
Eddystone 358X, with 9 coils and A.C. Power-pack. 100 kc/s to 30 meg. Perfect ... £20 0 0
Charles Amplifier (1948 model). 8 valves. 2 PX25's (p.-p.). In perfect working order ... £10 0 0
AR88D, in perfect condition with built-in 5 Meter and charts ... £45 0 0
AR88LF, as above ... £35 0 0

We have various items to clear out, which we have taken in part-exchange deals. Cheap mains transformers, chassis, Amplifiers, all perfect to callers only. Ex-W.D. sets, etc. No fixed condensers or small components stocked.

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE PAID UP TO 50 MILES.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

Phone GERrard 4447 and 8582. Hours 9 to 6. Thursdays 9 to 1.

YOU CAN MAGNETICALLY RECORD
using your Gramophone Motor as a Drive

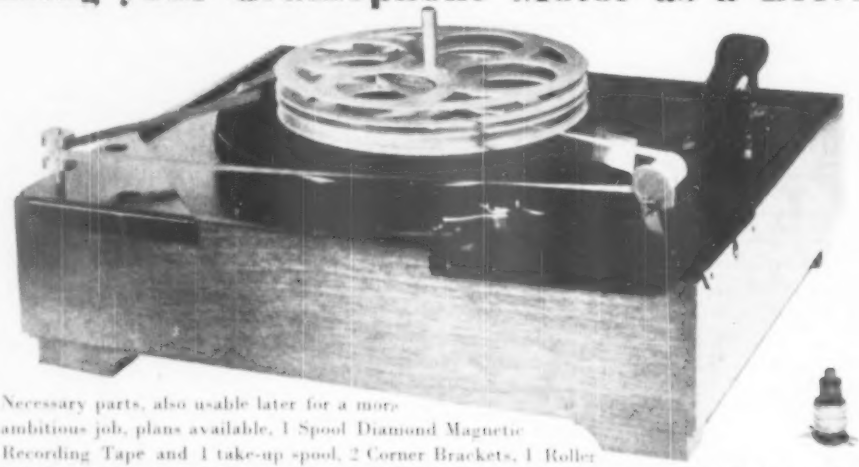

Necessary parts, also usable later for a more ambitious job, plans available, 1 Spool Diamond Magnetic Recording Tape and 1 take-up spool, 2 Corner Brackets, 1 Roller 1 Record-playback Head Kit, 1 Friction Clutch, 1 Dual-purpose Supersonic Oscillator and Two-stage Preamplifier and your Radio Chassis. Set of parts £7 . 15 . 0, or items supplied separately.

PARK RADIO OF MANOR PARK, 676/8, 783 Romford Road, London, E.12

RADIO EXCHANGE CO.

BRAND NEW 1350's. Those receivers made part of the Gee direction finding equipment, have established themselves during the last few years as one of the most popular TV conversion units available. With SIX IF stages (1.5 mc/s) det. and output stages, there is sufficient room on the chassis to accommodate a suitable power pack. Complete with 11 valves, and BRAND NEW in original maker's crates. £3/15/-

RECEIVER TYPE 18

Four battery operated valves make Eleven series superhet (no 11 to day's greatest bargain. Covering 6/9 mc/s they will receive dozens of stations when batteries, phones and aerial are connected. In new condition with circuit. 19/6.

HEADPHONES, matched for use with the above, and complete with jack plug. 2/6.

MERCURY BATTERIES, the new wonder dry batteries with an infinite shelf life, delivering 84 v. H.T. and 1.5 v. L.T. BRAND NEW. 6/9.

MIDGET L.T. ACCUMULATORS, made by Exide and Oldham to rigid naval specification, they measure 4 x 3 x 4. BRAND NEW. 2/6 (12 for £1).

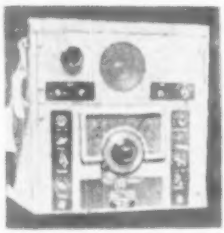

MIDGET MOTORS, 2½ in. long × 1½ in. dia. developing 1,150 R.P.M. with 27 v. input. These are U.S. motors as new condition. ONLY 9/6 each.

RECEIVER TYPE 3586 (Mark 4B/3586) two 6SH7's, one EF50, one EF36, three EF36's and one EA50 (Ex "Y") 30 mc/s tuning, a bright dial and a number of pots, resistors and condensers. IN MAKER'S SEALED CRATES. OUR PRICE with 10 valves £5/12/6.

VIBRATOR PACK 21. Self contained for 6 v. supply and delivering approx. 175 v. at 40 mA. Fully assembled. New condition. In by-pass condition for only 19/9.

RECEPTION SET VRL

A fresh supply, this time in sealed maker's cartons, of this magnificent product of Vacuumver Radio Laboratories is again offered to the "ham" and commercial user who requires a really first class receiver.

- Four bands (1.8-29 mc/s) but is six position switch providing coverage extension.
- 19 valves in all.
- Variable selectivity (Six filter).
- Noise limiter.
- B.F.O. with control.
- A.F. gain control.
- Optional A.G.C. which may be keyed for C.W.
- Magic eye.
- Built in speaker.
- Full view dial.
- Crystal calibrator providing 100 c/s, 1 kc/s or 5 kc/s.
- Provision for phones with optional muting of speaker.
- Top grade components.
- Self contained for 12 v. input ... and an output is available step-down transformer. PRICE £26/10/- or with 19 spare valves ... £29/10/-. Send stamp for pamphlet VRL.

POWER UNIT 10, with a 240 v. 10 mA., 275 v. 110 mA. rotary transformer, plus a 275 v. vibrator pack, this double unit operates from 12 or 24 v. input. Alternative leads, and in good condition. ONLY 12/6.

HEAVY DUTY OUTPUT TRANSFORMERS, suitable for 2 x EL32 valves, 3 x 3 ohms output, and 240 v. primary. ONLY 4/6.

TRANSFORMERS. Fully screened and potted, these may be used as step-down transformers handling some 75 watts. OUR PRICE 6/- each.

RADIO EXCHANGE CO., (W), 9 CAULDWELL STREET, BEDFORD. Phone 5563

All goods sold as used unless otherwise stated.

PLEASE WRITE YOUR NAME AND ADDRESS IN BLOCK LETTERS

BARGAINS IN EX GOVT. AND SURPLUS RADAR RECEIVERS, TRANSMITTERS, TRANSMITTING AND SPECIAL VALVES, AND COMPONENTS

LASKY'S RADIO

World Renowned for Service & Reliability

EVERYTHING FOR THE AMATEUR, SERVICEMAN, EXPERIMENTER, RADIO AND TELEVISION CONSTRUCTOR.

V.H.F. RECEIVER UNITS. These units are packs stripped but contain a wealth of components, resistances, condensers, coils, I.F. transformers, etc. Also 4 valves: 2 EF50, 1 EB50, 1 EL32. Overall dimensions: 19in. x 7½in. x 6in.
LASKY'S PRICE 10/- carriage 3/6.

RECEIVER UNITS, Type 158 (45 Mc/s Fixed strip. Contains 4 R.F. stages, detector, video amplifier and phase splitter. Uses 6 EF50 and 1 EA50. A complete vision receiver. BRAND NEW and UNUSED.
LASKY'S PRICE 67/6.

CATHODE RAY TUBES, Type VCR97. Brand new ex-Government. Fully guaranteed. Supplied in spring wood transit case. Characteristics: Heater 4 volts, 1 amp. H.T. 2.5 kv. maximum. Tested before despatch.
LASKY'S PRICE 35/-, carriage free.

VCR97 SCREEN EVLARGERS. Latest type plastic oil-filled lenses. Will give a bigger, better, clearer and sharper picture from your tube. Ideal for any tube.
LASKY'S PRICE: 1st grade, 29/6.
2nd grade, 25/-.
Postage 1/6 per lens extra.

BUSHES MASKS FOR CATHODE RAY TUBES.
5in. Round, black. Price 3/6.
5in. Square, white. Price 7/6.
9in. Square, white. Price 11/-.
9in. square, black. Price 12/-.
12in. square, white. Price 21/-.
12in. Square, black, solid. 12/6.

SAFETY GLASS SUITABLE FOR 12in. CATHODE RAY TUBES. Size 12in. x 12in. x ¼in. thick. Price 4/11 per piece.

I.F.F. RECEIVERS. Brand new and unused. Supplied in maker's original cartons. Contains 9 new valves: 4 SP41, 1 EA50, 1 VR78, 2 OV6. Also hosts of components, coils, condensers, resistances, switches, etc. A useful generator with an input of 24 volts and output of 400 volts.
LASKY'S SPECIAL CLEARANCE PRICE 19/11, carriage 3/6 extra.

8 STATION PRE-SET COIL UNITS. Any 8 coils, mixed and 1 long wave station may be selected by a single switch. Very compact. Dimensions: 7in. x 4in. x 1½in. Supplied complete with full data and circuit.
LASKY'S PRICE 15/-. Postage 1/6 extra.

Ex-A.M. MOVING COIL HAND MICROPHONE AND HEAD SETS. Robustly constructed. Price 6/6 per pair, post free.

CHOKES. 60 mA. 10-20 Henrys. Price 3/11 each, post 6d. extra.

MULTI-RATIO OUTPUT TRANSFORMERS. Standard type. Price 3/11, post 6d. extra.

MIDGET OUTPUT TRANSFORMERS SUITABLE FOR PENTODE. Price 3/6.

MINIATURE OUTPUT TRANSFORMER SUITABLE FOR PERSONAL RECEIVERS. Price 3/- each.

THE VIEWMASTER

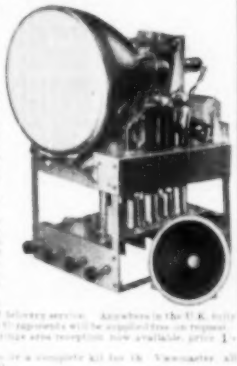

The television set you can build at home from standard parts.
★ London or Midlands Operation.
★ Brilliant high definition black and white picture.
★ Superb reproduction.
★ Uses 9in. or 12in. Cathode Ray Tube.
★ Table or Console Model.
★ Incorporates all the latest developments.
Television for the home constructor at its finest.
Send today for 1/- CONSTRUCTION ENVELOPE, a 20-page booklet crammed with top-rate information and all the necessary data, also a full-size working drawing and stage by stage wiring instructions. Model "A" for use in London and Home Counties.
Model "B" for use in Sutton Coldfield Area.
PRICE 5/- per copy, post free.
See the View Master working. Demonstrations every day during transmitting hours 9in. and 12in. Cathode Ray Tubes in stock for immediate delivery. Manufactured to Marconi, Mullard, G.E.C., Brimar. PRICES: 9in., £11 6 10, including Tax; 12in., £15 2 5, including Tax; Brimar 12in. discontinued, £16 1 4 including Tax.
If you cannot call to collect Cathode Ray Tubes, please enquire for details of our special delivery service. Anywhere in the U.K. fully insured. Complete Price List of Viewmaster components will be supplied free on request. Full details for building a pre-amplifier for fringe area reception now available, price 1/- per copy.
We can supply by return of post any item, or a complete kit for the Viewmaster, all components always in stock. NO WAITING.

BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL CARTON. EX-A.M. UNIT TYPE 567 C.W.W.
Containing 11 new valves: 2 5Z4G, 2 EC50, 1 VU39, 1 EA50, 1 EF50, 1 EF36, 2 VR78 (voltage calibrator).
Dozens of various components, including high voltage condensers, chokes, potentiometers, resistances, condensers (8 mfd. 500 v.w.), etc.
Totally enclosed in metal case, size: 17in. x 11½in. x 8in. Weight 35 lbs.
LASKY'S PRICE 49/6. Carriage 5/- extra.

BRAND NEW BY FAMOUS MANUFACTURERS. RADIO-GRAM MOTORS. 200/250 volts 50 c/p.s. Motor supplied complete with magnetic pick-up and turntable. Adjustable and chart.
LASKY'S PRICE 75/-. Carriage and insurance 5/- extra.
FINEST QUALITY. YOUR MONEY REFUNDED IF DISSATISFIED.

EX. AMERICAN AIR CORPS RECEIVER TYPE BC312D.
Supplied complete with 10 valves: 2 12SK7, 1 12SQ7, 2 12SG7, 2 12SA, 1 12SH7. Also 6 ring in type crystals. This compact unit is built in a black metal case, cradle mounted, with removable sides. Size: 10in. x 7in. x 10in. Weight 15 lbs.
LASKY'S PRICE 39/6. Carriage 3/6 extra.

RECEIVER TYPE 1084A. BRAND NEW. LASKY'S PRICE 59/6. Carriage 7/-

CIRCUITS NOW AVAILABLE. Circuit of the 1084A. Price 1/- post 3d. extra.
Conversion of the Receiver type 1084A to television sound and vision. Price 1/6, post 3d. extra.
Full circuit diagram giving suggested sound and vision television receiver, time base and all associated circuits, power packs, etc., utilising available ex-Government equipment (1084A VCR97, etc.). Price 2/-, post 3d. extra. Data for London and or Sutton Coldfield now available.
Owing to the great demand for these circuits we have been able to reduce their prices, and now offer the complete set of 3 for 4/6, post free.

CO-AXIAL CABLE SUITABLE FOR TELEVISION.
Screened, ¼in. diam. Price 9d. per yard, post extra.
Screened, ½in. diam. Price 8d. per yard, post extra.
Twin balanced feeder. Price 5d. per yard, post extra.
Any length cut to your requirements.

R.F. UNITS, Type 24. Brand new. In maker's crating. Frequency 38-50 Mc/s. Contains 3 EF50 valves and complete tuning.
LASKY'S PRICE 12/6, post 1/6 extra.

MAINS TRANSFORMERS. All 200/250 volt, stripped primary.
SRT 1. 350-0-350 volts, 80 mA. 6.3 v. 3a., 5 v. 3a. Price 15/-, post 1/6. Semi-shrouded, black finish.
SRT 5. 350-0-350 volts, 150 mA. 6.3 v. 3 a., 5 v. 3 a. Price 16/11, post 1/6. Semi-shrouded, black crackle finish.
SRT 6. 350-0-350 volts, 200 mA. 6.3 v. 3 a., 4 v. 4 a. Price 42/-, post 1/6. Heavy duty transformer. Tapped input 190/250 volts, 50 c/p.s.
SRT 7. 350-0-350 volts, 250 mA. 6.3 v. 3 a., 5 v. 3 a. Price 37/6, post 1/6. Chassis mounting.
SRT 8. 500-0-500 volts, 250 mA. 6.3 v. 3 a., 5 v. 3 a. Price 32/-, post 1/6. Upright chassis mounting.

MBA/2 MIDGET MAINS TRANSFORMER. 200/250 volts 60 mA. 6.3 v. 2a. Price 12/6, post 1/- extra. Fitted with voltage adjustment plugs.

PHOTO ELECTRIC CELLS, Type VA96. Receives 100 volts D.C. at Peak A.C. to function. Price 12/6 each, postage 1/6 extra.

MINIATURE 2-GANG TUNING CONDENSERS. 0.0005 mfd. Size: 2in. x 1½in. x 1½in. spindle.
LASKY'S PRICE 5/- each, post 6d. extra.

MIDGET I.F. TRANSFORMERS. 465 Kc/s. Iron cored. Size: 2½in. high, 1½in. wide, 1½in. deep.
LASKY'S PRICE 8/6 per pair, postage 6d. extra.

THROAT MICROPHONES. LOW LEVEL No. 2, Mk. II.
LASKY'S PRICE 2/11 per pair, postage 6d. extra.

CONDENSER BARGAINS. BRAND NEW STOCK. FULLY GUARANTEED. FAMOUS MANUFACTURER'S SURPLUS. 8 mfd. 500 v.w., 3/- each, 4 for 20/-.
Other electrolytic condensers now in stock:
4×32 mfd. 450 v.w., at 4/11 each.
16×16 mfd. 450 v.w., at 4/11 each.
1×8 mfd. 500 v.w., at 4/11 each.
16×8 mfd. 500 v.w., at 4/3 each.
High voltage smoothing condensers 4/6 mfd. 4 Kv. working. Price 1/6. Very high voltage T.C.C. Vitamol 8/6 mfd. 7 Kv. working. Price 4/6.

EX-A.M. COMMUNICATION RECEIVER TYPE R.1155.

Brand new in Wood Transit Case. Complete with 10 valves. Aerial tested before despatch. Circuit: R.F.O., A.V.C., R.F.AMP., 2 I.F. stages, Magic Eye, etc., 3 wave bands. Frequency range 18.0-7.5 Mc/s., 8.5-2.9 Mc/s., 1,500-600 Kc/s., 500-200 Kc/s., 200-75 Kc/s.
LASKY'S PRICE £12 10/-, carriage (in transit case) 7/6 extra. Full modification data and circuit details supplied free with each Receiver.

RECEIVER TYPE 69. Perfect condition, contains 6SK7G and 4 EBC33 valves. Dozens of useful components, condensers, resistances, etc. Also rotary transformer type 19, input 12 volts a.input, H.T. 250 volts, L.T. 12 volts. Totally enclosed in metal case, size: 10in. x 7½in. x 9½in.
LASKY'S PRICE 34/-. Carriage 5/- extra.

6 and 12 VOLT VIBRATOR TRANSFORMERS SUITABLE FOR CAR RADIOS. Price 6/11 each.

LOW VOLTAGE METAL RECTIFIERS HEAVY DUTY 12 volts 5 amps. Price 27/6 each. Post extra.

STRONG METAL CHASSIS DRILLED FOR 4-VALVE HOLDERS I.F. TRANSFORMERS, etc. Size 12in. x 4½in. x 2in. by 1½in.
LASKY'S PRICE 1/- each. Post 4d.

MINIATURE I.F. TRANSFORMERS. TYPE M400B. 465 Kc/s. Iron dust cored. Size 1½in. high by ⅞in. by ⅞in.
LASKY'S PRICE 12/6 per pair. Postage 6d. extra.

Send a 1½d. stamp with your name and address (in block letters please) for a copy of our current stock list giving full details of our Ex-Government Radio Radar and Surplus equipment. THE LASKY'S RADIO BULLETIN.

370 HARROW ROAD, PADDINGTON, LONDON, W.9 (Opposite Paddington Hospital)

TELEPHONE: CUNningham 1979. Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. half day 1 p.m.

E

BAFFLED?

THEN LET US HELP YOU!

CONSTRUCTORS of home televisors such as "VIEW MASTER," "ELECTRONIC ENGINEERING," etc., have often encountered unexpected snags. If you are resident in the London area bring your troubles to us. We will issue a report and estimate for 10s. **This service is for personal callers only and no correspondence can be exchanged.** We believe we are the only firm offering such a comprehensive technical service to the amateur TV constructor.

EVERYTHING FOR THE ENTHUSIAST

YOU can obtain ALL your TV requirements from us. Here is a small selection from our huge and varied stocks —

AERIALS from **21s. Co-axial** cable, 75 ohm, new and standard, **9d.** per yard.

R1355 Units, RF units, rectifiers and numerous other essential units and components in stock.

ALL "VIEW MASTER" PARTS, ETC., ALWAYS AVAILABLE

More Bargains for May

RECEIVER R1155A. Brand new, unused, and in transit cases. A very high grade communications receiver at a modest price. The R1155A is renowned the world over. **£11.19.6** carriage paid to your door.

INDICATOR UNIT 116H. A more up-to-date version of the famous 6A and the ideal Indicator Unit for **TV** use. The **R1355** and **116H** make an admirable combination. The 116H we offer is brand new, in impeccable condition and contained in manufacturer's or original wooden crate. Contents include x VCR97 tube, valves—4 of EF50, 3 of EB34 and innumerable useful components associated with a superb unit of this type. Only **£4.10.0** plus 7/6 carriage and packing.

RECEIVER R1355. The **TV** constructor's most popular unit—as specified in the booklet "Inexpensive Television." Valve line-up: 8 of SP61, 1 of VR92, 1 of VU120 and a 5Z4. In new and unused condition but slightly store soiled. Order while still in stock. **59/6** carriage paid.

PERFORMANCE METER No. 2. For A.C. mains 230 v. operation and complete with the following valves: 2 of EF50, 1 of ECS2, 1 of 5Z4G, 1 of EA50 and a Y63 (Magic Eye). Brand new condition. Housed in a robust grey steel case size 9 x 10 x 8in. Constitutes a most desirable basis for an amplifier, measuring bridge, etc. A recent purchase enables us to offer these once again at **£2.5.0** carriage paid.

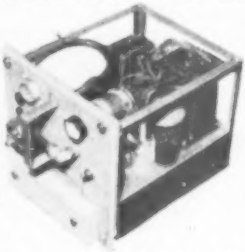

RECEIVER TYPE 81B. Housed in case size 10in. x 8in. x 7in. Frequency coverage 2.4 to 6.7 mcs. Output 560 kcs. The dial is exceptionally well-geared and calibrated. Valve line-up: 4 of EF50, 1 of EBC33, 1 of EF39, and 1 EA50. With standard .0005 two-gang condenser. In good condition. **29/6**, plus 2/6 carriage and packing.

RECEIVER UNIT 25/73. Receiver portion of the TR1196. Valve line-up: 2 of EF39, 1 of EK32, 1 of EBC33 and 2 EF36; and one pair of 460 kcs. I.F. Transformers, resistors, condensers, etc. Easily and rapidly converted to a fine superhet receiver. Circuits and conversion data supplied. In unused and exceptionally good condition. **27/6** each carriage paid.

LIMITED NUMBER OF HRO's FOR CALLERS ONLY. PRICES FROM £3.10.0

ALL YOUR REQUIREMENTS FROM A 1/20th WATT RESISTOR TO A COMPLETE TRIPLE-DIVERSITY RECEIVER ARE OBTAINABLE FROM US. PAY US A VISIT. A COMPETENT TECHNICAL STAFF IN ATTENDANCE AND AT YOUR SERVICE.

Best Buy at Britain's

CHARLES BRITAIN (Radio) Ltd.

11, UPPER SAINT MARTIN'S LANE, LONDON, W.C.2 TEM 0545

3 minutes from Leicester Square Station (up Cranbourn Street)

Shop Hours: 9-6 p.m. (9-1 p.m. Thursday). Open all day Saturday

OUTSTANDING OFFERS

for the discerning buyer

RADAR PROJECTION PATTERN VGI INDICATORS 59in. x 34in. x 35in. Picture diameter 24in. Horizontal viewing screen. Range Accuracy ± 1%. Bearing Accuracy within ½ degree. Nett weight 1,000 lbs. Gross weight in original unopened crates 1 ton. 9 only. All Wireless Colleges should have one of these. Price on application.

RECEIVER TYPE R1155A. Frequency coverage in five switched bands. 18-7.5 Mc/s, 7.5-3 Mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s. Complete with all valves, 100-1 ratio slow motion drive, B.F.O., A.V.C., etc. Power requirements: 210 v. D.C. approx. at 60 mA.; 6 or 6.3 v. D.C. or A.C. at 3.5 A. Price **£9.10**.-. Carriage 7/6. Perfect condition.

R1132A RECEIVERS. 11 valves 100-126 Mc/s. Grey cabinet, 19in. x 11in. x 10in. Brand new in original crates. **£4.19.6**, plus carriage 5/-. 12 only available.

12 VOLT CAR RADIO. Comprises a type 26 ARC5 Ex.-Govt. Command Receiver modified to tune 200-500 metres. Receiver has six valves and is supplied complete with 5in. loud speaker. Dimensions, 11in. long 4½in. wide, 5½in. deep. Ignition suppressor included. No aerial supplied. Any standard pattern suitable. Price **£5.10**.-. Carriage paid.

ABK1 10-VALVE IFF RECEIVERS. Have 6 of 6SH7, 2 of 6H6, 2 of 7193. Motor Gen. with reduction gear, 3 relays, etc. New condition. **20**/- each, carr. 5/-.

TELEVISION PRE-AMPLIFIER. Just the thing you have been looking for. This Ex.-Govt. One Valve pre-amplifier is of very high sensitivity and makes an amazing improvement in vision and sound reception in all fringe areas. Available for Birmingham Transmission only. Ready for Instant Use. Very small dimensions. Length 4in. Width 3½in. Chassis Depth 1½in. Overall depth to top of valve 4½in. Fitted with EF50 valve. Ideal for the "Inexpensive Television Receiver" or the "Electronic Engineering Television Set" and any set where 6 v. LT and around 200 v. HT can be obtained. Can be used on any Commercial set if fitted by a competent TV engineer. Co-Ax Input and Output sockets. 3 connections only to Power supply. HT, Common and LT. Price less than that of a new EF50 valve. **15**/-, postage 1/-. All tested and guaranteed before despatch.

ANTENNA REELS TYPE R1142. Motorised; 1/13th h. motor. 23 V. 5 A. Detachable pulley, elaborate reduction gearing instantaneous positive stop; works well on only 12 V. Ideal for rotary beams. Brand New in Sealed Cartons. Price **30**/-. Post 1/-.

PLUG-ON POWER PACKS, for Command Receivers **BC453/4/5.** No alterations to wiring. Complete with rectifier valve **59**/-, carr. paid.

MODULATOR UNITS. Type 64. 7 valves: 2 VR91, CV73, CV85, 2 VU133, VT604A, 3 relays, 4/5 2,000 V. 1/.05 3,500, and many useful parts, **18/6** each, plus carr. 5/-. Brand New.

CONDENSERS. SPECIAL OFFER 25, 1 μF. 1,000 V. and 25, 25 μF. 500 V. Brand new goods, **10**/- the lot of 50, post paid.

TU6B TUNING UNITS. Equal to Brand new (less outer case). 3-4.5 Mc/s. **10**/-. Carr. 1/4. TU5B complete, 1.5-3 Mc/s. **22/6**. Carr. paid.

BC456B 40W. MODULATOR UNITS. 1625, 1215, VR150 Stabiliser, 3 supersensitive relays, modulation trans., etc. Brand new in sealed cartons. 10 only. **19/6** plus 1/4 carr. Few used models perfect condition less valves. **7/6**, post paid.

PAMPHONIC PA SPEAKERS. 10in. in handsome maroon metal cabinet. In original makers' packing (not surplus). **55**/- each. Less than cost.

BC306 AERIAL TUNING UNITS. Aerial Variometer; 5 way Ceramic 3 pole switch, Porcelain lead through insulators, precision slow motion dial; 3, 6,000 V. 80 μF. condensers. **10**/- each, carr. 1/4.

AIRCRAFT COMPASSES. Diameter 6½in, depth 4in. Perfect condition, **21**/-, carr. paid.

SCR522 TRANSMITTER CHASSIS. Less valves. (Modulation trans., choke and crystal switch, included but not fitted) **19/6**, carr. 3/6. (Exceptional offer).

VCR97 6" CATHODE RAY TUBES. Brand new in original crates. **£1.9.6**. Carr. 1/4.

MOVING COIL HEADPHONES combined with Moving Coil Microphone. Res. 50 ohms each unit. **5**/-, post 9d.

APN4 INDICATORS. Black Crackle Case. Multitude of valuable components. Size 18 x 12 x 9. No valves. **15**/- each. Carr. 5/-.

PROMPT DELIVERY AND SATISFACTION GUARANTEED AS ALWAYS.

2½d. stamped envelope must accompany all enquiries.

Lists Available

H.P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House

Estd. 1935

55 COUNTY RD., WALTON, LIVERPOOL, 4

Tel. **Aintree 1445** Staff Call Signs, G3DGL, G3DLV

M·O·S

DELIVER AND GUARANTEE the

BURGOYNE 7-SECOND SOLDER GUN

We can offer immediate delivery of the BURGOYNE SEVEN-SECOND SOLDER GUN, and all guns which **WE** supply are **GUARANTEED** for **2 YEARS.**

How often do you leave your soldering iron on all evening, or all day, so that when you want it it will be ready for use? How often do you have to re-tin the bit? How much electricity do YOU waste?

The Burgoyne Solder Gun gives you heat in seven seconds, and what is more important, all the heat where you want it. When it's not in use it's cold, so there's no waste of electricity, no danger of burning yourself by picking up the "wrong end," no constant re-tinning.

The Burgoyne Solder Gun is easy to handle, being a balanced instrument. It is robust, and practically everlasting. No elements to burn out, and no mica to crack with the danger of making the bit "live."

The Burgoyne Solder Gun has been supplied to over 70 leading manufacturers, and exported to over 30 countries. Owing to a blocked export order, we can offer this fine instrument at only 52.6 (makers' list price 79.6).

52/6

Makers list price 79/6.
A.C. ONLY.
200-250 volts 50 c/s.

WE GUARANTEE FOR 2 YEARS every gun we supply.

POWER UNIT 35A.

Designed for use with the R1155 receiver, and also giving the heater voltage for the 1154 transmitter. Complete with all smoothing gear. INPUT 18 volts, OUTPUT 7.2 volts at 13 amps. and 220 volts at 110 mA.

The motor generator unit used in the power unit is the type 31, and can be very simply converted to a ¼ h.p. mains motor.

The converted motor generator is of sufficient power to drive a small power drill or any small machine. Can also be used for a grindstone and buff.

EACH POWER UNIT 35A IS SUPPLIED WITH A FULLY ILLUSTRATED LEAFLET ON CONVERTING THE MOTOR GENERATOR TO A ¼ H.P. MOTOR.

BRAND NEW, IN MANUFACTURERS' CARTONS, each, **20/-**
Carriage and packing 5/-.

IMPEDANCE MATCHING UNIT MC385-D.C.

These units measure 2 × 1 × 1in. and provide the solution to obtaining a match between low impedance phones and high impedance output.

AS NEW, **2/-** each ONLY.
Post and packing 6d.

Although designed for use with the HS33 and HS38 headsets, it has been found that these units give a much better match with any low impedance phones, giving greatly increased sensitivity of operation.

Each unit contains a miniature transformer, and if desired the connections can be reversed so that high impedance phones can be matched to low impedance line or output. The high impedance match of these units is 2,000/4,000 ohms.

A standard jack plug is fitted to the body of the unit, and also a standard jack plug socket.

A PAIR OF HIGH IMPEDANCE PHONES FOR 5/3.

Because of a special purchase of the impedance matching units illustrated above, we can offer a pair of brand new DLR1 headphones and a matching unit for the bargain price of **5/3.**

The DLR1 headphones are 30 ohms per earpiece, diaphragm type. By use of the matching unit supplied they can be used for all applications requiring high resistance phones.

BRAND NEW **5/3.** *Post and packing 9d.*
DLR1 low impedance phones ONLY for **3/6** (brand new). *Post and packing 9d.*

1.5 KV ELECTROSTATIC METERS.

A 2½in. round, projecting mounting meter, ideal for measuring all voltages above 600 volt but not exceeding 1,500 volts. Negligible current consumption.

BRAND NEW IN CARTONS, each, **15/-**
Postage 9d.

CV1297-RL18.

The RL18, which is the same as the Mullard EC53, is a VHF triode fitting into the same diode holder as the EA50, having its grid and anode connections brought out to wire top leads. The RL18 is only a little larger than the EA50 diode.

This valve finds applications in both MF and VHF signal generators and as a local oscillator in converters. By use of a suitable circuit oscillation can be secured up to a frequency of 300 m/cs. (tuned line).

Due to its small physical dimensions, the RL18 allows a neat and compact layout to be obtained and it can be used in place of most small triodes of the 6J5/6C5 class, with a consequent reduction in the size of the instrument. The rated voltages of the valve are as follows: Heater 6.3v. at .25 amp.; anode 200v., anode current 7.5 milliamperes.

BRAND NEW, boxed inc. Valveholder, each, **5/6**
Postage 9d.

HIRE PURCHASE FACILITIES on the

COLLARO RC500

AUTOMATIC RECORD CHANGER.

The RC500 Automatic Record Changer has been designed for simplicity and reliability at low cost. Pick-up can be moved to any position while the machine is stationary, or raised without interfering with the mechanism. It is impossible to jam the mechanism, and it should never go out of adjustment.

The machine will play nine 10in. or nine 12in. records, and can be used to play single records.

The RC500 is for operation on 100/125 or 200/250 volts A.C. (50 c/s.) ONLY. It is NOT suitable for use on D.C.

The RC500 is supplied with a crystal pick-up giving high fidelity reproduction. The pick-up is fitted with a twin ball race ensuring perfect freedom of movement. The whole unit is spring mounted in three positions, and incorporates check springs to eliminate acoustical feed back.

H.P. TERMS £4 DOWN,
6 MONTHLY PAYMENTS OF **22/6.**

Note: no interest is charged on these facilities. 10 per cent discount for cash.

RECEIVER TYPE 184.

This receiver contains a tuneable Klystron type CV67. The tuning range of the CV67 is 3,226 to 3,370 m/c., and it has a dissipation of 10 watts. The reflector is connected to the top cap and the resonator to the frame. The 4-volt heater, grid, and cathode connections are to a standard international octal holder. Also contained in the unit are four EF50; six SP61; one VU111; approximately 60 assorted condensers and 60 assorted resistors, four pots; platinum contact relay, I.F. strip, etc.

For those interested in centimetric or television work, this unit is a first class bargain.

AS NEW, **45/-.** *Carriage and packing 7/6.*

500 YARDS BEAM RANGE

FOCUSING TORCH!

Type H
22/6
complete.
Post free.

This latest addition to our range of American Type Focusing Torches uses five U2 batteries and the illustration shows the comparison in size between battery and torch. NO OTHER TORCH ON THE MARKET WILL GIVE SUCH A SUPER LONG BEAM!

Solid brass nickel-plated construction with pull-out carrying loop in base and spare bulb container.

ADJUSTABLE RING FOCUS HEAD.

This torch is specially suitable for protective purposes. Spare batteries 5d. each. Spare bulbs 6d. each.

Our other long beam torches as previously advertised are still available from stock.

Overall length 15in. FULLY GUARANTEED.

18 A MULTIRANGE METER WORTH 18.6?

This D.C. portable test instrument covers the following ranges: 0-1.5v., 0-3v., 0-30v., 0-300v., 0-3,000v., 0-60 m.a., and 0-5,000 ohms, when converted.

As supplied the following voltage ranges are covered: 0-1.5v. and 0-3v. and also ohms and m.a. By means of the resistors and terminals which we supply, the voltage ranges are extended to cover 0-30, 0-300, and 0-3,000v.

A fully detailed and illustrated leaflet is supplied with each kit, giving precise instructions on the conversion. The conversion can be effected in a very short time.

Post free.

METER ONLY **18/-**
KIT AND INSTRUCTIONS ONLY **3/11**
METER, KIT AND INSTRUCTIONS **18/6**

PATCH CORDS.

A brand new 3-way linking cord fitted with P.O. jack plug at each end. Length 3ft. 6in. **2/-** each (*6d. postage and packing*).

INDICATOR MODULATION TYPE 2.

An easily adapted valve voltmeter. Supplied complete with 3in. dia. scale 0-500 microammeter. Calibrated for percentage modulation. Frequency coverage 2.4-6.2 m/cs. In carrying case. ONLY **29/6.** *Carriage and packing 3/6.*

ANODE LOADING A.F. CHOKES.

60 m.a. rating. Ideal for anode loading where a capacity feed output line is required.
2/6 each (*9d. postage and packing*).

D.C.-A.C. CONVERTERS.

In BLUE-GREY STEEL CABINET. Input 24v. D.C. Output 230v., 50 c/s., 100 watts. Single phase. Complete with plug, leads, clips, and fitted with 3-way 15 amp. socket and control switch.

BRAND NEW. *Carriage paid.* **£4 10 0**
Slightly soiled (exterior) models at **£3 10 0**

MODULATOR 51.

These radar Modulators represent one of the best bargains we have offered. They contain nine valves, the types being one VU120, two VR65, one 6V6, one 807, three CV57, one VU508; a 24v. Blower motor suitable for conversion for use on A.C. mains; 18 assorted condensers including .01 mfd. 5 Kv. types; 30 assorted resistors from 50 watts to ¼ watt types; three high voltage variable resistors, valve bases, relay, transformers, etc., etc. The whole contained in a case measuring 19 × 12 × 9in.

BRAND NEW.

A real "GIVE AWAY" at **17/11.** Callers only.

W.B. JEWEL EXTENSION SPEAKERS.

In handsome cream cabinet, comprising 5in. P.M. speaker with multi ratio output transformer and volume control. BRAND NEW **36/-.** Post and packing 2/-.

HAVE YOU SEEN THE NEW M.O.S. NEWSLETTER?

Now in magazine style. Brings you the news and goods of the world. Send 6d. for specimen copy.

Terms: Cash with Order

M·O·S MAIL ORDER SUPPLY CO.
The Radio Centre
33 Tottenham Court Road
London, W.1. MUS. 6867

U.E.I. CORPN.

The Radio Corner, 138, Grays Inn Rd., London, W.C.1

(Phone : Terminus 7937)

We offer below many items for the Television and Radio Constructor. Note them carefully—it will pay you.

RECEIVERS R.1355. As specified for "Inexpensive Television." Complete with all valves and a copy of the booklet. New condition. ONLY **55 -** (carr., etc., 7 6).

R.F. UNITS TYPE 25, specified with above for London Area Station. ONLY **17 6** (postage, etc., 1 6).

R.F. UNITS TYPE 26, specified for Birmingham Station, now all sold, but we can supply one of the other R.F. Units with full details of Modification, which has been fully tested some 70 miles from Sutton Coldfield. BRAND NEW IN CARTONS. ONLY **25 -** (postage 1 6).

INDICATOR UNITS TYPE 6. As specified for "Inexpensive Television." Complete with valves and VCR97 C.R. tube. BRAND NEW IN CRATES. ONLY **90 -** (carriage, etc., 7 6).

INDICATOR UNITS TYPE 62. Contains 16 valves SP61, two of EB34, two of EA50 and VCR97 C.R. tube. ONLY **75 -** (carriage, etc., 12 6).

TRANSFORMERS for "Inexpensive Television" can be supplied as follows : Time Bases and Vision Transformer, 350-0-350v. 160 m.a., 5v. 3 a., 6.3v. 6 a., 6.3v. 3 a., ONLY **36 -**. Sound Receiver Transformer, 250-0-250 v. 100 m.a., 5v. 3 a., 6.3v. 6 a., ONLY **27 6**. E.H.T. Transformer for VCR97 tube, 2-0-2v. 1.1 a., 2-0-2v. 2 a., 2,500v. 5 m.a., ONLY **30 -**. POSTAGE 1 6 per transformer, please.

MAGNIFYING LENS for 6in. C.R. tube. Brings up the picture size to approx. that given by a 9in. tube. First grade, oil filled. ONLY **25 -** (postage, etc., 1 6)

TELEVISION PRE-AMPLIFIER. A first class T.V. Pre-amp. can be built with very little trouble from the ex-R.A.F. Amplifier Unit 6046 6050, which contains two valves VR91. Supplied complete with full modification data for London and Sutton Coldfield. ONLY **22 6** (postage, etc., 1 -).

TELESCOPIC AERIALS as used on Canadian 58 Walkie Talkie. 15in. in length extending to 103in. Completely enclosed in metal case with dust cap. ONLY **12 6** (postage, etc., 1 -).

HEADPHONES AND MICROPHONE SET, also as used on Canadian Walkie Talkie. A pair of first grade High Resistance phones fitted with rubber noise excluders, and a beautiful carbon mike. ONLY **12 6** (post etc., 1 -).

WAVEMETERS CLASS D. Another purchase of these superb instruments. Covering 1.9-8.0 mc/s., and within G.P.O. requirements for accuracy, these are an ideal meter for the Amateur Station. Complete with two valves ARTH2 and two vibrators, in metal case. Please note that this form of supply cannot be varied. Intended for use on 6v. D.C., but easily adapted for use on 6v. A.C., full details being supplied. A suitable mains transformer is available at **7 6** extra to the cost, of ONLY **79 6** (packing and carriage 2 6)

RADAR RECEIVER R1084. An ideal unit for constructing a superhet T.V., suggested details being supplied with every set. Contains a 30 mc/s. I.F. Strip, two valves EF54, one of ECS2, seven of EF50, one of VU39A, one of HVR2, and one of EA50. Brand New in maker's cases. ONLY **75 -** (carriage 10 -).

RECEIVER TYPE 25. The receiver portion of the TR.1196. Covers 4.3-6.7 mc/s., and makes an ideal basis for an all-wave receiver, as per "Practical Wireless" August issue. Complete with valves types EF36 (2), EF39 (2), EK32 and EBC33. ONLY **25 -** (carriage 2 6).

INDICATOR UNIT 162B. Contains 6in. tube VCR517 and 3in. tube VCR139, three valves SP61, one of VR17, two of EA50, two of D1, and Klystron CV67. Also fitted with 0-1 m.a meter and a blower motor. ONLY **67 6** (carriage 12 6).

Cash with order please, and print name and address clearly.

MIDLAND INSTRUMENT CO.

FOR GOVT. SURPLUS STOCK ETC.

ALTIMETERS, [illegible] 25 -, post 9d. **ASTRO COMPASSES**, new boxed, 10 -, post 1/-. **MAGNETIC COMPASSES**, type P.8, new boxed, 10 -, post 1/-. **RUBBER VACUUM PUMPS**, rotary vane type, new boxed, 20 -, post 1/-. **HEYWOOD AIR COMPRESSORS**, rotary type, delivers 600 lbs. sq. in., new boxed, 25 -, post 1/-. **MOTOR BLOWERS**, 24 v. A.C./D.C., fitted enclosed centrifugal fans, unused, 10 -, post 1/6. **MAGSLIPS** 3in. **TRANSMITTER MK-11**, 3 can be used in parallel from 24 v. A.C. or in series from 100 v. A.C. single phase, when the shaft of one is coupled to the other with fabric drive, 3 for 15 -, post and packing 1/6. **MAINS TRANSFORMERS**, [illegible] **MOTORS**, [illegible] **R.D.C. ROTARY CONVERTORS**, input 24 v. D.C., output 230 v. 50 cycle, single phase A.C. at 75 watts, each wheel in perfect order, 35 -, carriage 5/-. **HEADPHONES**, balanced armature high resistance, new boxed, 7 6, post 9d. **TELEPHONE CABLE D-8**, twin twisted rubber covered and braided, yellow black, 1mm. wound on wooden drums, new unused, 25 -, carriage 5/-. **FLEXIBLE DRIVES**, [illegible] approx. 1in. dia., male 1/2 screw fitting, suitable for light power transmission, tachometers, remote control etc., 3 different lengths, brand new unused, 1ft. 1 6, 2ft. 2 6, 3ft. 3 6, 4ft. 4 6, 5ft. 5 6, all post 9d. **L.F. CHOKES**, [illegible] **SERIES MOTORS**, [illegible] **P.V.C. FLEXIBLE**, twin flat figure 8, [illegible] post 9d. **SELECTOR SWITCHES**, [illegible] **MASTER OSCILLATORS TYPE M1-10487-A**, [illegible] **PERMANENT MAGNETS**, very powerful, fitted handle, [illegible] 50 -, carriage 1/6. **UNIDA SPRAY GUNS**, [illegible] 12 6, carriage 2/6. **COIL PACKS**, 3-waveband, [illegible] 19 6, post 9d. **TELEPHONE SETS**, [illegible] 20 -, post 9d. **TELEPHONE HANDSETS**, [illegible] **RU-19 DUAL COIL SETS**, [illegible] **UNIT SELECTORS**, [illegible] **POLARISED BUZZERS**, [illegible] **BELLS**, [illegible] **SANTON ROTARY SWITCHES**, [illegible] 3 6, post 9d.

Also hundreds of other items. Send S.A.E. for full current list. Trade C.O.D. service is cancelled for the time being.

MOORPOOL CIRCLE, BIRMINGHAM 17.

Tel. : HARborne 1308 or 2664

YOUR RADIO CAN BE "WELL-CONNECTED" IN A FEW MINUTES!

As specified for conversion of the Type 25 unit of the T.R. 1196

With only 5 connections and 1-hole fixing, the job is done in double quick time, yet efficiently and cheaply. A simple answer to your coil and switching problems—is this **Midget** Coilpack. Full circuit diagrams and instructions are supplied with each pre-aligned coilpack.

OSMOR

'Q' COILPACKS

A Portable Superhet Battery model is also available.

Send stamp for FREE circuits and our new lists of coils, Coilpacks and matched radio components, also "**Bargain Bulletin.**"

Trade and Export enquiries invited.

OSMOR RADIO PRODUCTS LTD. (Dept. W.6)

BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY

Telephone : Croydon 1220

CLYDESDALE

Bargains in Ex-Services Radio and Electronic Equipment

Brand New in original wood case.
Ex. Cdn. Army. SUPPLY UNIT RECTIFIER, FO.71 No. 4; TRANSMITTER.
Inputs: 110 v. A.C. 50/60 cys. 1.7 K.V.A.
Outputs: 2100 v. H.T., 375 mA.; 500 v. H.T., 400 mA.; 385 v. regulated; 450 v. H.T. line; 275 v. H.T. line; 415 v. neg. bias; 250 v. neg. bias; 150 v. neg. bias; 80 v. neg. bias.
The unit consists of 3 complete power supplies, one of which provides various stabilized L.V. supplies. All are fed via double chokes, condenser input circuits. 8 Valves: 4 866-866A's, 5Z3, 6SJ7, 2 6SA's, plus 1 v. time delay and VR150/30 stabiliser.
Other components include: Power Trans. 2100-500-0-500-2100 v.; Power Trans. 450-0-450 v., 13 v. ct., 6.3 v. ct., 6.3 v.; Fil. trans. 2.5 v. ct., twice, Fil. Trans. 6.3 v. (thermal starter). Chokes, 2.15H. 375 mA., 15H. 450 mA., 2.15H. 110 mA., 20H. 162 mA., plus various H.V. condensers, resistors, etc.
The complete unit mounted in metal case with lid, 2ft. 6in. x 1ft. 6in. x 1ft. finish olive-drab crackle with shock absorbing feet. Weight, 420 lbs.

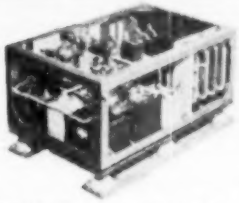

CLYDESDALE'S PRICE ONLY £16 CARRIAGE PAID

Brand New in maker's original carton.
TRANSMITTER TUNING UNITS.
Each having vernier tuning dial; variable capacitors. Tank coil unit on ceramic former; ceramic switch; R.F. chokes, etc. In metal cabinet 17½ x 7½ x 8in. Finish black.
TU5B, 1500-9000 kcs.
CLYDESDALE'S PRICE ONLY 22/6 each. CARRIAGE PAID.
TU6B, 3000-4500 kcs. TU7B, 4500-6200 kcs.
TU8B, 6200-7700 kcs.
CLYDESDALE'S PRICE ONLY 17/6 each. CARRIAGE PAID.
TU26B, 200-500 kcs.
CLYDESDALE'S PRICE ONLY 10/- each. CARRIAGE PAID.

16 FOOT SECTIONAL AERIAL WITH BASE.
Comprising 4 lengths copper tubing, tapering from ¾in. to ¼in., each section sleeved into the other with insulated bases.
CLYDESDALE'S PRICE ONLY 10/6 CARRIAGE PAID.

INFRA RED IMAGE CONVERTER CELL.
Sniperscope.
Snooperscope.
The famous wartime "Cat's-eye" tube used in "Tabby" for night sniping and observation.

Provides a Silver Caesium Oxide Screen for the conversion of Infra-Red rays to visible rays, using an Infra-Red light source. Data provided. Dimensions overall: dia. 2in. x 1¾in. Screen dia. 1¼in.
CLYDESDALE'S PRICE ONLY. 12/6 each. POST PAID.

R.C.A. VIBRAPACK.
Input, 6 volts.
Variable output: 200-240 v. 40-50 mA.
Controlled by 4 position output switch. Complete with 6p UX synchronous vibrator, OZ4 rectifier, in metal case, 4½ x 4 x 6in.
Unused, but vibrator contacts stuck due to long storage.
CLYDESDALE'S PRICE ONLY. 29/6 each. POST PAID.

Ex. Tank Corps. MORSE KEY.
Enclosed type with knee straps, dimensions 5½ x 2 x 2in., with lead and jackplug, easily removed from case. Key and Plug Assembly No. 5.
CLYDESDALE'S PRICE ONLY 2/11 each. POST PAID.

Brand New, in maker's carton.
Ex. U.S.A.S.C. CRYSTAL MULTIPLIER, TYPE MI-19468.
A frequency Multiplier to cover 2-20 mcs. with 807 and spare (2 valves) 0/10 mA grid current meter, variable condenser, calibrated micrometer control, etc., external power supply required (no X'cals supplied). In metal case 13in. x 10in. x 6in., with Instruction Books.
CLYDESDALE'S PRICE ONLY. 39/6 each. CARRIAGE PAID.

VIEWMASTER TELEVISION.
Circuit and data, 8/-.
Components Kits available.
State whether London (A) or Sutton Coldfield (B).

Brand New in maker's cartons.
AN ARC-5-SCR-274-N. Ex. U.S.A.A.F. "COMMAND" RECEIVER UNITS, R-26 ARC-5 or BC-454.
Frequency 3.0-6.0 mcs., 100-49 metres.
I.F. 1415 kcs. 6 valves, 12SK7, R.F., 12K7 F.C., 12SK7 1st I.F., 12SF7 or 12SK7 2nd I.F., 12SR7 det. B.F.O., 12A6 output, 3-gang tuning condenser (remote controlled) complete unit (less dynamotor) in metal case 11 x 5½ x 5in. Input 24 v.
CLYDESDALE'S PRICE ONLY 50/- POST PAID.
Circuit of R-26 ARC-5 available at 1/3 post paid.
Circuit of BC-454 A & B available at 1/3 post paid.

MEDIUM WAVE CONVERSION COIL ASSEMBLIES.
Cat. H67 for BC-453 or H68 for BC-454 or H69 for BC-455.
CLYDESDALE'S PRICE ONLY. 10/- each. POST PAID.

Brand New, Ex. U.S. Navy, in maker's original carton.
CONTROL BOX CCT-23155, equal to U.S. Army, BC-496-A.
For Two Command Receivers, with dual tuning and volume controls, switches, Inlet and Outlet Points, black crackle finish box. Dim.: 6½ x 4 x 1¾in.
CLYDESDALE'S PRICE ONLY. 10/6 each. POST PAID.

JEFFERSON TRAVIS VIBRAPACK POWER SUPPLY U.F.I.
Input, 12 volts.
H.T. output, 150-120 volts, 30-40 mA.
Choke Capacity smoothed, also grid bias and L.T. outputs.
Complete, self-contained vibrator unit, with synchronous vibrator, etc., mounted on a chassis 7in. x 3in. x 1¾in., enclosed in a black metal box 7in. x 6in. x 4in., with circuit inside, plus 1½ yards of cable with croc. clips for batt. connections.
Unused, but vibrator contacts stuck due to long storage.
CLYDESDALE'S PRICE ONLY. 19/6 each. CARRIAGE PAID.

Ex. R.A.F.
BATTERY AMPLIFIER UNIT A1134A.
A two-stage, two-valve, VR35 (24QP) VR21 (210HL) inter-comm. and Tx. mod., pre-amplifier with transformers, etc. (less batteries). Could be simply modified for use as gram amplifier or input pre-amp. Used, good condition.
CLYDESDALE'S PRICE ONLY. 15/- each. POST PAID.

BRAND NEW JUNCTION PANEL 10D/13336.
Type 19D for A1134 and A1134A units, has 10-way and 4-way sockets, six 2-way and two 3-way terminal blocks, DPST switch, mounted on board 6 x 4½in.
CLYDESDALE'S PRICE ONLY. 4/6 each. POST PAID.
Circuit of A1134A available at 1/3 post paid.

Ex.-R.A.F. Flying Helmet type.
ELECTRO-MAGNETIC MICROPHONE.
E16 for A1134A, etc., approx. impedance 50 ohms. Dim.: 2in. dia. x 1¼in. with switch, short lead and 2-way socket. Brand New.
CLYDESDALE'S PRICE ONLY. 5/6 each. POST PAID.
E16T. This microphone, with midget matching transformer, are available at
6/6 per set, post paid.

Ex. Royal Navy.
SOUND POWERED TELEPHONE

No batteries required, gives long service without attention. Complete, with warning indicator lamp and generator, giving a high-pitched note, which can be heard through any noise. Where a number of units are used the lamp would indicate which one is being called. Dim.: 7½in. x 9in. x 7½in. overall, for wall mounting. Designed for ships' use, but suitable for the home, office and factory.
CLYDESDALE'S PRICE ONLY. 27/6 each. CARRIAGE PAID.

Brand New, Ex. Army. No. 3 CARBON HANDSET MICROPHONE.
E.12, with handle switch, flex and standard Jackplug.
CLYDESDALE'S PRICE ONLY. 7/6 POST PAID.

Brand New in maker's original carton. U.S.A. made by R.C.A.
INSTALLATION KIT FOR WS-No. 19.
Complete kit comprises Con. 12 pt. 12ft. 2in. 12W. cable with 12W. Skt. each end, disco 6ft. Bin. Con. 4 pt. with 4ft. 1in. 6-way cable and 6W. Skt. one end, co-ax. con. 2 1·5W. Jumper leads, 2 satchels, 3 sets M.C. Mic/H'phone Assy., Aerial Base, Beam Ant. mtg. Control Unit No. 2 with O.P. leads, control unit No. 1 with 6W. lead. Junction Box No. 3 with O.P. leads, and 6W. lead, mtg., etc., etc., screws, nuts, washers, plus Installation and wiring diagrams.
CLYDESDALE'S PRICE ONLY 42/6 each. CARRIAGE PAID.

Ex. Army. WS-18 RECEIVER UNIT.
A 4-valve superhet chassis. Range 6·9 mcs. (52-33.3 metres), with ARP12 (VP23) F.C., 2 ARP12's I.F. and ARB (HL23DD) Audio Det. Osc., 2nd det. and A.V.C. slug-tuned I.F. trans. 465 kcs., etc. The complete receiver mounted on a chassis 8½ x 5 x 1in., all control front panel 9½ x 5½in. Unused, good condition.
Power requirements approx.: 3 v. 0.2 a. L.T. 120 v. 15 mA. H.T., 1·5 v. bias.
CLYDESDALE'S PRICE ONLY 17/6 CARRIAGE PAID.
Circuits for WS-18 Rcvrs. Mk. I, II and III available at 2/3, post paid.
Circuits for WS-18 R/T. Mk. II and III available at 4/6, post paid.

Order direct from —
CLYDESDALE SUPPLY CO. LTD. 2 BRIDGE STREET GLASGOW · C.5
Phone: Bridgeton 2191/2
Visit our Branches in Scotland, England and Northern Ireland

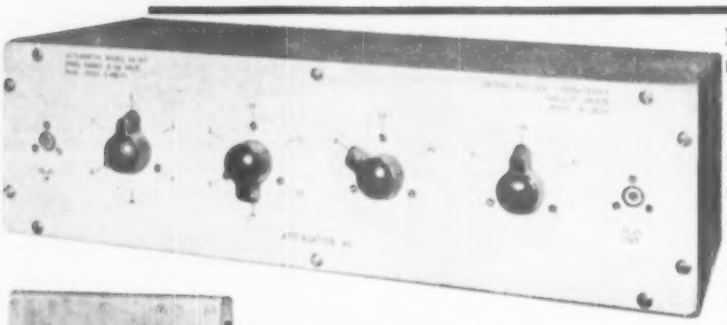

FIXED PADS
UP TO 60 db

★

STEP TYPE
UP TO 100 db

★

ACCURACY 1%
D.C TO 50 Mc/s

AN ENTIRELY NEW
RANGE OF

CO-AXIAL ATTENUATORS

For particulars of these and our full range of measuring instruments, write to :—

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone : RADlett 5674-5-6

STOP
AND SEND FOR DETAILS
LOOK INTO ALL THE FACTS
LISTEN TO RECORDINGS

Grampian Direct Disc Recorder, Type S.R.2, used in conjunction with Grampian Transportable Recording Amplifier, Type R.A.2 See models above. List Price (combined) £237

DON'T CHOOSE UNTIL YOU HAVE ENQUIRED ABOUT

GRAMPIAN DISC RECORDERS

Grampian recording equipment has been supplied to The Egyptian State Broadcasting Corporation, Swedish State Broadcasting Corporation, G.P.O. Research Station and other authorities, and to a large number of private Recording Studios.

GRAMPIAN REPRODUCERS LTD.

Manworth Trading Estate, Feltham, Middlesex
'Phone: Feltham 2657 Grams: REAMP, FELTHAM

G2AK **This Month's Bargains** G2AK

Vibrator Packs, 12v. input. Output 300 v. at 100 mA, fully smoothed, **19/6**, plus 1/6 post.

Vibrator Packs, 6 v. input. Output 150 v. at 40 mA, complete with all smoothing (metal rectifiers), **17/6** each, plus 1/6 post.

Tub. Condensers, .01 5 kv. **1/6**; .02 8 kv. **2/-**, plus post 6d.

Special for AR88 Users. Matching speakers, 2.5 ohms, black crackle case. **£3 15s.**, carr. paid.

AR88 Spare Crystals for D model only, 455 kcs., **15/-** each.

Power Transformers. 320-320 130 mA, 6.3 v., 5 a. C.T., 5 v., 3 a. Primary 200-250 v., 50 c. Drop through type, **22/6**, post 1/6.

Special Offer. Four 807 valves for **£1**.

H.T. Dry Batteries. These are heavy duty 157 v. plus 5.2 v. in hermetic sealed metal cases. 10½in. x 4½in. x 4in. Weight 11 lb. These are special mercury type batteries and are first-class value at **8/6**, plus 1/6 postage.

H.R. Headphones, brand new, **8/6** per pair, plus 1/- postage.

Moving Coil Hand Microphones, with switch, **3/11** each.

Transformer, for above, **2/-** each.

500 Micro-amp Meters, scaled 0-600, **5/-** each.

13/t. ¼in. dia. Co-Ax Cable, with Pye plug each end, **2/6**, postage 6d.

70 Ohm ¼in. Dia. Co-Ax Cable, **8d.** per yard. Postage 1/6 any length.

70 Ohm Twin Feeder Cable (not screened), **5d.** per yard.

300 Ohm Twin Ribbon Feeder, **5d.** per yard. Postage 1/6 any length.

Moving Coil Headphones, with Moving Coil Hand Microphone, **6/-**, postage 1/-.

PLEASE PRINT YOUR NAME AND ADDRESS

CHAS. H. YOUNG, G2AK

All Callers to *110 DALE END, BIRMINGHAM*
Mail Orders to *102 HOLLOWAY HEAD, BIRMINGHAM*
Telephone: MIDLAND 3254

The world's greatest display of labour-aiding equipment

OLYMPIA LONDON 6-17 JUNE, 1950

BRITAIN'S MECHANICAL HANDLING EXHIBITION

The 1950 Mechanical Handling Exhibition at Olympia, London (Grand and National Halls) will provide a practical answer to the world-wide demand for mechanical aids in the battle for greater output and lower costs of production. Covering a total floor area of more than 200,000 square feet, it will be the world's largest exhibition of its kind.

The diversity of exhibits will include :—

CONVEYORS · ELEVATORS AND RUNWAYS · CRANES (*FIXED AND MOBILE*) · AERIAL ROPEWAYS · INDUSTRIAL POWER TRUCKS · DUMPERS AND MECHANICAL SHOVELS · COAL, COKE AND ASH HANDLING PLANTS · FORK LIFT TRUCKS · STACKERS · HOISTS AND PULLEY BLOCKS · PNEUMATIC HANDLING PLANTS · SACK AND BAGGING MACHINES · SCREENING AND WASHING PLANTS · CONVEYOR BELTS, GEARS, MOTORS AND ACCESSORIES OF ALL KINDS.

The Exhibition will embrace all forms of bulk and package handling, and many of the exhibits have never before been on view at any exhibition.

The very wide range of equipment in operation will demonstrate the potential increase in production resulting from the adoption of mechanical handling methods.

Working exhibits will include :—

DISCHARGE OF RAILWAY WAGONS BY TIPPERS · HANDLING OF GRAIN, CEREALS, ETC. BY PNEUMATIC SUCTION PLANTS · CONVEYING OF MATERIALS BY VIBRATING CONVEYORS · THE PNEUMATIC TUBE SYSTEM OF CONVEYING · CONVEYANCE AND STACKING OF GOODS BY FORK LIFT TRUCKS · CONVEYING, ELEVATING AND DUMPING OF BAGGED MATERIALS BY PORTABLE CONVEYORS · CONVEYING OF COMPONENTS TO INFRA-RED AND ENAMELLING OVENS · SHIP UNLOADERS.

The Exhibition is organised by "Mechanical Handling", the Journal of Britain's handling industry, with the support of the leading trade associations.

CONVENTION AND INDUSTRIAL FILMS

At the Convention, each day except June 17th, well-known authorities and large-scale users of mechanical handling plant will discuss its application to many different industries. At a special theatre in the Exhibition films will be presented showing various aspects of mechanical handling.

PLAN YOUR VISIT NOW

No industrialist or production executive should miss this demonstration of the value of modern methods in meeting rising costs, increasing production per man hour and improving overall efficiency. Please fill in the form below.

ORGANISED BY

"MECHANICAL HANDLING" *The Journal of Britain's Handling Industry*

AN ASSOCIATED ILIFFE PRESS LTD. PUBLICATION

SEND NOW FOR FULL DETAILS

To: "Mechanical Handling," Dorset House, Stamford Street, London, S.E.1., England

Please send me further particulars of the 1950 Exhibition, with Application Form for free admission tickets to the Exhibition and Convention, Travel information, etc.

Name ..... *Date* .....

Firm .....

Address .....

"WEYRAD"

INTRODUCE TWO NEW I.F. TRANSFORMERS

TYPE P.5

Of medium size and high efficiency. Permeability trimmed with cores accessible from two opposite sides of can. 460/470 Kc/s operation.

Size ..... 1⅞" × 1⅞" × 3½"
Nominal "Q" 130

TYPE P.5.A

Physically similar to the P.5, but having a switchable tertiary wind which enables variable selectivity to be obtained by changes in the coupling factor.

Write for full details and prices

WEYMOUTH RADIO MFG. CO., LTD., CRESCENT STREET, WEYMOUTH, DORSET, ENGLAND.

BRITISH SOUND RECORDING ASSOCIATION.

A PRIVATE

EXHIBITION

OF

SOUND RECORDING — REPRODUCING AND AUDIO EQUIPMENT

DEMONSTRATIONS — FILMS — MOBILE VANS

WALDORF HOTEL, ALDWYCH, LONDON

To be opened on Saturday, 20th May, 1950
BY
MR. FRANK PHILLIPS (B.B.C.)
AT 2.30 p.m.

Sunday, 21st May, 1950. 10.30 a.m. to 6 p.m.

Admission to Non-Members by Catalogue
Price 1/2d. Post Free, or at the door

Brochure and Membership Application Form from —
Membership Secretary —
H. J. King, 48, Mount View Road, North Chingford, E.4

FT.30J TRANSMITTERS Manufactured by Federal Telephone & Radio Corp. U.S.A. Four RF units operating on C.W. simultaneously at 3 kW output each. 2 Mc to 20 Mc.
RCA TRANSMITTERS. Type E.T. 4332B, 2 Mc to 20 Mc. 350 W. c.w. 250-w. r.t. two B13's output. Separate speech amplifier. Two 805 modulators. Rectifier—four 866's.
HALLICRAFTERS. BC610 with speech amplifiers, aerial tuning units, tuning boxes and coils.
HIGH SPEED TELEGRAPH equipment. "Boehme" (U.S.A.). Up to 400 words per minute on line or wireless. New. Working demonstration on request.
AR.88.D's. SX 28's. HRO's with 5 or 9 coils, power packs.
METAL RECTIFIERS type 78. Max. D.C. output at 36 v. 56 amp. Supply voltage. 200/250 v. Brand new.
All above items in excellent working conditions with new valves. Large stock of transmitting condensers, valves, crystals and other components. Alignment and repair of communication receivers and all other amateur equipment.

P.C.A. RADIO

THE ARCHES CAMBRIDGE GROVE, LONDON W.6. 'Phone RIV. 3279
Branch, 170, Goldhawk Road, W.12

RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialise in

AMATEURS' WINDINGS, TRANSFORMERS ALL TYPES, CHOKES, PICK-UP COILS, INSTRUMENT COILS, Etc.

Highest workmanship **Good Delivery**

☆

RADIOMENDERS, LTD.

Television & Radio Apparatus, Transformer & Coilwinders.
123-5-7 Parchmore Road, THORNTON HEATH, SURREY
LIV 2261. Trade enquiries invited. Established 16 years.

HIGH FIDELITY AT ANY LEVEL

Does your reproducer sound thin at low volume? Fit our fully compensated volume control and by automatically correcting for scale distortion experience real listening enjoyment with only one control, giving correct bass output from a whisper to full volume. Follows well known Fletcher Munson loudness curves. Fully screened will replace existing volume control send for leaflet CW50.

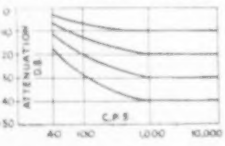

38/6
pos. paid
c.w.o.

C. T. CHAPMAN (Reproducers) Ltd. FLAxman 3217
RILEY WORKS, RILEY STREET, CHELSEA, S.W.10
Manufacturers of VENTEX cabinets

TRANSFORMERS

230V. A.C. INPUT
150-0-150 volts at 100 mA
Size 3¼" x 3¼" x 4½"

4/-
Plus 1/- post

SIMILAR
150-0-150 and 0, 10, 20, 30 and 40 volts
All at 70mA. Size 2½" x 3¼" x 3¼"

MONEY BACK GUARANTEE

FIELD'S 438-437 STRATFORD ROAD BIRMINGHAM 11

The TRUE TEST *of an instrument is* RELIABILITY

The "SELECTEST" is built for **the main job in radio servicing** — that of measuring VOLTS, AMPERES and OHMS — *and nothing else.* That was the intention. The result is that it does this job accurately and reliably — and will continue to do it. *There is no better instrument for the job.* You can rely on a "SELECTEST" — it's a G.E.C. Measuring Instrument.

Cat. No. M4111. Price **£16.5.0**

VOLTS	AMPS	OHMS
A.C. 7.5, 15, 75, 150, 300, 600, 750, 1,500	A.C. 75, 150, 750mA, 1.5, 7.5, 15 A.	1,000
D.C. 150mV, 300mV, 1.5, 3, 15, 30, 75, 150, 300, 600, 750, 1,500 V.	D.C. 1.5, 3, 15, 30, 150, 300 mA, 1.5, 3, 15, 30 A.	10,000
		100,000
		1 Megohm.

Please send for leaflet No. X334 F.S.D. 1 mA

SELECTEST

MULTI-RANGE MEASURING INSTRUMENT

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2

ALEC Davis SUPPLIES Ltd.

18, TOTTENHAM COURT ROAD,
LONDON, W.1.

Phone: MUSeum 2453, 5439

SHOP HOURS: *Mondays to Fridays 9—5.30 Saturdays 9—1*

FULL MAIL ORDER FACILITIES :: PLEASE ADD POSTAGE

"VIEWMASTER"
ALL COMPONENTS AS SPECIFIED IN CONSTRUCTIONAL ENVELOPE

	LONDON £ s. d.	BIRMINGHAM £ s. d.
Constructional Envelope, with Blueprints	5 0	5 0
T.C.C. Condensers	6 15 0	7 0 0
Whiteley Components	6 5 0	6 5 0
Plessey Equipment	5 12 6	5 12 6
Westinghouse Rectifiers	3 2 6	3 2 6
Wearite Coils and Chokes	1 2 0	1 10 0
Colvern Wire-wound Pots	19 3	19 3
Morganite Carbon Pots	9 0	9 0
Morganite Resistors	1 6 9	1 6 0
Belling & Lee Accessories (including fuse)	8 6	8 6
Bulgin Accessories	12 6	12 6
G.E.C. Neon	2 9	2 9
5 Mullard EF50 Valves (at 21/4 each)	5 6 8	5 6 8
1 Mullard EB91	12 10	12 10
1 Mullard EBC33	11 7	11 7
1 Mullard ELL33	12 10	12 10
2 Mazda 6K25 (at 12/10 each)	1 5 8	1 5 8
1 Mazda 6F28	1 1 4	1 1 4
1 Mazda 6P25	15 10	15 10
9in. C.R.T. Mullard, Mazda or G.E.C.	11 6 10	11 6 10
12in. C.R.T. Mullard, Mazda or G.E.C.	15 2 5	15 2 5

ELECTRONIC ENGINEERING TELEVISOR

Comprehensive Television Catalogue now available, giving full itemised parts list for London and Birmingham editions 7d. post free

BULGIN PRODUCTS (Every Item Boxed)—

Heavy Duty Wire-wound Resistors on ceramic formers. May be tapped at any point. Approximate rating 20 watts. Available in following values: 50R, 300, 750, 1,000, 5,000, 10,000 ohms each 3/3

Miniature Signal Lamp Fitting for single-hole fixing. Takes standard M.E.S. lamp, available in three colours—red, green and orange each 2/3

Rotary Toggle Switches—Double Pole On/Off 4/-
Double Pole Change Over 4/-
Single Pole On/Off 3/3

Normal Toggle Switches—Double Pole Change-over 3/9
Single Pole Double Throw 3/3

Plugs and Sockets—Octal Cable Plugs 2/-
Flush-mounting Mains Plug and Socket 2/-

WESTINGHOUSE AND STANDARD TELEPHONES RECTIFIERS

W6	36v Peak Input, 250 microamps max. F.C. Current	3/5
WX1	6v Peak Input, 100 microamps. max. D.C. Current	3/5
HT49	120v 20mA D.C. Output Battery Eliminator type	10/6
H18-30-1R	420v 150mA D.C. Output, Standard Power Pack type	21/9

LATEST ADDITIONS

Acos Microcell Pick-up for standard or microgroove records Type GP20	£3 11 5
Goodmans Axiom 22. The 20-watt High Fidelity speaker incorporating the latest exponential twin cone assembly	£12 13 0
Stentorian Concentric Duplex Loudspeaker complete with matching transformer and filter condenser	£6 6 0
Collaro Mixed Record Changer for A.C. mains operation. Type RC49	£14 6 8

IS YOUR HOBBY RADIO?

. . . . *Silverstone's Cater for That*

Perhaps your other hobbies or your work come under the headings of:

PHOTOGRAPHY, DRAWING-OFFICE, ELECTRICAL ENGINEERING, ETC?

Then you will find Silverstone's cater for them all. In fact, we claim to have the largest range of Government Surplus Goods in the country.

You will realise this if you send 2½d. stamp for our beautifully produced illustrated Catalogue, full of Government Surplus Bargains, all carrying the famous Silverstone guarantee of absolute satisfaction or money unconditionally refunded.

UNIVERSITIES, MUNICIPAL AUTHORITIES, GOVERNMENT DEPARTMENTS AND EMINENT INDUSTRIAL FIRMS ALL OVER THE WORLD HAVE BOUGHT, AND CONTINUE TO BUY FROM SILVERSTONE'S.

WE SHOULD WELCOME THE OPPORTUNITY OF BEING OF SERVICE TO YOU.

H. SILVERSTONE

20, OXFORD ROAD, MANCHESTER 1

Tel.: CENtral 2001

PRATTS RADIO

1070 Harrow Road, London, N.W.10

Nr. S'BURNS LANE. Tel. LADbroke 1734.

MODEL AC10E £8.18.6

AMPLIFIERS. College general purpose units. **Model AC10E** 10 watt 4 valve unit. Neg. feedback. Separate Mike stage, separate inputs for mike and gram. with twin faders. Tone control. Complete in case with chrome handle. **£8.18.6.** (Carriage 5/- extra).

Model AC18E, 6 valve unit with output of 18½ watts. Push-pull output with feedback over 3 stages. Separate mike stage. Inputs as AC10E. Twin faders and tone control. Complete with case and chrome handles. **£13.19.6.** Carr. Paid. **Model U10E**, 6 valve unit for DC/AC mains, specification as AC18E. 10 watts output with feedback over 3 stages. Separate mike stage. **£11.11.-** (carriage 5/- extra). All above have outputs to match 3, 8 or 15 ohm speakers, and are ready for immediate use. Input volts average, mike .003, gram., 3 v. No preamplifier required. **Model AC8C**, Record/Radio amplifier, 5 valves P.P. output with feedback over 3 stages. Output 8 watts. Chassis model. Supplies H.T., L.T. for tuning unit. Output to 3, 8 or 15 ohms speaker. **£9.18.6.** Carriage paid. **Model AC4C**, A.C. or **U4C**, AC/DC, 3 valve chassis units. 4 watts to 3 ohms. **£4.19.6** (carr. 2/6 extra). Stamp for fuller details. Above are as supplied to Clubs, Schools, Hospitals, etc.

TRANSFORMERS. E.H.T. 2,500 v. 5 mA. 4 v. 1½ A. 4 v. 2 A. C.T. (for VCR97) input 200-240 v. (in 10 v. steps) **27.6**; 2 x 350 v. 6 v. 6 A. 5 v. 4 A. 4 v. 3½ A. **35.-**; 2 x 350 v. 80 mA. 6 v. 4 A. 5 v. 2 A. **22.6**; Heavy-duty output, 30 watt 10 ratio (20:1 to 140:1 C.T.) **23.9**; Ultra midget for 154, 354, etc., **3.11.** Filament 115/230 v., 6 v. 2½ A., **7.6.** All above are new manufacture, not surplus.

SPEAKERS. Truvox 2½in. **17.6**; 8in. **14.6**; 12in. **37.6**; Truvox Sup., **10.-**; Plessey 8in. **11.9**; 10in. **18.6**; Rola Mains Enc., 6½in. 700 ohm, **10.-**; Goodman's 8in. P.M., **16.6**; 10in. **28.6**.

CONDENSERS. 8:1 500/550 v. C/b'd. Blocks 8 mfd. **3.3**; 8 + 8, **4.9**; 8 + 16, **6.-**; Midget 450 v. Can type, 16 + 8, **3.9**; 8 + 8, **3.6**; 16 + 16, **4.-**; 25 mfd. 25 v. **10d.**; 2 mfd. 350 v. **1.-**; 1 x 350 v., **2.6** doz.

VARIABLE CONDENSERS. 2 gang .0005, **4.3**; 3 gang, **6.9**; with feet and long shaft, presents 50pf. ceramic, **4d.**; 100 and 500 pf., **1.3.**

MISCELLANEOUS. U.S. Octal bases, Paxolin, **4d.**; Volume controls, all values, SK to 2 meg., w. switch, **4.6**; less switch, **2.9**. Voltage droppers with ½ and 2 sliders, 3 A. 800 ohm or 2 A. 950 ohm **4.6**; Chokes (not W.D.) 60 mA. 20 Hy. 400 ohm, **6.6**; 90 mA. 10 Hy., **10.6**; 150 mA., 10 Hy. **14.3.** Bulgin jack sockets, **1.6**; Plugs, **9d.**; Wearite "P" coils, **3/-** each. Wearite I.F.'s Standard **10/-** each.

Open 10-6. Callers very welcome. Nearest Tube Kensal Green. All Goods New and Unused. C.O.D. or C.W.O. Post Free over £1.

NEON TEST PROD

★ FOR 200-250v. MAINS.

HAS A 1,001 USES.
CONSUMES ONLY HALF A MILLIAMP.
FULLY SHROUDED WATERPROOF.

Tests on A.C. & D.C.

NEW

A.F. BULGIN & CO. LTD.
BYEPASS RD., BARKING, ESSEX

THE *Fidelia*
LUXURY 8-VALVE
RADIOGRAM CHASSIS

Pressure-to-life variable selectivity, infinite impedance or active electronic band-and-treble controls, push-pull triode output stage, wavelength coils, twin-unit and 3 band-pass tuner. Audio amplifier response 30-15,000 c/s. Bass, treble and volume controls operate on gramo. Weight 14 lb. Dimensions 12 inches. Price £21.5.-

ELECTRO *Acoustic* DEVELOPMENTS

18 BROAD ROAD, WILLINGDON, SUSSEX

ELECTRONIC INSTRUMENT

METAL CASES and CHASSIS

and General
SHEET METAL WORK

CHASE PRODUCTS (Engineering) LTD.
27, Packington Road, South Acton, London, W.3.
Tel.: ACOrn 1153/4.

THE IDEAL MICROPHONE FOR TELE-COMMUNICATION

MODEL
C 51
MOVING-COIL
MICROPHONE
BY

Designed and developed essentially for G.P.O. handsets, with mobile tele-communication and P.A. work in view, LUSTRAPHONE Model C.51 is fast establishing itself wherever a good microphone is called for. It provides maximum intelligibility at extreme range and under adverse conditions, and is used extensively by Broadcast Engineers and others needing quality and dependability. Available as inserts units, or complete hand instrument. Data sheet on request.

LUSTRAPHONE LUSTRAPHONE LTD.
14, BELSIZE LANE, N.W.3

Wireless World Classified Advertisements

Rate 6 - for 2 lines or less and 3 - for every additional line or part thereof, average lines 6 words. Box Numbers 3 words plus 1 -. Trade discount details available on application. Press Day: June 1950 issue, first Post Monday May 1st. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

UNIVERSAL ELECTRONIC PRODUCTS, 39, Marylebone High St., London, W.1. Wel. 4056.

SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 10-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.X.501) with independent bass and treble outputs provides the most satisfying standard of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.) and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements. [5352

BERNARDS, makers of television, radio, amplifier equipment, available disc recording, television time-base chassis and E.H.T. supply combined, 5 valves, complete, well tested, only new components used, £7 12 6. BERNARDS, 12, Chiverton Rd., Putney, London, S.W.15. Put. 7589. [5137

TV receiver, 26 valves plus stabilised power supply, choice of three stations (switched), designed for rack mounting but easily fitted in cabinet, unique automatic no blather deflection system, nearest offer to £100; also 95-102 m.c. F.M.-A.M. tuner, nearest £35. Full details from J. Mort, BCM/HIFIDEL, London, W.C.1. [5172

A SOUND investment.—Our 5-valve all-wave superhet radiogram chassis is really value for money, large fully illuminated glass scale in attractive colours, easy to fit and attachable to any radiogram cabinet, aerial tested output via speaker; price with 8in p.m. £12, with 10in p.m. £12/10. 2½d. stamp for illustrated leaflet. (Note ellipses.) Invited.—Bayly Bros., 46, Pavilion Drive, Leigh-on-Sea, Essex. [5360

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19, designers and manufacturers of Telrad quality amplifiers for commercial and domestic use, unique amplifiers, with exceptional quality, built to satisfy the discriminating ear, bass and treble independent controls, provide a wide range of variation to suit all recordings and varying acoustic properties of one room with another; £18, complete, full details on request.—Write, call or 'phone Livingstone 4078. [5019

CONNOISSEUR'S receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-1,500-metres, visible wide results on highly sensitive 10-valve receiver, comparable with any good communication set, or by change of switch, maximum fidelity reception of local stations on non-superhet receiver with high quality, 2-PX4 push-pull amplifier incorporating all refinements, bass and treble tone control, thermo to roll, whistle filter and gram input, etc., basic result R1155, write for details or call for demonstration. FEEDER units as above, for use with external high-quality amplifiers, R1155 specialists, receivers repaired and re-aligned, also modified as above, or to your requirements; R1155 circuit and values 2/- post free. R.T.S., Ltd., 5, Gladstone Rd., Wimbledon, S.W.19. Tel. Lib. 3568.

MIDCO radio, new product! R/F1 radio feeder, high quality superhet feeder (nominal impedance detector, tuning eye slide (pile dial with flywheel drive), M. and S. waves, aural fidelity control of IF selectivity, wide bands (with on locals narrow high gain on distant stations), bass and treble tone control in high gain pre amp stage, excellent for gram or radio, complete with 6 valves, £10. F.P1 amplifier power pack may be used with the RF/1 feeder, 5-10 watts high fidelity push-pull output, receiver and power pack, 2 NW valves, £15/10, price for PF/1 and RF/1, £25, carr. paid, delivery 10-14 days; also AA/5 5 watt amp., £5/10. AA/3T as with bass and treble tone control, £6/17/6. AA/10 10 watt push-pull (4/8 in-puts, £10. PA/12T superb portable amplifier for dance halls, etc., 12/15 watts, bass/treble control, twin input mixers, £14, any type of audio amplifier supplied for quotation. Details, enquiries, trade terms, gratis.—Midland Radio (Sol) Products, 19, Newcomen Rd., Wellingborough.

Partridge News

Now-hermetically sealed

IN OIL!

Illustrated is a typical Partridge Transformer (Type DN) in its Mumetal Screening Box. It is merely to remind you that all Partridge Precision Components (standard or "to specification" types) are now available as hermetically sealed units.

★

Then there's the 'PPO' range, designed to meet more fully the particular demands of push-pull output transformers where wide A.F. range with low distortion are vital.

FULL DATA ON REQUEST

PARTRIDGE TRANSFORMERS LTD

HOEBUCK ROAD, KINGSTON-BY-PASS
TOLWORTH SURREY
Telephone ELMbridge 6737 8

NEW RECEIVERS AND AMPLIFIERS

HALLICRAFTERS dual diversity receivers complete with power units and feed speakers, few only available.

MELBURY ADAMS MPG. GROUP, Ltd. (Hallicrafters), 46, Greyhound Rd., London, W.6. [5211

TWEETONE amplifiers and tuners built to your requirements by high quality experts from 5-30w., £5 upwards. For demonstration write or phone, A. S. Coleman, 1, St. Stephen's Gdns., W.2. Bay. 5661 after 7 p.m. [5176

REDUCED in price.—The Rolls-Royce of amplifiers—the R.T.M.C. version of the now world famous "Williamson" amplifier, no other amplifier in the world can equal this wonderful reproducer; neither can the quality of parts used or final performance be improved upon, hundreds of pounds have been spent in advertising this product and we therefore offer it with confidence and emphasise that the R.T.M.C. version still leads on performance and price any other similar make of advertised product. Owing to increased production we now offer the original improved 7-valve model at £25/10 and the 5-valve model with built-in pre-amplifier at £29/10 (covers extra), but right and for the best, compact performance figures or better still come and hear; to special requirements catered for, do not confuse with Junior model amplifiers, the R.T.M.C. version is still the best; tuners supplied, also speakers, etc. Write for full details to R.T.M.C. (Ealing), Ltd., Laurel House, 141, Little Ealing Lane, W.5. Ealing 5062. [5674

RECEIVERS, AMPLIFIERS, SURPLUS AND SECONDHAND

MARCONI V.R.L. and B.C.312 comm. receivers for sale, brand new. J. RAE, 38, Penn Rd., Wolverhampton, Staffs. [5316

NEW R1155 mod. output stage, power pack, rec. disc speaker, transit case, £11. Box 5364. [5254

MIDWEST receiver, 16-valve, 5 wavebands, 12in Magnavox speaker, 110 to 260v. a.c. mains supplied, £10/10.
WESTERN electric air-dry portable, £5.—6, Vale Croft, Pinner, Middx. [5497

HALLICRAFTER S-38, a.c./d.c., (1947 model), complete with transformer, £19/15.—Fowler, 12, Marquerite Terrace, London, S.W.5. Flaxman 7053. [5263

R1155 receiver, converted with output valve and attached power pack, laboratory tested, excellent condition, £12.—Liberty 1927, 137, Grand Drive, London, S.W.20. [5258

COMMUNICATIONS receivers (above) H.R.O.—Senior RX, in good condition, complete from £12/10, plus carr., also AR77, AR88, SX24 etc., state requirements to R.T. & T. Service, 54, Grove Green Rd., E.11. Lex. 4996. [5052

A PERFECT E.M.G. radio record player 1946 model, c.i.f. long used, wave of gold cabinet with separate R.M.S. speaker, desk, all for a.c. mains, complete except speaker, £35. Heard by appointment.—Letters first, Vickers, 46, Belgrave Rd., London, S.W.1. [5274

BC-348, built-in, 230v a.c. supply, excellent condition, £15/10, also BC-348, built-in (100/220v. a.c.) supply and speaker, valve line up, 2 12K7 RF, 12J7 FC, 12J5 FC osc., 1 12C7 IF and det., 12J5 BFO, 50L6 output and 5Z4 rect., suitable shipboard use, £20.—Morris, 37, Eastfield Rd., Bridlington. [5270

CANADIAN 103 Communication receiver 400.—16 metres, S.T.C., i.f. gain 7 valves, a.c. mains 10kms. 6-volt, 8ms. as new; Marconi 15-valve, 1-9-16 mcs. marine radio, crystal, check built-in speaker, Lakeha, Philco table radios, as new, all-wave a.c. mains 8ms., several a.c. d.c. amplifiers and tape recorders.—Collins Radio, 24, Lilyville Rd., S.W.6. Renown 4178. [5336

NEW LOUDSPEAKERS

WHARFEDALE series Super 3, 70/-. Super 5, C.S. 105/-, W.15 C.S. 145/-, W12 C.S. 150/-, W15 C.S. 240/-.
WB Concentric Duplex with transformer, £6/6.
WB Concentric Duplex, not transformer, £5/8/6.
BARKER Lion, £7/7. Barker 150, £10/18.
TRUVOX 303DA, £6/17/6.
GOODMANS Axiom 12, £6/8. Goodmans Axiom 22, £12/15.
ALL available from stock, post free; send orders to M.O. Dept.
ROGERS DEVELOPMENTS Co., 106, Heath St., Hampstead, N.W.3. Hampstead 6301.
FOR further attractive offers, see our advert. on page 40. [5291

LATEST type WB concentric duplex speakers, see p. 34, Feb. "W.W.", for full details, £6/6, complete with OPT. Wharfedale de luxe cloth suspension tripes, with new super magnets, Super 3 CS, £4, Golden 10 CS, £4/10, W10 CS, £7/5, 5 or 15 ohms, W12CS, £7/15, W15 CS, £12, 15 ohms only. Goodman Axiom 12, twin cone, £6/8, all post free from stock and fully guaranteed.
FRITH RADIOCRAFT, Ltd., Leicester. [5092

FURTHER INFORMATION ON THE NEW

HARTLEY-TURNER PRODUCTS

The two new very low distortion amplifiers are now ready. Except for different output power they are identical in circuit, layout and performance. Requiring 0.5 volt input, they give 20 or 14 watts output with extremely low distortion and phase-shift. Negative feedback is variable within wide limits, and operates over the whole amplifier and output transformer. Even a high percentage of feedback does not cause incipient instability on transients.

Power unit and amplifier are assembled on one chassis, 12 x 8in. Overall height is 8½in. Weight of 20 watt amplifier is 26 lb.; of the 14 watt, 23 lb. Power supply for a radio unit and a pre-amplifier is provided.

20 watt Amplifier £33 0 0
14 watt Amplifier £30 10 0

Tone-control and pre-amplifier unit

This unit is of very advanced design, and will give the proper correction for all types of pick-ups and recordings, whether standard or microgroove. Continuously variable bass and treble boost and cut are available without using resonant circuits. It can be used remote from the main amplifier, and where complete tone-control is required on the playing desk, it is ideal for the job. Can be used with any good amplifier. Price and further details on request.

New Lightweight Pick-up for all types of records. This pickup was primarily designed for microgroove vinylite records which demand extreme freedom of stylus movement and very light weight. We have evolved a system of interchangeable styluses which will never need replacing—diamond for shellac records and tungsten carbide for non-abrasive plastic records. In case the price of a diamond stylus is beyond the means of the user, a sapphire or tungsten carbide stylus can be used with shellac, but must not be removed until worn out. Until microgroove records are available on the British market this restriction of use is not important, but with our new pickup you will be ready for them when they come. The price is very low and will come as a pleasant contrast to the existing high cost of high-fidelity pickups. Price and further details on request.

Send today for free descriptive literature on these and our other products. In particular the Hartley-Turner 215 Speaker is winning hours of new friends in what is usually called the dull season of radio. At £9 it is absolutely unapproached for three-dimensional wide-range reproduction even in speakers costing much more.

If you have not read "New Notes in Radio" send for your copy today, price 2/6. It is now accepted as a completely honest and impartial guide to high-fidelity reproduction.

Subscribers to our technical data sheet service (2/6) will shortly receive new data sheets dealing with new developments.

H. A. HARTLEY CO. LTD.
152, HAMMERSMITH ROAD
LONDON, W.6. *RIVerside 7387*

NEW LOUDSPEAKERS

HI-FI reproducer cabinets and playing desks in oak, walnut, mahog., leaflets.—Cabinetmaker, 1A, Hayes St., Blackburn. [3930]

LOUDSPEAKERS, SURPLUS AND SECONDHAND

VOIGT H.C. corner horn bass chamber with twin tone speaker and field rectifier unit, all in good condition; £20.—Carter, 80, Winchcombe St., Cheltenham. [5255]

STOCK of P.A. contractor for sale: horn and cabinet speakers, hall microphones, stands, amplifiers, batteries, charger, pick-ups, Ammeter, etc., also Austin van, typewriter, bicycle; bulky, 211, Garratt Lane, S.W.18. [5315]

LOUDSPEAKERS in stock for immediate delivery, brand new by famous makers at abnormal prices. PM 5-in. 10/-, 6½in with transf. 12/-, 8in. 16/-, 10in. 22/-; mains energised 12in ohm field 30/-, 15/-, 10in with transf. 22/-, (add 9d post).—Rolling Lane, 70, Lord Avenue, Ilford. [4153]

NEW P.M. speakers, all carriage paid, 8in Celestion, 12/- each, or pair of 4 at 45/-; 10in Goodman with dust cover, 19/- each, or pair of 4 at 70/-; Rola metal in moulded bakelite frame, 6½in, 8in, 10in, all 27/-; 12in 54/-; 6 at 150/-.—Ward, "Corfield," West Cliff, Dawlish, Devon. [5015]

SELLING out: As new Voigt Twin, with French polished h.c. horn and power supply, 52ft rack, line panels, 4x6 mains lamp, with metal rectifier VG150 and p.w. supply, 40ft upward extension compments, 12 band rotary coil tuner, two stage, best offer.—Sir, Dartmoor Rd., Fleetwood. [5279]

TRANSMITTING EQUIPMENT

TR9 transmitter-receivers, these were formerly sold at £45 each, the remaining few to be cleared at 25/-, carriage paid.—THE STAMFORD RADIO Co., 195, Stamford St., Ashton-under-Lyne, Lancs. [4730]

TWO Finch Facsimile Transmitter/Receivers, type FHS 140-C, for sale, in good condition, used less than 50 hours.—Apply Box 3365. [5250]

HALLICRAFTER transmitters, Type HT44 (PCS10) complete to makers' latest specification, covering all frequencies from 1.5 to 30mcs, complete with speech amplifier, connecting cables, etc.; limited quantities only now available.

PANORAMIC adaptor, Type MCA44, British made, suitable fitment to any good-class communication receiver, in addition to all Hallicrafter models, immediate delivery.

HALLICRAFTER official sole agents in U.K. including service and spares.

MERLEY ADAMS MFG. GROUP, Ltd., 46, Greyswood Rd., London, W.6. Tel: Fulham 1802. Cables, Hallicraft, London. [5212

NEW DYNAMOS, MOTORS, ETC.

BATTERY chargers, 4 models 2-6/12v 1/2-4 amps D.C., also mains rectifiers, also Battery types special transformers, chokes, test gear, interval taxi heaters, etc.—The Bonner Electric Co., Ltd., Hoddesdon, Herts. [2214

JANETTE d.c. to a.c. rotary converters, 200/250 volts d.c. input, 200/250 volts, 50 cycles 1-phase, a.c. output at 500 watts, new, £20/500 watts £25, complete with smoothing for television and radio.—Johnson, 51a, Kensington Rd., London, S.E.11. Reliance 1412-5.

ALL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers, as actual manufacturers we will be glad to quote for any quantity for home or export.

REVOLVING armature alternators, with separate exciter generators 4-pole ball bearing, 1,500 rpm, output 250V, 50 cycles, 2.25kva, excitation at 24-30v price £29; ditto, 2-pole, ball bearing, 3,000rpm, 4kva output, £29.

ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 500v d.c. permanent magnet field, 20/-; ditto, input 28v d.c. and 1,250v, 10ma d.c. output, energised field, 35/-; ditto, input 24v d.c. output 500v, 50ma d.c. energised field, 35/-.

PETROL electric generator plants, comprising a J.A.P. No. 2a single-cyl. engine coupled by vee rope drive to an alternator, giving an output of 230v 50 cycles, 400 watts, with governed ignition and filtering on generator, eminently suitable for operating television and radio on farms, etc., price £40; such plants can be supplied with various outputs, a.c. or d.c., for other applications.

CHAS. F. WARD, Lordscroft Works, Haverhill, Suffolk. Tel. 253. [3059

ELECTRIC motors, new, 1ph, 230v a.c., 3 phase, shaft 1½in x 4in, 85/12/6, pair 4/6, bench grinders, ex-Govt., 230v a.c., fitted with 4in carborundum on radio or low interference 37/6; twin flat 10ft/ft cab tyre cable, flexible 1/-, per yd. 60-watt fluorescent control ballast 210-240v a.c., with tube holders, ready for use, 49/3.—Maiden Transformer Supplies, The Arcade, opposite G.P.O., George St., Richmond, Surrey. [4054

THE THEORY AND DESIGN OF INDUCTANCE COILS

By V. G. WELSBY
PH.D., A.M.I.E.E.
Post Office Research Station

Intended primarily to assist the circuit designer to select the coil design most suitable for a given purpose, and predict the changes to be made in a given design to obtain changes in performance; it will also appeal to electrical engineering students.

Illustrated 18/- *net*

MACDONALD & CO.
(Publishers) Ltd.,
43 Ludgate Hill, E.C.4.

NEW STC SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products, NOT surplus. Revised prices following makers' increase on Nov. 11 last. E.H.T. H4.200, W.W. Televisor, 29/6, H4/100, VR97, 19/6 post free.

HALF-WAVE RECTIFIERS.
16v., 2a., 7/-; 1a., 8/6; 2a., 9/10; 3a., 16/9, all post 6d. 4a., 18/-; 6a., 22/6, post 10d. 30v. 1a., 12/6; 2a., 14/8; 4a., 26/-; 6a., 38/6; 48v. 1a., 16/6; 2a., 21/-; 4a., 37/6; 6a., 54/-; 100v. 2a., 36/6; 4a., 69/-; 6a., 100/-, all post 1/-.

HALF-WAVE HEAVY DUTY, 7½in. SQUARE COOLING FINS.
16v. 5a., 22/6; 10a., 24/6; 30v. 5a., 37/-; 8a., 40/6; 48 v. 2.5a., 27/6; 5a., 50/6; 8a., 57/-, all post 1/-.

BRIDGE CONNECTED FULL WAVE.
17v. 1.25a., 12/9; 2a., 16/4; 2.5a., 21/3; 3a., 23/-; 4a., 26/-; 5a., 27/6; all post free. 33v. 1a., 19/6; 1a., 22/6; 1.5a., 29/6; 2a., 32/6; 3a., 37/6; 4a., 45/6; 5a., 46/6, all post 10d. 54v. 1.5a., 41/-; 2a., 50/-; 3a., 57/-; 5a., 70/-; 72v. 1.5a., 53/-; 2a., 64/-; 100v. 1.5a., 76/-; all post 1/-.

BRIDGE CONNECTED HEAVY DUTY 7½in. SQUARE COOLING FINS.
17v. 6a., 36/2; 10a., 46/-; 12a., 76/-; 20a., 84/-; 33v. 6a., 68/-; 10a., 75/-; 12a., 132/-; 20a., 148/-; 54v. 6a., 95/-; 10a., 106/-; 72v. 6a., 122/-; 10a., 138/-; 100v. 10a., 200/-, all post 1/4.

BRIDGE INDUSTRIAL FUNNEL COOL.
17v. 12a., 80/-; 20a., 92/-; 30a., 130/-; 50a., 198/-; 33v. 6a., 73/-; 10a., 84/-; 12a., 132/-; 20a., 152/-; 54v. 6a., 97/-; 10a., 114/-; 72v. 6a., 120/-; 10a., 144/-; 100v 6a., 168/-; 10a., 202/6, all post 1/6.

VALVE CHARGER REPLACEMENTS.
No wiring alterations. Philips & Tungar. 2-12v. 4a. Chargers, 200/250 A.C., £5/10/-, del. free.

Wholesale & Retail

T. W. PEARCE (Est. 18 yrs.)
66 GREAT PERCY STREET, LONDON, W.C.1
(Off Pentonville Rd., between King's Cross and Angel)

DYNAMOS, MOTORS, ETC., SURPLUS AND SECONDHAND

ROTARY convertor, perfectly smoothed, both d.c. and mech., 230 d.c.-250 a.c., 250w. offers.—Rom. 2847. [5208

E.D.C. rotary converters, 12v d.c. input 250v a.c. output 150 to 300 watts in cabinet. Sets.—Collins Radio, 24 Lilybole Rd., S.W.5. Renown 4178. [5507

PUSH-BUTTON start, Ohmax, new, unused, 30-36v, 1.25kw d.c. lighting and charging plant, 1 cylinder, 4-stroke, side valve, air cooled, petrol tank, only 900 rpm, ammeter, cut out, etc., £28 delivered.

CHORE HORSE push-button start, 15v 500watt d.c. plant, 4-stroke, air cooled, exhaust box, ammeter, auto cut out, field reg., etc., £12; used, good condition, tested.

J.A.P. No. 4a engine 1.4hp complete, petrol tank, etc., instruction book, tools, new and unused, this engine is not ex-Govt. or surplus, £14 del.

14-32v generators 200watt (for above J.A.P. engine) with, or without, control box, ammeter, cut out, etc.

WISCONSIN petrol engine 4-stroke air cooled by fan, side valve, 375cc complete, petrol tank, 1½gall. and filter, exhaust box, handle start, mag. impulse coupled 15mm pulley, detachable head, oil, piston 1¼in shaft, big end, magnetos plate fitted governor 2,000 rpm, guaranteed new unused external paint sealed, £12/10, and 10/- carr. Eng. and Wales; 12-18v 550watts heavy duty lighting plants complete with control box, petrol or T.V.O., 6v 35amp (at 10hr. rate), h. duty batteries in crate, new, £5/10 del., new but slightly damaged, perfectly usable, £3 del.; 12-36v 1½ 2kw units charging boards and field circuit reg., 4 12a charging circuits, 5mc ammeters, 1mc v/meter, switches, fuses, 2 var. res., 2 out outs steel case, new, crated, £4/15 del.; h. duty rubber covered cable 50mm 10mts 19/6; 25v 240watt lamps 2/6; 12v 350watt 5/-; new Selenium rectifier units 200/250v input, 160-200v d.c. output 1amp, steel case, 53/- and £3 each; Zenith res. 2/2, 1ea., 50, 10s. 10/6; p. free; see displayed add. page 76 for S.T.C. rectifiers.

PEANCE, 66 Gt. Percy St., London, W.C.1. [0014

NEW TEST EQUIPMENT

AVAILABLE for early delivery, two-beam switch unit, 6 valves, self-contained power pack, variable switching frequency, provisional price £10/14/6, enables two separate traces to be standard on standard oscilloscope.—BERNARDS, 12, Chelverton Rd., Putney, London, S.W.15. Put. 7069. [5198

OSCILLOSCOPE and Wobbulator complete, £30; T.B. c/s 10 to 550,000 c/s X and Y plate amplifiers easy to handle, has outstanding performance, fully guaranteed, immediate delivery with 10 days' free trial basis.—Oscilloscope Technique, further details from the manufacturers.—Engine Laboratories, Ltd., Bexley, Bardsley-vale. [5456

TEST EQUIPMENT SURPLUS AND SECONDHAND

INSTRUMENTS.

TIN SQUARE all meters, sealed 0-120° F.R.D. 150 micro-amps. 5/-; 2½in m/c 0-10 milliamps 7/6; 4½in hot wire, 0-2 amps. 6/6; 2½in m/c 500 microamp. sealed 0-15-600 volts reg. est. 4/6; 4½in thermal indicators with 2-60 microamp movements, 6/6; 2in. 0-40 m/c voltmeters, 5/11; send 2½ stamp list.—Pavingham, 95, North St., Keighley. [0092

SURPLUS and almost unused test equipment best offer accepted.

MODEL T.50 range universal Avo meter, with carrying case.

MODEL T.P.1002 beat frequency oscillator (Marconi).

MODEL T.F.429B/1 valve voltmeter (Marconi).

COSSOR double beam oscillograph.

SET transportable wireless masts.

P. & D. MOTOR DEVELOPMENT Co., Ltd., 135, Kensington High St., London, W.8. [5266

HUNT'S capacity bridge, as new, unused, perfect; £10/10.—C. R. Young, 154, Old Shoreham Rd., Southwick, Sussex. [5520

MULLARD Master test board, 500 test cards; Weston 1040 test set, multi-range; Weston 536 signal generator, the lot, £7.—Box 5560.

CLOUGH-BRENGLE oscilloscopes, 250-volt, £12/10; also Marconi V.V.M.; Gelte and General Radio R series; Taylor valve testers, etc., etc.—List on request to R.T. & I. Service, 294, Grove Green Rd., London, E.11. Ley. 4906. [0056

ENTIRE contents of well-equipped electrical and chemical laboratories for sale, covering G. meters, radio, frequency measuring instruments, Bridges R.F., moving coil instruments, ammeters, scales, microscopes, etc.—Apply for complete list to Trusvox Engineering Co., Ltd., 130, Mount St., W.1. [5242

NEW GRAMOPHONE AND SOUND EQUIPMENT

MAGNETIC tape, Emitape type 65 on 1,200ft. sp. ot. 25/-; paper tape, 20/-; blank recording discs, 12in 4/6, unbreakable, 4/6; all from stock; full trade terms available.

SOUND DISCS (SUPPLIES), Ltd., 173, Bispham Rd., Southport, Lancs. Tel. 6155. [5555

GALPINS

ELECTRICAL STORES

408 HIGH STREET, LEWISHAM, LONDON, S.E.13

Telephone: Lee Green 0309. Near Lewisham Hospital.

TERMS: CASH WITH ORDER. NO C.O.D.

EARLY CLOSING THURSDAY FROM 9a.m. UNTIL 4p.m. SATURDAYS

EXTENSION P.M. SPEAKERS, 3½ inch by well-known makers will handle 1½ watts. New boxed, 7/6 each. Post 9d.

EX-R.A.F. D.C. TO D.C. MOTOR GENERATORS, 24/28 Volts input 1,200 volts 72 M/amps. output, as new 7/6 each post 1/6.

EX. R.A.F. MICROPHONE TESTERS. These contain a 2½in. scale 0 to 450 Microamp meter shunted to 1 m/amp. calibrated 0 to 10 volts moving coil, complete with 1 m/a. rectifier, "Mike transformer," etc., all contained in polished wood box, as new, 17/6 each.

EX NAVAL SOUND POWER TELEPHONE HANDSETS, comprising earphone and microphone, no batteries required, complete with wall bracket, as new, 15/- per pair, 1/6 post.

MAINS TRANSFORMERS, 230 volts A.C., 50 cycs. input 17½ volts 50 amps. output, 52/6 each carriage 5/-; another auto wound, output 14 and 17 volts output at 30 amps., 35/- each, carriage 3/6; another with 2 x 4 volt 20 amp windings, 25/- each, P.P.

EX NAVAL ROTARY CONVERTORS, 220 volts D.C. input 50 volts, 3 phase, 50 cycles at 3½ amps. output, 55/- each carriage 5/-.

MAINS TRANSFORMERS, 230 volts, 50 cycles, 1 phase input, 700/0/700 volts 70 m/amps. 4 volts 2 amps., 12 volts 1 amp. output, 25/- each, post 1/6.; another auto wound "booster" transformer tapped 0, 200, 215, 235, 250, and 265 volts at 1.25 amps., 10/6 each, carriage 1/-.

PRE-PAYMENT 1/- SLOT ELECTRIC LIGHT CHECK METERS, all electrically guaranteed, 200/250 volts 50 cycs. 1 ph., A.C. input, 2½ amp. load, 27/6 each; 5 amp. load, 35/- each; 10 amp. load 42/6 each; 20 amp. load, 50/- each, carriage 2/- extra; in quantities of one dozen or more a special discount of 10/-.

MAINS TRANSFORMERS, 200/250 volts 50/1 ph. in steps of 10 volts. Output 500/0/500 volts 300 m/amps., 6.3 v. 8a., 6.3v. 8 a., 6.3v. 4a. 5v. 4 a., 4v. 4 a., at 67/6 each, another same input, outputs, 450/0/450 volts 300 m/amps, 6.3 v. 8 a. 6.3v. 8 a., 4v. 4 a., 5v. 4 a. at 62/6 each.

POWER TRANSFORMERS AUTO WOUND voltage changer tapped 0, 110, 150, 190, and 230 volts at 1,600 watts, £5/5/- each, carriage 3/6; ditto 2,000 watts, £6/5/- each, carriage 3/6; another tapped 0, 110, 200, 230 volts at 350 watts, at 47/6 each, carriage 2/-.

ELECTRIC LIGHT CHECK METERS, quarterly type, for sub-letting garages, apartments, etc., all fully guaranteed electrically, for 200/250 volts A.C. mains 50 cys. 1 phase, 5 amp. load, 17/6 each; 10 amp. load, 20/- 20 amp. load, 25/- each; 50 amp. load, 37/6 each; 100 amp. load 45/- each; carriage 2/- extra on each; special discount of 10/-, on quantities of one dozen or more.

ISENTHAL MAIN VARIABLE, Resistances (Dimmers) 700/750 watts from full bright to blout, worm wheel control, as new 27/6 each, carriage 2/- total resistance 60 ohms.

MAINS TRANSFORMERS INPUT 200/250 VOLTS, 50/1 in steps of 10 volts, output tapped 0, 6, 12 at 24 volts at 10/12 amps., 47/- each; ditto as above but at 25/30 amps. output, 60/6 each.

MAINS VARIABLE SLIDER RESISTANCES, protected type by well-known makers, 450 ohms, 9 amps., 22/6 each; ditto 1,500 ohms to carry 45 amps. 22/6 each, not protected, 0/4 ohms to carry 25 amps., 10/- each; 14 ohms to carry 1/4 amps., 12/6 each; 5/7 ohms to carry 8½ amps., 15/- each; 60 ohms to carry 1½ amps., 15/- each.

MAINS TRANSFORMERS, input 200/250 volts in steps of 10 volts, output 350/0/350 volts 300 m/amps. 4 volt 8 amp., 4 volt 4 amp., 6.3 volts 6 amp., 6.3 volts 2 amp. tapped at 2 volts (electronic) at 57/6 each; another same input as above output 500/350/0/350/500 volts 250 m/amps 5 volts tapped at 4 volts 4 amps twice, 6.3 volts tapped at 2 volts 2 amps, 67/6 each.

SWITCH-BOARD A.C. D.C. AMPMETERS, Otto 14 amps. 4½in. scale by well-known makers, as new, 25/- each.

MAINS TRANSFORMERS, 200/250 volts input in steps of 10 volts, output 350/0/350 volts 180 m/amps. 4 volts 4 amp., 5 volts 3 amp., 6.3 volts 4 amp., 37/6 each, ditto 500/0/500 volts 150 m/amps. 4 volts 4 amp., 5 volts 3 amp., 6.3 volts 4 amp., 42/6 each; ditto 425/0/425 volts 180 m/amps. 6.3 volts 3 amps twice, 5 volts 3 amps. (Williamson Amplifier), 39/6 each; Ditto, 350/0/350 volts 180 m/amps. 6.3 volts 8 amps 5 volts tapped 4 volts 3 amps. 39/6 each.

CELL TESTING VOLT-METERS, moving coil, reading 3/0/3 volts by well-known makers, complete with test leads, 7/6 each.

EX. R.A.F. ALTERNATORS, 230 volts 50 cycles input, 250 volts 625 cycles 1 phase output at 60 watts. These are separately energised by 24 volts at 0/4 amps., 65/- each, carriage 5/-.

I.F.F. UNITS, EX. R.A.F., containing 10 valves all useful, also a 24 volt input 450 volt output rotary transformer and many useful condensers and resistances. The rotary transformer can easily be arranged to work off A.C. mains as a motor, approx. ¼ h.p. A few only, to clear 20/- each, carriage paid.

MAINS TRANSFORMERS, 200/250 volts input in steps of 10 volts, output 350/0/350 volts 300 m/amps. 4 volts 4 amp., 5 volts 4 amp., 6.3 volts 8 amp., 6.3 volts 8 amp., 62/6 each. Smoothing chokes 10 Henry 100 m/amps. 200 ohms D.C. resistance, 5/- each.

EX G.P.O. GALVONOMETERS, vertical type, reading 30/0/30 polarised, 6/6 each; rectifiers, output 50 volts 1 amp. D.C. from a 70/75 volt A.C. input, 8/6 each, post 1/6.

METERS ALL BY WELL-KNOWN MAKERS as new, 2in. scale moving coil 0 to 20 volts, 8/- each; 0 to 40 volts 7/6 each, 0/10 amps. 12/6 each post 6d. Thermo coupled 2½in. scale 0 to 4 amps 7/6 each 2½in. A.C. D.C. 0 to 10 volts 10/- each.

EX GOVERNMENT AUTO WOUND TRANSFORMERS (as new) 1,000 watts output 115/230 volts or vice versa £4/10/- each, carriage 5/-; another 1,000 watts from 5 to 230 volts with 32 various tappings inclusive of 110, 150, 60, 90 etc., etc., all tapping at 1,000 watts £5/10/- each carriage paid.

MAINS TRANSFORMERS 230 VOLTS, 50 cycles 1 phase input/output, 4 volts 5 amps three times, 16/- each; another 6/65 volts 5 amps twice 16/6 each; another input as above, output 150/0/150 volts 150 m/amps. 6.3 volts 8 amps 5 volts 2 amps, 16/6 each; all carriage paid.

EX GOVERNMENT CHARGING SW TCH BOARDS, 550 watts containing five moving coil 2in. scale volt and ampmeters, five variable resistances, three cut-outs, good condition, at 75/- each, carriage 5/-.

MAINS BOOSTER TRANSFORMERS, 1,500 WATTS, tapped 0, 6, 10, 19, 175, 200, 225, 240, and 250 volts, good condition, electrically guaranteed, £4/10/- each, carriage 5/-; another double wound 4,000 watts, 130 to 250 volts or vice versa £7/10/- each, carriage 10/-.

D.C. MOTORS 110/230 VOLTS, rated at 1/12th h.p. with laminated fields suitable when fields are rewound for A.C. mains, 17/6 each; ditto half the above size, 10/- each; another 100 volts D.C. approx. ¼ h.p. shunt wound solid field 1,500 R.P.M., 10/- each.

EX. R.A.F. CRYSTAL MONITORS (less valves and crystals) sold for component value only, containing many useful parts, condensers, resistances, transformers, the whole a very good basis for a miniature 3-valver, complete in wooden carrying case (condition as new), 5/- each, post free.

EX NAVAL CATHODE RAY INDICATOR UNITS, as new, containing loads of very useful components, condensers, resistances, transformers chokes, etc., etc., weight 96 lb. (as few to clear) 25/- each, carriage paid.

MAINS TRANSFORMERS, 230 VOLTS INPUT, 525/0/525 volts 150 m/amps. 6.3 volts 5 amps., 5 volts 3 amps., 55 volts 50 m/amps output, 30/- each; another 12 volts 12 amps output, 27/6 each; another tapped 35 at 45 volts at 20 amps. output, 65/- each.

ALL GOODS SENT ON 7 DAYS' APPROVAL AGAINST CASH, all letters answered. We regret we have no lists available at present. We would be pleased to quote.

DUKE & CO.

SHORT WAVE SUPERHET. complete (mint as No. 18) for only 25/-. Fully tested and only receiver requiring tuning up. Complete 9-9 with 1000 only available.

WALKY TALKY No. 38. All new valves in G.st (low condition, one valve (ATP4) and switch needs attn) only required 17/6 bargain. 1000 only available. Circuit and switch connections supplied.

100 RESISTORS 10/-. Assorted sizes and wattages. (New are all popular sizes. We are receiving many repeat orders.)

SPEAKERS. 5in. P.M. 9/6. 6in. P.M. with trans former 15/3. 6in. P.M. less 16/6. 10in. P.M. 19/6. Trans. extra. 12in. P.M. 19/6. 10in. P.M. Tweeter 35/-.

HORSE KEYS. Good condition 9d.

METERS. 2½in. flush, reads 2/6 each.

ELECTROLYTICS. Bargain packets — 100 mfd. 50v and 24 mfd. 500v, all 6/- (lb) lot.
16+8 mfd. 450v. 2/6. 32 mfd. 350 v., 3/6.
8 mfd. 2/6. 4+4 mfd. 3/6. 16 mfd. 3/6.

HEADPHONES. Low resistance. 2/6 per pair (D.L.R. super sensitive balanced armature, 3/6 pair). Super quality with hard rubber ear 8/6.

GRAM-MOTOR. New A.C. complete with turntable. No. Rim Drive. 39/6. P.T. 20/7.

T.V. MAST BRACKETS to fit 10/16ft. mast, galvanised 4/6.

T.V. AERIAL. Hearts only to fit extension arms, correct to reader. 2/6.

STEEL SPARE VALVE BOXES. Lined and embossed with felt. To make space for 4 valves. Thus ensured little or no other gear damage at all. Size 14×4×2½ins. 10/4 each.

FIBRE AERIAL MAST. 10ft. high. 10/-. 30ft. high. 25/-.

STRAINERS. 4 eggs in wire, adjustable strainers at 1/9.

SMALL PORCELAIN Egg Aerial Insulators 6d each. Heavy porcelain wind-off insulators, ideal for overhead lines to wash, rails, poles, etc. 1/6 each.

CHOKES. Midget, made by well-known firm, 40 m.a. 10hen. Low resistance. 5/-.

ADJUSTABLE PRESSURE SWITCHES. Ideal for wind or air. 2/6.

PLY-WOOD. Pre-war well, maplewn sizes 5/16in. 14×8ins. 10/-. 10/-. 18/-. 3/-. 30/-. 1/16in. 2/-. 3/-. Regular 4/- lb. Limited supplies.

DUNLOPILLO in composite covered wate or backs 12/6 each, plus carriage 2/-. When enquiring C.W.O. please allow sufficient for postage. Send stamp only for Special Amateur Price List. Trade inquiries invited. Order now to combat one of our many lock guarantee.

219 ILFORD LANE, ILFORD, ESSEX Ilford 0986

"You can rely on us"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

IMMEDIATE DISPATCH

SPEAKER TRANSFORMERS

Super Midget for "Personal" 7in speaker 3½ ... 4/3
Push-pull output type, standard size, 30/- ... 4/6
Whole output type, standard size, 30/- ... 4/6
Push Pull 40/-, 17/6, to match 15 ohm or 3/3 ohm ... 8/6

FILAMENT TRANSFORMERS

200/240 v. to 6.3 v. 1½a. black crackle finish, sized ... 8/6
200/240 v. to 6.3 v. 2½a. black crackle finish ... 12/6

LOUDSPEAKERS

Celestion Trio, 25/6; 5in. with mot cone 9/9; 6in. Television lightweight cone magnet 10/6. 6in. 12/6. 6in. with Transformer 15/-; 6½ with transformer 19/6. 10in. Lightweight 21/6. 10in 39/6. All Standard 2.5 ohm speech coils.

CHOKES

Midget type 30 m.a. 4/6. 60 m.a. type ... 6/-
20 m.a. 10hen. specially made based 10hen 5/-
100 m.a. 10 hen ... 11/6
200 m.a. 10 hen. 100 ohms, shrouded ... 21/-

ELECTROLYTICS

1 mfd. Cardboard tube, 500 v. 1/6; 8 mfd. 450 v. Midget ... 3/-
8 mfd. 500 v. Card Tube, 3/-; 16 mfd. 350 v. Aluminium Tube ... 3/6
8+8 mfd. 450 v. Midget, 4/-; 8+8 mfd. 500 v. Card Block ... 4/9
16+16 mfd. 450 v. Alt. Tube, 7/6; 8+16 mfd. ... 5/6
16 mfd. 350 v. Card Tube, 6/-; 8+8 mfd. 450 v. Alt. Tube ... 5/6
32 mfd. 350 v. Alt. Tube, 3/-; 32+32 mfd. 450 v. ... 9/6
32 mfd. 50 v. Alt. Tube ... 1/6

COILS

Aerials: P. Coils, full range ... each 3/-
T.R.F. MW/LW with reaction (Ferrite) ... 7/6
Medium Wave (non-cored) with reaction ... 3/6

VIEWMASTER TELEVISOR

1 Tube to position and beaded, positive ... 5/6
State London or Midland. All components stocked.

HOST OF OTHER LINES

Write, phone or call G.P.

NEW CATALOGUE 9/-. 7 and 6d. 2/6 Illust.

RADIO SERVICING Co.

444, Wandsworth Road, London, S.W.8

Phone: MACaulay 4182.

22, 27A, Bus: 29, Trams. Wandsworth Rd. S.E. Station. Open 9.0-5.30 p.m.

NEW GRAMOPHONE AND SOUND EQUIPMENT

INFINITE baffle corner deflectors scientifically designed acoustic chambers for 8 to 15in speakers. Info.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [9004

TRANSFORMERS, tone control and loudspeaker filter chokes for all W.W. circuits special designs promptly made.—R. Carter, 81, Langland Crescent, S. Stanmore Middx. Wor. 5321. [5976

CINE-VOX disc recording machines, type CTJ, a precision-built unit in chassis form, fully assembled and ready for immediate bin to 15in recordings from existing amplifier and microphone equipment or from conventional radio or radiogram apparatus, price 25gns ex works.

COMPLETE recording channels with amplifier and moving-coil microphone from 80gns.

WRITE for details to Kine-Technic Services, Ltd., 60, Aylward Road, London, S.W.20. Tel. Liberty 2456. (callers by appointment only). [5210

TAPE recording decks, a precision finished deck comprising two motors, high fidelity sound and erase head, high speed capstan of unique design suspended between ball races with heavy fly wheel to insure freedom from wow, no unlacing of tape for rewind, deck finished in black crackle, size 14½×12½, £20; ¼in. tape heads standard type, record/playback, £1/10; erasing head, £1/10.

HIGH fidelity tape heads as fitted on our decks record/playback, £4/10; erase head, £4/10; osc coils, 15/-; bias circuits supplied free, trade enquiries invited.

MUSICRAFT SOUND SERVICE, 4-6, Green St., Morecambe. Tel. 1161. [9078

MOTORS, BSR shaded pole type for recorders, size R1 52/- P.P. 8/6; BSR synchronous type, drive direct turntable, £5/15/-. Collaro AC47, centre drive, variable speed, 12in turntable, £5/10/2; gram units, Collaro 4-speed motor and magnetic PU, £5/5/-; 2 speed crystal PU, £5/12/6. Garrard 3-speed motor and magnetic PU, £5/10/6. Garrard RC70A autochanger, non-mixer, £10/7/7. Marconi AC100, lightweight PU, non-mixer, £10/0/6; all prices include PT, all sent post free.

FRITH RADIOCRAFT Ltd., Leicester. [9027

GRAMOPHONE AND SOUND EQUIPMENT SURPLUS AND SECONDHAND

BRIERLEY ribbon pick-up and transformer, as new, unused, £5.—42, Station Rd., N.21. [5330a

RECORDING turntable in case with tracking mechanism, 110 to 220 volt a.c./d.c. complete with 16ohm cutter, £10.—6, Vale Croft, Pinner, Middx. [5326

SLIGHTLY used pickups, Decca 50/-, Brierley armature with trans., £6; Lexington Senior with trans., £2.—Hutchley, Arlington Rd., Southend-on-Sea. [5259

MAGNETIC sound recording wire, stainless steel, temporary wooden spools, approx. 1½ hours running time at 2ft. per sec., 14/- per spool.—A. Smart, 81 Grange Rd., Halesowen.

NEW COMPONENTS

TELEKIT SUPPLY Co.

S.L.C.S. monitor units, 11in×9in×9in, detachable cover, hinged, viewing hood incorporating 5in VCR 138 Mullard valve, nothing complete, the basis of an excellent oscilloscope, complete with suitable conversion drawing, 36/-; ditto but less VCR 138, 15/-; ditto, less all valves, 6/-; ditto, empty unassembled cases, black crackled, superior finish, 10/6.

WE are stockists for the "Wireless World," "Electronic Engineering," and "Viewmaster" television construction kits, and have extensive experience of their building, a free technical advice service is available to all purchasers who obtain their kit from us.

TELEVISION pre-amplifiers of universal application for either balanced or unbalanced input, with built-in power pack, to feed into any commercial receiver, overall bandwidth 5-8 mc/s, gain 20 db, 37/6.

TELEVISION coil sets, we manufacture and supply coils for all the recognised kits for either the London or Birmingham frequencies, prices on application, all goods are guaranteed. Wound to designer specification, power and audio transformers up to 500 watts, wound to any specification, quotation by return of post, we also hold stocks of ex-W.D. valves and surplus equipment; s.a.e. for lists and price list (no catalogue).

TELEKIT SUPPLY Co., 51 Addington Rd., West Wickham, Kent. [5204

WIRELESS World television.

FOR approved components all enquiries should be addressed to "The Manager," Hendy's, 226-229, Merton Rd., Wimbledon, S.W.18. Lib. 3461. S.a.e. for replies. [9055

W.W. television components to exact specification.

LINE O.P. transformer, 50/-; deflector coil assembly mounted on adjusting panel complete and wired 50 tags, 50/6; mains transformer, 90/-; L.F. choke, 30/6; blocking osc transformer, 15/-.

E.P.D. TRANSFORMER PRODUCTS, 81, Queenstown Rd., Lavender Hill, Battersea, S.W.8. Tel. Macaulay 4182. [5352

It Pays to Purchase
ELECTRADIX • BARGAINS

TRANSFORMERS. B.T.H. double wound 200/230/250 volts input 2 volts 20 amps. and 75 volts 6 amps output with 15 taps, 45/-, carr. 5/-, extra. Foster 100 watt 50 volts 2 amps. suitable for soil warming, 15/-, postage 2/-. Large double wound Transformer 230 volts 50 cy. input 53 volts 15 amps. 6 volts 5 amps. 0-30 and 0-60 volts 1 amp. output, £5. Auto Transformers 230 volts to 110 volts 85 watts 25/-, 1 K.W. £6/10/-.

LIGHTING PLANTS. The famous CHORE-HORSE 300 watt plant; portable, for Caravan, Bungalow or Farm outhouse lighting; 1 h.p. single cyl. 4-stroke engine 12/15 volt D.C. Generator with Fuel Tank and Switchboard, £12, carriage extra. Write for List "L.P." of A.C. and D.C. Lighting Plants 300 watts to 3 K.W. in stock.

MOTOR PUMPS. 12 volt D.C. Motor Pumps 100 g.p.h. for caravan or motor boat 10ft. head, £5. Stuart Turner 230 volt A.C. Motor Pump for garden fountains, etc. 100 g.p.h., £5/15/-, foot valve and strainer 21/- extra.

DYNAMOS. 12 volt 10 amp. for windmill 1,400 r.p.m. C.A.V. 40/-, carr. 5/-. 24 volts 10 amp. 2,500 r.p.m., 70/-, carr. 5/-. 24 volts 30 amps. 1,200 r.p.m., totally enclo., £15. 24 volts 18 amps. 1,200 r.p.m., vent. enclo., £12/10/-, carriage 5/-.

METERS. Voltmeters 2in. flush panel 30 volts 4/-, 2½in. C.Z. 100 volts 6/-. Ammeters 2in. C.Z. 50 amps. 4/6, 20 amps. 4/6. Milliamps 2½in. 0-15 m.a. 4/6. **Cell Testing Voltmeters,** moving coil Evershed and Walsall in leather case with spikes, reading 3-0-3 volts, 12/6. **Galvanometers,** in pol. wood case with glass front, 100 ohms calibrated 2½ microamps. per div. at 1 metre, moving coil mirror reflecting Lab. type, £5.

FREQUENCY METERS. Ironclad flush Panel Meters 5in. dia. 45/60 cy. 230 volts, £4/10/-.

RECTIFIER UNITS, ex G.P.O. Westinghouse Rectifier units 230 volts A.C. to 24 volts 3 amps. D.C. in ven. metal case, £8.

Please include postage for mail orders.

ELECTRADIX RADIOS

214 Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

OPPORTUNITIES IN RADIO

Get this FREE Book!
"ENGINEERING OPPORTUNITIES"
reveals how you can become technically-qualified at home for a highly-paid key-appointment in the vast Radio and Television Industry. In 176 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of **TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.**

We definitely Guarantee
"NO PASS—NO FEE"

If you're earning less than £10 a week, this enlightening book is for you. Write for your copy today. It will be sent **FREE** and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
3885 SHAKESPEARE HOUSE
17-19 STRATFORD PLACE, LONDON, W.1

BIET

LIQUIDATORS DISPOSAL AGENCY

(RADIO & ELECTRICAL)

BARGAINS DIRECT FROM OWNERS

Taylor 45A Valve-Tester, A.C. 110-250 volts, tested and perfect **£11 0 0**

Collaro new centre-drive Gramo. Units with 12in. turntables, 12 only each **£6 0 0**

Donco (1949) 5 wave-band Radio in cabinet, perfect **£11 0 0**

S.T.C. Ball and Biscuit Mike, complete with plug, lead and transformer, in perfect condition. **Model 4021A £8 0 0**

S.T.C. 4017A moving coil mike with transformer, perfect **£8 0 0**

Recording Unit (Will Day) in oak cabinet, spring-drive motor, Permarec tracking-gear, German cutting head, meter etc., with 2 spare springs. The lot **£15 0 0**

Office Intercommunication Set, comprising Master Unit, 4 extensions, all leads, etc., perfect **£9 0 0**

16 mm. Talkie Film on spools, approx. 2,000 feet, perfect and modern. The lot **£10 0 0**

Ekco all-wave Radiogram (1949-50), cost £72. Our price, as new ... **£37 10 0**

250 Classical 12in. Records, all best makes, 18 months old, very little used. In lots of 12 ..... Each record **2 0**

R-1155 Receiver, with A.C. power-pack and speaker. In good working order **£10 10 0**

G.B. model L.516 Sound on Film Projector, complete with speaker and resistance, in new condition. A genuine bargain **£82 0 0**

Crystalite Spray Outfit. Cost £28 in 1948. In new condition **£10 0 0**

MK58 Transmitter and Receiver, complete and perfect **£11 0 0**

B.P.L. A.C. D.C. Super-range Test-Meters, 1,000 o.p.v. Brand new, 2 only each **£12 17 6**

Hickok Valve-Tester and Test-Meter combined. 110 volts A.C., perfect **£9 10 0**

Weston A.C. D.C. Test-Meter, battery Signal Generator and Valve-Analyser in portable case, complete with leads, etc., perfect **£11 10 0**

G.E.C. 2½ kw. factory type Fan Heaters, 2 only, perfect, each **£6 0 0**

Avo Meter, model D, A.C. D.C. (like model 40) perfect **£9 10 0**

Evershed & Bridge Megger, 500 volt, 1,000 megohms, less resistance box. Cost about £45. Our price, in new condition **£15 0 0**

Emor Globe Radio Sets, A.C., all waves, in chrome, less valves, but checked and perfect. 4 only ... each **£6 10 0**

G.E.C. heavy-base Mike Stands, perfect **£2 2 6**

WE WELCOME CALLERS!

We have other bargains arriving daily

Cash with orders only.
All items carriage extra.

PHONE : GERRARD 5507

39a, LISLE ST., LEICESTER SQUARE LONDON, W.C.2.

NEW COMPONENTS

HANNEY OF BATH offer:

WIRELESS World T.V. superhet, complete set of 20 coils wound exactly to designer's specification, 45/-.
POLYSTYRENE formers, 1½in×⅝in, tapped 0 B.A. for slug with fixing hole, 1/-, 2½×⅝, 9d.
PAXOLIN formers, 1½in×⅝in, tapped 0 B.A. with fixing hole, 9d. 2in or 1½in×⅝in, 8d. 1½×⅝, 9d. Polystyrene varnish, large bottle, 1/10.
0 B.A. screwed rod, copper, 2/- ft, brass, 1/- ft.
Eddystone 565 split stator, T.6, B.T.H. C.O.L.-C. crystals, 11/3. B.A.200 rectifiers, 2k/-, co-axial cable, 1/3 yd. Dubilier condensers, type 560, 5,000v test, 0.001, 6/6 doz. 0.002, 7/-. Reliance pots, 1k, 2k, 10k, type T.W., 4/6; 100k, 150k, 2 tags, type B.O., 5/-. Erie resistors, ½ watt, all values, 4d., also T.C.C. condensers. Dubilier drillings, valves, tube masks, aerials, etc., complete list, 2½d stamp please.
THE Viewmaster everything in stock. T.C.C. condensers, 1.0on £6/15. B/Ham £7. W.B. chassis speaker, transformers, £6/5. Plessey transformers and focus coils, £5/12/6. Morganite resistors, 20/-. Co-vern pots, 15/-. Westinghouse rectifiers, 62/6. Wearite coils, 22/-. Britain panels, switches, 12/6, detailed list on request, 2½d stamp please. Mullard 9in tube MW22-14C, £11/6/3. Mullard 12in tube MW31-14C, £15/2/3.
WILLIAMSON amplifier, Gardner output transformer, 105/-. Woden ditto, 82/6, mains transformer, 55/-. Reliance 100Ω pots, 4/6. high stability resistors (all specified values), ¼ watt ±5%, 1/-; ±1%, 2/3. ½ watt ±5%, 1/-; ±1%, 2/-; other values to order, silver mica condensers, 25 to 500pfd, —5%, 9d. ±1%, 1/3; 1,000 pfd, 1/-; 4,000pfd, 2/-. 5 bank 6 position switch, 7/6, matched resistors supplied, send for detailed list, 2½d stamp please.
EDDYSTONE and Raymart S.W. list, 1d stamp.
Wearite P coils, all ranges, 5/- ea. Denco type C.T.R.F. coils, 6/6 pr.
MARCONI ac 100m auto-changer, with the new lightweight P.U., £10/0/6, matching trans., 15/-.
COLLARO R.C.500 auto-changer, with either crystal or lightweight P.U., £10/15.
B.S.R. T.U.2 gram. motors, £5/4/3.
ACOS G.P.29 P.U., £3/11/5. Goonmour lightweight P.U., £5/17. Marconi No. 14 P.U., lightweight high fidelity complete with matching trans., 96/-.
GOODMAN speakers, 12in, T1205/15, £6/15.
AXIOM 12in high fidelity, £8/8.
AMPLION universal test meter ac/dc, £5/17/6.
WE supply components for all Wireless World designs, order us as for all goods (inc. valves) advertised by leading makers or get our quotation by return, retail only.—L. F. Hanney, 72, Lower Bristol Rd., Bath. [5812

THE simplest a'het pack, type M1, M.L. waves, 22/6, thousands in use.
DOUGLAS COIL Co., Brinkley, Nr. Rlsbr.

VIEWMASTER all parts in stock, valves, tubes, cabinets.—H.G. Radio, 1350, Stratford Rd., Birmingham, 28. [5092

CHAMPION PRODUCTS, 43, Uplands Way, N.21.—Still at your service, see our displayed advertisement on page 82. [5814

BRAND new telephone handsets, carbon mike, 4-way cord and plug, latest streamline type, 10/6 each, post 9d, or 2 for £1 post free, fully guaranteed.
FRITH RADIOCRAFT, Ltd., Leicester. [5909

CRYSTAL microphone inserts (Osmosond Mic-6), guaranteed brand new, 15/6 post free.—Radio-Aid, Ltd., 29, Market St., Watford. 'Phone Watford 5966. [5056

EHT Transformers, mains transformers, output transformers and chokes, open or potted types; transformers designed to individual specification, singles or in quantity.
WILLESDEN TRANSFORMER COMPANY, Ltd., 781, Harrow Rd., N.W.10. Ladbroke 2646. [5075

VIEWMASTER and E.E. specified components also surplus components, e.h.t. transformers 5kv 4v. 50/-, high-class job, new radios from £8/8/0.—F. King, 5, Hartfield Crescent, Wimbledon. [5157

THE brain of any good radio is an Osmor Q coilpack used with our matched components you can build a radio worth boasting about, write to-day for free circuits and our latest lists, including the Bargain Bulletin.
OSMOR RADIO PRODUCTS, Ltd., Bridge View Works, Borough Hill, Croydon. (Cro. 1226.)

TELEBOOSTERS for long range television reception, super high gain single-stage preamplifier, 2-stage, 1 VR91 valve slug tuned L/London or Birmingham, co-axial plugs and sockets flying leads for high and low tension, fully screened, low noise, price £3/12/6, power units for above, £5/10, s.a.e. for trade test report.
BOSCOMBE RADIO & ELECTRIC, 595, Christchurch Rd., Boscombe, Bournemouth. Tel. 36522.

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19, television components for "View Master," Belling & Lee Bulgin, Colvern, Morganite, Plessey, T.C.C., Wearite, Westinghouse, Whiteley, complete parts as specified in stock, also E.E. chassis, Baxtra transformers, etc.—Write, call or 'phone your order Livingstone 4879. [5020

GOOD SOUND REASONS

We do a lot of apologising these days, to our friends who await the speakers they have on order. This situation is two-edged, because much as we, in common with any producing unit, like to have a nice head of orders in hand, the fact that three weeks or more intervene between the order and delivery of standard 150 or 148a, and quite double this time for specials, may divert some who want our speakers into acceptance of a lesser standard.

Our sales are in fact well up on those for the same time last year, and we are making more, but we will not hurry or skimp the job, nor put untrained hands to it. No one who really wants NATURAL sound from radio or records will mind waiting a short while for a speaker which is going to bring such enduring and satisfying pleasure.

You may ask why we keep on advertising; to which our answer is that there are still many thousands of "Wireless World" readers who do not yet know how and why BARKER 148a and 150 speakers have in a little over two years established such a commanding reputation, and why we send them to so many places abroad as well as to hundreds of friends in Great Britain.

There are several very good sound reasons, in more senses than one, for these facts. If you seek NATURAL reproduction, write now for details.

BARKER NATURAL REPRODUCERS

BCM/AADU
LONDON, W.C.1.

THE
BRITISH NATIONAL
RADIO SCHOOL
ESTD. 1940

WELL-MEANING FRIENDS, *and we have many*, SOMETIMES ASK WHY WE NEVER ADVERTISE

"MONEY BACK IF UNSUCCESSFUL"

AND THIS IS WHAT WE TELL THEM —

"NO B.N.R.S. STUDENT HAS EVER FAILED"

to pass his examination(s) after completing our appropriate study course.

"THIS IS FACT NOT FABLE, BUT IT DOES CONTAIN A MORAL"

A.M.I.E.E., A.M.Brit.I.R.E. and CITY and GUILDS Radio and Telecommunications Exams., etc., etc.

* *in specially approved cases.*

Six months' trial period without obligation to continue.

Send for free booklet to —

STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
66, ADDISCOMBE ROAD, CROYDON
Phone: Addiscombe 3341

GARLAND RADIO

Amplifier ACI: For operation from A.C. Mains (state voltage). Two valves plus metal rectifier. 3 watts output for 3Ω sp. Incorporating volume control, tone control and variable negative feedback. Complete kit with circuit and instructions £2 15/-.

METERS: 3½in. sensitive 200μA. Calibrated 0-15, 0-5, 0-1·5 v. Ideal basic instrument for valve voltmeter. New and unused. 37/6.

Muirhead Slow Motion Dials: New and unused 6/-.

Modulator Type 50: Containing 50 spc. power pack with metal rectification (bridge) giving 150v. D.C. and 700v. D.C., 2 of 6J5, 1 of 6J7, 1 of 6C5. Callers only, £2.

Dimmer Switches: for lamps, etc., 9d. each.

Throat Microphones: Ideal electronic pianos, guitars, etc., 1/9 per pair.

Amplifier ACIII: For operation from A.C. Mains 200-250v. 7 valves (incl. rectifier), output 10w. (2 — 6V6G1 to 3Ω or 15Ω speaker (state which). Output available for tuning unit 280v. @ 30mA, 6.3v. @ 2A. High and low gain inputs. Separate bass and treble controls. Partridge Output Transformer, negative feedback over three stages. Complete kit, with circuits and instructions, £7.

GARLAND RADIO
Chesham House, Deptford
Broadway, London, S.E.8
Phone: TIDeway 4412/3

NEW COMPONENTS

MIDGET volume control of the future, diameter the size of a halfpenny. Its uniqueness from 50,000 ohms to 2 ohms, with switch, 6/-; 6 p. switch, 7/6; less switch, 4/-. Post free. Trade enquiries invited.—D. Diamond, 45 Hanson St., Manchester, 8. [illegible]

TELEVISION — Wireless World television complete chassis sets 30/-, 10/-, 2 pack chassis, full sets, 52/6, line transformers, 42/-; deflection coils, modelled, 35/-; focus coils, 37/6; looking tube, 15/-; shielded brackets, 1/-; pick brackets with iron screw, 10d.; polyterene rod and cement.

EE full sets, Midland 16/6, with spare coils and video chassis, 2 pack and 1 base chassis, plated steel, 35/-; pr. Linked receiver, 20/-; the pair, plus chassis, 30/-; turntables, 20/-; eg. 21/-; any size tube material sets.

FOCUS rings, triode 25/- and 35/-, tetrode 20/- and 32/6 (reviewed "E.E.", March); television standard I.F. trans., 5/6 each, 3/- and 15/6 pair, 6/9 eg., grinding sets (unassembled), 2 valve, 1/- in B. 5/6 in. Practical Wireless I.F.T. and chas. coils and chassis, Williamson type I.F.T. coils, 7/- pair; trade enquiries invited; lists free.

BEL SOUND PRODUCTS Co., Marlborough Yard, Archway, London, N.19. Tel. North 1955. [illegible]

"WIRELESS WORLD" television complete, 2 pack and 1 base chassis, full assembly, above focus coil, 4/-; back cap, trans., 4/-; expected coils, London or Birmingham, 5/6; chassis, 30/-; rectifier H.T. 20/-; main transformer, 30/-; 3-way chassis, 6/9; 6/- 6/3/- 6a, 7/-; stocks.—R. F. Houlton, 19, Carendon Rd., Salisbury, Wilts. [illegible]

5/4 only for the famous Model M tuning unit, containing of 3-ganged Model M superhet unit pack, pair I.F. transformer, 2-gang condenser and adjustable dial, 6/6 extra, each component individual selected, pre-aligned, sealed and the whole matched to perfect as a unit, the superhet you build with this unit, ready to fit, fully aligned, 12/- supplied mixed with the superhet J.B. horizontal tuning unit, complete with dial assembly at 25/6, full details of these and our other high quality tuning units (EE Feb.) 1/- to build (Model M, number with main circuit and constructional tips, contained in the "Home Constructor Handbook," price 1/-.—Mail order office, HIPACOILS, 40, Greenway Ave., London, E.17.

COMPONENTS, SURPLUS AND SECONDHAND

BRAND new guaranteed goods.

MAINS transformers, fully interleaved and impregnated, primaries 200-230-250v., 50-60c. screened, d.p. through type, full shrouded, 250-0-250 60ma. 6.3v. 2a., 19/6; as above, 2½v. 2a., 14/11; standard 200-230-250v., 70ma. 6.3v. 2a., 12/6; separated, 14/11. 350-0-350v. 80ma. 6.3v. 3a. 5v. 2a., 17/6. 350-0-350v. 150ma. 6.3v. 4a. 5v. 3a., 21/6; fully shrouded, 200-230-250v. 2a. 6v. 2a. 6v. 2a. 6

DONT MISS THIS BARGAIN

A Personal Radio for your Holidays

EX-W.D. CHASSIS with valves in brand-new condition. 1R5, 1T4, 1S5, 3S4, complete with Circuit Diagram, showing how this can be converted to a very excellent set for Boats, Lakes, Picnics, etc. Bargain price only **97/6** post.

EX-R.A.F. 2-VALVE MORSE OSCILLATOR, battery operated, reduced from 37/6 to **15/-**, valves 1/6.

OBSOLETE DK1, DAC1, DF1, DLF1 can now be replaced with equivalent valves and ready to plug-in adaptors. Price of valves in advertisement.

12/10, 9/2, 11/-, 11/-, etc. **3/9** each adaptor.

OLD CABINETS—LIKE NEW with Scratch Remover Kits, also suitable for furniture generally **5/6** post 6d.

HOW TO REPLACE DIFFICULT VALVE TYPES 6K6, 6F6, 6X5, 6F5, 6C5, 6H6, 12A7, 12SQ7, 12H6, 12D1, 35A5, 35L6, 35W4, 35Z4, 41, 42, 43, 50L6, 75K2, 80, 82A, etc. We can help you here, too.

EASY TERMS Up to 12 months—and very next cash price on all Valve Means.

FREE Catalogue, Payment Plan and Application form.

SERVICE SHEETS The one you require FREE in a Lucky dip at **10/6**.

"DEMOBBED VALVES." Service Valves and their commercial equivalents **2/8** post free.

BOOK-LIST FREE

"TELEVISION RECEIVER CONSTRUCTION." "Wireless World" Reprint **2/8** post free.

AMERICAN Service Manuals, below, **12/6** each. Model 19 Receiver **12/6**.

EX-GOVT. ANTENNAE RODS, close jointed sections interlocking, 10ft. **5/-**.

CONDENSERS. 4-gang, 400 v., **2/-**; 50 fold, 25 v., **1/6**; ditto 100 v., **1/-**.

POTENTIOMETERS. Mono ohms, **2/-**.

MINIATURE CABINETS in wood, cream sprayed, with fabric grill, for 7in. speakers **6/-**.

HIVAC, X66, X96, XR, XD, XL, XLO, XP, XY and Holder. New Boxed Valves, 1/6 each. Valves fully checked and well assorted. Lists sent. Equivalent books **2/8**.

MORSE BUZZER, trembling set. Silver mint. Ebonite base, with coil bobbin, adjustable for high and low pitch, with diagram on back, **5/-**.

AMPLION all purpose test meter, 12 ranges, A.C./D.C., nothing else. New. Bargain **£3/7/6**.

"VIEW MASTER" T.V.

The Television set service that build at home from standard parts.

9in. or 12in. screen ● 12 valves only ● Magnificent cabinetry ● Automatic interference suppression ● Totally adjusted without Oscilloscope ● Construction manuals containing 8 full-size stage by stage assembly drawings with full instructions and a 32pp. book on construction, aerial erection, lining up, faults and servicing, simple non-technical explanation of how T.V. works. **5/-**, 6d. post.

We have also the necessary components, and are setting a few aside.

"VIEW MASTER" COMPONENTS

WHITELEY BONEHAM	
Chassis 12in. Tubes and Speaker	£6 5 0
A. F. BULGIN	
Switch and Tag Strip	12 6
T.C.C.	
All Condensers	£6 15 0
Metapolite Resistors	£1 8 0
Metapolite Pots (2)	9 0
Metapolite Coils and Chokes	£1 2 0
PLESSEY	
Pots and Chokes, Magnetic	£5 12 6
WESTINGHOUSE Rectifiers	£3 2 6
SELLING LEE. Plug and Socket and Fuse Holder	7 6
COLVERN Pots	19 3
G.E.C. Neon Lamp	2 9

VALVES

AMERICAN (9VA) TYPES. 0Z4, 1AH5T, 1AD6, 1E5G, 1A5, 1A7, 1N5GT, 1T5, 1P4, 1R5, 1T4, 1S5, 1S4, 1S5, 3S4, 3V4, 3Z4G, 5Y3G, 5Y3GT, 5Y4G, 5Z3, 6A4, 6A6, 6A7, 6A8, 6AB5, 6AC7, 6AG5, 6AG7, 6AH6, 6AK5, 6AL5, 6AL7, 6AM6, 6AQ5, 6AQ6, 6AQ7, 6AQ8, 6AS5, 6AS7, 6AT6, 6AU6, 6B8, 6BA6, 6BE6, 6BG6, 6BH6, 6BJ6GT, 6J5, 6J6G, 6J6GT, 6J7, 6J7G, 6J7GT, 6K6GT, 6K7, 6K7G, 6K7GT, 6K8, 6K8G, 6K8GT, 6L6, 6L6G, 6L6GT, 6R7, 6T6G, 6T8, 6U5G, 6U6GT, 6V3, 6V6G, 6V6GT, 6X4G, 6X5GT, 6Y6G, 6Y7G, 6Y7GT, 6Z4, 6Z7, 6AB7, 6BK7, 6BL7GT, 6BN7GT, 6SQ7, 6SR7, 6U5G, 6U7G, 6V6, 6V6G, 6V6GT, 6X5G, 6X5GT, 6Y6G, 6Y7G, 6Y7G/GT, 6Y6G, 7B6, 7B7, 7C5, 7C6, 7C7, 7H7, 7J7, 7N7, 7Q7, 7R7, 7S7, 7Y7, 12A6, 12AT6, 12BA6, 12D6, 12H6, 12J5GT, 12J7GT, 12K7GT, 12K8GT, 12Q7GT, 12SA7, 12SG7, 12SH7, 12SJ7, 12SK7, 12SL7, 12SQ7, 12SR7, 14A7/12H1, 14H7, 14R7, 14S7, 19, 25AG, 25L6GT, 25Z5, 25Z6GT, 26, 27, 30, 31, 32, 33, 34, 35/51, 36, 37, 38, 39, 40, 41, 42, 43, 50, 50L6GT, 75, 76, 77, 78, 80, 84, 807.

MULLARD. AC/041, AC/044, AZ1, AZ31, AZ40, C1, C2C, CBL1, CBL31, DCH35, CL4, CL33, CY1, CY31, DAC32, DAF91, DAF92, DF33, DF91, DF92, DK32, DK91, DK92, DL33, DL35, DL92, DL96, DL98, DM70, DW2/500, DW4/500, EA50, EAC91, EAF42, EB34, and hundreds of others omitted through lack of space. Also Brimar, Cossor, Marconi, Osram, Tunsgram, Philips—any type. If required as Valve Problem—write to us, marking envelope W.W.

RADIO BULB VALVES
246 HIGH ST. HARLESDEN

246, High St. Harlesden, N.W.10.

COMPONENTS SURPLUS AND SECONDHAND

RATHONIC DISTRIBUTORS

AMPLIFIER, 3/4 watts a.c./d.c. 2 valves and rectifier, gram and speaker sockets, warbling tone, mains on, separate volume and tone control, complete ready for use in metal case with carrying handle, £5/- (limited number only).

CONDENSERS (electrolytic) cap. 450v. 8mfd. 4/-, 4+8, 2/3, 8+16, 2/9, 16mfd 500v (as-Genl.), 6/- doz. 8+24mfd 450v block cap., 2/6, 8+16 350v. 1/9, 16+16 ditto, 2/-, 25mfd 50v. 1/- doz. 0.01, 1,000v. 5/- doz. 0.1 ditto 500v. 4/- doz. 4mfd 2,000v. 3/- doz. 1mfd 500v. 4/- doz. 0.02 tubular 2,000v. 5/- doz. 0.005, 0.01 (2,000v.) 0.001, 0.0005, 0.0002, 0.0001 mica, 2/6 doz. 0.05, 500v tubular, 1/6 doz. 0.01, 0.02, 2/- doz. condenser Bakelite clips, 2/- doz.

HEADPHONES, low resistance, 5/-, with band mic. complete, 3/3.

INDICATOR lamps with holder, red, silver band springs, 3/- doz.

MAINSBRIDGE condensers, 8mfd 2,000v. 3/3, 8mfd 1,000v. 3/-, 4mfd 1,000v. 1/9, 2mfd 350v. 7d. ditto 700v. 9d. 1mfd 700v. 7d.

RESISTORS, 270, 470, 1,500, 2,200, 10,000, 100,000, 500,000Ω, 1/- doz.

SPEAKERS, 8in with transformer, 4in box, 12/6 each.

TOGGLE SWITCHES, D.P., 1/3 each, S.P. 1/- each.

VOL. CONTROLS, ½ and ½ meg. with switch, 2/3 ea., 0.1 meg. 1/9.

VALVE screen and base, 4 for.

VIEWMASTER television book, layouts and instructions, 5/4 each.

WIRES, 1.5mm str., 5/6; 20mm ditto, 5/-; 100 ft. enamelled cotton and silk wires, all gauges. Nuts, bolts, washers, soldering tags, etc. best prices, all goods offered subject to being unsold, owing to fluctuation in prices, no lists available, send us your order, now, or inquiries to: 63, Old Hill Rd., London, N.16. Bis. 2661. (5209

LITTLEWOODS North London's best selection of radio and television components, get on a visit or post us your enquiries, to: LITTLEWOOD & GRUNER, Ltd., 27 Bassett Gdns., Finchley, N.3. Fin. 5080. (10035

CONDENSERS, 01.F 1kv 6d., 25v. 3/4 C. doz., 1uF 350v 4/- doz., 25uF 50v. 6/9 50v 4/6 doz., 1000uF 50/100v 6/9 doz., all post free.

HATFIELD RADIO, 78, Bishop Green Rd., N.9. (1424

VACUUM relays, thermal type 6v 30ma (approx.), will switch 450v 10 amps, length 5cm. diam. 1in. fitted with standard 4-pin valve base, 6/6 ea.

VELODYNES, Magslip and selsyns, many types in stock, send for list, technical advisory service available.

HOPTON RADIO, 1, Hopton Parade, Streatham High Rd., London, S.W.16. Streatham 6165.

RELAYS, Elliot type H d.c. moving coil resistance 1,000 ohms, pivs minus 100 ohms, operating current 250-520 micro-amps, s.p.c.o. contacts, price 35/-, each.

CLARE 450ohm coil, 5 amps, normally closed contacts, miniature type, price 2/6.

ADVANCE, 16-32 volts operating, s.p.c.o. contacts, miniature type, price 5/-.

STRUTHERS-DUNN 175ohm coil, s.p. normally open, heavy current contacts, price 5/6.

P.O. type 10,000ohm coil 2 sets, d.p.c.o. contacts, price 4/-.

VARIOUS types of relays in stock.

RECORD electric tachometers, 0-5,000r.p.m. 3-phase alternator and indicator complete, £4 each.

Infra-red lamp, osram, CVI45, complete unit, with series, ready for operation, price £2/15/-.

ALL the above items are brand new, tested and guaranteed, add 1/6 for carriage and packing.

WILFRID PRODUCTS, 216/222, Hurlet Rd., Glasgow, C.5. Tel. South 2565. (5225

TELEVISION, all parts in stock for 9/9 television, Vinal, Harries loops and focus coils, the trans model on view.—H.G. Radio, 1330, Hitchford Rd., Birmingham, 28. (4413

100 pf silver mica, 3/1 each; 20 pf ceramicons, 2/- doz. 0.01mfd mica wire ends, 2/6 doz. 0.1mfd 500v, 5/6 doz. 3.01mfd 1,000v, 5/6 doz. TRF coils, L and MW, with reaction matched pairs, with trimmer, 4/9 pair, all guaranteed.—List from T. C. Howell & Co., 20, McWilliam Rd., Brighton, 7. First only. (5224

GUARANTEED new surplus condensers, 1,500 sq. cd., 1,500 ld. 0mfd 450v 2/6, 8+8, 450 2/3, 8+16 3/3, 16+16 450v 3/4, 32mfd 450 3/9, 32+32 450v 4/6, 25+25, & 50+50 ditto 5/-, in metal holders amph. 6d. 8/10, 4mfd 500v 3d. EF50 holders, 1/2, fully shielded trans. 350-350 6v 2a, 20/6, 4, 22/6, 250-250, 6v 2a, 20/6, 4, 19/-, 350-350, 6v 3, 19/6, 4, 18/-, 4 pentode output, 7,000 ohms, 5/6, midget 4/11; multi-radio, twin ant. 5/9, heavy duty, 6/9/11, 12/6, resistors, big stock, ¼ & ½ watt 2½d. 1 watt 4d. Yaxley type switches, 1 pole 2 pos. 5d. Bakelite terminal set, 8BA, 32/BT 1/3, 6/10/11 0-40 ammeter 5/11; m.i. 0-25 ammeter 2/11, Dubilier mica, new, 1nd. 1/11, twin coil buzzer, 1/4, 1436 record matches, box 22pds 7/6, 5/pds P.M. speakers 14/9, elliptical 10in P.M. 25/-, 12in P.M. 2+3 ohms 35/-, resistance, in weatherproof cabinet, 22/6, hundreds other lines, new list available.

RADIO UNLIMITED, Elm Rd., London, E.17. Tel. Ker. 4815. (5223

L·R·S

FOR

PROMPT & EFFICIENT SERVICE

CASH OR EASY TERMS

When you purchase on L.R.S. Convenient Terms Formalities are reduced to a Minimum and you deal direct with us from beginning to end.

ARMSTRONG ALL WAVE CHASSIS

(incl. speaker and output transformer)

Model EXP/83.3. Cash price **£18.17.1** or £4 . 12 . 0 with order and 12 monthly instalments of 26/-.

Model RF/103.3. Cash price **£25 . 12 . 6** or £5 . 10 . 0 with order and 11 monthly payments of £2 . 0 . 0.

All other Armstrong Chassis are available on similar terms.

Also available on Easy Terms

GOODSELL-WILLIAMSON AMPLIFIER and TUNER UNITS

●

SOUND SALES AMPLIFIERS and TUNERS

●

PARTRIDGE TRANSFORMERS and CHOKES

●

"W.B." CONCENTRIC DUPLEX

a New speaker for the quality Enthusiast

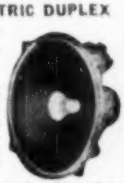

This twin speaker with Series Gap Magnet of Alcomax 3 covers frequency range from 50 to 14,000 c.p.s. Fitted with individual matching transformer. Flux in gap: L.F. 12,000 gauss. H.F. 13,000 on lin. pole. Speech-coil impedance at 1,000 c.p.s. L.F. 3 ohms, H.F. 30 ohms. Handles 6 watts. Cash price **£6 . 6 . 0** or £2 with order and 5 monthly payments of £1

●

A. C. BARKER'S LOUDSPEAKERS

●

GOODMAN'S LOUDSPEAKERS

Axiom 12 and 22 also 12" Standard Unit

●

HARTLEY-TURNER LOUDSPEAKERS

●

WHARFEDALE LOUDSPEAKERS

●

COLLARO RADIOGRAM UNITS

A.C. 505 M.B. Cash price **£7 . 6 . 3** or £2 . 2 . 0 with order and six monthly instalments of £1 . 0 . 0.

and other High-Grade Equipment advertised in "Wireless World."

All prices include carriage and packing

Please let us know your Radio requirements (enclosing 2½d. stamp) and we shall be pleased to quote.

Personal attention to all enquiries

THE LONDON RADIO SUPPLY CO.

Est. 1925

BALCOMBE, SUSSEX

SOLONS FOR YOUR SOLDERING JOBS !

Types available—65 watt oval tapered bit.
65 watt round pencil bit.
125 watt oval tapered bit.
125 watt round pencil bit.
240 watt oval tapered bit.

These five models will satisfy practically every soldering demand whether for the occasional household job or continuous soldering under workshop or factory conditions. With the Solon the heat is in the bit itself . . . continuously . . . hour after hour; all connections housed at end of handle away from heat. Each model complete with 6 feet Henley 3-core flexible. Now available from stock. Write for folder Y.10.

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden, London, E.C.1

PRESS BUTTON OHMMETER

FOR THE

SPEEDY

MEASUREMENT OF RESISTANCE

An instrument for high speed modern production, enabling continuity and resistance checks to be made on all types of electrical equipment.

Features

- Six ranges selected by press buttons
  0-100 ohms.
  0-1,000 ohms.
  0-10,000 ohms.
  0-100,000 ohms.
  0-1 Megohm.
  0-10 Megohms.
  Accuracy ± 1%
- Large eight inch diameter easily read meter
- Accuracy unaffected by variation of mains volts
- Mains operated 200-250v. 40-100 ~
- Low price—£25

For further particulars of this and other high-grade electronic instruments write to

HATFIELD INSTRUMENTS

175 Uxbridge Road, Hanwell, London, W.7

Telephone EALing 0779

COMPONENTS, SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1.

60-WATT amplifier kits for constructing the McMurdo 8-valve A.C./D.C. amplifier, low impedance input (suitable for moving coil mikes, etc.), by triple shielded mu-metal trans to E.F.37, R.C. coupled to triode, stragged stage (E.F.37), with switched bass and top cut provided, trans coupled to output stage, using 4 CL33s in parallel push-pull, large Partridge O.P.T. to 15Ω, rectifiers, 2 DR30s, parallel alternative input, high impedance to second stage for Xtal pick-ups, tuner units, etc., required input for full output, hum imp. 0.5v R.M.S., low imp. 3 millivolts. V.C. operates on both inputs, chassis isolated from mains, complete kit of first-class components (including Partridge trans. and valves, black crackle chassis ready drilled), black crackle and chromium case (15½×9½×8in.), circuit diagram, everything required for the construction of a fine job, £19 19s., carr. paid. Mansbridge condensers, 8mf. 1,000v. wkg. (4½×1½×3), 5/-; 2mf. 2,000v. test (5×1×1¼), 4/-; 8mf. 2,500v. test (6½×3½×2½), 2/6; 0.25mf. 9,000v. test (7×5×4), 5/6; 2mf. 2,500v. wkg. (6×5½×2½), 4/-; 4mf. 1,000v. wkg. (4×5×2), 4/6; 0.5mf. 3,000v. wkg. (3×2×1in.), 5/-, post extra.

PERSONAL receivers, 5-valve T.R.F. receivers, using 1.T.4s, contained in handsome bakelite case, with lift-up lid, size 7½×6½×5in. with lid closed, plastic carrying handle, frame aerial in lid, these receivers cover the medium waveband and operate from self-contained dry batts., standard types, W.1455 and 102, output to a pair of lightweight high-res. phones, controls of M. tuning and reaction, opening lid switches on, supplied brand new, with valves, batteries, phones, an ideal set for many purposes, invalids, camp, patients, etc., these receivers are top-flight surplus and are offered ready to play, £5/19/6, carr. paid; chassis (steel), 5×3½×1½in. drilled 4-button base holes, 1/3; 5½×3½×1½in. drilled 4-button base holes, 2/3. All 17×9½×2½in. drilled 7 int. oct and square, open ends, 5/3. E.H.T. trans. 4kv. 1ma. 2v 2a. secs. Pri. 230v. 50~, gives approx. 1,500v. with metal rectifying, 20/9, with tapped 200-250v. 50 c/s to 110v 40w. enclosed, 18/-; smoothing chokes, SH. 120ma. 140Ω 5/3, SH 200ma 100Ω 4/11, SH 200ma 100Ω 5/6, spectro. 10mf. 150v 1/3, 8mf. 350v 1/6, 8mf. 450v 2/3, 8+32 450v Can 4/-, 16+8 350v Can 5/-, 32+32 350v Can 5/6, 16+24+8 450v Can 4/-, 16+16 450v+20mf. 25v Can 4/-, 32mf. 450v Card 5/-, 52 450v Card 5/-, 50+100mf 350v Can 5/-, 16+8 double-ended Can 450v 5/-, 25/25v 1/3, 25/50v 1/3, 50/25v 1/6, 100mf 12v 1/-, 100/6v 6d, 50/12v 9d, 500mf 15v Can 2/-, 50+50 mf 450v+20mf 25v Can 4/6.

P.M. SPEAKERS, 5in. less trans. 9/11, with trans 4,500Ω, 11/6, 6½in. less trans. 10/11, 10in. with trans. P.P. 4,500Ω 21/-, output trans. 2,000/2½, 2,000/2½, 2,750/2½, 3,000/2½, 5,000/2½, 7,000/4½, all at 5/-, heavy duty, 7,000/2½ 5/6, 5 ratios, 7,000-3,500-1,750/2½ 6/6, 7,000-3,500-1,750/4½ 4/-; switches, standard tile, 2P.4W.W.B.M. 1P.10W.B.M. 2P.4W2B 2/6, 2P4W1B, plus additional wafer with shorting plate, 2/9, all have 5in spindles, resistors, 100 assorted, 47 values, ranging 180Ω-1μ, 100k 7/-; all standard types, best makes 10/6, post 6d. trimmers ceramic 5-50PF 2 on bar 9d, 5 on bar 1/3, single 1-15PF 4d, single 5-50PF Philips concentric airspace 6d. G.E.C. 5-25PF single 5d, 15-45PF twin 4d, 10-60PF variables, ceramic bases, 1½in spindles, 1in long, straight 25PF 9d, 50PF 1/-, 100PF 1/3, preset 50PF 6d, 50PF butterfly, spindle but. 1½in. dia. 1/-, rad. radio valves, valve 4s with 12v. 4-pin vib and 1G4 valve on chassis, 5½×3½×1½, output 250v 60ma. brought out on 8B screened lead, 17/6, meters, metal cased, 2in circular, 0-500 micros, 0-5, 0-10, 0-50, 0-100, 0-250, 0-500ma 0/-0.5a, with shunt, 5/-, bakelite cased, 2in square, 0/1ma 7/6, 0/5ma 6/-, 0/50ma 7/-, 0/500v series res. supplied, 7/-, 0/20v 5/-, bakelite cased, 2½in circular, 0/500 micros 16/-, 0/1ma 0/5ma 0/-, 0/50ma, 0/100ma, 0/200ma 6/6, desk type, 2½in, 0/1ma, 15/-, all meters flush mounting, visual indicators, type 1, crossover needle, 2/40 micros, with commutator magnet 5/-, B.M. dials as on R.F.26, less cutout, 3/11, rotary power units, type 104, 12v D.C. input, output 250v 80ma, 6.5v 2.5a, P.M. rotary, mounted on chassis with supp. 3/11, type 87, 24v input, output as 104, 3/11, 10-valve rec. R28/ARC5, covers 100-150 mc/s, with valves (inc. 4-717A) 42/6, carr. paid; Wilcox Gay V.F.O. covers 2-10 mc/s, with 0-10ma meter, supplied brand new, in original cartons with 807, accessories (plugs, leads, etc.) and instruction book, 45/-, carr. paid; 5-gang condensers, 500, 5-gang, 5in. spindle, 4/6; 2-gang, 500Ω, with spindle, fitted, 3/6; superhet coils, 1½-2½in. formers, M.W., H.F., A.E. or Osc., L.W., H.F., A.E. or Osc., 1/6 per set; I.F. trans. 465 kc/s, 2-gang, 2/6 per set; I.F. coils and band pass, 2/6; 10-pin plugs and sockets, with keyway, 1/6 pr.; 9-way plugs and sockets, with cover, 1/6 pr.; 7-way cables with 3W, 2½in spindle, 25K, 50K, 1M, 2M, 5M, 3/6; 4-way wire-wound twin 2.5K 2/6, twin 500Ω 2/6, twin 50K 3/-, twin carbon, 1M/1M, 2/6; telescopic aerials, all 13in. closed, 7ft. 6in. extended, 1/-; receivers, 15B, 4-valve, R.F., R.A.F. valves, ARC3B, VR52, VR53, I.F. output 560 kc/s, brand new, in transit case 22½×14×9in., carr. paid, bakelite cases, with lid, inside meas. 6×6½×3½in. without lid, 3/6, 12in. deep with lid, 4/6; frame aerial, lid requires fitting, ideal for portable set meters, etc., 8/6, post paid; lightweight headphones, high res., 2,000Ω, 5/6 pr.; aircraft radio receiver, type CRV 46115, 6-valve receivers, covers 42-165 kc/s, 4-5.3, 6.2-9, 9-12, 12-18, 18-30, 30-80 Mc/s, complete with valves, 4 Sockets, 195-260

(Continued on next page)

AMC

TELEVISION

Manufactured to "*Electronic Engineering*" Televisor Specification.

MIDLAND T.V. Sound and Vision Panels fitted with bezels and dust cores now available.

LINE OUTPUT TRANSFORMERS

NEW Improved SET OF GANTRIES COMPLETE

FOCUS COILS

LINE AND FRAME SCANNING COIL ASSEMBLIES

All Steel CADMIUM PLATED POWER AND TIME BASE CHASSIS valve-holders, 4 point and single socket and all necessary cut-outs.

SOUND PANEL CHASSIS ASSEMBLY, fitted with screens, valve holders, formers and dust cores.

VISION PANEL CHASSIS ASSEMBLY, fitted with screens, valve-holders, formers and dust cores.

9" C.R. TUBE SUPPORT for mounting on top of Gantry Assembly

9" CREAM MASKS.

5, SHAKESPEARE RD., FINCHLEY, N.3

Phone: FINchley 2188

BATTERY CHARGERS AND KITS SELENIUM H.T. AND L.T. RECTIFIERS

NEW GOODS, FULLY GUARANTEED

Per post

FOOLPROOF CHARGER KIT, 6 v. or 12 v. 2 amp. rectifier, no-exit interrupted and impregnated transformer, switch, fuse, 6v., 12v. 3 amp. charger 46/6, post 1/-; 6 v. 3 amp. rect. and 10 watt trans. 55/-. Mansbridge case with terminals, screws, etc. 17/6. Lamp indicator, 6v., 12v. as above 36/6, or with case 48/-, post 1/-. Mansbridge, 6v. 2 amp., 12v. 1 amp. with case 42/-, 6v., 12v. 2 amp. kit with another case, switch, etc. £5 10/-, wt. 10 lb.

HEAVY DUTY KITS for 6v., 12v. 6 amp. max., transformer, large fused rectifier, overcontrol, ammeter £4 10/-, or with 4 amp. £5 15/-, post 2/-.

"AUTOMAT" HEAVY DUTY 6v., 12v. charger, 3 amp. 4 fuse, foolproof, with 18 months guarantee, without rectification, only 65/-, post 2/-. Ditto as 3 amp. 79/-, 1 amp. 53/-, 12v. 1 amp. 84/-, 12v. 2 amp. 3 v. 6 amp. £6 10/-.

STC L.T. RECTIFIERS All new, not surplus, no 6-volts 4/10, 12v. 2 amp. 18/-, 12/15v. 4 amp. 21/-, 2 amp. 25/-, giant 60ma/6 amp. 30/-, 12v. 10 amp. 35/-, small type 75v. 1 amp. 9/6, 12v. 2 amp. 42/-, 12v. 6 amp. 62/-, many others with fuses if required.

SELENIUM SMALL SPACE H.T. rectifiers, 75ma. max. 5/10, 125v. 6/-, 250v. 9/-, 250v. 60ma 12/6, 250v. 120ma 18/-, 400v. 120ma bridge 12/6, 400v. 60ma bridge 18/-, 400v. 120ma bridge 25/-, 500v. 60ma 10/-, add post 6d.

ELIMINATOR KIT Trans., 2 rects., 2/4 mfds. condensers for 120v. 30 ma. eliminator with full amp. smoothing 35/-, with case 42/-, post 1/-.

CHAMPION PRODUCTS

43 Uplands Way, London, N. 21.

Phone LAB 4457.

A WINDOW WORTH LOOKING INTO —BARGAINS IN EVERY CORNER

Each s.	d.	
	3	**Ex Bc 522 Transmitter Chokes.**
	6	**Ex Bc 522 Transmitter Modulation Transformers.**
	9	**1in. Wafer Switches,** 1 pole 7 way. 3 pole 4 way.
1	0	**1in. Wafer Switches,** 4 pole 2 way.
1	3	**1in. Wafer Switches,** 2 pole 6 way. 1 pole 11 way.
1	0	**Co-ax. Cable,** 3ft. long fitted with Pye plugs each end.
	5	**Television Polystrene Coil Formers.** 1in. x ¼in. single hole fixing complete with iron slug.
	7	**Television Wound Coils,** as above.
	6	**Television H.F. Chokes.**
	6	**Television E.H.T. Valve Tops.**
	4	**Television Midget Moulded Mica Condensers,** 1,000 and 500 P.F.
	3	**Television Diode Holders.**
	3	**Television E.F.50 Holders,** Amphenol type.
	5	**Television E.F. 50 Holders,** Ceramic type.
	3	**Silver Mica Condensers,** all values.
	3	**¼ and ½ watt Resistors,** all values.
1	6	**Carbon Pots,** all values.
3	6	**L.F. Chokes,** ex W.D., 5 Henry 200 m.a.
4	3	**L.F. Chokes,** ex W.D., 25 Henry 20 m.a.
19	6	**Mains Transformers,** ex W.D., 380 x 380 volt 300 m.a. input 200/250 volt.
17	6	**Mains Transformers** ex W.D., 700 volt 20 m.a., 4 volt 2 amp., twice tested at 5,000 volt, input 230 volt. Ideal for scope.
3	6	**Midget L.F. Chokes** ex W.D. 7 Henry 60 m.a.
17	6	**Mains Transformers** ex W.D. 22 volt 4 a. 5 v. 6 a. 6.3 v. 6 a. 185 x 185 x 40 m.a.
17	6	**Heavy Duty Slider Resistances,** 5.7 ohms 8 amp.
2	6	**Mansbridge Condensers,** 6 mfd. 1,000 volt.
4	9	**0-5 M.a. Meters,** 2in. square, brand new and boxed.
92	6	**Ex R.A.F. Type A3531 Amplifiers,** complete with 45 Mc/s Television Strip with 10 E.F. 50 Valves, I.E.A. 50 and I.E.F. 54.
3	0	**"Trouble Free" High Voltage Condensers,** Mansbridge Oil Filled Type, 1 mfd. 4,000 volt.
3	3	**Ditto., ditto.,** 1 mfd. 5,000 volt.
15	0	**Type 24 U.H.F. Units,** complete with valves, brand new and boxed.
6	0	**24 Volt Blower Motors A.C. D.C.**
1	0	**Philips Trimmer Tools.**
Pair.		
1	3	**Ex R.A.F. 4 way plug and sockets.**
Doz.		
	3	**All Screws, Nuts, Bolts, Washers, Solder Tags** 2, 4 and 6 B.A.

Open all day Saturday.

3, LISLE STREET, LONDON, W.C.2

Telephone: Gerrard 8204.

COMPONENTS SURPLUS AND SECONDHAND

(Continued from previous page)

560-1,600 kc/s, 1-4-8 v. 4.5-120 mcs, switched, B.F., mixer, 9-1 F.s. det, output, using 4-125P7s, 1-125A7, 1-125R7, S.M. dial calibrated in k.c.'s, size 8", 7", 16in, provision for aerial or loop, powered from 230v, self-contained dynamotor, supplied with valves and dynamotor, used, £5/19/6, carr. paid. Mains trans. PRI 230/250v, 50 c/s, sec. 460v, 200ma, 210v, 15ma, 6.3v, 5a, 14/-.

RADIO compass MN26C 12-valve and containing 7-valve receiver covering the broadcast band 150/1,500 kc/s (2,000/200 metres) in 5 bands with 6W output. Valves: 3-6K7m's, 2-6N7m's, 2-6J5m's, 1-6L7m, 1-6H6m, 1-6F6. Powered by self-contained 28v dynamotor. Good condition, £5/19/6 (carriage paid).

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel: Museum 9188. (3015

FULL wave rectifiers, 12v 1a, 5/6, 12v 4a 12/6, 12v 7a 17/6, 36v 4a 35/-, all sizes available; mains units, 12v 16a d.c., 12v 50a a.c., £9/10; meters, 2-3in, at low prices; mains types w.w. vitreous resistors, 5-watt to 1,000 ohm 50watt from 5/- per doz.; time sw. controls, 15,000 and 1meg, 11/6; crystal oven thermostats, 44 C to 47 C, 5/-; everything available, s.a.e. stating requirements.

C. J. EMMS, Ltd., 26a, Colebrooke Mews, S.W.10. Fremantle 8941. (4889

OIL-FILLED condensers, 2μF/500v w., 6/-; doz., 6μF/500v w., 7/-; each; 4μF/2,000v w., 5/-; each; electrolytic condensers, 20μF/50v w., 6/-; doz.; 100μF/50v w., 1/-; each; tubular condensers, 0.1/50v a.c., 0.15/350v w., 2/6; 1/500, 2/6; doz.; 0.1/1,000v w., 3/-; doz.; 3/6; doz.; silver mica, standard mica, many values, 2p.f. to 0.01, 2/-; doz.; wafer switches, 2p, 4s, 1/3 each; please add sufficient postage.

J. E. LYNCH, 155, St. James Rd., Blackburn. (5319

SYNCHRONOUS clock units, self-starting, 200-250v ac, 50 cycle, fitted Sangamo motors, consumption 2½ watts, size 2½in dia, 2in deep, geared 1 rev 60 min, friction reset, ideal movements for making electric clocks, time switches, etc., nickel plated finish, complete with 12 to 1 dial train and 5in hands, price 22/6, post paid. Sangamo as above, final speed, one rev. per min., less dial train, ideal for dark-room process time, etc., price 20/- each, post paid.

THERMOSTATS—made by Unity, voltages up to 250-15/20 amps, temperature variable from 35/70 degrees Fahrenheit, price 26/- each; trade supplied.

G.E.C. 20mfd condensers, for power factor correction, with internal safety leak, rating 275 volts, 50 c/s/ac, price 8/- each; special quotation for quantities.

INDICATOR units, type 194a, fitted 5in and 6in cathode ray tubes type ACR.10 and V.C.R. 517B, and 17 valves, viz., 4 V.R.92, 3 V.R.91, 5 V.R.54, 5 V.R.65, metal rectifiers, metal transformers, potentiometers, resistances, condensers, etc., £5/10 each, carriage 10/-.

CRATER rotary switches, 250v 10 amps or single pole 5-way series, price 1/-, ideal for photo studio, etc., price 4/- each or 40/- per doz., post paid.

15 AMP Mercury switches, fitted with saddle and clip, 4/- each, postage paid.

A LARGE quantity of single items which we do not list, which are available to callers, also assortment of various ex-W.D. radar and radio equipment, relays, power packs, oscillograph units, gears, photographic apparatus, s.a.e. for lists.

H. FRANKS, 58, New Oxford St., London, W.C.1. One minute from Tottenham Court Rd. Station. Tel. Museum 9594. (3057

VIBRATOR packs, 6v input, 120v 50mA output, 9/6; co-axial plugs and sockets, 4/6 doz.; blower motors, 12/24 volt 10/-; two board 15/-; midget 2 amp accumulators 2/6; W619 variometers, 2/-; hand generators, 25 volts, 175mA and 500v 40mA, 7/6; variable condensers, 500pfs with high voltage, 0002 micro fixed condensers, 1/3, 12/3 doz.; 0-6A thermocouple meters 5/6; 0-2.5 and 0-5A thermocouple meters 5/6; moving coil headphones, with mikes attached, 4/6; carbon mikes 3/9.—Harbourn, 14, St. Mary's, Bedford. (3012

UNUSED ex-A.M. modulator unit type 64, in grey-finished case, size 23in x 9in x 9in made by Metropolitan-Vickers, valves, CV95, CV75, VT60A (807), two VR91, two VU133, also contains resistors, 4kv oil-filled transformer, two oil-filled h.v. condensers, relays, potentiometers, valveholders, metal rectifier, 6 Mansbridge condensers, S.M. and tubular condensers, transformers, chokes, suppressors unit and other useful items, price 29/9 each, carriage paid, or 24/6, without the VR91 valves.—Ward, "Corfield," West Cliff, Dawlish, Devon. (5014

WALTON'S OF WOLVERHAMPTON offer three amazing bargains, all post paid, partly stripped 1154TX, 4/11; 1196, 5/6; No. 187X, 6/-; R.5084, brand new in case but less valves 17/6; co-ax cable, 6d per yard, any length supplied; brand new 8in speakers, 12/6; TR.9 receivers less valves, 7/6; 24v camera motors, 12/6 (were 25/-); 0-500 micro-amp meters, 6/-; porcelain aerial mast fittings (insulators, 5/-; RF units, type 24 or 25, 17/6; EF 50 valve holders, 6d each; 22ft steel masts, 20/-, 11ft, 10/-; wood masts, approx. 15ft, 20/- for 4, and hundreds of other bargains; send s.a.e. today for list.

WALTON'S WIRELESS STORES, 203, Staveley Rd., Wolverhampton. (3061

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

Denco T.R.F. Matched pair Medium and Long Waves **6/6** each. Waymouth T.R.F. Matched pair M. and L. Waves **8/6** pair. Superhet Matched pair S. M. and L. Waves **8/9** or **11/6** pair. All types Wearite "P" Coils **3/-** each, in stock. Waymouth Midget Trimmers, 2in. 2ins. 1ins. Dias. Actual **6/3** or two **3/6** each.

Aluminium Chassis. Substantially made of gauge 16 S.W.G. with four sides. 3in. x 4in. x 2in. **3/3**; 4ins. x 5ins. x 2ins. **4/-**; 10ins. x 6ins. x 2ins. **4/11**; 10ins. x 8ins. x 2ins. **5/6**; 12ins. x 8ins. x 2ins. **6/9**; 14ins. x 9ins. x 2ins. **6/11**; 16ins. x 9ins. x 2ins. **7/3**; 18ins. x 9ins. x 2ins. **8/6**.

Meter Rectifiers. Westinghouse 250 micro-amp., **11/6**; 1 mA. **10/6**; 5 mA. **4/9**.

Selenium Rectifiers. H.T.L. Wave, 250 v. 50 mA. **5/6**; 100 v. 100 mA. **5/9**; 120 v. 100 mA. **7/6**. Bridge Rectifier 6 v. 1 amp. **6/9**; 12 v. 1½ amp. **12/6**; 12 v. 3 amp. **19/6**; 12 v. 6 amp. **25/-**; 24 v. 1 amp. **23/6**.

Charger Transformers. Each has input of 230 volts. Output 4a 9a volts tapped 12 v. 9 v. and 4 v. at 3 amps. **21/6**; 0/30 volts tapped 15 v. and 9 v. at 3 amps. **22/-**; 0/15 volts tapped 9 v. at 3 amps. **14/3**; 0/15 volts, 18 amps. **11/3**; set 18 volts tapped 9 v. at 6 amps. **19/9**; 15 v. (tapped 9 v.) 1½ amp. **11/9**.

Filament Transformer. Input 230 volts, output 6.3 v. 1½ amp. **7/6**; 4 v. 1½ amp. **7/6**. Input 200/250 v. output 4 v. 0/3 v. (1) amp. 4 v. 2 amp., 6.3 v. 2 amp. **19/6**. Input 230 v. output 6.3 v. 4 amp. **16/3**; or 4 volt 2 amp. **16/9**.

A Midget T.R.F. Battery Portable "Personal" Kit. A complete Kit of Parts to build a Midget 4-valve All-dry Battery Personal Set. Consists of Regenerative T.R.F. Circuit employing Flat Tuned Frame Aerial, with Denco Iron Dust Cored Coil, thereby ensuring maximum gain for Single-Tuned Stage covering medium Waveband.

Valve Line-up: 1T4 (R.F. Amp.), 1T4 (Detector), 1S5 (1st A.F.), and 3S4 (output). Includes latest Rola 5in. Moving Coil Speaker, and a Chassis already drilled and shaped. A consumption of only 7 mA. ensures long battery life. The Kit is designed for a cabinet, minimum size 8½in. x 6½in. x 6in. Detailed Building Instructions with Practical Layout and Circuit included with Kit make assembly easy.

Price for Complete Kit £3/18/9 (plus **16/7** P.T.) Built-in-the upgraded Cabinet as illustrated, **12/9**. Super Ready Rola Battery, **9/7**. Building Instructions, Circuit, etc., supplied separately, **1/6**.

"Wireless World" Midget A.C. Mains 3-valve Receiver. We can supply all the components, including valves and Moving Coil Speaker to build this set as specified in the March issue at a total cost of **£3**. Reprint of detailed assembly instructions and circuit supplied separately for **9d.** (incl. postage). A complete assembly outfit is now available to convert the 3-valve Receiver to the 3-valve Receiver, covering Medium and Long stations, at a total cost of **35/-** (inc. P.M. Speaker). **10/-** extra for drilled and shaped and complete assembly instructions. (Supplied separately for **9d.** incl. Postage).

"Wireless World" Midget A.C. Mains 3-valve Receiver covering S Long and Medium Wavebands. We can supply all the components, including drilled chassis, valves, moving coil speaker, etc., to build this set as specified in the February issue at a total cost of **£4/5/-**, including a reprint of the Assembly Instructions, showing component layout and circuit (reprint supplied separately for **9d.** incl. postage).

We can supply all the Components, including Valves, M.Coil Speaker, etc., **to build a Midget A.C. D.C. Mains T.R.F. 3-Valve (plus Metal Rectifier) Receiver** as designed and specified by a popular Technical Magazine, at a total cost of **£4/17/6**. A reprint of the assembly instructions, and layout available for **9d.**, incl. postage.

An Entirely Complete 3-Valve Amplifier Kit of Parts (operating on A.C. or D.C. Mains 200/250 volts). Has an output of max. 3 watts. Incorporating a 6in. M.Coil Speaker, Volume and Tone Controls. Price, including Wiring Diagram, **75/-**; (or without speaker) **65/-**.

"ELECTRONIC" VALVE VOLTMETER. We can supply the COMPLETE KIT OF PARTS, including the Valves, Diode and Meter, etc., to build this instrument as described in the January issue of "Electronic Engineering," complete with a reprint of the wiring diagram and assembly instructions (reprint supplied separately for **9d.** at a total cost of **£3/5/-**.

TELEVISION. The "Viewmaster" Televisor assembly instructions showing Wiring Diagrams and Practical Component layout, now available for **5/-**. We have the specified Components, including the Mazda Cathode Ray Tube, in stock. Mazda—Phoney—Cossor, etc., cathode ray tubes in stock. Separate Components also available.

"Electronic" Televisor. Complete range of specified Components to Scott's design, including assembly booklet available for **2/6**, London area, and **4/6** for Midland area.

• Please state voltage when ordering any of above Mazda Kits, etc.

• Send 3d. stamp for our **New Comprehensive Stock List**, this now shows the various Kits we have available, and also the latest Television Kits, with the individual Component Prices. Please never postage and packing when ordering.

STERN RADIO LTD.
109 & 115, FLEET STREET, E.C.4
Telephone: CEntral 5814 and 2280

SUCCESSFUL SALES! SATISFIED CUSTOMERS!

PENNINE RADIO

THE ALL SEASON SENSATION. ACCLAIMED THE COUNTRY OVER. THE INTIMATE RECEIVER WHICH COMBINES APPEARANCE AND PERFORMANCE. HOUSED IN A BEAUTIFUL WALNUT CABINET. EACH SET FULLY GUARANTEED.

HEIGHT 10", WIDTH 12½", 4 Valve SUPERHET DEPTH 5½"

THE SET THAT SELLS ITSELF! UNBEATABLE VALUE £11 9 7 INC. TAX

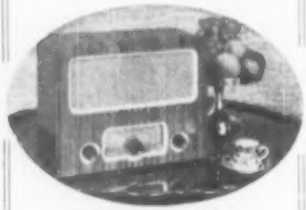

"THE ROVER"

SUPPLIED ONLY THROUGH SELECTED WHOLESALERS. ILLUSTRATED LEAFLET AND ATTRACTIVE DISPLAY CARDS.

PENNINE AMPLIFIERS

ELLAND YORKS ENGLAND

TEL. ELLAND 2107

SPECIAL BARGAINS

Govt. Surplus, Manufacturers' Surplus & Bankrupt Stocks.

We can offer for immediate delivery

Bakelite Accumulators. Ex-Govt. S.W.
Metal Rectifiers.
Condensers. All Types.
Meters.
Switches. Toggle and Taxley.
Headphones, L.R. and H.R.
Vibrators, 6 and 12 v.
Speakers. All types.
Volume Controls.
Output Transformers.
Chokes.

Receivers. R115S and 13SS, brand new in original cases.

Your enquiries are invited.

Wholesale and Export only

Please enquire for our 12 Page Bulletin

RADIO MERCHANDISE Co. Ltd.

65, Farringdon Road, London, E.C.1.

Telephone: Holborn 6377

COMPONENTS, SURPLUS AND SECONDHAND

MANUFACTURERS.—Enamel, copper wire, 4A silk spaces, demonstrations, all types, tuner blocks radio components, a.c. m.m., p.v. and black condensers, close tolerance and high stability resistors by City, all goods guaranteed.—E. R. Simmonds Ltd., 1a, Bevois Rd., Barrow Mills, Telephones: Harrow 2524 and 0515.

EX-GOVERNMENT heavy duty mains transformers, primary 100-250v 50 cycles, secondaries 500-0-500v at 250 MA., 500v at 100 MA., 12v 1 amp., 6.3v 5.5 amp. with common centre tap, and 4v 5.5 amp., massive job, weighing 25lb, size 7½in long x 7½in wide x 6½in high, brand new, in original installers, £3 each, carriage paid, England and Wales.—Weatherheads, Bletchley, Bucks. 5604

LONDON CENTRAL RADIO STORES.—Set of 4 heavy contacts for relays, etc., new, ex-G.P.O., 10/- doz. Mag and lack 4-v. thread mica with gold and silver, 3/- pair, low resistance headphones new, 4/6 pair, projector lamps, 12v 100watt, new, 5/6; camera mirrors, 21s. ea.; R.A.F. new, 7/6; centrifugal fans, 20s. new; 4/6, new carbon mike inserts, 2/6; moving coil inserts, 500ohm for miniature speakers, mikes, etc., 2/6; hand generators, 4/7; 4-gang selector switches, 5/6; high voltage relays, 1,000-ohm, 2/6; ex-tank, complete with aerials, 12/6; with remote impedance, 4/3; table stand mike inserts, 6/-; 200 Magslip receivers, Mark II, 5/6; 5,000ohm variable resistance on round porcelain base, 5/6; mains transformers, new, made to Haven, 11/5v input, 450v 60ma output, 6/6; small sliding resistance, ex-Admiralty, for voltage control, speed regulator, 50ohm 0.5amp, dimensions 6in x 4in, 2/6 each; we buy surplus gravel advert. P. 41.—London Central Radio Stores, 23, Lisle St., London, W.C.2. 5415

SUPREME RADIO, 746a, Romford Rd., Manor Park, London, E.12. Tel. GE 1260. Est. 16 years.—Potter type line tuner, with provision for EY51 valve, 22/6 ea.; one and three wanting coils, 25/6 ea.; mains trans. for R.F. receivers, £3/10 ea.; 5 to 250 m.a. choke, 15/9 ea.; 10 to 60 m.a. choke, 7/6 ea.; all parts in stock for London or Birmingham R.F. receivers; ceramic L.F.30 valve holders, 6d ea.; 3/6 doz. moulded filing for same, 8d ea.; cassette E.A.50 valve holders, 6d ea.; ½ watt resistors, 10K, 22K, 47K, 47K, 82K, 120K, 150K, 250K, 350K, 500K, 820K, 1 Meg., 2.2 Meg., 3.3 Meg., 4.7 Meg., 6.8 Meg., 1/9 doz or ass. 15/6 gross assd.; ½ watt resistors, 2.2 KΩ, 6.8 KΩ, 16 KΩ, 18 KΩ, 33 KΩ, 100 KΩ, 150 KΩ, 220 KΩ, 2/- doz. or ass. doz 21/- gross assd.; 1 watt resistors, 33KΩ, 47KΩ, 1 KΩ, 3.3 KΩ, 8.2 KΩ, 12 KΩ, 33 KΩ, 56 KΩ, 68 KΩ, 1 MΩ and 2 MΩ, 4/- doz or ass. doz 45/- gross only. CV 102 crystal diodes, 2/6 ea.; condensers, mild tub cardboard 40p, 1/6 ea.; 4+4mfd cardboard 450v, 2/- ea.; 16+16mfd 450v, 2/3 ea.; 16+16mfd cardboard, 2/9 ea.; 450v 250mfd, 20v 50mfd, 50v can or cardboard mfd, 1/- ea.; 2/- doz or ass. 8+8mfd 350v Dryfix, metal case mfd, 1/9 ea.; Midget mica mfd 0.0001mfd, 0.0002mfd and 0.001mfd, 9d ea., 5/- doz or ass. doz; fixed mica mfd, 3/3 type 30pf, 50pf, 100pf, 150pf, 200pf, 300pf, 400pf, 500pf, 600pf, 700pf, 1,000pf and 4,000pf, all at 2/- doz or ass.; 0.1mfd 2.2kv and 0.01mfd mica, tag end mfd, 2/6 doz or ass.

MANY other bargain lines in stock; terms n.r.p., no c.o.d.; send 9d extra for postage orders under £5, 2/6d extra all enquiries and lists. 10021

H.R.O. receivers, complete with 7 coils and power pack, £35. Hallicrafter S.27 receiver, £45; Hallicrafter S.27, SX24, ARR7, ARR18 and Hammerlund Super Pro receivers from stock at reduced prices; ex Army R107 receivers, complete and in good order, £10; Jotarc receivers all voltages and values, 20-watt rack mounting amplifiers, complete with heavy duty a.c. power pack, 200-250v, PX25 p.p. output, less valves, new, £5 each; 1/1 transformers, 5v-50v, all current ratios, special types to order at competitive prices, we invite your enquiries. 6 meters for AR88, H.R.O., Hammerlund, etc., available, mag slips, 10 strs. based, 5in, new, £5/5/- ea.; Bendix 522 transmitter, chassis, including 2 832 ball coils, etc., etc., 5/6 each, special offer of new meters, 5 m.a., 6/6; 100 m.a., 5/-; 3-inch moving coil speakers, 3/6; all 200 ex-Government, D.T.C. ball microphones, perfect, £4/17/6, 12ft and 15ft extended and p.m. speakers, Rola G12, Manaphons 8s. etc., low resistance phones, 3/6 pair; high resistance 4/6 or, U.S.A. m/coil, 7/6 pr. special offer of first grade m/coil meters, 500 m.a., 2½in scale, flush mounting, 7/6 each, 500 micro amp., with 2½in scale, 10/- each, 100 micro amps., 2½in scale, flush mounting, 65/- each, 50 micro amps., lin, projecting type, 50/- each; 1 m.a. meter rectifiers, 5/- each; telescopic aerial masts, adjustable, 25/- each; new, bearing compass, with heaters compartment in handle, new, 45/- each; transmitting valves, 807, 6/6, 813, 45/-, 211, 45/-, 50, 35/-, 4-65, 22/6, 866, 25/-, 1625B, 30/-, 721A, 851A, 721A, 1/- each available; h.t. rectifiers, type H 116, 5/- each; Bendix receiver, type 26, ARC5, 3-6 mcs., complete with 6 valves and 28v dynamotor, new, in sealed carton, £4 each; ex-Admiralty, 2½ cwt. 3-phase 50cycle/5½h, 5/6 each; a.c./d.c. 1-20hp motors 200-250v, suitable for sewing machines, 40/-; auto transformers from 100w up to 7kw in stock; new and competitive prices; wide stock of valves, tubes 600-3000 and Siemens high speed uniselectors, telephone handsets, press tacks, switches, etc.; ex-aerial units, special offer of mains transformers, 230-250v a.c., tapped 230-240-250, 100 m.a., 6v amp. 5v amp. 4½ each; postage extra on all items.

WRIGHT'S RADIO SPARES, 4, Lisle St., London, W.C.2. Tel. Ger. 1754. 10513

WE DON'T

supply anything Ex-Government

ALL BRAND NEW GOODS

—fully guaranteed—

AUTOCHANGERS IN STOCK

GARRARD, RC65A. A.C./D.C. Mixed Records. Standard lightweight Magnetic Head, **£20 15.-.**

GARRARD, RC65A. A.C. Mixed Records. Standard lightweight Head, **£15 13 6.**

GARRARD, RC70A. A.C. Non Mixed. Rim Drive, Standard Lightweight Head, **£10 9 1.**

E.M.I. MARCONI, A.C. Auto Changer, non mixed, Hi-Fi Head, complete with Transformer, **£10 10 8.**

COLLARO, RC500. A.C. Auto Changer, non mix, Crystal or Hi-Fi Head, **£10 15 0.**

CABINETS. Unpolished for all above changers. Motor Boards ready cut to fit plate, **£3 10.-.**

MOTOR AND TURNTABLE, with magnetic Pick-up and Auto Stop, **COLLARO** A.C., **£9 13 6**; **GARRARD,** A.C./D.C., **£12 9 2.**

MOTOR AND TURNTABLE ONLY—COLLARO, Induction type, A.C., **£5 18 4**, A.C./D.C., **£9 5 6.**

TAYLOR TEST GEAR

The entire range by this famous maker is now available on HIRE PURCHASE. S.A.E. for Catalogue and Terms.

ALL AVO TEST GEAR NOW IN STOCK

AVO 7, Leather cases, **£2 2 6.**

We are the largest actual stockists of Avo Meters in England. S.A.E. for Catalogue and Price List.

All items can be supplied C.O.D. up to 15lb in weight. Otherwise Cash with order please.

Special attention to Overseas Orders, which are free of Purchase Tax.

MODERN ELECTRICS LTD.

164, Charing Cross Road, London, W.C.2.

Telephone: Temple Bar 7587.

ELECTRONICS **DUPLEY** LTD

CRANMER AV. EALING. W 13.

Transformer and Coil Manufacturers to the Trade

Trade Enquiries Only

THE HAYES COMPANY · BIRMINGHAM

ARMSTRONG 83 chassis, 7 valve, 3 waveband, with 8-watt push-pull output. Mazda valves, ample gain for p.u. operation, large 3-colour glass dial, flywheel tuning, 10in. f.s., tone control, ready for cabinet mounting, tax paid **£18 17 1.**

The superb **ARMSTRONG 125** chassis. One of the most outstanding receivers marketed to-day. Specification includes 6F15 high gain R.F. stage, 2 I.F. stages with variable selectivity, coverage 11-200 metres in 3 bands, 190-560 and 900-2,000 metres. 4 switched positions of bass and treble boost, output stage of 4 6P28's in parallel push-pull with neg. feedback giving 15 watts, twin 5Z4 rectifiers and tapped output transformer. Total of 14 valves, tax paid **£41 1 -.**

ARMSTRONG TELEVISION CHASSIS, superhet receiver with R.F. stage, ample gain for "fringe area" operation. Two main controls, noise limiters on sound and vision, blocking oscillator time bases and a total of 21 valves. The complete receiver is on one chassis, ready for mounting in cabinet. Definition is outstanding, picture quality compares with any TV set, irrespective of price. Complete with 10in. speaker, **£66 3 4.** Write for details of these and other chassis. T.V. demonstrations daily, and on Wednesday evenings. All Armstrong chassis in stock. We despatch same day by passenger train.

THE HAYES COMPANY

1 ALCESTER RD., MOSELEY, BIRMINGHAM, 13

MAINS TRANSFORMERS

(Postage Extra under £2)

As supplied by us to the Ministry of Supply, B.B.C., Education Authorities, Admiralty, etc.

Interleaved and impregnated. Screened primaries (screened pattern).

Also built to your specification, prompt delivery quotations per "Return of Post."

DROP THROUGH TYPE TOP SHROUD

(a) 230-0-230 v. 60 mA. 5.0 v. 2a., 6.3 v. 2a. 15/6
(b) 350-0-350 v. 80 mA. 4 v. 4a., 4.3 v. 2a. 15/6

Following types have Universal L.T. windings: 4 v., 4 v., 5 v., 6.3 v., 2 v.

(1) 350-0-350 v. 80 mA. 17/6
(2) 350-0-350 v. 80 mA. 17/6
(3) 350-0-350 v. 80 mA. 17/6
(4) 350-0-350 v. 100 mA. 19/6
(5) 350-0-350 v. 100 mA. 19/6
(6) 350-0-350 v. 120 mA. 19/6

FULLY SHROUDED UPRIGHT TYPES

(1) 350-0-350 v. 100 mA., 6.3 4.0 v. 6 a., CT. 4.0 v. 2a. 39/-
(2) 450-0-450 v. 100 mA., 6.3 v. 6 a., CT. 6.3 v. 4 a., CT. 2 v. 2 a. 42/6
(3) 450-0-450 v. 120 mA., 4 v. 4 a., CT. 4 v. 4 a., CT. 4 v. 4 a. 44/6
(4) 450-0-450 v. 150 mA., 6.3 v. 4 a., CT. 4 v. 2 a., CT. 4 v. 2 a., CT. 4 v. 2a. 47/-

Note. Model (4) suitable for Mullard and Williamson Amplifiers.

Williamson Pre-Amp Mains Transformer

Single height, supplied by Wilkins. 19/6

WILLIAMSON AMPLIFIER REPRINT

Design details published by Wilkins. 3/6

WILLIAMSON OUTPUT TRANSFORMER.

Built to Author's specification. 1/12

Interleaved type £3.12 6

WILLIAMSON SMOOTHING CHOKES.

Choke No. 1. £1 2 6 Choke No. 1. 12 6
PRE-AMP CHOKE. 20H. 10 mA. 12/6 15/6

FEEDER UNITS.

High-class H.F. feeder unit with H.F. stage, switched aerials, three wave, completely aligned.

MODEL A. Gives 16/50, 195/550 and 800/2,000 metres. Price, including Purchase Tax £10 8 6

MODEL B DE LUXE. Gives 49/51, 195/550, 800/2,000 metres and six ranges of band spread. Price, including Purchase Tax £18 7 6

MODEL K. As Model A, but with Variable Selectivity and Inductive Impedance Coupling. Price, including Purchase Tax £19 15 0

"VIEW MASTER" TELEVISION RECEIVER.

All individual parts stocked, or will be complete kits of parts made as set out below.

CONSTRUCTOR'S ENVELOPE, containing full instructions, diagrams, diagrams, etc. 5/-, post free.

W.B. Chassis and Speaker, etc.	£6 5 0
T.C.C. Condensers Without £7	£6 15 0
Westinghouse Rectifiers	£3 2 6
Morganite Resistor Kit Without £1 6/-	£1 6 9
Morganite "Q" Type Pots	9 0
Pioneer Transformers, Focus Coils, etc.	£5 17 6
Colvern Wire Wound Pot meters	19 3
Bulgin Panels and Switches	12 6
Wearite Coils and Choke (Nil) £1 10/-	£1 2 0
Bulgin Low 70V Centrescale Dial	7 6
W.B. Table Cabinets	£6 17 6
12in. Tallon Console Cabinets	£13 7 6
9in. Tallon Console Cabinets	£13 7 0
12in. Tallon Table Model	£7 17 6
9in. Tallon Table Model	£6 5 6
9in. Mullard or Mazda C.R.T.	£11 6 10
12in. Mullard, Ferranti or Mazda C.R.T.	£15 2 5

S.T.A. AND TUNGSRAM VALVES.

Send for the valve you actually require. (10/0 post free.)

POLISHED ALUMINIUM CHASSIS, 16 S.W.G., 4 SIDES, 3 in. DEEP.

10in. x 8in. 8/6 12in. x 9in. 10/6
14in. x 9in. 11/6 16in. x 9in. 12/6

EDDYSTONE SHORT-WAVE COMPONENTS.

Full range available. Please quote required catalogue 64

SPECIAL OFFERS

.0005 3-gang T. Condensers	6 6
Coil Packs 3 W.B. Miniature	£1 9 6
465 Kc/s I.F. Transformers, pair	12 6
T.M.C. 1 mfd. T.Kc. Condensers	12 6

INSTRUMENT WIRES.

Comprehensive range in enamelled, cotton and silk covered copper wires from 36 S.W.G. to 40 S.W.G.

EX-GOVT. SURPLUS.

A good range of equipment at bargain prices.

S.T.C. Ball Microphones, fully screened £2/- £4 15 0
500 V.A. Auto Transformers, 115/230v. £2 2 0
PACKARD BELL PUSH-PULL PRE AMPS. In sealed cartons with screen and tag valve. 12/17 and 21/6 16 6

TRANSMITTING VALVES

Nil 6/-; 931 23/6; 832 27/6; 832A 9/6; QS 9/6.
VCR97 C.R.T. with maker's guarantee £1 12 6
Quantity discounts on Ex Govt. Valves.

SEND NOW 5d. in stamps for 64 PAGE CATALOGUE

Terms C.W.O. or C.O.D.

COULPHONE RADIO

"The Return of Post Mail Order Service"

53 BURSCOUGH STREET ORMSKIRK, LANCS.

Phone 987

NOTICES

BRITISH SOUND RECORDING ASSOCIATION.

MEMBERSHIP is open to all professional and amateur recording engineers. High quality tape-production enthusiasts are also specially catered for.

THE B.S.A.R. Diary for 1950 is available to non-members, price 4/6; it contains valuable data on recording and reproducing topics, full information, with brochure and membership application form from the Membership Secretary, Harrie J. King, 48, Mount View Rd., North Chingford, London, E.4. (2119

WANTED, EXCHANGE, ETC.

WANTED Magnetophon Type B with spares (adjuster not required).—Box 2505. (5024

WANTED for Bendix radio compass, loop LP 21A or LP 51A, and relay BR22A.—Hagmart, Kingsweir, S. Devon. (5279

WANTED, airplane relays and push-button units, any condition, large or small quantities; highest prices paid.—Box 5435. (5552

WE pay top prices for used test equipment, all types.—University Radio, Ltd., 22, Lisle St., London, W.C.2. Tel. Ger. 4447 and Ger. 5582. (1990

WANTED, ARSDs, SX25s, each in part exchange, no obsolete stuff or repair.—P.C.A. Radio, Cambridge Grove, London, W.6. Tel. Riv. 5279. (1990

WANTED, all kinds of laboratory test equipment, standard signal generators, broken oscilloscopes, "Q" meters, etc.; send price and details to HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 3079. (3307

WANTED all types of radio equipment, test instruments, radio receivers, personal sets, television, components, etc., etc.; call, write, send or phone.
MILLER'S RADIO, 86a, Newport Court, Charing Cross Rd., London. (5221

WANTED, 12-inch roll winder complete with paper interleaving attachments. Lancashire or Anglo-preferred; price, condition and where may be inspected.—Box 5456. (5329

WE buy for cash, new, used radio, electrical equipment, all types, specially wanted: radios, radiograms, test equipment, motors, chargers, recording gear, etc.—If you want to sell at the maximum price call, write or phone to University Radio, Ltd., 22, Lisle St., Leicester Sq., W.C.2. Ger. 4447. (1990

REPAIRS AND SERVICE

MAINS transformers rewound, new transformers to any specification.
MOTOR rewinds and complete overhauls. Brewster's Rewinding Service, guaranteed.—F.M. ELECTRIC Co., Ltd., Forest Bldgs., Waterloo Gate, Nottingham. Tel. 13117. Tel. 5655.

MAINS transformers rewound promptly, usual guarantee. Radio Rewind Service, Brighton, nr. Dolgelley, N. Wales. (5248

REWINDS. Our winding dept. having been extended and re-equipped with the latest machines, now offers an unrivalled service.
ALL types of transformers, field coils, chokes and solenoids, up to 1lb. weight, rewound promptly, rewound as an exact replica or to your specification, incorporating the following special features:—
LAYERS paper interleaved, wound with Lemex insulated wire, vacuum impregnated, full comprehensive testing during all stages of rewind and final high voltage interwinding insulation test of at least 2kV, connections made to tag panels or left to required length, insulated, small external appearance.
SEND (quoting name and model of receiver or giving particulars of requirements with number and type of valves used.
TO: Ash & Co., Ltd., Vanguard Works, Corfe Mullen, Wimborne, Dorset. Tel. Poole 600. (5280

MAINS transformers rewound or constructed to any specification, prompt delivery.—Bede Transformer Co., Ltd., Bedcross, Bede Trading Estate, Jarrow. (5146

TELEVISION sets converted from London to Midland station, radio repairs and assembly service to home builders.—S. W. Shackle, Bush St., Harlington, Hayes, Middx. (5165

MAINS transformers rewound or constructed to any specification, prompt deliveries.—Avon Transformer Co., 20, Heath Terrace, Leamington Spa, Warwicks. (5426

REPAIRS to moving coil speakers, filter coils fitted. Send rewound or altered; speaker transformers, field coils rewound; guaranteed satisfaction, prompt service.
L.S. REPAIR SERVICE, 48, Trinity Rd., Upper Tooting, London, S.W.17. Balham 2559.

TELEVISION, radio and amplifier repairs or modifications. Home built receivers aligned and tested, quotations by return, any type transformer or coil supplied.
BERNARDS, 12, Chesterton Rd., Putney, London, S.W.15. Put. 7536. (3199

THE AMAZING 103

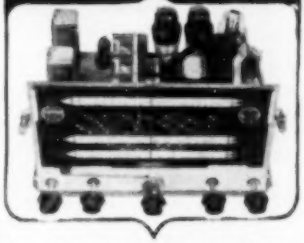

No other receiver in its price-class can approach the Armstrong RF103 Type 3 with its 20-valve circuit, highly efficient R.F. stage and its two stages of I.F. amplification with a selectivity better than 7 Kc/s. Among its many refinements are the three stages of A.V.C. negative-feed-back, slide rule dial and flywheel tuning. Wave band coverage is from 16-50, 195-550 and 800-2,000 metres, and mains voltage is 200-250 A.C. When the chassis is used as a gramophone amplifier the large amount of amplification available enables a high quality pick-up of the miniature type to be used without additional amplification.

19 Gns. plus P. Tax

OTHER ARMSTRONG CHASSIS

Model EXP83 2. An eight-stage all-wave radiogram chassis is designed to provide quality radio and record reproduction for the "not-so-rich." **£15 . 8 . 9** Plus P. Tax

Model 125 2. The "Armstrong" triumph—a 14-valve all-wave radiogram chassis with a S.W. band down to 10.9 metres. The chassis for the man who wants the best. **£33 . 12 . 0** Plus P. Tax

ARMSTRONG TELEVISION—MODEL T.V.20. A wide-range 21-valve instrument incorporating a 12in. C.R. Tube. **£52 . 10 . 0** Plus P. Tax

Write now for full information

ARMSTRONG

THE CHASSIS PEOPLE

Armstrong Wireless & Television Co. Ltd., Warlters Road, Holloway, London, N.7. Tel. NORth 3213

3559

AMERICAN RADAR INDICATORS

Type ID-6 APN-4, with 5-inch 6.3 v. 5CPI electrostatic Television or Oscillograph C.R. Tube, and 26 Int. Octal 6.3 v. Valves : sixteen 6SN7-GT twin triodes ; three 6SL7-GT high-mu twin triodes ; one 6SJ7-GT R.F. pentode ; and six 6H6-GT twin diodes. 100 Kc/s Crystal Unit ; 23 Potentiometers, countless Resistors and Capacitors, all oil-filled or moulded mica. Hundreds of pounds worth of super quality gear with countless applications, for only **£6 17 6** carr. paid, subject unsold. Limited quantity, immediate despatch, cash with order.

WIRELESS SUPPLIES UNLIMITED,

264-266 Old Christchurch Road, Bournemouth, Hants.

TELEVISION RECEIVERS
SCANNING and FOCUS COILS
TIME BASE COMPONENTS
7KV. EHT. RF. UNITS and TRANSFORMERS

Publications post free

HAYNES RADIO LTD.
Queensway, Enfield.

WILCO ELECTRONICS

POWER PACK. Input 200/250v., 50 c/s Output 500-0-500v. 120 m.a. 4v. CT 4 amps. 4v. CT 4 amps. 4v. CT 3.5 amps. Rack mounting. **£4 10 0.** Carriage extra.
TRANSFORMERS ONLY, as above. **45/-**.
L.F. CHOKES. 20 henry 150 m.a., **22 6** each.
CONDENSERS. 8 mfd. 750v. D.C. block type. **10/6** each.
VCR 139A C.R TUBES. 2½in. electrostatic. **15/-** each.
VCR 97. 6in. electrostatic, **35/-** each. Postage and packing 2/6 holders for 139A, **2/-** each.
VCR 140. 12in. magnetic, **£6**. **VCR 516**, 9in. magnetic, **£5**. For callers only.
RACKS P.O. Standard 19in., with heavy angle iron base, 5ft. **60/-** 6ft **70/-** 5ft. 6in. Lighter Type **50/-**.
OPERATORS DESKS. Standard 19in. Rack mounted 12in. deep, **15/-**.
SPEAKERS P.M. 5in. Rola, in case, **17 6**.
AMPLIFIERS. Push-pull PX25s. 15 watts output. Complete with Power Pack. Less valves. Rack mounting, **£6**, carriage extra.
CO-AXIAL CABLE for Television down leads. 75 ohms, **10½d.** per yard.
MICROAMMETER—F.S.D. 25 microamps. scaled 0-500. 2½in., **57/6**.
VOLTMETERS. 0-100 A.C. M.I. 2½in Flush. **17 6** each. 3½in., **22 6** each.

304 LOWER ADDISCOMBE ROAD, CROYDON ADD. 2027

REPAIRS AND SERVICE

LOUDSPEAKERS rewound and cones fitted, any make, prompt service.—Dodds Radio Service, 24a, Bullington Rd., Oxford. [5509

ALL types of ammeters, voltmeters, Avos, etc., repaired; quick, efficient service, estimates free.—Dauvin Instrument Co., 91, Princedale Rd., London, W.11. Tel. Park 4465. [5656

ELECTRICAL measuring instruments of every make repaired and standardised.—The Electrical Instrument Repair Service, 328, Kilburn Lane, London, W.9. Tel. Ladbroke 4166. [5715

A REWIND service which duplicates or modifies as required; transformers, loudspeakers, etc.; prompt returns.—Haidel Services, 49, Lr. Addiscombe Rd., Croydon. Cro. 6527.

REPAIRS.—E.H.T., mains and O.P. transformers, field coils and choices, also attenuators and pottles; new coils, chokes (ex) to any specification, all work fully guaranteed.—Wilkinson, 21a, Offerton Rd., Lond., S.W.4. 751, Harrow Rd., N.W.10. Tel. Nr. Ladbroke 2846.

SERVICE with a smile.—Repairers of all types of British and American receivers, coil rewinds, American valves, spares, line cord.—P.R.I., Ltd., 22, Bowland St., W.1. Museum 9075. [5575

RADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs, armatures, F.H.P. motors, vac. units, portable tone arm, speed, devices.—159, Fieldhurst Terrace, N.W.6. Mal. 5135. [5625

STUNDY rewinds, mains transformers, chokes and fields.—First-class work, prompt delivery and satisfaction guaranteed.—Stundy Electric Co., Ltd., Dipton, Newcastle-on-Tyne. [2450

REWINDS and conversions to mains and output trans., pick-ups, fields, clock coils, mic vibrator units, etc., from 4/6, p.p. equipment a specialty, all work guaranteed.—N.L. Rewinds, 4, Hitchcock Rd., N.3. [5551

A SECOND-to-none rewind service, reliable, neat, return of post service, your television requirements promptly executed. EHT, LHT and heater transformers, stamp for quotations.—R. E. P., 172a, Ashton Rd., Oldham. [5519

24-HOUR service, 6 months' guarantee any transformer rewind, mains outputs and choks, etc., all types of new transf., etc., supplied to specification, business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth.

METROPOLITAN RADIO SERVICE for rewinds, mains and E.H.T. transformers, chokes and fields, also dedicated 5-6 daily, new transformers designed and manufactured singly or in quantities.—Metropolitan Radio Service Company, 100a, Finchley Rd., London, N.W.11. Tel. Speedwell 5000.

NATIONAL RADIO SERVICE & TELEVISION Co.—the complete service for high fidelity installation and maintenance, high fidelity new service and amplifiers built to specification, converted and modernised, also transformer and armature rewinds and speaker repair service.—32, High St., St. John's Wood, N.W.8. Tel. Primrose 6725. [5555

WORK WANTED

SPECIAL receivers, test gear, electronic apparatus, experimental and design work.—If you have a problem which needs expert handling, write, 'phone or call.—J. Mott, B.Sc., A.M.I.E., BCM/HIFIDEL, London, W.C.1.

DRAUGHTING, tracing and photoprinting services, estimates free, contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications, sub-contracting work of this nature undertaken.—DRAWING & TRACING Ltd., 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 5606. [4185

WE offer the facilities of our modern factory to the radio trade, our surplus capacity includes light electrical and mechanical assembly, equipped with Flowline conveyors readily adaptable to radio trade requirements; modern tool design office and tool room, for press and jig operations, machine shop including automatics, capstans, power and hand presses, rotary swaging, production work undertaken. A.D. and A.R.B. approved; competitive prices and quality assured.—SUTER ELECTRICAL ENGINEERING, Ltd., Fuseite Building, Welsh Harp, London, N.W.9. [5501

MISCELLANEOUS

ALUM chassis, punch, or fully drilled to your requirements.
12in.×8in.×2½in. open ends, 5/6 post paid.
14in.×10in.×2in. four sided, 6/9 post paid.
9in.×7in.×2in. four sided, 5/9 post paid.
12in.×9in.×2in. four sided, 5/6 post paid.
16in.×9in.×2½in. four sided, 7/9 post paid.
14in.×8in.×2in. four sided, 6/6 post paid.
12in.×8in.×2in. four sided, 6/6 post paid.
INT octal holes 3d. other valve holes 6d. other prices on application, s.a.e. please.
TAYLOR & TOY, Dog & Duck Ferry, Worcester. [5511

ALL THE BEST
at one address.

HOLLEY'S RADIO STORES

CALL AND HEAR

LEAK AMPLIFIERS, TUNER AND PICK UP.
WILLIAMSON AMPLIFIER AND TUNER.
VORTEXION "STEREOPHONIC" AMPLIFIER AND ACOS "GP20" PICK UP.
SOUND SALES AMPLIFIERS, T.C. UNITS, RADIO TUNERS AND PICK UP.
ACOUSTICAL AMPLIFIER AND R.F. TUNER.
RADIO TUNERS BY RUCO.
LOUDSPEAKERS BY A. C. BARKER.
GOODMANS "AXIOM" SPEAKERS.
WHARFEDALE NEW CORNER SPEAKER.
ALSO, ARMSTRONG ALL-WAVE CHASSIS, from **£18 7 1.**

at 285, Camberwell Road, S.E.5

Phone RODney 4988

Open all day Saturday.

TESTOSCOPE *Mains Tester*

For high & low voltage testing:—
100 & pre-set volts A.C. or D.C. With fuse-indicator holder gold.

VISIT STAND C732 B.I.F.

RUNBAKEN · BIRMINGHAM 1

POST RADIO SUPPLIES

OFFER EX STOCK

COPPER INSTRUMENT WIRE, ENAMELLED, TINNED, LITZ COTTON AND SILK COVERED.

Most gauges available.

B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets.

EBONITE AND BAKELITE PANELS, TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.

Latest Radio Publications.

THE CRYSTAL VALVE
as used in radar receivers.

These Crystal Valves or Diodes are not Government Surplus but brand new goods manufactured by one of the largest and most famous Radar Equipment Manufacturers in the country.

3/6 each, postage 2½d.

Protective Tube and Fixing Brackets, 3d. extra. Send stamped addressed envelope for comprehensive lists. Trade supplied.

POST RADIO SUPPLIES

33, Bourne Gardens, London, E.4.
'Phone: Clissold 4688

VOIGT PATENTS LTD.

March 1950

From Mr. Voigt.

Readers will remember from my message (Sept. "W.W." page 33) that I intend to cross the Atlantic, lecture etc. from Toronto as centre, explore the "hi fi" position out there, and maybe sell a few Voigt speakers.

Recently, when my health curve was rising, passages were booked for April. An X-Ray since then proved a spinal fault to be involved, and a support (nothing like this!) — has been rushed through. The address for Voigt speaker demonstrations in Toronto is not yet known. Interested Toronto enthusiasts please send in your names.

In my absence correspondence will be dealt with by others. Also a part time demonstration service point is being organised at No. 7 The Parade, Wells Park Road, Sydenham, S.E.26. Here my instrument maker when not away at sub-contractors will demonstrate by appointment. Evening demonstrations can be arranged for Fridays 7 p.m. (No phone yet).

If your amplifier delivers an undistorted output, you should have A horn-loaded Voigt speaker with remotched diaphragm. The open P.M. Type is **£40** ex-works. Horns (in the white) **£19 10/-** or **£47 10/-** ex-works.

You can order direct. (*Trade also supplied against pro-forma*).

VOIGT PATENTS LTD.
C.O BCM/VOIGT, LONDON, W.C.1

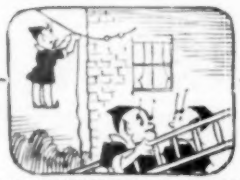

THE "FLUXITE QUINS" AT WORK

"We must FLUXITE our aerial" "and E.H. "Let's climb without further delay."
"I say, don't look down!"
"There'll be a fine row"
"I've taken his ladder away!"

See that **FLUXITE** is always by you—in the home, garage, workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, **10d., 1/6** and **3/-**.

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire AND SOLDER. It's simple — with FLUXITE — but IMPORTANT.

The **FLUXITE GUN** gets **FLUXITE** where you want it for a simple pressure. Price **2/6**, or filled, **3/6**

FLUXITE

SIMPLIFIES *ALL* SOLDERING

Write for Book on the Art of "SOFT" Soldering and for Leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1/6 each

FLUXITE LTD. (Dept. WW) BERMONDSEY STREET, LONDON, S.E.1.

MISCELLANEOUS

FOR sale, large number "Radio News" and "W.W." mid 1940.—Box 5357. [5216

SUPERB quality walnut radiogram cabinets, stamp, leaflets.—Cabinetware, 1A, Hryce St., Blackburn. [5081

RADIO and television cabinets made to individual requirements.—Sketch and details to Burman's, 64, Reighton Rd., London, E.5. [5080

WALNUT radiogram and television cabinets, manufacturer's samples, few only, stamp details.—Walters, 501, Hale End Rd., E.4. [5310

MEGATRON selenium photo-electric cells, all standard sizes in stock from 17mm. dia. 25/6 to 57 x 16 5mm 5/-; s.a.e.—full details. G.R. PRODUCTS, 19, Repton Rd., Brixton, 4. [5182

ALUMINIUM chassis and panels, any size manufactured quickly, holes punched for valveholders, etc., plain or anodised finish.—E. A. D., 19, Broad Road, Wallington, Sussex.

ALL new ideas, inventions and contributions particularly television tubes which make the manufacture of cheap TV set possible, will be well paid for if practical.—Full details to Box 5435. [5435

TELEVISION mast sections, 8ft 9in x 8in dia. 1 9in light 11lbs, weld-free steel tubular, reach any height, 15/6 ea., 6 or more 13/9 ea., all carr. paid.—Foundation Oil Co., Ltd., Oxford Hill, Norwich. [4971

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A.O. Engraving Co., Windmill Rd., London, S.W.19. Brass, bronze, etched, perspex, dials, one knob or repetition equally entertained. [5084

W.W. Scope (May '49) with separate p.pack appt. "W.W." and set details supplied, well made, £10, both vols. "Sources R.D." Design, "Tremain's Measurements," and 5 other books on design and constr., all good, mint 25 "W.W.s" from '47, 40-odd I.P.E. Journals, accept £2/10 the lot.—Write The Villa, Oddington Rd., Stow, Glos. [5244

COPPER wire enamelled, tinned, Lits, cotton, silk covered, all gauges, BA screws, nuts, washers, soldering tags, eyelets, ebonite and laminated bakelite panels, tubes, coil formers, Tufnol rod, headphones, fuses, etc.; latest radio publications, full range available, list s.a.e. Trade supplied.—Post Radio Supplies, 33 Bourne Gardens, London, E.4. [1454

FLUORESCENT lighting, 80 watt tapped, £3/28/6; 40 watt, diffuse, 27/6; 80 watt chokes (tapped), 17/6, power factors, 4/6, starters, 5/-, holders, 1/-; 80 watt ballast (tapped) unit, 31/6; 40 watt, diffuse, 28/6; 40/40 watt fitting complete, 56/-; 25 models to choose from; all goods guaranteed, post and packing extra, send 2d. for inquiries.—Radionic Industries (Dept. WEW), Works, 63, Oldhill St., London, N.16. Sta. Stoke. [5269

SITUATIONS VACANT

GOVERNMENT OF IRAQ

CHIEF Radio Engineer required for Basrah Port Directorate for one tour of three years in first instance, salary I.D.80 (rising to I.D.110) a month. Cost-of-living allowance between I.D.10 and I.D.14 a month. Free Dinar I.=£1. Provident fund. Free passages. Candidates must possess P.M.G. 1st Class Certificate in Wireless Telegraphy and be A.M.Brit.I.R.E. or hold City and Guilds Final Certificate in radio communication or be A.M.I.E.E. with specialised knowledge of telecommunication work. They must have practical experience of commercial wireless transmitters and receivers and electrical equipment, experience at a large civil airport an advantage. Apply at once by letter stating age, whether married or single, and full particulars of qualifications and experience, and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M.N.24077/3B, on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications, and will communicate only with applicants selected for further consideration. [5266

SERVICE department of large radio manufacturers in North London has vacancies for:—

(a) Radio Engineers.
(b) Receiving Clerk.
(c) Office Junior (male or female) and workshop junior.

APPLICANTS for (a) must have at least secondary school education and hold matriculation or school certificate and have adequate training in radio theory and practice.

FOR (b) qualifications should include education to school certificate standard and some practical knowledge of radio.

THE vacancies under (c) offer opportunities for boy or girl with good education, capable of accurate and conscientious work, and anxious to learn and progress. Some interest in radio would be an advantage.

APPLICANTS, in own handwriting, must include full particulars of education, qualifications, technical and commercial experience, age and salary required.—Box 406, c/o Rio Publicity Ltd., 7, Pitfrey St., London, W.1. [5264

STANDARD ENCLOSED RACK

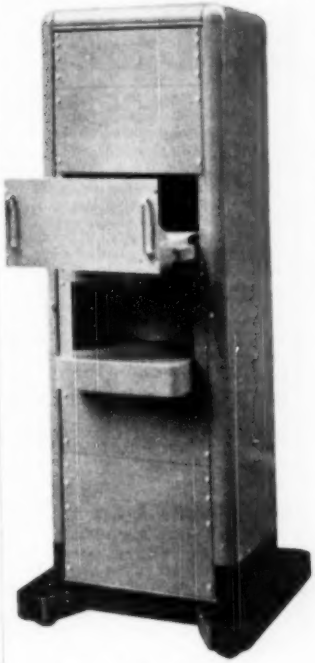

Registered Design No. 858451

The Imhof 6ft. and 4ft. enclosed racks are standard articles, available from stock. They embody several unique features in their design. For example, both sides as well as back door are swung on lift-off hinges, and multiple units may be formed using only two end doors. Panels, chassis, chassis runners—telescopic and fixed, desk unit, gram unit and mobile base are all standard accessories.

Write for leaflet giving full details or catalogue of our complete range of standard cases, chassis, handles, etc.

IMHOF'S

112-116 NEW OXFORD ST., LONDON, W.C.1
TELEPHONE: MUS. 7878 (20 lines)

Thinking of building a Television Set ?

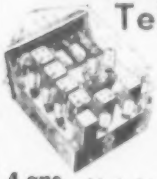

10 VALVE
1½ METRE
SUPER-HET

4 gns. Carriage Paid

Ideal for conversion into Television Receivers. I.F. 12 Megs. Band width 4 megs.

Co-axial input and output sockets. 10 Mazda Mains type VR65 (SP61) valves. 6·3 volt filaments.

This receiver comprises a one pre H.F. amplifier, diode mixer, oscillator, five I.F. stages, second detector and audio stage. It requires a power supply of 300 volts 60 mills. H.T. and 6·3 volts 4 amperes L.T. It may be modified either as a vision or sound only receiver or sound and vision receiver. The H.F. frequency changer and oscillator tuned circuits can be modified to the television frequencies by shunting the coils with 30 p.f. trimmers.

Dept. W.W.,
WIRELESS INSTRUMENTS (LEEDS) LTD.
54-56 The Headrow, Leeds. Tel. 22262.

TRANSFORMERS & COILWINDERS

NEW AND REWINDS

All transformers Interleaved & Impregnated Tested or (1) Shorted turns (2) Insulation at 2 K.V. minimum. E.H.T. A SPECIALITY.

"K.E." MIDLAND SOUND & VISION COILS 15/6 SET. C.W.O.

J. E. THORNBER & SONS
3 DEAN AVE. MANCHESTER 16

CHO 1049 EST. 1921

SAMSONS SURPLUS STORES

Ex Govt.

H.T. TRANSFORMERS

[illegible] 17/6 post free.

[illegible] 4 v 5 a. 35/- Post 6/6.

[illegible] 35/- Post 6/6.

[illegible] 65/- Post 6/6.

[illegible] 45/- Post 6/6.

[illegible] 12/6. Post 1/-.

Sound Serv. H.D. Transformers. Price 30/-. Sec. 1v 1.5 a and 4v 0·5 amps. £4 10/-. Post 4/-.

Grand Serv. Varac Transformer. Input adapted [illegible] 65/-. Post 4/-.

Heavy Duty Auto Transformers. [illegible] 4/-.

169-171 Edgware Road, London, W.2. Tel. Paddington 7851
125 Tottenham Court Road, W.1. Tel. Museum 4002
All orders and enquiries to our Edgware Road branch please

SITUATIONS VACANT

CROWN AGENTS FOR THE COLONIES

ELECTRICAL ENGINEER (ELECTRONIC) required for the Institute of Geriatrics, Colonial Office. Salary scale £750 x [illegible] rising to £1,000 a year. Extra duty allowance of 5 per cent in addition; salary and passage at present. Establishment will be considered for this post, after satisfactory service, and on vacancies occur, of appointment to the established and pensionable staff and promotion to a higher grade. Candidates should preferably have an honours degree in electrical engineering (telecommunications and electronics) or be corporate members of the Institution of Electrical Engineers. They should have served an apprenticeship with a firm of electrical engineers manufacturing radio or associated equipment and have had subsequent experience on the manufacturing and servicing side of the industry. The appointment will, in the first instance, be to the Inspection Department and candidates should be capable of dealing with the whole service from the inspection of a wide variety of electronic equipment to a staff of Inspecting Engineers. Apply at once or telegraphic age, whether married or single, and full particulars of qualifications and experience, and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M.7c 42335 (W). [illegible] and passage. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. [5256

BRITISH ELECTRICITY AUTHORITY. London Division.

GENERAL ASSISTANT ENGINEER.

APPLICATIONS are invited for appointments at general assistant engineer in the communications section of the technical department.

DUTIES will be in connection with testing and maintenance of the private communications system owned and maintained by the Authority including equipment using line transmitter and radio telephones.

APPLICANTS should have a degree or Higher National certificate in engineering or equivalent and should preferably have had works experience. Scientific qualifications will be considered.

THE remuneration will depend on qualifications and experience but will be within the range of £477 per annum to £568 per annum, plus 5/5 or £25 per annum, whichever is the greater, in London Allowance, in accordance with National Joint Board Scheme Class AX Grade 6.

THE appointment will be superannuable under the terms of the British Electricity Authority's superannuation scheme.

APPLICATIONS giving full particulars of education, training, and experience, should be forwarded to the Acting Divisional Secretary, British Electricity Authority, London Division, Regent House, Heddon St., Regent St., Westminster, S.W.1, so as to be received within 14 days of date of publication of this issue.

J. N. WAITE,
Divisional Controller.
[5261

TELEVISION RADIO engineer, age, experience and wages required to Marshall's, 24, High St., Clay Cross. [5261

WANTED, radio mechanic, some television useful; man out of Forces might suit; able to drive. East Anglia. Box 2661. [5060

TELEVISION testers required by North London manufacturers.—Please give full details regarding past experience, etc., to Box 3354. [5241

WANTED for employment in various parts of the United Kingdom and N. Ireland, personnel experienced in maintenance and repair of radio and electrical fire control equipment. SALARY scale £400 per annum (rising to £525 annually) according to factors. Full details of age, practical experience, technical qualifications held and in which part of the U.K. they would be re-employed, to be addressed to D.D.M.E. H.Q.A.A. Command, Readmore, Middlesex. [5267

SERVICE engineer age 25-30 years for watch making equipment with good knowledge of electronics wide-ranging salary and prospects for talent in electronic operation. London area.—Box 3420. [5317

PILOT RADIO LTD. requires immediately fault finders, testers and mechanical inspectors for radio and television assembly, experienced in factory production. Five day week, with good rates of pay.

APPLY or write to—Park Royal Rd., London, N.W.10. [5294

A large radio and television manufacturer in the outer suburbs of London is expanding manufacturing capacity and requires additional testers and fault finders; applicants should give full details of experience to Box 3371. [5270

ENGLISH ELECTRIC and Marconi's Wireless Telegraph Co. require qualified senior and junior engineers, research and development engineers for their television departments at Liverpool and Chelmsford; vacancies cover studio and domestic equipment; unqualified engineers with suitable practical experience will be considered.

Write giving full details, quoting reference TVG to Central Personnel Services, 24, Golden Sq., Westminster, S.W.1. [5076

NEW! NEW! NEW!

SYMPHONY NO. 3 [illegible] £5 19 6.

SYMPHONY No. 1 AMPLIFIER. [illegible]

NO. 1 4-WATT AMPLIFIER [illegible] £5 19 6.

NO. 2 P.A. AMPLIFIER. [illegible] 10 guineas. [illegible] £9 10/-.

[illegible] £5 10/-.

NO. 1 HIGH QUALITY TUNER. [illegible] £5 10/-.

NO. 2 L.M. & S.-WAVE SUPERHET TUNER. [illegible] £8 10/-. [illegible] £7 10/-.

SPECIAL BARGAINS. [illegible] £12 19 6. [illegible] £10. [illegible]

NEW UNUSED BARGAINS. [illegible] £14 10/-. COLLARO MICROGRAMS [illegible] £13 10/-. MICROGRAM CABINETS [illegible] £7 6. [illegible] COLLARO SINGLE RECORD PLAYERS. [illegible]

[illegible] WHARFEDALE SPEAKERS [illegible] CROSSOVER UNITS [illegible]

BARGAIN CATALOGUE 2/4 [illegible]

NORTHERN RADIO SERVICES,
16, Kings College Road, Swiss Cottage, London, N.W.3. Phone: PRimrose 8314

BULLANCO, 66 QUEENS Rd S.E.15 TEL NEW CROSS 1082

ALUMINIUM

SHEET EXPANDED TUBES, ANGLES, BARS, RODS, MOULDINGS, RIVETS

S.A.E. FOR LIST

ANY SIZES CUT OR FOLDED

LYONS RADIO

Receiver Type R3515. Adaptable for reception of Television sound or vision. Fitted with 10 VR65's, 5 VR56's, 3 VR66's and 1 each of VR54 and VR92. 19 Mc. I.F. strip, condensers, resistors, etc. Price 50/-. Carriage 5/-.

Telephone Set "H." Mk. 3. A sound powered telephone set (batteries NOT required), housed in metal box 10 x 5 x 4½, complete with hand set, call bell and hand generator for ringing impression bell. Ideal in the home, factory or office. Price 25 6 each, post 1/6, or 50/- per pair carriage free.

Coaxial Cable. First class quality, 80 ohms impedance, not right for the Television lead-in, coke-cable, etc. Price 9d per yard. Flat set (12 yds).

Condensers. New and unused, paper, metal cased.

[illegible] 5/- each, post 9d, or 3 for 15/-, carriage free.

A.C. Voltmeters. New boxed moving type, 0/300 v. A.C., 6in. scale in thin, wide length 6in. dia. over fixing flange, etc. Price 35/-. Post 1/6.

3, GOLDHAWK ROAD (Dept. M.W.)
SHEPHERDS BUSH, LONDON, W.12
Telephone: Shepherds Bush 1729

THE MODERN BOOK CO.

The Radio Amateur's Handbook, 1950 edition. By A.R.R.L. **28s.** Postage 9d.

Radio Amateur Call Book Magazine. **16s.** Postage 9d.

Radio Servicing Equipment. By E. J. G. Lewis. **25s.** Postage 9d.

The Principles of Television Reception. By A. W. Keen. **30s.** Postage 9d.

Television Servicing Manual. By E. N. Bradley. **6s. 6d.** Postage 3d.

Magnetic Recording. By S. J. Begun. **42s. 6d.** Postage 9d.

Radio Valve Data. Compiled by "Wireless World." **3s. 6d.** Postage 3d.

Wireless Amplifier Manual, Number 2. **3s.** Postage 2d.

Loudspeakers. By G. A. Briggs. **5s.** Postage 3d.

Radio Receiver Servicing and Maintenance. By E. J. G. Lewis. **8s. 6d.** Postage 6d.

Basic Television. By Bernard Grob. **55s. 6d.** Postage 9d.

Radio Engineering. By E. K. Sandeman. Volume 1. **45s.** Volume 2. **40s.** Postage 9d. each.

Amateur Radio Receivers. By S. K. Lewer. **3s. 6d.** Postage 2d.

Radio Receiver Design. By K. R. Sturley. 2 volumes. **28s.** each. Postage 9d.

The Amplification and Distribution of Sound. By A. E. Greenlees. **16s.** Postage 6d.

Radio Data Charts. By R. T. Beatty. **7s. 6d.** Postage 6d.

We have the finest selection of British and American radio books in the Country. Complete lists on application.

19-23 PRAED STREET

(Dept. W.4)

LONDON W.2

PADdington 4185

COPENHAGEN WAVE-CHANGES

"Quality Reception" better than ever!

Lowther's particular attention to Long-wave (Light programme) is of great benefit.

Tuner Units, for all circumstances, by craftsmen.

Further details, please write :—

THE LOWTHER MANUFACTURING CO.

(The Laboratory Production Unit)

Lowther House, St. Mark's Road, Bromley, Kent RAV. 5225

SITUATIONS VACANT

FERRANTI, Ltd., have a vacancy at their radio works, Manchester, for a draughtsman-designer of cabinets for radio and television, experience in design of high-class modern furniture is an essential qualification. APPLICATION forms from the Staff Manager, Ferranti, Ltd., Hollinwood, Lancs. [5271]

TELEVISION service engineers offered progressive position with leading manufacturer; must be fully experienced in outdoor reception and build-back current driving licence, resident all areas 30-mile radius London.—Apply Box 2692. [5128]

PHYSICISTS and electrical engineers graduate with experience in dielectric research or capacitor manufacture, required by leading London firm of component manufacturers. Write giving full details and salary required to Box 5301. [5262]

RADIO valve engineer required as technical assistant in the factory valve engineering department; at least ten years' experience in this kind of work and minimum academic qualification equivalent to Higher National Certificate necessary.

WRITE in confidence to the Personnel Officer, Standard Telephones & Cables, Ltd., Foots Cray, Sidcup, Kent, giving details of qualifications, experience and salary required. [5246]

DRAUGHTSMAN required for detail and assembly drawing of R.F. heating equipment; new air-conditioned factory in Reading area; excellent opportunity for experienced draughtsman who must be quick and able to produce good drawings from rough sketches.—Write Box 2683. [5247]

DESIGNER DRAUGHTSMAN required in drawing department engaged on the design of electronic test gear for large light electrical engineering manufacturer in the London area; the position is permanent and pensionable to applicant with experience of similar work.—Kindly state full details to Box 5477. [5330]

DESIGNER draughtsman required for the engineering laboratory of a large light engineering firm in the West London area; for development work should have a knowledge and experience of tool design; apply giving details of age and experience to—Box 5302. [5292]

TELEVISION engineer with first-class knowledge and experience of modern television product on and development, required by North London manufacturers; only applicants in similar position with full qualifications should apply; giving details of experience and salary required to Box 5350. [5240]

IN any grade or capacity there is usually a job for the right man at Sound Sales, Ltd., Acoustics, who should be ex-British, should state age, details of experience, salary required; to letter, testimonials should be forwarded with photo; previous factory experience essential.

THE Managing Director, Sound Sales, Ltd., West St., Farnham, Surrey. [5294]

A NUMBER of senior and junior vacancies for radio, radar, electronic, television, etc., development, service engineers, draughtsmen, wireless testers, inspectors, etc. (especially ex-Signals); 50 vacancies in service engineers.—Write in confidence, Technical Employment Agency, 179, Clapham Rd., S.W.9. (Brixton 5467). [5191]

SENIOR draughtsmen required with experience in design of manual or trunk telephone equipment and apparatus; these vacancies carry good salaries and offer scope for advancement; write giving full details of experience to Personnel Manager, Telephone Manufacturing Co., Ltd., Martell Rd., West Dulwich, S.E.21. [5421]

JUNIOR designer draughtsman required for the engineering laboratory of a large light engineering firm in the West London area; should be between 20 and 25 years of age, experienced in domestic appliance design, and preferably with mechanical training; apply giving details of age and experience to Box 5295. [5295]

A leading firm of mobile radio equipment producers requires sales engineers for technical sales duties, primarily with the automobile industry; applicants between 25 and 35, and possessing sound radio engineering training should apply in writing, giving age, qualifications, details of experience and salary required to Box 5320. [5265]

ENGLISH ELECTRIC VALVE Co. Chelmsford, require a young graduate engineer interested in micro wave or general work on electronic valves; an interesting position with good prospects after probation; applicants should give full details quoting Ref. 152 to Central Personnel Services, 24, Gillingham St., Westminster, S.W.1. [5062]

ENGLISH ELECTRIC, Stafford, invite applications from senior draughtsmen for detail design on gyroscope watch-dog meters, instruments and relays, permanent, pensionable, accommodation.—Apply, quoting reference 112, giving full details to Central Personnel Services, The English Electric Co., Ltd., 24, Gillingham St., Westminster, S.W.1. [5243]

NUSOUND PRODUCTS

136 WARDOUR ST., LONDON, W.1

Tel. GERrard 8845

HOME BUILT TELEVISION AND AMPLIFIER SPECIALISTS

Full Mail Order Facilities (Add Postage)

Mon.-Fri. 9-6.30 p.m. Sat. 9-1 p.m.

A QUALITY AMPLIFIER AND RADIO FEEDER.

The 3 valve Amplifier Chassis has an output of approx. 4 watts. Includes 3 stage neg. feedback circuit and incorporates independent bass and treble boost controls and pre-amplifier stage. Chassis dimensions of KF30 Pre Amp. (1936 Boost tale 6V6 and special quality output line driver). Full constructional booklet for A.C. and A.C./D.C. models price **1/6**. The A.C. model can be built for as little as **£7**, using surplus valves and A.C./D.C. for **£8** with new valves. Built up complete and tested, both models cost **10 ens** complete with new valves. The radio feeder is a wide band T.R.F. using air spaced trimmers and preset to three stations with switched control. It is plugged straight into the Amplifier and together you have a high fidelity combination which nothing but the most expensive radiogram can compete with. Full constructional booklet price **1/6**. Time to build **£3 10/-**.

VIEWMASTER TELEVISOR (working model on view). Full constructional envelope for London or Birmingham 5/-. All components in stock. Pre-aligned and tested tuner/chassis. Viewmaster cost **£6 17 6** post free.

ALL MAKES OF TUBES IN STOCK. Mw. **£11 6 10**/-, Ow. **£15 2 5**. **RUBBER MASKS** (Mw.) 9in. **18/-**, 12in. **21/-**, 14in. **6 6**, 16in. **11/6**. **SCANCO** DAY E.H.T. transformer **60/-**, DAY **48/-**, DAY transformer **35/-**. **SCANCO LINE TRANS.** **25/6**. **SCAN COILS** **25/6**. Focus coil **30/-**. Deflection Yoke Birmingham **18/6**. London **15/-**.

GRAMOPHONE EQUIPMENT

Complete PU **£3 19/-**, 2 SPEED **13/-**. Goldring Lenpreight **£14**, with Acoshot **£19 10** PU. **ACOSHOT 71/3**.

Complete PU Bond Diamond **£3 0 8**. Monitor sapphire **6/6**, Ruby **8/6**. Gramophone needles 20 for **2/10**. Lenco motor **£4 19/-**. Pickering AC Sel. **MAG PU** **£5 3 3**.

Garrard record changer 6L 30 6 10 PU **£17 7 9**. Collaro 3RC with pick-up, charger **£10 15/-**. With crystal PU **£5 17 6**. Collaro 3RC record changer with Ceramic with pick-up **£5 18 2**. Latest Garrard record changer 12H with pick-up **£8 8/-**. Also Acoshot Microphones **£6 15/-**. Fullerphone Electric Telephones (Mk. 3) (Pair) **4 9**.

NUSOUND TRANSFORMERS. Tapped pri. unless otherwise stated.

A few specimens from our wide range and we can offer to your own spec. delivery 4 days. Retouch tpm. 2040-0-2040, 120 mA, 6.3 v. 4 a., 5 v. 3 a. **42/-**. Mains 4 v. 4 amp mA. 6.3 v. 3 a., 5 v. 3 a., 2 v. 4 a. centre. **£1 5 3**.

2040-0-2040, 120 mA, 6.3 v. 3 a., 5 v. 3 a., 2 v. 4 a. centre. **£1 1 9**.

2040-0-2040, 120 mA, 6.3 v. 3 a., 5 v. 3 a., 2 v. 4 a. centre. **£1 0 3**.

2040-0-2040, 120 mA, 6.3 v. 3 a., 5 v. 3 a., 2 v. 4 a. centre. **18 9**.

6.3 v. 1½ a. Heater trans. 230 pri. sec. **6/9**.

2½ v. 2 a. Heater trans. 230 pri. sec. **6/9**.

6.3 v. 1½ a. C.T. Heater trans. 230 pri. sec. **15/6**.

6.3 v. 3 a. **12/6**.

NUSOUND CHOKES.

5 Hen. 10 H. 50 ohms, 50 ma. **4/6**.

5 Hen. 10 H. 100 ohms, 60 ma. **4/6**.

5 Hen. 10 H. 100 ohms, 80 ma., shrouded **10/9**.

5 Hen. 10 H. 100 ohms, 100 ma., shrouded **9/6**.

5 Hen. 10 H. 100 ohms, 150 ma., shrouded **12/9**.

5 Hen. 10 H. 50 ohms, 200 ma., shrouded **19/6**.

Television sections can be sent to any part of the country (send for list). Let us quote you by return of post for components of all types.

This comprehensive list on TV., Radio and Gramophone equipment, etc., is now available. Price **4d.** post free.

MORSE CODE TRAINING

There are Candler Morse Code Courses for **BEGINNERS AND OPERATORS**

Send for this Free **"BOOK OF FACTS"** It gives full details concerning all Courses.

THE CANDLER SYSTEM CO.

(Room 55W), 121 Kingsway, London, W.C.2

Candler System Co., Denver, Colorado, U.S.A.

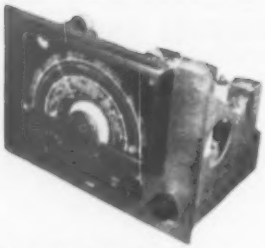

PEERLESS

RADIOGRAM CHASSIS TYPE 1150

This receiver forms the basis for a Radiogram of unsurpassed performance, and at great saving in cost.

Principal features include:

11 Osram Valves	10 watts output
4 Wave Bands	Push-pull Amplifier
2 I.F. Stages	Magic Eye Tuning
R.F. Amplifier	Wave-band Indicator
4 Stages A.V.C.	Bandspread Dial
Treble Control	Negative Feed-Back
Base Control	Tropical Specification

10 to 2,000 Metres, 12 months' guarantee.

Write for full particulars —

PEERLESS RADIO LIMITED
374 KENSINGTON HIGH STREET, LONDON, W.14
Telephone: WEstern 1201

INSTRUMENT WIRE
ENAMELLED, D.C.C. SILK COVERED
ETC. all sizes from 10 s.w.g. to 42 s.w.g. in stock.
INSULATING MATERIALS, Empire cloth, leatheroid, paxolin, sleeving etc.
Send S.A.E. for list to
STAN. HOLT,
349, HIGH ST. SMETHWICK, STAFFS
Telephone: WOODGATE 3789

WALTON'S OF WOLVERHAMPTON

The leading Midland Store for all your Radio and Television accessories and units, including stocks of many lines unobtainable elsewhere.

It will pay you to make a special visit to 48, Stafford Street or 65, Trysull Road. If unable to call send S.A.E. today to 203, Staveley Road: all of Wolverhampton, Staffs.

A few Special Clearance lines for callers only. Partly stripped 1154's, **16**; 1196 TX, **2-**; No. 38 TX, **5-**; No. 18 TX, **5-**; 3515, **12 6**; 1355, **37 6** and many hundred of other items.

SITUATIONS VACANT

BELLING & LEE, Ltd., Cambridge Arterial Rd., Enfield, Middlesex, require the services of a keen and inventive research assistant of British nationality for work in connection with television aerials and radio components, applicants should be 25 to 35 years of age and possess qualifications at least to Grad. I.E.E., together with previous research experience. Five-day week. (5275

SALES engineer representative for old established West London firm of radio and electrical component manufacturers. Applicants must have good personality, initiative and drive and be capable of technical and commercial negotiations with customers of standing, salary £400-£500, pension scheme.—Write full details of experience, qualifications, age, etc., to Box 1866. (5257

RADIO mechanics are required by British Insulated Callender's Cables, Ltd., in their research laboratories at Kirkby, nr. Liverpool. Applicants should be capable of constructing and testing electronic equipment under supervision.—Applications stating age, qualifications and experience, should be addressed to the Staff Officer, British Insulated Callender's Cables, Ltd., Prescot. (5283

SENIOR draughtsman required with experience in design of telecommunication equipment or small electrical apparatus for quantity production, good salaries to selected applicants and the positions offer good prospects for advancement. Apply in writing, giving full particulars details of experience to—Personnel Manager, Telephone Manufacturing Co., Ltd., Martell Rd., West Dulwich, London, S.E.21. (5322

OPPORTUNITIES are offered to young men preferably with radio or radar service training who are prepared to do short-term service overseas by leading manufacturers of radio communication equipment in the M.F., H.F., and V.H.F. field; selected personnel will receive factory training on installation, test and service work generally. Apply, stating experience and salary required to Box 3562. (5251

SEVERAL young men required as technical assistants for television tube (cathode ray production) performing three shift duties; technical experience on electrical, chemical or mechanical work essential, with equivalent standard to H.N.C. or 4th year National Certificate, salary range £300-£400.—Apply, Personnel Superintendent, The Edison-Swan Electric Co., Ltd., Ediswan Works, Brimsdown, Enfield, Middlesex. (5250

APPLICATIONS are invited from electrical design draughtsmen for development of heavy switchgear; applicants should have at least H.N.C. in electrical engineering or equivalent and manufacturing and D.O. experience of switchgear of not less than ten years, permanent staff position, accommodation.—Apply, quoting reference 1128, to Central Personnel Services, English Electric Co., 24, Gillingham St., S.W.1.

ELECTRONIC engineer, age 23-26, required for design and development work of functional horse-power and other small electrical motors. Qualifications: Training in physics or engineering and two or three years' experience in this field, salary according to age and qualifications.—Please write giving full details and quoting J.D.8, to Personnel Dept., E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. (5262

DESIGN and detail draughtsmen (preferably with workshop training and qualifications to H.N.C. standard) with experience of small mechanisms and electro-mechanical instruments, the mechanical design of electronic apparatus, are required for development work on new and interesting projects by leading manufacturers in the Middlesex area.—Apply in confidence giving age and full details of training and experience to Box 3563. (5264

DRAUGHTSMEN.—Vacancies exist with the English Electric Co. for draughtsmen of all grades in various parts of the country; men with D.O. experience on heavy or light mechanical or electrical equipment are invited to apply, stating type of work in which they are interested, the location they prefer, and the salary they require.—Apply quoting Ref. 155, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., S.W.1. (5280

ELECTRICAL designer required for the F.H.P. motor laboratory of a large light electrical engineering company in the West London area; applicants should have a sound technical and practical training, with initiative to accept full responsibility of a project from the initial design stage to factory production, excellent prospects if qualifications and experience are suitable.—Apply, giving details of age, education and industry, to Box 3421. (5325

MURPHY RADIO, Ltd., are expanding their Electrical Design Laboratory and urgently require the services of Electrical and Radio Engineers having good academic qualifications (Honours Degree in Physics or Electrical Engineering) and experience in industrial design laboratories. There are also openings for graduates trained in these branches, without industrial experience.—Applications, giving full particulars of training and experience should be forwarded to Personnel Department, Murphy Radio, Ltd., Welwyn Garden City, Herts. (5042

A COMPLETE RANGE OF TELEVISION COMPONENTS

- Line and Frame Scanning Assemblies.
- Focus Coils and P.M. Focus Units.
- Line and Frame Output Transformers.
- Line and Frame Oscillator Transformers.
- Combined Line Output transformers and E.H.T. Generators.
- Width controls.
- Video correction chokes.
- Filament transformers. E.H.T. transformers and Smoothing chokes.

Allen Components are specified for the Electronic Engineering Home Televisor and the range includes components suitable for use in all of the popular Home Constructor Sets.

ALLEN COMPONENTS LTD.
1, Shrewsbury Road, Stonebridge, N.W.10
Telephone: Willesden 3675 and 4901.

★ **"Globe-King"** (REGD) MARVEL IN MINIATURE
SHORT-WAVE RADIO KIT
Probably the smallest six valve Short-Wave Radio receiver in the world using standard parts with Bandspread tuning device. "Magnificent performance" . . . with incomparable British tone and Musical Result and designed to precisely standards, complete kit cost only 49/6d.—write today for descriptive catalogue.
JOHNSONS (RADIO SPECIALISTS) **MACCLESFIELD** CHESHIRE (ENG)

100 kcs. QUARTZ CRYSTAL UNIT *Type* Q5/100

for Secondary Frequency Standards

★ Accuracy better than 0.01% ★ Temperature coefficient 2 parts in a million per degree Centigrade temperature change. ★ Gold electrodes applied by cathodic sputtering direct to the faces of the crystal, giving permanence of calibration. ★ Simple single valve circuit gives strong harmonics at 100 kcs. intervals up to 20 Mcs. ★ Octal based mount of compact dimensions. PRICE 45 - Post Free

Full details of the Q5/100 including circuit are contained in our leaflet Q1. Send stamp today for your copy.

THE QUARTZ CRYSTAL Co., Ltd.
63-71 Kingston Road,
NEW MALDEN, SURREY
Telephone: MALden 0334

★

A useful new handbook

The Principles of Television Reception

By A. W. Keen, M.I.R.E., A.M.BRIT.I.R.E. An important new book by a practising electronic research engineer. The entire receiving system is examined stage by stage, complete circuits are given of four up-to-date commercial receivers, and the problems of colour television are fully discussed. It is recommended as a textbook for all examinations which include in their syllabuses the principles of television, and is invaluable to service engineers and technicians generally. With over 200 illustrations.

30/- net.

Pitman

Parker Street, Kingsway, London, W.C.2

CABOT RADIO

A New Television Pre-amplifier

Model B. Has an effective gain of 10 times, and an extremely high signal noise ratio. Capable of operating at an input of 5 microV. without showing deterioration of picture quality due to its own generated noise. Uses Mazda 6F1 valve in an up-to-date circuit. Bandwidth 5 mcs. Entirely self-contained, and operates from 200-250 v. A.C. 50 c.p.s. only. Size: App. 4in. cubed. Available for London or Birmingham frequencies from your own dealer.

Price £5.15.0

Including 6F1 valve.

If in difficulty write direct to:

Cabot Radio Co. Ltd.,

28, Bedminster Parade,

Bristol 3

Tel: 64314

SITUATIONS VACANT

QUALIFIED television service engineers required, only those with practical experience of domestic sets need apply.—J. & P. Electric Lighting & Radio Ltd., 331, Mare St., Hackney, E.8. [15331

MARCONI WIRELESS TELEGRAPH Co. Ltd. require draughtsmen for work at Acton in London on radio communication equipment, involving drawing office experience essential, preferably on radio or electronic equipment. Apply quoting Ref. D.D.127, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [15278

ENGLISH ELECTRIC have an urgent vacancy for a press tool designer to work at Coventrid; an experienced man capable of working on his own initiative and able to supervise other technical staff is required; previous experience on the design of high speed strip forming machines desirable; apply giving full details quoting ref. 422, to Central Personnel Services, English Electric Company, Ltd., 24-30, Gillingham St., London, S.W.1. [15290

ENGLISH ELECTRIC, Stafford, require technical sales representatives for their industrial electronics department; previous experience in this field is essential, and the successful candidates will be employed in the Birmingham and London areas; a car will be provided; write giving full details of engineering training and experience quoting Ref. 756 to Central Personnel Services, English Electric Co., Ltd., 24, Gillingham St., Westminster, S.W.1. [15045

ELECTRONIC engineer required in the electro-medical division of large manufacturing organisation in London, the technical qualification required must be equal to final City & Guilds (radio Communication) and applicants should have previous technical commercial experience, preferably in this field; successful candidate aged 25-35 will be required to travel, and own car will be an advantage. Full details of qualifications, experience, age and salary required to Box 3366. [15265

TECHNICAL assistant, age 20-30, required by "The Wireless Trader" Laboratory to assist with and eventually take over preparation of radio-servicing information; must be conversant with commercial radio and television practice, able to convert circuit diagrams to conform to a standard style and explain technical matters clearly in writing; sound technical knowledge essential. Applications in writing only, stating age and salary required, should be addressed to the Technical Editor, "The Wireless Trader," Dorset House, Stamford St., London, S.E.1. [15334

MARCONI'S WIRELESS TELEGRAPH Co. Ltd., Chelmsford invite applications for the position of chief of studio equipment section. Applicants should be qualified electrical engineers, age 30 to 40 and fully experienced in all branches of video and audio equipment, including installation, operation and maintenance of British broadcast television (B.B.C. standard) qualifications and experience.—Write, giving full details quoting reference 421, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [15279

ADDITIONAL lecturers are required immediately for E.M.I. Institutes College of electronics, applicants should possess a good physics or electrical engineering degree and also experience in radio, television, etc., commencing salary according to age, qualifications and experience not less than approximate Burnham scale, superannuation benefits in addition. Apply giving full details to the Principal, Professor H. F. Trewman, M.A., (Cantab.), M.I.E.E., M.I.Mech.E., M.Brit.I.R.E., F.M.I. Institutes, 16, Pembroke Square, W.2. Tel. Bayswater 5151. [15304

SENIOR engineers and physicists are required for research and development work in the following fields: (a) microwave circuit design and measurements, including waveguides and concentric lines, (b) design of microwave aerial systems, (c) intermediate frequency amplifiers; appointments will be given to experienced leading research groups and with considerable experience in one or more of these fields.—Applications should be sent to the Personnel Officer, Research Laboratories, The General Electric Co., Ltd., North Wembley, Middlesex, stating age, qualifications and experience. [15251

AUSTRALIA.—Large manufacturers of electrical automotive and electronic products require chief engineer; applicants must possess qualifications to Minimum standard University Degree or diploma covering any or all mechanical, electrical, radio and electronics, with emphasis on electrical and mechanical training; applicant must also possess first-class ability in engineering field with sound knowledge and experience in manufacture, mass production methods and factory organisation and control, age 30-35, highest references essential, excellent post for right type of engineer presenting an opportunity to start life afresh in a new country offering tremendous possibilities.—Write giving full details of age, education, qualifications, experience and salary required to Box 2745, New Era Advertising Service Ltd., Lodge House, 107, Fleet St., E.C.4. [15246

SUPACOILS OFFER

THE LATEST EDITION OF THE

HOME CONSTRUCTOR'S HANDBOOK

No keen radio enthusiast should be without this invaluable booklet which is of equal use to beginner, amateur or professional radio engineer. It contains, among other things :—

- Circuits of feeder units, superhet receivers, amplifiers and power packs, etc.
- Pages of servicing and constructional information which will assist you in YOUR radio problem.
- Complete resistance colour code.
- A considerable amount of invaluable general Radio information.
- A comprehensive catalogue.
- Above all it is profusely illustrated with half tone blocks and costs 1/- only or a copy will be given **FREE** with every order for £1 or more.

We also offer the following selection from our stocks of quality components.

- **COILS.** A complete series of High Q variable iron dust cored coils in wavelengths 10-30, 16-50, 30-75, 75-200, 190-550 and 800-2000 metres: Aerial, H.F. or Oscillator at the remarkable price of 2/3 each.
- **MODEL 30** famous 3 waveband superhet Coil Packs, aligned 27/9 inc. Full connection details and instructions given with every pack.
- **MODEL 40** Coil Packs—similar, with R.F. stage, aligned 34/6 inc.
- **I.F. TRANSFORMERS.** iron-cored high stability, aligned to 465 kc/s 12/- pair.
- **MODEL 30 TUNING UNIT** consisting of 30 Coil Pack, pair of "M.M." I.F. Transformers, matched 2-gang and attractive Dial. Components aligned together as a unit and sealed 54/9 inc.
- **MODEL 40 TUNING UNIT**, similar, with R.F. stage 88/3 inc.
- **SLS.** Either of the above tuning units with the latest J.B. Horizontal Spinwheel tuning assembly and dial (SLS) 21/9 extra
- **COMPONENTS.**—Complete range of radio, television and gram components in stock at lowest prices.

SUPACOILS MAIL ORDER OFFICE

98 Greenway Ave., London, E.17

MUMETAL and RADIOMETAL TRANSFORMERS and CHOKES

As Specialists with many years of experience we can design and supply practically any type of transformer or choke with a wider frequency range than is usual without the frequency range.

1 c/s to 150 kc/s

Available for prompt delivery: **Microphone Transformers, Input Transformers, Line Transformers, Pickup Transformers, Output Transformers, Rectifier Transformers, Vibrator Transformers, High Fidelity Transformers, Recorder Transformers, Midget Transformers, High Q Chokes, High Inductance Chokes, etc., with or without Mumetal Shields.**

MAINS COMPONENTS ARE ALSO STOCKED.

SOWTER TRANSFORMERS

E. A. SOWTER, 1-B HEAD STREET, COLCHESTER.

Phone: COLCHESTER 3405.

"Q-MAX" SQUARE HOLE PUNCH

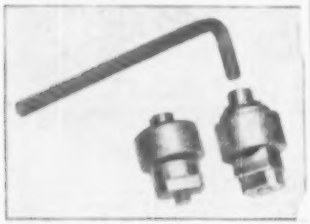

FOR SQUARE OR RECTANGULAR HOLES FROM 1" UPWARDS

PRICE 19/6 (KEY 1/-)

BERRY'S (SHORT WAVE) LTD.

25, HIGH HOLBORN, W.C.1

THE SMALLEST COILPACK IN THE WORLD

BRIDISCO

(Regd.)

Three wave bands—1¼ – 2¼ = 2¼ ins. Specially designed to eliminate second channel interference. All metal chassis with a 1" spindle. High Q permeability tuned coils, on low loss formers. Complete with full circuit diagram for 5 valve superhet.

30/6 including P.T.

From your local retailer, usual terms or direct —

BRITISH DISTRIBUTING CO.
66, HIGH ST., LONDON N.8.

THE NEW SPENCER-WEST TYPE AC.3 TELEVISION PRE-AMPLIFIER.

"Unquestionably the best TELEVISION Pre-Amplifier, as a consideration of the specification and a trial will prove."

Circuit Specification.

● Two triode stages ensuring low noise. ● 1st stage neutralized, 2nd stage operating as a low impedance load for the neutralized stage, thereby still further reducing the "noise," without sacrifice of gain. ● Self-contained power supply to suit 200-250v. A.C. mains. ● Balanced and unbalanced socket connections to suit all receivers. ● Gain 16.5 dbs at full bandwidth. Noise factor, 6-8 dbs. compared with normal pentode valves. ● An improved performance is guaranteed. Types AC/3L (London) and AC/3B (Birmingham). Price 10 gns. complete. Further particulars on request.

Spencer-West, Quay Wks., Gt. Yarmouth, N'f'k

SITUATIONS VACANT

SENIOR test engineer required to manager small electronics works in Kent; knowledge of T.V. essential; good prospects for right man.—Box 3565. [3565]

SITUATIONS WANTED

ENGINEER representative, radio, television, electrical recorders, projectors, etc., seeks new car; desires position.—Box 5572. [5572]

MANUFACTURER'S export manager seeks official appointment; handling radio and electrical appliances; excellent personal connections, commercial and export procedure; experienced in sales, travelled, good sales records and referees; aged 44, M.I.Ex.—Write Box 5455. [5455]

AGENTS WANTED

LIVE commission representatives or manufacturers' agents required for most parts of England, Wales, products suitable for radio, electrical trades; state area, age, covering present lines handled, etc.—Box 5561. [5561]

LIVE commission representative or manufacturers' agent required for Yorkshire; products suitable for radio and electrical trades; state present lines handled; if car owner; persons with proven selling records only need apply. Full details to—Box 5404. [5404]

LIVE commission representatives or manufacturers' agents required for Beds., Bucks., Herts., Suffolk and Essex; products suitable for radio and electrical trades; state present lines handled; if car owner; persons with proven selling records only need apply. Full details to—Box 5370. [5370]

LIVE commission representatives or manufacturers' agents required for Cumberland, Northumberland and Durham; products suitable radio and electrical trades; state present lines handled; if car owner; persons with proven selling records only need apply. Full details to—Box 5405. [5405]

LIVE commission representatives or manufacturers' agents required for Cheshire, Shropshire and Wales; products suitable for radio and electrical trades; state present lines handled; if car owner; persons with proven selling records only need apply. Full details to—Box 5406. [5406]

LIVE commission representatives or manufacturers' agents required for Oxford, Berks., Hants., Surrey, Sussex and Kent; products suitable for radio and electrical trades; state present lines handled; if car owner; persons with proven selling records only need apply. Full details to—Box 5410. [5410]

LIVE commission representatives or manufacturers' agents required for Glos., Wilts., Somerset, Dorset, Devon and Cornwall; products suitable for radio and electrical trades; state present lines handled; if car owner; persons with proven selling record only need apply. Full details to—Box 5411. [5411]

LIVE commission representatives or manufacturers' agents required for Staffs., Derbys., Warks., Worcs., and Herefordshire; products suitable for radio and electrical trades; state present lines handled; if car owner; persons with proven selling records only need apply. Full details to—Box 5407. [5407]

LIVE commission representatives or manufacturers' agents required for Lincs., Notts., Leics., Northants., Rutland, Cambridge, Norfolk and Hunts.; products suitable for radio and electrical trades; state present lines handled; if car owner; persons with proven selling records only need apply. Full details to—Box 5408. [5408]

FINANCIAL PARTNERSHIPS

ADVERTISER seeks working partnership in radio, electrical business; willing to invest considerable capital; 20 years experience electrical engineer, radio serviceman.—Box 2621. [2621]

TECHNICAL TRAINING

A.M.I.E.E., City and Guilds, etc.—on "no pass no fee" terms; over 95% success. For full details of modern courses in all branches of electrical technology, send for our 176-page "Guide to Careers," free.—B.I.E.T. (Dept. 55A), 17, Stratford Place, London, W.1. [5420]

TUITION

WIRELESS officer attendance and Radio certificate (practical course).—Apply Manager, The Wireless School, Manor Office, London, N.7.

WIRELESS, land, sea and air; students, both sexes, age 14 upwards, trained for interesting appointments in all branches of radio; for form, bearers awarded, 2d stamp for prospectus.—Wireless College, Colwyn Bay. [9018]

WELL-PAID jobs await those trained in radio and television and other applications of electronics; our free booklet describes the wide range of postal and daytime courses, and the types of jobs awaiting those who have qualified themselves.

WRITE to E.M.I. Institutes, Dept. W.W., 10, Pembridge Sq., Notting Hill Gate, London, W.2. Bayswater 5131-2. [9001]

HILL & CHURCHILL LTD.
BOOKSELLERS
SWANAGE · DORSET

Available from stock:

"Radar Scanners & Radomes"—Cady & others	59/6
"Theory of Servomechanisms"—James & others	42/6
"Technique of Microwave Measurements"—Montgomery	85/-
"Microwave Transmission Circuits"—Ragan	72/6
"Microwave Magnetrons"—Collins	76/6
"Pulse Generators"—Glasoe & Lebacqz	76/6
"Radar Aids to Navigation"—Hall	42/6
"Radar System Engineering"—Ridenour	64/-
A.R.R.L. Handbook (1950)	20/-
The A.R.R.L. Antenna Book	12/6

(Postage extra)

CATALOGUE ON APPLICATION

★

"Radiospares" Quality Parts

The Service Engineer's First Choice

★

RADIO TECHNICIANS
SERVICE ENGINEERS
"SEE FOR YOURSELF"
BY JOINING THE E·T·U

THE ELECTRICAL TRADES UNION
CATERS FOR YOU

IT IS IN YOUR INTEREST TO JOIN YOUR LOCAL BRANCH

A LETTER TO THE SECRETARY
E.T.U.
HAYES COURT, WEST COMMON RD., BROMLEY, KENT.
WILL BRING YOU BY RETURN OF POST DETAILS AS TO HOW TO JOIN.

POTENTIOMETERS

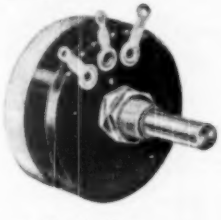

by RELIANCE

Wire wound and Composition types, Single, Ganged, Tandem Units.

Characteristics: linear, log, semi-log, non-inductive, etc.

Full details from

RELIANCE

Manufacturing Co. (Southwark) Ltd.

Sutherland Rd., Higham Hill, Walthamstow E.17

Telephone: LARkswood 3245

SOUTHERN RADIO'S WIRELESS BARGAINS

R.A.F. BOMBS-sight COMPUTERS.—Complete with motors, gears, bowls, pegs, etc., etc. Ideal for model makers and experimenters. The best component value ever offered. 55/-, plus 1/- carriage.

SERVO UNIT ASSEMBLY. For bombsight computer, consisting of servo motor, gearing, blowers, etc. 17/6.

CONTACTOR TIME SWITCHES. 10-hour movement with thermostatic control. 2 impulses per second. Complete in sound proof case. 10/- plus 1/6.

TRIMM SIX VALVES SUPER-HET RECEIVERS.—Complete with valves, etc., 22/6.

PERISCOPES. Ex-U.S.A. Type M.8, complete with removable telescope. 17/6.

COMMAND RECEIVERS. B.C.454 (49/100 metres). B.C.455 (100/40 metres). Complete with 6 valves. Ideal for easy conversion to mains receivers or car radio. 35/-, plus 1/6. Conversion circuit to mains, etc., 1/6.

CAMERA CONTROL UNITS. Type 35 No. 26. Complete in wooden box. 20/-.

LUPERA HOLE CUTTERS. Adjustable from 1½ to 3½ in. For use on wood, metal, plastic, etc. 5/6.

RADIO COMPASS INDICATORS, with Selsyn motor, 3½ in. dial 360 degrees. 13/6.

ROTOTHERM. Temperature gauge, from 20° to 200 degrees Fahrenheit. Chromium finish. 6/-.

SECTIONAL AERIALS. 30 interlocking 3/6, base for same 2/6.

WESTECTORS. W.6 and W112 types. 7/6 per dozen.

THROAT MICROPHONES. Complete with lead and plug. 3/6.

CRYSTAL DETECTORS. Semi-permanent type. 2/6.

RESISTANCES. 100 Assorted values from ¼-watt to 5-watts. All useful values. 9/- per 100.

CONDENSERS. 100 Assorted values. All useful sizes. Mica and tubular. 15/- per 100.

INDICATOR UNITS. Types BC.929A. 7 valves 3X3, 4X1 (2), 6H6 (2), 6J6 (1), and 6P1 Tube, switching motor, etc., etc. Ideal for oscilloscope conversion. 44/-, plus 5/- carriage.

DRIVE CABLES. For B.C.453-4-5. 14ft. long × 3/16 in. diameter at either end. 8/6, post 1/- extra.

RADIO RECEIVERS TYPE R-28 ARC-5. Complete with 10 Valves, 7/7 (4), 12SR7 (1), 12SK7 (2), 12A6 (1), etc., etc. 100-156 mcs., designed for Crystal Control. 55/-, plus 5/-. Full List of Radio Publications, 2½d.

RECEIVERS TYPE R1155—Brand new complete with 2 valves. 17/6.

THOUSANDS OF BARGAIN LINES FOR CALLERS

SOUTHERN RADIO SUPPLY LTD.

46, Lisle Street, London, W.C.

GERrard 6653

TUITION

TELEVISION.

THE Gothic Television School specialises solely in training in television. All tutors possess university degrees and/or corporate membership of professional institutions and are appointed individually to postal course students to ensure complete and thorough training. Principals M.B.E., B.Sc., M.Brit.I.R.E., education committee members, etc. Courses assume no previous television knowledge and provide guaranteed training for Brit.I.R.E. and N.T.R.B. examinations. Numerous well-known companies have adopted the School's Basic Television Course as standard television training for their staffs. Moderate fees.—Details from Gothic Television School, 18, North Avenue, London, W.15. (3051

RADIO training.—P.M.G. exams. and I.E.E. Diplomas; prospectus free.—Technical College, Hull. (3611

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc., on "no pass, no fee" terms over 95% successes. For details of exams. and courses on all branches of engineering, building, etc., write for 170-page handbook, free.—B.I.E.T. (Dept. 167B), 17, Stratford Place, London, W.1. (1577

TELEVISION postal course for radio trader Examination Board's diploma, also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. (40 years' experience in coaching students in wireless telegraphy and allied subjects.) (2590

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade. Fees and enrolments limited, fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. (3000

BOOKS, INSTRUCTIONS, ETC.

WEBB'S 1950 radio map of world, new multi-colour printing with up-to-date rail routes and fresh information on heavy art paper, 4/6, post 6d.; on linen, on rollers, 11/6, post 9d.—Webb's Radio, 14, Soho St., W.1. Gerrard 2089.

RCA valve enquiries for their technical publications and tube handbooks, information is also available on their range of electronic products.—Apply to RCA Photophone, Ltd., 36, Woodstock Grove, London, W.12. Tel. Shepherds Bush 1200. (5110

SUPACOILS stock the complete range of Bernards technical books. These publications treat radio and television from every aspect, and cost from as little as 1/- each. Full list on application.—Mail Order Office, Supacoils, 40, Greenway Av., London, E.17. (5175

I.P.R.E. Technical Publications: 5,000 alignment peaks for superheterodyne, 4/9 post free. The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free, membership and examination data, 1/- post free.—Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8. (3089

SUTTON Coldfield edition of the "View-master" now available, 5/- plus 6d. post, includes a full-size, stage-by-stage assembly drawings and 52-page instruction book. Demonstration set may be inspected during programme hours, and our service dept. will put you right if you have any troubles in building. FRITH RADIOCRAFT, Ltd., Leicester. (3326

"RADIO Valve Data: Characteristics of 1,600 Receiving Valves." Compiled by the staff of "Wireless World." Gives the main electrical characteristics for normal operating conditions, arranged in tabular form, and diagrams showing base connections. Index enables any valve to be found by type designation. Size 11in. wide × 7in. deep. 3/6 net, from all booksellers, or 5/9 by post from The Publishing Dept., Dorset House, Stamford St., S.E.1. (Pt

"RADIO Circuits: Step-by-Step Survey of Superhet Receivers." 2nd Edition. By W. E. Miller, M.A. (Cantab.), M.Brit.I.R.E., Editor of "The Wireless and Electrical Trader." Although this deals mainly with the superhet receiver it is equally applicable to the straight set. The circuit of the superhet is dealt with section by section up to the complete receiver. Size 8½in. × 5½in., 60pp., 5/6 net, from all booksellers, or 5/9 from The Publishing Dept., Dorset House, Stamford St., S.E.1. (Pt

"BASIC Mathematics for Radio Students." 2nd Edition. By F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. Presents the whole subject in an easily understandable and interesting form. The author deals first in a general manner with the fundamental mathematical processes that are the foundation of all applied science, and then discusses the application of mathematical ideas to radio problems. Size 9in. × 6in., 264pp., 77 diagrams. Price 10/6 net, from all booksellers, or 10/10 by post from The Publishing Dept., Dorset House, Stamford St., S.E.1.

THE "MAJOR" INSULATION TESTER

Compact and light in weight, this latest addition to the Record family has a Constant Pressure generator of patent design. Ranges up to 500 volts. 50 megohms with or without Continuity range of 0-30 ohms are available. Send for leaflet D/b.

THE RECORD ELECTRICAL CO. LTD.
BROADHEATH, ALTRINCHAM, CHESHIRE

Phone: Altrincham 2021. Grams: "Infinitus" Altrincham. London Office: 20, Victoria St., S.W.1. Phone: Abbey 3147

GOVT. SURPLUS, UNUSED

CONDENSERS

of all types . . .

We can offer, FOR IMMEDIATE DELIVERY from very generous stocks, a wide range of ultra-high quality fixed paper Condensers, from .001 μF to 8 μF. Also STOCKS of small, genuine MICA Condensers from .00001 (10 pf) to .01 μF (10,000 pf). *Prices are exceedingly moderate.*

Enquiries are invited for manufacturers' requirements, wholesale and export only for bulk quantities, and for scheduled deliveries over a period, as required.

Most condensers are now available for immediate delivery.

Please request our 4 page bulletin CONSEVEN/1114

CLAUDE LYONS LTD.

180 Tottenham Court Rd., London, W.1

and 76, Oldhall St., Liverpool 3, Lancs.

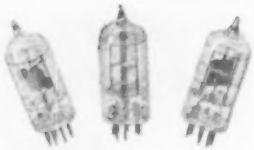

TYPE G (B7G BASE)

ENQUIRIES FOR ALL TYPES INVITED

BROOKES CRYSTALS LTD.
10 STOCKWELL STREET, GREENWICH, LONDON, S.E.10.

PHONE GRE. 1828. CABLE. XTALS LONDON.

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE.
3,000 STANDARD STOCK SIZES
No Quantity too Small *List on application*
London: H. ROLLET & Co., Ltd. Liverp'l.
6, Chesham Place, S.W.1. Kirkby Estate.
SLOane 3463 *SIMONSWOOD 5271-3*

RADIO GOOD OFFERS

BUILD YOUR OWN SUPER CAPACITY H.T. BATTERY with inert cells! The cheapest way. You just have to fill them up with ordinary tap water for a year. **12/6**, plus 2/6 carriage; 100 v., **20/-**, plus 2/- carriage; enough 1.5 v. cell, **7/4**, 3 for **2/6**.
POTENTIOMETERS, 25 K. to 1 megohm, 1 long-fine and most other values, **2/-** each; **20/-** a dozen, assorted values.

TRADE AND OVERSEAS ENQUIRIES INVITED

ARTHUR HOILE 55, UNION ST., MAIDSTONE
Phone 3156 KENT

TELEBOOSTER

For long range Television Reception. R.F.2L. 40/48 Mc/s. Variable tuned input for maximum sound or vision, 3 stages 2 Valves E.F.50, slug tuned inter stage and output, coaxial plugs and sockets, flying leads for 6.3 volts heaters, 200 H.T. to tap into receiver, high gain, fully screened. Price **£4 12 6**. R.F.1L. 40/48 Mc/s. 2 slug tuned stages, single valve, **£2 12 6**. For Birmingham R.F.2B. 55/65 Mc/s twin, and R.F.1B single as above. New and improved design combined twin Pre-amp. and valve rectifier power unit, very compact, fully screened, low noise, high gain and wide bandwidth. Type R.F.2B.P. 55/65 Mc/s, R.F.2L.P. 40/48 Mc/s. Price **£8 10/-**. Single valve combined power units R.F.1B.P. and R.F.1L.P. Price **£7 10/-**.

BOSCOMBE RADIO & ELECTRIC,
595, Christchurch Road, Boscombe, Bournemouth. Phone: Boscombe 36522

AMPLIFIERS *Quality* **KIT for HOME CONSTRUCTORS**

A complete set of components to construct a 10 watt amplifier including Woden potted mains transformer, 5 valves, 10in. speaker with transformer. Components of the highest quality. No Govt. surplus. Three switched inputs, negative feed back, push-pull output, tone control, steel chassis. Suitable home or small hall.
CASH WITH ORDER
Price Complete to the last screw **£7 10 0** (Subject)

BEETHOVEN LTD
ELECTRIC EQUIPMENT
Chapel Lane Sands, High Wycombe Tel. 1152-3

BOOKS INSTRUCTIONS, ETC.

"TELEVISION Superheterodyne Unit." A reprint of articles from "Wireless World" giving constructional details for a long-range receiver for reception of Alexandra Palace transmissions, with a map showing the service area of A.P. Size 9½in.×7½in. Price 2/6 net from all booksellers, or 2/9 by post from The Publishing Dept., Dorset House, Stamford St., S.E.1.

"TELEVISION Receiver Construction." Reprint of articles in "Wireless World." This book contains a full description of constructional details, including special components, of a modern television receiver for the London area. Size 9½in. wide×9½in. 44pp. with 54 diagrams and illus. 2/6 net, from all Booksellers, or 2/9 by post from The Publishing Dept., Dorset House, S.E.1. [P4

"WIRELESS Servicing Manual." 7th Edition. By W. T. Cocking, M.I.E.E. A reliable guide to which the professional can turn for reference. Essential testing apparatus and logical testing methods are described and the process of defining and remedying defects explained. Size 7in.×4½in. 32pp. Price 10/6 net, from all booksellers, or 11/11 by post from The Publishing Dept., Dorset House, Stamford St., S.E.1. [P1

LOCKWOOD
makers of
Fine Cabinets
and woodwork of every description for the Radio and allied trades
LOCKWOOD & COMPANY
Lowlands Road, Harrow, Middlesex. Byron 3794

B. & H. RADIO
EAST STREET, DARLINGTON

BASS & TREBLE SEPARATOR
Enables the use of separate speakers for bass and treble. Permits adjustment of amount of treble relative to bass and also allows speakers of different impedance to be used. Kit of parts.... £1 9 6

SCRATCH FILTERS.
Gives marked reduction of scratch level without serious effect on treble response 15 0

VARIABLE SELECTIVITY I.F. TRANSFORMERS. 465 k/cs. Give 3 degrees of selectivity. Per pair £1 0 0

WHISTLE FILTER.
Steep trough, adjustable from 4 k/cs upwards. Eliminates 9 k/cs. whistle etc. 15 0

All items complete with diagrams and full instructions. Also available tone control units, amplifiers, standard or to specification etc.

SPECIAL OFFER
NO. 2 PARCEL

of new components, contains 100 resistors, 50 condensers, 50 yds. sleeving, 20 valve holders, volume controls, knobs, tuning condenser, wire, nuts, screws, washers, tag strips, grid clips, and many other useful components. Only 250 parcels offered at the low price of

30/- post paid (overseas 35/-).

Exceptional value, less than half cost price. Satisfaction guaranteed or money refunded.

COVENTRY RADIO
Component Specialists since 1921
100, DUNSTABLE ROAD, LUTON, BEDS

YOUR METER DAMAGED ?

Leading Electrical Instrument Repairers to the Industry.

Repairs by skilled craftsmen to all makes and types of Voltmeters, Ammeters, Microammeters, Multimeters, Test sets, Electrical Thermometers, Speedos, Instruments, Switchboard Clocks, &c. Quick deliveries—for speedy release send defective instrument by registered post to

L. GLASER
Electrical Instrument Repairers
341 CITY ROAD, E.C.1.
Tel. Terminus 2489

Instrument wire, leatherette, film, varnish, etc.
ASTROGRAPHS, 1 in. Pattern, in smart cases, **12/6**, carriage 2/6. Case easily worth double.
Parmeko Transformers, input 230 v. 50 cycles.
Many other Radio, Electrical and Mechanical bargains. Motors, all types.

L. C. NORTHALL
416, HIGH ST., SMETHWICK.
Telephone WOD 3166.

VISIT STAND C.735, F.I.F.

RUNBAKEN · MANCHESTER 1

ENGINEERS !

Whatever your age or experience, you need read "ENGINEERING OPPORTUNITIES". Full details of the various exams. in Civil, Mech., Elec., Aero., Auto., Radio, etc., Building, etc. A.M.I.Mech.E., A.M.I.C.E., A.M.I.E.E., A.M.I.Mun.E., CITY & GUILDS, MATRIC., etc. NO PASS NO FEE. Home and Abroad. Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. Even starting less than £10 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

176 PAGES Free!

B.I.E.T.
307, Shakespeare Hse., 17-19, Stratford Place, London, W.1.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

TELEVISION COILS
(Suitable for the latest viewing kits. Type EE also supplied)
MIDLAND WAVELENGTH 25/6
LONDON WAVELENGTH 18/6
per complete set
FROM YOUR LOCAL RETAILER.
USUAL FACTOR OR:—
BRITISH DISTRIBUTING CO.
66 HIGH ST., LONDON, N.8

TAMSA

High Quality Tape Recording Components

RECORD HEADS | OSCILLATORS
PLAYBACK HEADS | AMPLIFIERS
ERASE HEADS | PRE-AMPLIFIERS

COMBINED RECORD-PLAYBACK HEADS
TAPE. Plastic Base, 600ft., 1,200ft., 3,250ft.
Comprehensive Booklet "Magnetic Tape Recording." Price 5/4 Post Free (G.B.).
Constructor Envelope: Complete Amplifier Equipment. Price 3/6, postage 3d.
Write for latest Price List

AUDIGRAPH LTD.
Dept. MR1, 74, Great Hampton Street, HOCKLEY, BIRMINGHAM, 18

HAVE YOUR
TELEVISION
CONVERTED FROM
LONDON TO MIDLAND
RADIOS REPAIRED & HELP TO HOME BUILDERS
E. W. SHACKLE HIGH ST., HARLINGTON, HAYES, MIDDX.

MALVYN ENGINEERING WORKS
Precision Engineers.
Manufacturers of—
High-class Chromium Plated Panel Handles.
Chassis, Panels, Racks and Mechanical Assemblies to specification.
All enquiries receive prompt attention.
100, Park Road, Ware, Herts

You can master
MATHEMATICS
If you wish to understand radio really thoroughly you must know Mathematics. Our new Home-Study Courses make them really interesting and easy to learn.
T. & C. RADIO COLLEGE
Specialists in Home-Study Tuition in Mathematics, Radio & Television
Write for free booklet "W" to:—
R. Heath Bradley, T. C. R. C.,
50, Horland Road,
SOUTHBOURNE, BOURNEMOUTH.

RADIO UNLIMITED

*MOBILE (6/12v.) AMPLIFIER, for Mic. and Gram., 4 valve, 7 watts, tapped output. Offered at 9 Gns., now sold.
*CHROMIUM PLATED FOLDING MICROPHONE STAND. Normally 3 Gns., 29/6.
*Bluth P.M. SPEAKER, high grade, 14/9.
*ENLARGING LENS, for 3, 4 or 5in. tube, 25/-.
*AMPLION TEST METER, A.C. D.C. ohms, £3 17 6.
*STANDARD 2-3 ohm LOUDSPEAKERS, 8in., 10/-; 10in., 11/6; 12in., 12/6; 16in., 15/-.
*TRANSMITTING VALVE, ref. New, boxed, 7/6.
*MAINS TRANSFORMER, 350-350, 4v., 5v., 4v., 50 m.a. Fully Guaranteed, 20/-.
* New surplus list now available.

RADIO UNLIMITED
ELM ROAD, WALTHAMSTOW, LONDON, E.17
Tel. KEY 4813

YOU SHOULD HAVE A NEW TAYLOR

We can supply the latest Taylor Test-Equipment, and take your used Equipment in part exchange. Balance by cash or hire purchase.
Write, phone or send your gear along for inspection and offer.

UNIVERSITY RADIO LTD.
22 LISLE ST. Tel. GERRARD 4447 & 8882

URGENTLY WANTED
Frequency meters BC221
Receivers BC348 & 312
Preferably not converted, accepted if in good condition. Also interest for other American receivers and instruments.
Quote to Box No. 3080 c/o. Wireless World

SAVAGE TRANSFORMERS OF DEVIZES LIMITED
INTRICATE TRANSFORMER CONSTRUCTION
SAVAGE TRANSFORMERS LIMITED
NURSTEED ROAD • DEVIZES • WILTS
TELEPHONE DEVIZES 515

KERSHAW'S KORNER KALLING!!!
T.V. AMATEURS
BARGAINS IN GOVERNMENT SURPLUS ELECTRONIC TELEVISION COMPONENTS
MODULATOR TYPE 20 consisting of 2 valves VU111, 4 volt 5kV E.H.T. rectifiers, 5 valves type KT44 (very suitable for line output), and 1 valve type MH41. This modulator is a marvellous unit for spare parts and is offered for the very low price of **42/-** inc. carriage.
RCR.3515. I.F. strip 13.5 Mc/s. ideal for "W.W." Televisor. 6 I.F. stages with 3 Mc/s band width. EA50 Detector and EF39 Video O.P. Our price, **30/-** each, complete with valves.
INERT 1.5 v. CELL BATTERIES, long life, fill with plain water and have continuous use. Ideal for every purpose. 3 for **2/6**. Post paid.
All Goods post paid. No lists or Catalogues.
S. KERSHAW
KERSHAW'S KORNER, PERSHORE STREET, BROMSGROVE STREET, BIRMINGHAM 5.
Phone Midland 4282/7097

RELAYS AND KEY SWITCHES

LARGEST EX-GOVT. STOCK IN GT. BRITAIN
Types 600-3000 Relays — Siemens High Speed
Also A.C. 250 volts 50 cycles
Uniselector Switches, Carbon Insets, Telephone Components, Plugs, Jacks, Handsets, Co-Axial Cables — **Government Contractors**
JACK DAVIS (Dept. W.)
30 PERCY STREET, LONDON, W.1
Phones: MUSeum 7960, LANgham 4821

Designed and developed essentially to give best performance at lowest cost, the following apparatus is fast establishing itself wherever good telecommunication equipment is called for

1 kW TELEGRAPH TRANSMITTER 3.5-16 MC/S
60 W RADIOCOMMUNICATION TRANSCEIVER 2-8 MC/S RT/CW
20 W RADIOCOMMUNICATION TRANSCEIVER 2-16 MC/S
Ask for quotations!
MANUFACTURERS:
ATA SCIENTIFIC PROGRESS LTD.
63, Kensal Rd., London, W.10. *Tel. LAD. 1598*

INDEX TO ADVERTISERS

PAGE

Acro Electric Tool Mfg. Co., Ltd., The ... 55
Adcola Products, Ltd. ... 96
Air Ministry ... 15
Airmec Laboratories, Ltd. ... 11
Aish & Co., Ltd. ... 80
Albert Mfg. Co. ... 92
Allan Richard, Radio Ltd. ... 14
Allen Comp.nents, Ltd. ... 90
Alpha Accessories, Ltd. ... 4
Ambassador Radio ... 14
Amiferrous, Ltd. ... 12
Armstrong Wireless & Television Co., Ltd. ... 8
Ashworth, H. ... 8
ATA Scientific Progress, Ltd. ... 92
Audigraph, Ltd. ... 35
Automatic Coil Winder & Electrical Equip. Co., Ltd. ... 1
Automatic Telephone & Electric Co., Ltd. ... 51

B. & H. Radio ... 94
Baldwin Instruments Co., Ltd. ... 53
Barker, A. C. ... 72
Beethoven, Ltd. ... 84
Belling & Lee, Ltd. ... 8
Berry's (Short Wave), Ltd. ... 92
Bird, S. E. & Sons, Ltd. ... 23
Birmingham Sound Reproducers, Ltd. ... 44
Bournemouth Radio & Electric ... 94
Box 500, (c/o "Wireless World ... 95
Brierley, J. H. (Gramophone & Record-ings), Ltd. ... 84
Britain, Chas. (Radio), Ltd. ... 92
British Communication Corp., Ltd. ... 92
British Distributors Co. ... 92, 94
British Institute of Engineering Tech-nology ... 78, 94
British Insulated Callender's Cables, Ltd. ... Cover ii
British National Radio School ... 80
British Physical Laboratories ... 78
British Rola ... 47
British Sound Recording Association ... 72
Brookes Crystals, Ltd. ... 94
Brown, S. G., Ltd. ... 16
Burgin, A. F. & Co., Ltd. ... Edit. 199, 71
Bull, J. & Son ... 61
Bullers ... 38
Bullers, Ltd. ... 10

Cabot Radio Co., Ltd. ... 91
Candler System Co. ... 80
Champion Products ... 92
Chapman, C. T. (Reproducers), Ltd. ... 72
Charles Amplifiers, Ltd. ... 6
Chase Products (Engineering), Ltd. ... 74
Chloride Batteries, Ltd. ... 9
Cinema-Television, Ltd. ... 13
Clerkenwell Supply Co., Ltd. ... 69
Cohen, D. ... 96
Quinwood, Ltd. ... 40
Cossor, A. C., Ltd. ... 21
Crystalone Radio ... 85
Coventry Radio ... 94

Davis, Aer. Supplies, Ltd. ... 74
Davis, Jack ... 80
Drayton Regulator & Instrument Co., Ltd. ... 20
Dubilier Condenser Co. (1925), Ltd. ... 25
Duke & Co. ... 71
Duplex Electronics, Ltd. ... 84

Edison Swan Electric Co., Ltd. ... 11
Electradix Radio ... 94
Electronic Trades Union ... 92
Electro Acoustic Development ... 74
Electronic Instruments, Ltd. ... 15
Electronic Precision Equipment ... 40, 61
E.M.I. Institutes ... 54
Elu Tool Co. (Leicester), Ltd. ... 14

Fielden (Electronics), Ltd. ... 7
Fletcher ... 72
Flexible, Ltd. ... 87

Frith Radiocraft, Ltd. ... 92
Furzehill Laboratories, Ltd. ... 45

Galpins ... 77
Gardners Radio, Ltd. ... 92
Garland Radio ... 80
General Electric Co., Ltd. ... 5, 57, 73
Glaser, Ltd. ... 94
Gothic Industries, Ltd. ... 47
Goodwell, Ltd. ... 42
Grampian Reproducers, Ltd. ... 93, 95
Gray, A., Ltd. ... 92

Hallam, Sleigh & Cheston, Ltd. ... 24
Hartley, H. A., Co., Ltd. ... 75
Hatfield Instruments ... 92
Hayes Co., The ... 92
Haynes Radio, Ltd. ... 88
Henry's, W. T., Telegraph Works Co., Ltd. ... 92
Henry's ... 92
H. & Chandler, Ltd. ... 92
Hivac, Ltd. ... 39
Hoey, F. Livingston ... 94
Hajek, Anthony ... 94
Holroyd Radio Stores ... 94
Holt, Stan ... 90
Houghton & Gilbertson, Ltd. ... 93
H.P. Radio Services, Ltd. ... 66
Hunt, A. H., Ltd. ... 18

Ibsen, A., Ltd. ... 87
International Correspondence School, Ltd. ... 18

Jackson Bros. (London), Ltd. ... 4
Johnsons (Radio) ... 90

Kershaw, S. ... 95

Lasky's Radio ... 67
Lawrence, G., & Co. ... 82
Leak, R. J., & Co., Ltd. ... 55
Liquidators Disposal Agency ... 73
Lockwood & Co. ... 84
London Central Radio Stores ... 85
London Radio Supply Co. ... 81
Lowther Mfg. Co. ... 89
Lustraphone, Ltd. ... 74
Lyons, Claude, Ltd. ... 45
Lyons Radio ... 88

Macdonald & Co. (Publishers), Ltd. ... 76
Macryn Engineering Works ... 95
Mail Order Supply Co. ... 67
Marconi Instruments, Ltd. ... 43
Marconi Wireless Telegraph Co., Ltd. ... 81
McMurdo Instrument Co., Ltd. ... 86
Measuring Instruments (Pullin), Ltd. ... 54
"Mechanical Handling" Exhibition ... 71
Metro Pen, Ltd. ... 87
Metropolitan-Vickers Electrical Co., Ltd. ... 29
Midland Instrument Co. ... 66
Miers, N. & Co., Ltd. ... 16
Modern Book Co. ... 80
Modern Electrics, Ltd. ... 84
Morgande Resistors, Ltd. ... 19
M.R. Supplies, Ltd. ... 20
Mullard Electronic Products, Ltd. ... 35, 46
Mullinex Solders, Ltd. ... Cover iv

Northall, L. C. ... 94
Northern Radio Services ... 90
Nuswind Products ... 89

Oliver Pell Control, Ltd. ... 26
Omnitor Radio Products, Ltd. ... 68
Oxley Developments Co., Ltd. ... 96

Painton & Co., Ltd. ... 6, 10
Park Radio ... 64
Parmeko, Ltd. ... 49
Partridge Transformers, Ltd. ... 75

P.C.A. Radio ... 72
Pearce, T. W. ... 70
Peerless Radio, Ltd. ... 92
Pennine Amplifiers ... 94
Pilmak, A., Isaac, & Sons, Ltd. ... 91
Post Radio Supplies ... 86
Pratts Radio ... 74
Premier Radio Co. ... 57, 93, 59

Quartz Crystal Co., Ltd. ... 90

Radiant Hooths, Ltd. ... 3
Radio Exchange Co. ... 68
Radiomenders, Ltd. ... 72
Radio Merchandise Co., Ltd. ... 94
Radio Servicing Co. ... 77
Radiospares, Ltd. ... 92
Radio Unlimited ... 90
Record Electrical Co., Ltd., The ... 13
Redifon, Ltd. ... 52
Reliance Mfg. Co. (Southwark), Ltd. ... 94
Regproducers & Amplifiers, Ltd. ... 12
Rifbendon & Co., Ltd. ... 39
Rodley Laboratories ... 89
Rogers Developments Co. ... 83
Rotell, H., & Co., Ltd. ... 94
Rotherme, R. A., Ltd. ... 94
Ruse Products ... 90
Rubinkam Electrical Products ... 94, 94

Salford Electrical Instruments, Ltd. ... 17
Samsons Surplus Stores ... 92
Sangamo Weston, Ltd. ... 52
Savage Transformers, Ltd. ... 83
Schaff, Erwin ... 92
Shackle, E. W. ... 93
Silverstone, H. ... 94
Simmonds Aerocessories, Ltd. ... 12
Simon Sound Service ... 94
Smith, G. W. (Radio), Ltd. ... 94
Sound Sales, Ltd. ... 94
Southern Radio Supply, Ltd. ... 94
Sowter, Transformers ... 94
Stability Radio Components, Ltd. ... 42
Standard Telephone & Cables, Ltd. ... 37, 50
Steatite & Porcelain Products, Ltd. ... 3

Stern Radio, Ltd. ... 63
Stewart Transformers, Ltd. ... 92
Sugden, A. R., & Co. (Engineers), Ltd. ... 24
Supavoils ... 71
Surplus Co., S. ... 92
T. & C. Radio College ... 94
Taylor Electrical Instruments, Ltd. ... 50
Taylor, Tunnicliff (Refractories), Ltd. ... 9
Telegraph Condenser Co., Ltd. ... Cover iii
Telegraph Construction & Maintenance Co., Ltd., The ... 28
Tele-Radio (1943), Ltd. ... 54
Thornley, J. E., & Sons ... 93
Transradio, Ltd. ... 93
Trix Electrical Co., Ltd. ... Edit. 197

United Insulator Co., Ltd. ... 93
Universal Electrical Instruments Corpn. ... 94
Universal Radio, Ltd. ... 65, 95

Vallance & Davison, Ltd. ... 93
Vaidulo ... 82
Vogt, Patents, Ltd. ... 93
Vortexion, Ltd. ... 31

Walton's Wireless Stores ... 92
Wayne Kerr Labs., Ltd., The ... 21
Westinghouse Brake & Signal Co., Ltd. ... 43
West, Spencer ... 92
Weymouth Radio Mfg. Co., Ltd., The ... 72
Wharfedale Wireless Works ... 22
Whiteley Electrical Radio Co., Ltd. ... 82
Wilton Electronics ... 93
Wireless Instruments (Leeds), Ltd. ... 93
Wireless Supplies, Unlimited ... 94
Wright & Weaire, Ltd. ... 45

Young, C. H. ... 70

'TECHNICAL EXCELLENCE'—

—combines with beauty and soundness of DESIGN in the

OXLEY

AIR DIELECTRIC TRIMMER

Patents Applied for

W. 1·5 in. Length 22 m.m. Height 1·5 in. Ref—7·0 m.m. 1·8 to 20pF—10 m.m. 2 to 26pF—11 m.m. 7 to 32pF—12m.m. Low Straight line capacity. Power Factor: Loss tang. .001. Insulation: Over 2,000 megohms. Voltage: 500 D.C.

OXLEY DEVELOPMENTS CO. LTD.

ULVERSTON NORTH LANCS. TEL: ULVERSTON 3101

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark

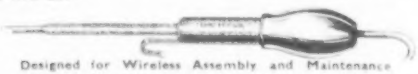

Designed for Wireless Assembly and Maintenance

SUPPLIED FOR ALL VOLT RANGES FROM 6.7v. TO 230-50v.

The three Adcola Models covering the requirements of the Television, Telecommunication and Radar Engineers assure thorough joining

1/4in. dia. Bit Standard Model — 22/6
1/2in. dia. Bit Standard Model — 25/-
1/4in. dia. Detachable Bit — — — 30/-

REPLACEMENT UNIT BIT ELEMENTS AVAILABLE.

Patented in England and Abroad.

Sole Manufacturers

ADCOLA PRODUCTS LIMITED

ALLIANCE HOUSE CAXTON STREET, WESTMINSTER LONDON, S.W.1 Tele. MACaulay 4272

Printed in Great Britain for the Publishers, Iliffe and Sons Ltd., Dorset House, Stamford Street, London, S.E.1, by The Chiswick Press Ltd., Paris Garden, Stamford Street, London, S.E.1. "Wireless World" can be obtained abroad from the following: Australia and New Zealand: Gordon & Gotch, Ltd. India: A. H. Wheeler & Co. Canada: Imperial News Co., Montreal & Toronto, Ltd. South Africa: Central News Agency, Ltd. South Africa: Gordon Drayton & Sons (S.A.), Ltd. United States: The International News Co.

Wax protected

TUBULAR PAPER CONDENSERS

TYPE 343
350 V. D.C. Wkg.

Cap. μF.	Lgth.	Dia.
.05	1¼in.	½in.
.1	1¼in.	11/16in.
.2	1¼in.	11/16in.
.25	1¾in.	5/8in.
.5	2 in.	¾in.

TYPE 743
750 V. D.C. Wkg.

Cap. μF.	Lgth.	Dia.
.005	1 in.	½in.
.01	1 in.	11/16in.
.02	1 in.	11/16in.
.1	1¾in.	5/8in.
.25	2 in.	¾in.

THESE condensers are used by the million — they meet the requirements of over 75% of the positions in electronic circuitry and are to be found in every well-known make of radio and television receiver.

The windings keep inductance to the minimum, the sealing is by several coatings of wax, and the simple but effective construction shows a considerable saving in cost.

Wax protected types are not recommended where permanent high insulation resistance under all conditions is essential, and here T.C.C. "Metalmite" or "Metalpack" condensers (in aluminium tubes with synthetic rubber end seals) should be used.

T.C.C. Condensers are extensively specified in the Visa Mentor or the Television Set now being or being from standard parts. Construction Envelopes (Model A, London, or Model B, Norton Coldfield) V. each from all Wireless Shops.

TYPE 543
500 V. D.C. Wkg.

Cap. μF.	Lgth.	Dia.
up to .002	¾in.	9/16in.
.01	¾in.	11/16in.
.02	1 in.	11/16in.
.1	1¾in.	5/8in.
.25	1¾in.	¾in.

TYPE 2043
1000 V. D.C. Wkg.

Cap. μF.	Lgth.	Dia.
.0005	1 in.	½in.
.001	1 in.	½in.
.005	1 in.	9/16in.
.02	1¾in.	¾in.
.1	2 in.	¾in.

THE TELEGRAPH CONDENSER CO. LTD
RADIO DIVISION NORTH ACTON LONDON, W.3 Tel. ACORN 0041

LEADING RADIO FACTORIES IN SCANDINAVIA

use ERSIN MULTICORE SOLDER

Soldering radio sets in the Oslo factories of Tandberg Radiofabrikk, Norway. ERSIN MULTICORE SOLDER has been used exclusively since the war.

Scandinavian manufacturers of radio and electrical equipment prefer to use British-made Ersin Multicore Solder, despite the freight charges and import duties which have to be paid on it. They find that Ersin Multicore effects great savings in material and labour costs, because it is the only solder which contains three cores of extra-active non-corrosive Ersin Flux, giving high speed precision soldering without waste, and eliminating "dry" or H.R. joints. Ersin Multicore Solder is supplied to manufacturers in 6 standard alloys, and 2 flux percentages. The handy size 1 carton (available in the 4 specifications shown below) is recommended for Service Engineers and Workshops.

ERSIN MULTICORE SOLDER being used in Bang & Olufsen's Radio Factories at Struer, Denmark. This is one of the largest factories in Denmark for the manufacture of radio, cinema projectors, wire recorders and many types of electrical equipment.

PRICES FOR SIZE 1 CARTONS

Catalogue Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. length per carton	List Price per carton (subject) s	d
C 16014	60/40	14	26 feet	5	0
C 16018	60/40	18	60 feet	5	0
C 14013	40/60	13	22 feet	5	0
C 14016	40/60	16	42 feet	5	0

Illustrated are the Nominal 7/8 reel (for factories) and the Size 1 carton (for Service Engineers and Workshops). Manufacturers and Service Engineers are invited to write for technical information, samples and bulk prices.

MULTICORE SOLDERS LTD.
MULTICORE HOUSE, ALBEMARLE STREET, LONDON, W.1 • Telephone: REGent 1411

ERSIN MULTICORE SOLDER is shown in use at the factories of Luxor, Motala, one of the largest manufacturers of radio sets in Sweden.